



Experiments in

**Electronics
Fundamentals**

and

**Electric
Circuits
Fundamentals**

4TH EDITION

B U C H L A

Experiments in Electronics Fundamentals and Electric Circuits Fundamentals

Fourth Edition

**To accompany FLOYD,
ELECTRONICS FUNDAMENTALS
and ELECTRIC CIRCUITS FUNDAMENTALS
Fourth Edition**

David Buchla
Yuba College



Prentice Hall

Upper Saddle River, New Jersey

Columbus, Ohio

Cover Photo: © 1996 by Photo Disc, Inc.
Editor: Linda Ludewig
Developmental Editor: Carol Hinklin Robison
Production Editor: Rex Davidson
Design Coordinator: Julia Zonneveld Van Hook
Cover Designer: Brian Deep
Production Manager: Laura Messerly
Marketing Manager: Debbie Yarnell

This book was set in Times Roman by The Clarinda Company and was printed and bound by Banta Company.
The cover was printed by Phoenix Color Corp.



©1998 by Prentice-Hall, Inc.
Simon & Schuster/A Viacom Company
Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Earlier editions entitled *Experiments in Electronics Fundamentals: Circuits, Devices, and Applications* © 1995 by Prentice-Hall, Inc. and © 1991 by Macmillan Publishing Company.

Printed in the United States of America

10 9 8 7 6 5

ISBN: 0-13-737164-0

Prentice-Hall International (UK) Limited, *London*
Prentice-Hall of Australia Pty. Limited, *Sydney*
Prentice-Hall Canada, Inc., *Toronto*
Prentice-Hall Hispanoamericana, S. A., *Mexico*
Prentice-Hall of India Private Limited, *New Delhi*
Prentice-Hall of Japan, Inc., *Tokyo*
Simon & Schuster Asia Pte. Ltd., *Singapore*
Editora Prentice-Hall do Brasil, Ltda., *Rio de Janeiro*

Preface

This laboratory manual is designed to be used with *Electronics Fundamentals: Circuits, Devices, and Applications*, 4th Edition, and *Electric Circuits Fundamentals*, 4th edition, by Thomas Floyd. This fourth edition of the lab manual retains the experiments that have made the first three editions successful, including

- Close correlation to Floyd's texts with exercises that build on those presented in the text. This is done by providing a workbook format for the experiments and including *Related Experiments* to augment the *Application Assignment* given in the text. In addition, *Checkup* pages have additional exercises that are taken from material presented in the text and the lab manual.
- Flexibility. A *Further Investigation* section, with less structure than the experiment, is included with each experiment as an enhancement. This section can be assigned as part of the experiment or used as an extra credit assignment depending on the particular time allowed and instructor preference.

Features from previous editions have been retained. These include the *For Further Investigation* section that provides a measure of flexibility, the *Checkup* page with questions from the text and the laboratory, the *Application Assignment* and *Related Experiment*, and the section entitled *Reference Guide to Laboratory Instruments*.

There are a total of 48 experiments covering the most important concepts in basic and linear electronics. Each experiment contains the following parts:

Reading: Reading assignments, which are referenced to Floyd's texts.

Objectives: Statement of what the student should be able to do after completing the experiment.

Summary of Theory: The Summary of Theory is intended to reinforce the important concepts in Floyd's texts with a review of the main points prior to the laboratory experience. In most cases, specific practical information needed in the experiment is presented.

Materials Needed: A list of the components and small items required but not including the equipment found at a typical lab station.

Procedure: This section contains a relatively structured set of steps for performing the experiment. Needed tables, graphs, and figures are close to the first referenced location to avoid confusion. Laboratory techniques, such as operation of the oscilloscope, are given in detail.

Conclusion: A space provided for the student to summarize the key findings from the experiment.

Evaluation and Review Questions: This section contains five questions that require the student to draw conclusions from the laboratory work and check his or her understanding of the concepts. Troubleshooting questions are frequently presented.

For Further Investigation: This section contains specific suggestions for additional related laboratory work. A number of these lend themselves to a formal laboratory report or they can be used as an enhancement.

Following the experiments designed for a specific chapter of Floyd's texts are the *Application Assignment* and *Checkup*. These pages are designed to be removed from the book for submission. The *Application Assignment* begins with an answer page for the student to complete from the application problem given in each of Floyd's chapters. Each *Application Assignment* includes a *Related Experiment*, which adds a problem requiring a laboratory solution. The *Checkup* begins with ten multiple choice questions and includes questions and problems from the text and the laboratory work. These items are cross-indexed on page vii.

Each laboratory station should contain a dual variable regulated power supply, a function generator, a multimeter, and a dual-channel oscilloscope. It is useful if the laboratory is equipped to measure capacitors and inductors. In addition, a meter calibrator, a commercial Wheatstone bridge, and a transistor curve tracer are useful but not required. A list of all required components is given in Appendix A.

While this manual is specifically designed to follow the sequence of Floyd's *Electronics Fundamentals* and *Electric Circuits Fundamentals* texts, it can be used with other texts by ignoring the references. The experiments work equally well for schools using electron flow or conventional current flow as no specific reference to either is made in the experiments.

I have enjoyed the close collaboration with Tom Floyd on this manual. I also would like to thank reviewers who have given suggestions for improving the experiments at various times. These include Carl F. Ervin from the Texas State Technical Institute, Waco, Texas, and George Borchers, Ernest Arney, and David Terrell of ITT Technical Institute. I appreciate the help of my colleagues at Yuba College, Phil Postel and Bill Frandrup. I would also like to thank Carol Robison, Linda Ludewig, and Rex Davidson of Prentice Hall Publishing Co. for their contributions and Colleen Brosnan for copyediting. Finally, I want to acknowledge the support and encouragement of my wife, Lorraine.

David Buchla

Contents

	Introduction to the Student	1
	Reference Guide to Laboratory Instruments	4
1	Metric Prefixes, Scientific Notation, and Graphing	11
2	Laboratory Meters and Power Supply	19
3	Measurement of Resistance	29
4	Voltage Measurement and Circuit Ground	35
5	Ohm's Law	43
6	Power in DC Circuits	49
7	Series Circuits	57
8	The Voltage Divider	63
9	Parallel Circuits	73
10	Series-Parallel Combination Circuits	83
11	The Superposition Theorem	89
12	Thevenin's Theorem	95
13	The Wheatstone Bridge	101
14	Magnetic Devices	111
15	The Oscilloscope	121
16	Sine Wave Measurements	127
17	Pulse Measurements	131
18	Capacitors	141
19	Capacitive Reactance	147
20	Inductors	157
21	Inductive Reactance	161
22	Transformers	171
23	Series <i>RC</i> Circuits	181
24	Parallel <i>RC</i> Circuits	187
25	Series <i>RL</i> Circuits	197
26	Parallel <i>RL</i> Circuits	205
27	Series Resonance	215
28	Parallel Resonance	223
29	Passive Filters	229
30	Integrating and Differentiating Circuits	239
31	Diode Characteristics	249
32	Rectifier Circuits	259
33	Diode Limiting and Clamping Circuits	265
34	Bipolar Transistors	275
35	Field-Effect Transistors	281
36	The SCR	287
37	The UJT	293
38	The Common-Emitter Amplifier	303
39	The Common-Collector Amplifier	311
40	FET Amplifiers	319
41	The Push-Pull Amplifier	325

42	Oscillators	331
43	The Differential Amplifier	341
44	Op-Amp Characteristics	347
45	Linear Op-Amp Circuits	353
46	Nonlinear Op-Amp Circuits	363
47	The Wien Bridge Oscillator	369
48	Active Filters	375
Appendix A	List of Materials for the Experiments	385
Appendix B	Manufacturer's Data Sheets	386

Cross Reference to *Electronics Fundamentals* and *Electric Circuits Fundamentals*, Fourth Edition, by Thomas L. Floyd

Floyd Chapter Reference	Buchla Experiment Reference	Application Assignment Pg. No.	Checkup Pg. No.
1	1 Metric Prefixes, Scientific Notation, and Graphing 2 Laboratory Meters and Power Supply		27
2	3 Measurement of Resistance 4 Voltage Measurement and Circuit Ground	39	41
3	5 Ohm's Law 6 Power in DC Circuits	53	55
4	7 Series Circuits 8 The Voltage Divider	69	71
5	9 Parallel Circuits	79	81
6	10 Series-Parallel Combination Circuits 11 The Superposition Theorem 12 Thevenin's Theorem 13 The Wheatstone Bridge	107	109
7	14 Magnetic Devices	117	119
8	15 The Oscilloscope 16 Sine Wave Measurements 17 Pulse Measurements	137	139
9	18 Capacitors 19 Capacitive Reactance	153	155
10	20 Inductors 21 Inductive Reactance	167	169
11	22 Transformers	177	179
12	23 Series <i>RC</i> Circuits 24 Parallel <i>RC</i> Circuits	193	195
13	25 Series <i>RL</i> Circuits 26 Parallel <i>RL</i> Circuits	211	213
14	27 Series Resonance 28 Parallel Resonance 29 Passive Filters	235	237
15	30 Integrating and Differentiating Circuits	245	247
16*	31 Diode Characteristics	255	257
17*	32 Rectifier Circuits 33 Diode Limiting and Clamping Circuits	271	273
18*	34 Bipolar Transistors 35 Field Effect Transistors 36 The SCR 37 The UJT	299	301
19*	38 The Common-Emitter Amplifier 39 The Common-Collector Amplifier 40 FET Amplifiers 41 The Push-Pull Amplifier 42 Oscillators	337	339
20*	43 The Differential Amplifier 44 Op-Amp Characteristics 45 Linear Op-Amp Circuits	359	361
21*	46 Nonlinear Op-Amp Circuits 47 The Wien Bridge Oscillator 48 Active Filters	381	383

**Electronics Fundamentals* only

Introduction to the Student

Preparing for Laboratory Work

The purpose of experimental work is to help you gain a better understanding of the principles of electronics and to give you experience with instruments and methods used by technicians and electronic engineers. You should begin each experiment with a clear idea of the purpose of the experiment and the theory behind the experiment. Each experiment requires you to use electronic instruments to measure various quantities. The measured data are to be recorded, and you need to interpret the measurements and draw conclusions about your work. The ability to measure, interpret, and communicate results is basic to electronic work.

Preparation before coming to the laboratory is an important part of experimental work. You should prepare in advance for every experiment by reading the *Reading*, *Objectives*, and *Summary of Theory* sections before coming to class. The *Summary of Theory* is *not* intended to replace the theory presented in the text—it is meant only as a short review to jog your memory of key concepts and to provide some insight to the experiment. You should also look over the *Procedure* for the experiment. This prelab preparation will enable you to work efficiently in the laboratory and enhance the value of the laboratory time.

This laboratory manual is designed to help you measure and record data as efficiently as possible. Techniques for using instruments are described in many experiments. Data tables are prepared and properly labeled to facilitate recording. Plots are provided where necessary. You will need to interpret and discuss the results in the section titled *Conclusion* and answer the *Evaluation and Review Questions*. The *Conclusion* to an experiment is a concise statement of your key findings from the experiment. Be careful of generalizations that are not supported by the data. The conclusion should be a specific statement that includes important findings with a brief discussion of problems, or revisions, or suggestions you may have for improving the circuit. It should directly relate to the objectives of the experiment. For example, if the objective of the experiment is to use the concept of equivalent circuits to simplify series-parallel circuit analysis (as in Experiment 10), the conclusion can refer to the simplified circuit drawings and indicate that these circuits were used to compute the actual voltages and currents in the experiment. Then include a statement comparing the measured and computed results as evidence that the equivalent circuits you developed in the experiment were capable of simplifying the analysis.

The Laboratory Notebook

Your instructor may assign a formal laboratory report or a report may be assigned in the section titled *For Further Investigation*. A suggested format for formal reports is as follows:

1. *Title and date.*
2. *Purpose:* Give a statement of what you intend to determine as a result of the investigation.
3. *Equipment and materials:* Include a list of equipment model and serial numbers that can allow retracing if a defective or uncalibrated piece of equipment was used.
4. *Procedure:* Give a description of what you did and what measurements you made.
5. *Data:* Tabulate raw (unprocessed) data; data may be presented in graph form.
6. *Sample calculations:* Give the formulas that you applied to the raw data to transform them to processed data.

7. **Conclusion:** The conclusion is a specific statement supported by the experimental data. It should relate to the objectives for the experiment as described earlier. For example, if the purpose of the experiment is to determine the frequency response of a filter, the conclusion should describe the frequency response or contain a reference to an illustration of the response.

Graphing

A graph is a pictorial representation of data that enables you to see the effect of one variable on another. Graphs are widely used in experimental work to present information because they enable the reader to discern variations in magnitude, slope, and direction between two quantities. In this manual, you will graph data in many experiments. You should be aware of the following terms that are used with graphs:

abscissa: the horizontal or x -axis of a graph. Normally the independent variable is plotted along the abscissa.

dependent variable: a quantity that is influenced by changes in another quantity (the independent variable).

graph: a pictorial representation of a set of data constructed on a set of coordinates that are drawn at right angles to each other. The graph illustrates one variable's effect on another.

independent variable: the quantity that the experimenter can change.

ordinate: the vertical or y -axis of a graph. Normally the dependent variable is plotted along the abscissa.

scale: the value of each division along the x - or y -axis. In a linear scale, each division has equal weight. In a logarithmic scale, each division represents the same percentage change in the variable.

The following steps will guide you in preparing a graph:

1. Determine the type of scale that will be used. A linear scale is the most frequently used and will be discussed here. Choose a scale factor that enables all of the data to be plotted on the graph without being cramped. The most common scales are 1, 2, 5, or 10 units per division. Start both axes from zero unless the data covers less than half of the length of the coordinate.
2. Number the *major* divisions along each axis. Do not number each small division as it will make the graph appear cluttered. Each division must have equal weight. Note: The experimental data is *not* used to number the divisions.
3. Label each axis to indicate the quantity being measured and the measurement units. Usually, the measurement units are given in parentheses.
4. Plot the data points with a small dot with a small circle around each point. If additional sets of data are plotted, use other distinctive symbols (such as triangles) to identify each set.
5. Draw a smooth line that represents the data trend. It is normal practice to consider data points but to ignore minor variations due to experimental errors. (Exception: calibration curves and other discontinuous data are connected "dot-to-dot.")
6. Title the graph, indicating with the title what the graph represents. The completed graph should be self-explanatory.

Safety in the Laboratory

The experiments in this lab book are designed for low voltages to minimize electric shock hazard; however, never assume that electric circuits are safe. A current of a few milliamps through the body can be lethal. In addition, electronic laboratories often contain other hazards such as chemicals and power tools. For your safety, you should review laboratory safety rules before beginning a course in electronics. In particular, you should

1. Avoid contact with *any* voltage source. Turn off power before working on circuits.
2. Remove watches, jewelry, rings, and so forth before working on circuits—even those circuits with low voltages—as burns can occur.
3. Know the location of the emergency power-off switch.
4. Never work alone in the laboratory.
5. Keep a neat work area and handle tools properly. Wear safety goggles or gloves when required.
6. Ensure that line cords are in good condition and grounding pins are not missing or bent. Do not defeat the three-wire ground system in order to make “floating” measurements.
7. Check that transformers and instruments that are plugged into utility lines are properly fused and have no exposed wiring. If you are not certain about procedure, check with your instructor first.
8. Report any unsafe condition to your instructor.
9. Be aware of and follow laboratory rules.

Reference Guide to Laboratory Instruments

This section is provided to help familiarize you with basic laboratory instruments and may be used as a reference as the instruments are introduced in the experiments. It is not possible to cover all possible variations between instruments, so only general features, common to a class of instruments, are described. Consult the operator's manual for detailed descriptions and safe operating practice of the particular instruments in your laboratory.

The Power Supply

Most electronic circuits require a source of regulated direct current (dc) to operate properly. A direct current regulated power supply is a circuit that provides the energy to allow electronic circuits to function. They do this by transforming a source of input electrical power (generally ac) into dc. Most regulated supplies are designed to maintain a fixed voltage that will stay within certain limits of voltage for normal operation. Voltage adjustment and current limits depend on the particular supply.

The power supply must provide the proper level of dc voltage for a given circuit. Some integrated circuits, for example, can function properly only if the voltage is within a very narrow range. You will normally have to set the voltage to the proper level before you connect a power supply to the test circuit. The power supply at your bench may have more than one output and normally will have a built-in meter to help you set the voltage. Some power supplies have meters that monitor both voltage and current. There may be more than one range or several supplies built into the same chassis, so the meter may have multiple or complex scales. These points are discussed in more detail in Experiment 2.

It is important that the user make good connections to the power supply output terminals with wire that is sufficient to carry the load current if the output were accidentally shorted together. Clip-leads are not recommended as they can produce measurement error due to high contact resistance. In situations where several circuits are operated from the same supply, the best policy is to operate each circuit with an independent set of leads.

The Multimeter

The digital multimeter (DMM) and analog volt-ohm-milliammeter (VOM) are multipurpose measuring instruments that combine the characteristics of a dc and ac voltmeter, dc and ac ammeter, and an ohmmeter in one instrument. The DMM indicates the measured quantity as a digital number, avoiding the necessity to interpret the scales as is required on analog instruments. Although in most labs the DMM has replaced the VOM as the instrument of choice, there are several advantages to the VOM. It is less susceptible to interference and has a much higher frequency response.

Because the multimeter is a multipurpose instrument, it is necessary to determine which controls select the desired function. In addition, current measurements (and often high-range voltage measurements) usually require a separate set of lead connections to the meter. After you have selected the function, you need to select the appropriate range to make the measurement. It is important to select the function and range *before* connecting the meter to the circuit you are testing. DMMs can be autoranging, meaning that the instrument automatically selects the correct scale and sets the decimal place, or they can be manual ranging, meaning that the user must select the correct scale. For manual ranging instruments,

when the approximate voltage or current is not known, always begin a measurement on the highest possible range to avoid instrument overload and possible damage. Change to a lower range as necessary to increase the precision. The life of range switches will be lengthened if you change ranges only with the probes disconnected from the circuit. On analog instruments the range selected should give a reading in the upper portion of the scale.

The voltmeter function of a DMM can measure either ac or dc volts. The dc voltage function is useful to measure the dc voltage *difference* between two points. If the meter's red lead is touching a more positive point than the meter's black lead, the reading on the meter will be positive; if the black lead is on the more positive point, the reading will be negative. Analog meters *must* be connected with the correct polarity, or the pointer will attempt to move backward, possibly damaging the movement.

The ac voltage function is designed to measure low-frequency sinusoidal waveforms. (Sinusoidal waveforms are discussed in Chapter 8 of the text and introduced in Experiment 15.) The reading on a meter is calibrated to read the rms (root mean square) value of a sinusoidal waveform. Frequency is the number of cycles per second, measured in hertz, for a waveform. All DMMs and VOMs are limited to some specified frequency range. The meter reading will be inaccurate if you attempt to measure waveforms outside the meter's specified frequency range. A typical DMM is not accurate on the ac scale below about 45 Hz or above about 1 kHz, although this range can be considerably better in some cases. A VOM can measure ac waveforms over a much larger range—up to 100 kHz.

The ohms function (used for resistance measurements) is used only in circuits that are *not* powered. An ohmmeter works by inserting a small test voltage into a circuit and measuring the resulting current flow. Consequently, if any voltage is present, the reading will be in error. The meter will show the resistance of all possible paths between the probes. If you want to know the resistance of a single component, it is necessary to isolate that component from the remainder of the circuit by disconnecting one end. In addition, body resistance can affect the reading if you are holding the conducting portion of both probes in your fingers. This procedure should be avoided, particularly with high resistances.

The Function Generator

The basic function generator is used to produce sine, square, and triangle waveforms and may also have a pulse output for testing digital logic circuits. Function generators normally have a knob or pushbuttons with a label or picture showing the various waveforms that you can select and other controls to adjust the amplitude and dc level. The peak-to-peak voltage is adjusted by the AMPLITUDE control. The dc level is adjusted by a control labeled DC OFFSET; this enables you to add or subtract a dc component to the waveform. (Some function generators have a disable switch on the dc offset control.) The AMPLITUDE and DC OFFSET controls are frequently not calibrated, so amplitude and dc level settings need to be verified with an oscilloscope or multimeter.

The frequency is selected with a combination of a range switch and vernier control. The range is selected by a decade frequency switch or pushbuttons that enable you to select the frequency in decade increments (factors of ten) up to about 1 MHz. The vernier control is usually a multiplier dial for adjusting the precise frequency needed.

The output level of a function generator will drop from its open circuit voltage when it is connected to a circuit. Depending on the conditions, you generally will need to readjust the amplitude level of the generator after it is connected to the circuit. This is because there is

effectively an internal generator resistance (sometimes referred to as the output resistance) that will affect the circuit under test. You can measure this resistance indirectly as described in Experiment 12, For Further Investigation. Common values of the output resistance are 50 Ω and 600 Ω .

Higher-priced instruments will add features such as trigger or sync outputs to use in synchronizing an oscilloscope, modulation, increased frequency ranges, fixed attenuators on the output, and so forth. Fixed attenuators are handy if you want to reduce the output by an exact amount or you want to choose a very small, but known signal. Some function generators have a SYMMETRY or DUTY CYCLE control that allows you to control the pulse width of the rectangular pulse. Details of the particular features of your function generator and the controls can be found in the operator's manual.

The Oscilloscope

An oscilloscope is the most versatile general-purpose measuring instrument, letting you "see" a graph of the voltage as a function of time in a circuit. Many circuits have specific timing requirements or phase relationships that can be readily measured with a two-channel oscilloscope. The voltage to be measured is converted into a visible display by a cathode-ray tube (CRT), a vacuum device similar to a television picture tube.

The oscilloscope contains four functional blocks as illustrated in Figure 15-1. The input signal is connected to the **vertical** section, which can be set to attenuate or amplify the input signal to provide the proper voltage level to the vertical deflection plates of the CRT. The **trigger** section samples the input waveform and sends a synchronizing trigger signal at the proper time to the horizontal section. The trigger occurs at the same relative time to superimpose each succeeding trace on the previous trace. This action causes the signal to appear to stop allowing you to examine the signal. The **horizontal** section contains the time-base (or *sweep*) generator, which produces a linear ramp, or "sawtooth" waveform, that controls the rate the beam moves across the screen. The horizontal position of the beam is proportional to the time that elapsed from the start of the sweep, allowing the horizontal axis to be calibrated in units of time. For this reason, the horizontal section is often called the time base. The output of the horizontal section is applied to the horizontal deflection plates of the CRT. Finally, the **display** section contains the CRT and beam controls. It enables the user to obtain a sharp presentation with the proper intensity. The display section frequently contains other features. Sometimes, the user can lose the displayed waveform by accidentally positioning it offscreen. One common feature in the display section is a beam-finder button, which enables the user to quickly locate the position of the trace. Controls for each of the functional blocks are usually grouped together. Frequently, there are color clues to help you identify groups of controls. Details of these controls are explained in the operator's manual for the oscilloscope; however, a brief description of frequently used controls is given in the following paragraphs.

Display Controls

The display system contains controls for adjusting the electron beam. FOCUS and INTENSITY controls are adjusted for a comfortable viewing level with a sharp focus. The display section may also contain the BEAM FINDER, a control which is used in combination with the horizontal and vertical POSITION controls to bring the trace on the screen. Another control over the beam intensity is the z-axis input. A control voltage on the z-axis input can

be used to turn on or off the beam or adjust the brightness. Some oscilloscopes also include the TRACE ROTATION control in the display section. TRACE ROTATION is used to align the sweep with a horizontal graticule line. This control is usually adjusted with a screwdriver to avoid accidental adjustment.

Vertical Controls

The vertical controls include the VOLTS/DIV (vertical sensitivity) control and its vernier, the input COUPLING switch, and the vertical POSITION control. Dual-trace and multiple-channel oscilloscopes will have a duplicate set of these controls for each channel and various switches for selecting channels or other vertical operating modes. The vertical input is connected through a selectable attenuator to a high input impedance dc amplifier. The VOLTS/DIV control selects a combination of attenuation and gain to determine the vertical sensitivity of the scope. For example, a low-level signal will need more gain and less attenuation than a higher level signal. The vertical sensitivity is adjusted in fixed VOLTS/DIV increments to allow the user to make calibrated voltage measurements. In addition, a concentric vernier control is usually provided to allow a continuous range of sensitivity. This knob must be in the detent (calibrated) position to make voltage measurements. The detent position can be felt by the user as the knob is turned because the knob tends to “lock” in the detent position. Some oscilloscopes have a warning light or message when the vernier is not in its detent position.

The input coupling switch is a multiple-position switch that can be set for AC, GND, or DC and sometimes includes a 50 Ω position. The GND position of the switch internally disconnects the signal from the scope and grounds the input amplifier. This position is useful if you want to set a ground reference level on the screen for measuring the dc component of a waveform. The AC and DC positions are high impedance inputs—typically 1 M Ω shunted by 15 pF of capacitance. High impedance inputs are useful for general probing at frequencies below about 1 MHz. At higher frequencies, the shunt capacitance can load the signal source excessively, causing measurement error. Attenuating divider probes are good for high-frequency probing because they have very high impedance (typically 10 M Ω) with very low shunt capacitance (as low as 2.5 pF).

The AC position of the coupling switch inserts a series capacitor before the input attenuator, causing dc components of the signal to be blocked. This position is useful if you want to measure a small ac signal riding on top of a large dc signal—for example, power supply ripple. The DC position is used when you want to view *both* the ac and dc components of a signal. This position is best when viewing digital signals as the input RC circuit forms a differentiating network. The AC position can distort the digital waveform because of this differentiating circuit. The 50 Ω position places an accurate 50 Ω load to ground. This position provides the proper termination for probing in 50 Ω systems and reduces the effect of a variable load which can occur in high impedance termination. The effect of source loading *must* be taken into account when using a 50 Ω input. It is important not to overload the 50 Ω input as the resistor is normally rated for only 2 W—implying a maximum of 10 V_{rms} of signal can be applied to the input.

The vertical POSITION control varies the dc voltage on the vertical deflection plates, allowing you to position the trace anywhere on the screen. Each channel has its own vertical POSITION control, enabling you to separate the two channels on the screen. You can use

vertical POSITION when the coupling switch is in the GND position to set an arbitrary level on the screen as ground reference.

Some oscilloscopes also have a vertical magnifier. The magnifier increases the scope sensitivity by providing more gain to the input signal but at the expense of the overall bandwidth. The vertical magnifier is useful for measuring very low level signals that are not bandwidth limited.

Horizontal Controls

The horizontal controls include the SEC/DIV control and its vernier, the horizontal magnifier, and the horizontal POSITION control. In addition, the horizontal section may include delayed sweep controls. The SEC/DIV control sets the sweep speed, which controls how fast the electron beam is moved across the screen. The control has a number of calibrated positions divided into steps of multiples of 1, 2, or 5, which allow you to set the exact time interval that you view the input signal. For example, if the graticule has 10 horizontal divisions and the SEC/DIV control is set to 1.0 ms/div, then the screen will show a total time of 10 ms. The SEC/DIV control usually has a concentric vernier control that allows you to adjust the sweep speed continuously between the calibrated steps. This control must be in the detent position in order to make calibrated time measurements. Many scopes are also equipped with a horizontal magnifier that affects the time base. The magnifier increases the sweep time by the magnification factor, giving you increased resolution of signal details. Any portion of the original sweep can be viewed using the horizontal POSITION control in conjunction with the magnifier. This control actually speeds the sweep time by the magnification factor and therefore affects the calibration of the time base set on the SEC/DIV control. For example, if you are using a 10X magnifier, the SEC/DIV dial setting must be *divided* by 10.

Trigger Controls

The trigger section is the source of most operator problems when using an oscilloscope. These controls determine the proper time for the sweep to begin in order to produce a stable display. The trigger controls include the MODE switch, SOURCE switch, trigger LEVEL, SLOPE, COUPLING, and variable HOLDOFF controls. In addition, the trigger section includes a connector for applying an EXTERNAL trigger to start the sweep. Trigger controls may include HIGH or LOW FREQUENCY REJECT switches and BANDWIDTH LIMITING.

The MODE switch is a multiple-position switch that selects either AUTO or NORMAL (sometimes called TRIGGERED) and may have other positions such as TV or SINGLE sweep. In the AUTO position, the trigger generator selects an internal oscillator that will trigger the sweep generator as long as no other trigger is available. This mode ensures that a sweep will occur even in the absence of a signal because the trigger circuits will “free-run” in this mode. This allows you to obtain a baseline for adjusting ground reference level or for adjusting the display controls. In the NORMAL or TRIGGERED mode, a trigger is generated from one of three sources selected by the SOURCE switch—the INTERNAL signal, an EXTERNAL trigger source, or the ac LINE. If you are using the internal signal to obtain a trigger, the normal mode will only provide a trigger if a signal is present and other trigger conditions (level, slope) are met. This mode is more versatile than AUTO as it can provide stable triggering for very low to very high frequency signals. The TV position is used

for synchronizing either TV fields or lines and SINGLE is used primarily for photographing the display.

The trigger LEVEL and SLOPE controls are used to select a specific point on either the rising or falling edge of the input signal for generating a trigger. The trigger SLOPE control determines which edge will generate a trigger, whereas the LEVEL control allows the user to determine the voltage level on the input signal which will start the sweep circuits.

The SOURCE switch selects the trigger source—either the INTERNAL signal, an EXTERNAL trigger source, or the ac LINE. In the INTERNAL position, a sample of the signal being viewed is used to start the sweep. Some multiple-channel scopes allow you to choose the triggering channel or use some combination of channels for triggering. In the EXTERNAL position, a time-related external signal is used for triggering. Trigger attenuation (divide by 10) is provided on many oscilloscopes. Attenuate large external triggers in order to extend the range of the trigger level control. The external trigger can be coupled with either ac or dc coupling. Couple the trigger signal with ac coupling if the trigger signal is riding on a dc voltage. Use dc coupling if the triggers occur at a frequency of less than about 20 Hz. The LINE position causes the trigger to be derived from the ac power source. This synchronizes the sweep with signals that are related to the power line frequency.

The variable HOLDOFF control allows you to exclude otherwise valid triggers until the holdoff time has elapsed. For some signals, particularly complex waveforms or digital pulse trains, obtaining a stable trigger can be a problem. This can occur when one or more valid trigger points occur before the signal repetition time. If every event that the trigger circuits qualified as a trigger were allowed to start a sweep, the display could appear to be unsynchronized. By adjusting the variable HOLDOFF control, the trigger point can be made to coincide with the signal repetition point.

Occasionally, a trigger signal contains interfering high- or-low frequency components. When this happens, the trace may flutter back and forth on the screen or produce the appearance of unsynchronized sweeps. A high-frequency component can be removed using HIGH FREQUENCY REJECT. Sometimes it is necessary to observe a high-frequency signal in the presence of a low-frequency signal, such as might occur in measuring a low-level transducer signal. In this case, LOW FREQUENCY REJECT can remove the low-level interference from the trigger signal.

Dual-Channel Oscilloscopes

Most oscilloscopes have two (or in some cases more) separate channels and controls to view more than one signal at a time. There are two types of dual-channel oscilloscope—dual beam and dual trace. A dual-beam oscilloscope has two independent beams in the CRT and independent vertical deflection systems allowing both signals to be viewed at the same time. A dual-trace oscilloscope has only one beam and one deflection system; it uses electronic switching to show the two signals. Dual-beam oscilloscopes are generally restricted to high-performance research instruments and are much more expensive than dual-trace oscilloscopes.

A dual-trace oscilloscope has user controls labeled CHOP or ALTERNATE to switch the beam between the channels so that the signals appear to occur simultaneously. The CHOP mode rapidly switches the beam between the two channels at a fixed high-speed rate so that the two channels appear to be displayed at the same time. The ALTERNATE mode first completes the sweep for one of the channels, then displays the other channel on the next

(or *alternate*) sweep. When viewing slow signals, the CHOP mode is best because it reduces the flicker that would otherwise be observed. High-speed signals usually can be best observed in ALTERNATE mode to avoid seeing the chop frequency.

Another feature on most dual-trace oscilloscopes is the ability to show the algebraic sum and difference of the two channels. For most measurements, you should have the vertical sensitivity (VOLTS/DIV) on the same setting for both channels. You can use the algebraic sum if you want to compare the balance on push-pull amplifiers, for example. Each amplifier should have identical out-of-phase signals. When they are added, the resulting display should be a straight line indicating balance. You can use the algebraic difference when you want to measure the waveform across an ungrounded component. The probes are connected across the ungrounded component with probe ground connected to circuit ground. Again, the vertical sensitivity (VOLTS/DIV) setting should be the same for each channel. The display will show the algebraic difference in the two signals. The algebraic difference mode also allows you to cancel any unwanted signal that is equal in amplitude and phase and is common to both channels.

Dual-trace oscilloscopes usually have an X-Y mode, which causes one of the channels to be graphed on the x -axis and the other channel to be graphed on the y -axis. This is necessary if you want to change the oscilloscope baseline to represent a quantity other than time. Applications include viewing a transfer characteristic (output voltage as a function of input voltage), measuring swept frequencies, or showing Lissajous figures for phase measurements. Lissajous figures are patterns formed when sinusoidal waves drive both channels and are described in Experiment 25, For Further Investigation.

Probes

Signals should always be coupled into the oscilloscope through a probe. A probe is used to pick off a signal and couple it to the oscilloscope. It reduces the loading effect on circuits. Probes also have a short ground lead that should be connected to a nearby circuit ground point to avoid oscillation and power line interference. The ground lead makes a mechanical connection to the test circuit and passes the signal through a flexible, shielded cable to the oscilloscope. The shielding helps protect the signal from external noise pickup. In addition, the probe can extend the oscilloscope's measuring ability by reducing the effects of circuit loading and extending the amplitude capability of the scope. Oscilloscope probes are provided with the instrument as part of the system. *The wrong probe, or one that is not adjusted properly, can affect the measurement to the point of making it worthless or misleading.*

Begin any session with the oscilloscope by checking the probe compensation on each channel. Adjust the probe for a flat-topped square wave while observing the scope's calibrator output. This is a good signal to check the focus and intensity and verify trace alignment. Check the front panel controls for the type of measurement you are going to make. Normally, the variable controls (VOLTS/DIV and SEC/DIV) should be in the calibrated (detent) position. The vertical coupling switch is usually placed in the DC position unless the waveform in which you are interested has a large dc offset. Trigger holdoff should be in the minimum position unless it is necessary to delay the trigger to obtain a stable sweep.

1 Metric Prefixes, Scientific Notation, and Graphing

Name _____
Date _____
Class _____

Reading:

Floyd Sections 1-1 through 1-5

Objectives:

After performing this experiment, you will be able to:

1. Convert standard form numbers to scientific and engineering notation.
2. Measure quantities using a metric prefix.
3. Prepare a linear graph and plot a family of curves on the graph.

Summary of Theory:

The basic electrical quantities encompass a very large range of numbers—from the very large to the very small. For example, the frequency of an FM radio station can be over 100 million hertz (Hz), and a capacitor can have a value of 10 billionths of a farad (F). To express very large and very small numbers, scientific (powers of ten) notation and metric prefixes are used. Metric prefixes are based on the decimal system and stand for powers of ten. They are widely used to indicate a multiple or submultiple of a measuring unit.

Scientific notation is a means of writing any quantity as a number between 1 and 10 times a power of 10. The power of 10 is called the exponent. It simply shows how many places the decimal place must be shifted to express the number in its standard form. If the exponent is positive, the decimal place must be shifted to the right to write the number in standard form. If the exponent is negative, the decimal place must be shifted to the left. Note that $10^0 = 1$, so an exponent of zero does not change the original number.

Exponents that are a multiple of 3 are much more widely used in electronics work than exponents which are not multiples of 3. Numbers expressed with an exponent that is a multiple of 3 are said to be expressed in **engineering notation**. Engineering notation is particularly useful in electronics work because of its relationship to the most widely used metric prefixes. Some examples of numbers written in standard form, scientific notation, and engineering notation are shown in Table 1-1.

Table 1-1

Standard Form	Scientific Notation	Engineering Notation
12,300	1.23×10^4	12.3×10^3
506	5.06×10^2	0.506×10^3
8.81	8.81×10^0	8.81×10^0
0.0326	3.26×10^{-2}	32.6×10^{-3}
0.000 155	1.55×10^{-4}	155×10^{-6}

Numbers expressed in engineering notation can be simplified by using metric prefixes to indicate the appropriate power of ten. In addition, prefixes can simplify calculations. You

can perform arithmetic operations on the significant figures of a problem and determine the answers prefix from those used in the problem. For example, $4.7 \text{ k}\Omega + 1.5 \text{ k}\Omega = 6.2 \text{ k}\Omega$. The common metric prefixes used in electronics and their abbreviations are shown in Table 1-2. The metric prefixes representing engineering notation are shown. Any number can be converted from one prefix to another (or no prefix) using the table. Write the number to be converted on the line with the decimal under the metric prefix that appears with the number. The decimal place is then moved directly under any other line, and the metric prefix immediately above the line is used. The number can also be read in engineering notation by using the power of ten shown immediately above the line.

Table 1-2

Power of 10:	10^9	10^6	10^3	10^0	10^{-3}	10^{-6}	10^{-9}	10^{-12}
Metric symbol:	G	M	k		m	μ	n	p
Metric prefix:	giga	mega	kilo		milli	micro	nano	pico
	0	000	000	000	.000	000	000	000

Example 1:

Convert 12,300,000 to a number with a metric prefix:

Metric prefix:	giga	mega	kilo		milli	micro	nano	pico
	0	000	000	000	.000	000	000	000
		12	300	000	.			

= 12.3 M

Example 2:

Change 10,000 pF to a number with a μ prefix:

Metric prefix:	giga	mega	kilo		milli	micro	nano	pico
	0	000	000	000	.000	000	000	000
							10	000

.010 μ F

The introduction in 1972 of the HP-35 scientific calculator by Hewlett-Packard revolutionized scientific calculations. It had a number of scientific functions including the ability to enter numbers written in scientific notation. On the HP-35, a key labeled EEX was used to enter the exponent portion of a number written in scientific notation. A similar key is used on all scientific calculators. In addition, scientific calculators can perform trig functions, logarithms, roots, and other math functions. To enter numbers in a scientific calculator in scientific notation, the base number (called the *mantissa*) is first entered. If the number is

negative, the +/- key is pressed. Next the exponent is entered by pressing the EE (or EXP) key followed by the *power* of ten.¹ If the exponent is negative, the +/- key is pressed. Arithmetic can be done on the calculator with numbers in scientific notation mixed with numbers in standard form.

For any experimental work to be useful, it must be documented. Results should be clearly presented. Frequently, the best way to present results from an experiment is to plot it on a graph. This enables the reader to quickly see the relationship between the variables. In this experiment, you will prepare graphs of data. Before proceeding, review the section in the *Introduction to the Student* on graphing.

Materials Needed:

Scientific calculator

Metric ruler

Procedure:

1. Many of the dials and controls of laboratory instruments are labeled with metric prefixes. Check the controls on instruments at your lab station for metric prefixes. For example, check the SEC/DIV control on your oscilloscope. This control usually has more than one metric prefix associated with the switch positions. Meters are also frequently marked with metric prefixes. Look for others and list the instrument, control, metric prefix and its meaning in Table 1–3. The first line of Table 1–3 has been completed as an example.

Table 1–3

Instrument	Control	Metric Unit	Meaning
Oscilloscope	SEC/DIV	ms	10^{-3} s

2. The actual sizes of several electronic components are shown in Figure 1–1. Measure the quantities shown with a bold letter using a metric ruler. Report in Table 1–4 the length in millimeters of each lettered quantity. Then rewrite the measured length as the equivalent length in meters and record your results in Table 1–4. The first line of the table has been completed as an example.

¹Note that when you are entering numbers in scientific notation, it is not necessary to enter the base ten, only the exponent.

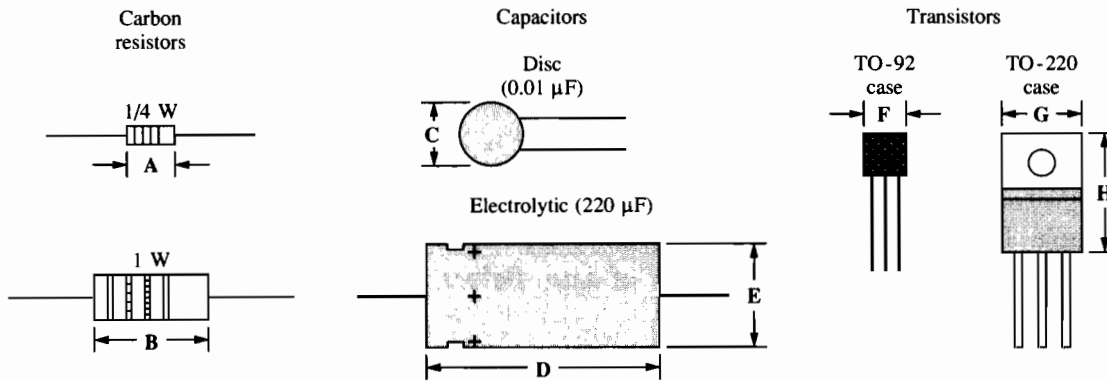


Figure 1-1

Table 1-4

Dimension	Length in Millimeters	Length in Meters
A	6.4 mm	6.4×10^{-3} m
B		
C		
D		
E		
F		
G		
H		

3. Rewrite the numbers in Table 1-5 of the report in scientific notation, engineering notation, and using one of the engineering metric prefixes. The first line has been completed as an example.
4. Convert the metric values listed in Table 1-6 to engineering notation. The first line has been completed as an example.

Table 1–5

Number	Scientific Notation	Engineering Notation	Metric Value
0.0829 V	8.29×10^{-2} V	82.9×10^{-3} V	82.9 mV
48,000 Hz			
2,200,000 Ω			
0.000 015 A			
7,500 W			
0.000 000 033 F			
270,000 Ω			
0.000 010 H			

Table 1–6

Metric Value	Engineering Notation
100 pF	100×10^{-12} F
12 kV	
85.0 μ A	
50 GHz	
33 k Ω	
250 mV	
7.8 ns	
2.0 M Ω	

5. Metric prefixes are useful for solving problems without having to key in the exponent on your calculator. For example, when a milli prefix (10^{-3}) is multiplied by a kilo prefix (10^{+3}), the metric prefixes cancel and the result has only the measuring unit. As you become proficient with these prefixes, math operations are simplified and fewer keystrokes are required in solving the problem with a calculator. To practice this, determine the metric prefix for the answer when each operation indicated in Table 1–7 is performed. The first line is shown as an example.

Table 1–7


Metric Unit in Operand	Mathematical Operation	Metric Unit in Operand	Metric Unit in Result
milli	multiplied by	milli	= micro
kilo	multiplied by	micro	=
nano	multiplied by	kilo	=
milli	multiplied by	mega	=
micro	divided by	nano	=
micro	divided by	pico	=
pico	divided by	pico	=
milli	divided by	mega	=

6. This step is to provide you with practice in graphing and in presenting data. Table 1–8 lists inductance data for 16 different coils wound on identical iron cores. There are three variables in this problem: the length of the coil (l) given in centimeters (cm), the number of turns, N , and the inductance, L , given in millihenries (mH). Since there are three variables, we will hold one constant and plot the data using the remaining two variables. This procedure shows how one variable relates to the other. Start by plotting the length (first column) as a function of inductance (last column) for coils that have 400 turns. Use Plot 1–1. The steps in preparing a graph are given in the *Introduction to the Student*.

Table 1-8 Inductance, L , of coils wound on identical iron cores (mH)

Length, l (cm)	Number of Turns, N			
	100	200	300	400
2.5	3.9	16.1	35.8	64.0
5.5	1.7	7.5	16.1	29.3
8.0	1.2	5.1	11.4	19.8
12.0	0.8	3.3	7.5	13.1

7. On the same plot, graph the data for the 300 turn coils, then the 200 and 100 turn coils. Use a different symbol for each set of data. The resulting graph is a family of curves that give a quick visual indication of the relationship among the three variables.

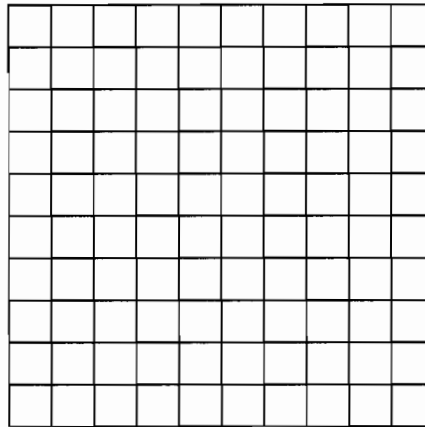

Plot 1-1

Conclusion:

Evaluation and Review Questions:

- For each metric prefix and unit shown, write the abbreviation of the metric prefix with the unit symbol:

(a) kilowatt	(d) nanosecond
(b) milliamperere	(e) megohm
(c) picofarad	(f) microhenry

2. Write the metric prefix and unit name for each of the abbreviations shown:

(a) MW

(d) mV

(b) nA

(e) k Ω

(c) μ J

(f) GHz

3. Using your calculator, perform the following operations:

(a) $(3.6 \times 10^4)(8.8 \times 10^{-4})$

(b) $(-4.0 \times 10^{-6})(2.7 \times 10^{-1})$

(c) $(-7.5 \times 10^2)(-2.5 \times 10^{-5})$

(d) $(56 \times 10^3)(9.0 \times 10^{-7})$

4. Using your calculator, perform the following operations:

(a) $\frac{(4.4 \times 10^9)}{(-7.0 \times 10^3)}$

(c) $\frac{(-2.0 \times 10^4)}{(-6.5 \times 10^{-6})}$

(b) $\frac{(3.1 \times 10^2)}{(41. \times 10^{-6})}$

(d) $\frac{(0.0033 \times 10^{-3})}{(-15 \times 10^{-2})}$

5. For each result in Question 4, write the answer as one with a metric prefix:

(a)

(c)


(b)

(d)

6. Summarize the steps in preparing a linear graph:

For Further Investigation:

In step 6, it is apparent that the data for the 100 turn coils is close to the x -coordinate, making it difficult to read on the same graph as the 400 turn data. A solution to this problem is to plot the data on a log-log plot. A logarithmic scale increases the resolution when data encompasses a large range of values. To help you get started, the axes have already been labeled and values assigned. Plot the data from Table 1–8 onto Plot 1–2. You should observe that each data set will plot a straight line. This result indicates the form of the equation which relates the variables is a power function.

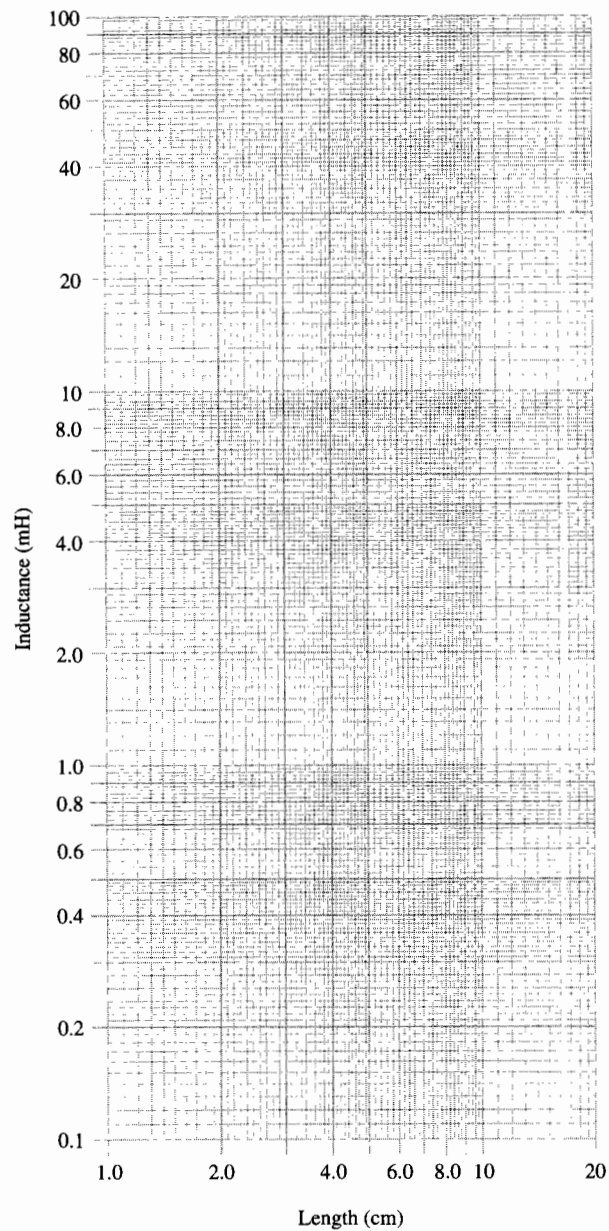

Plot 1–2

2 Laboratory Meters and Power Supply

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 1-1 through 1-5

Operator's Manual for Laboratory Multimeter and Power Supply

Objectives:

After performing this experiment, you will be able to:

1. Read analog meter scales including multiple and complex scales.
2. Operate the power supply at your lab station.
3. Explain the functions of the controls for the multimeter at your lab station. Use it to make a voltage reading.

Summary of Theory:

Electrical circuits contain a source of voltage and components connected in a manner to provide a path for current to flow. Components which do not amplify are called *passive* devices. Examples of passive devices are resistors, capacitors, inductors, and transformers.

Devices which have the ability to increase signal power are called *active* devices. Examples are the transistor and the integrated circuit. These devices usually require a very stable source of constant voltage. This voltage is called *dc* (for *direct current*) and is usually supplied by a regulated dc power supply. Regulated power supplies are circuits which convert ac line power into a constant output voltage in spite of changes to the input ac, the load current, or temperature.

The measurement of various electrical quantities is basic to determining circuit performance. These quantities include voltage, current, power, frequency, and many others. Many electrical quantities are measured with meters. The schematic symbol for a meter is shown in Figure 2-1. The meter function is shown on the schematic with a letter or symbol. One type of meter is the *multimeter*, an instrument which combines three basic instruments to measure either resistance, voltage, or current. Multimeters may be either *analog* or *digital* and may contain either active or passive circuitry. Analog multimeters use a pointer to indicate on a numbered scale the value of the measured quantity. One example of an analog meter is the VOM (for Volt-Ohm-Millammeter). A digital multimeter (or DMM) shows the measured quantity as a number. The digital multimeter is rapidly replacing analog multimeters because of superior performance and ease of use. Examples of a portable VOM and DMM are shown in Figure 2-2.



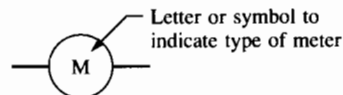


Figure 2-1 Meter Symbol

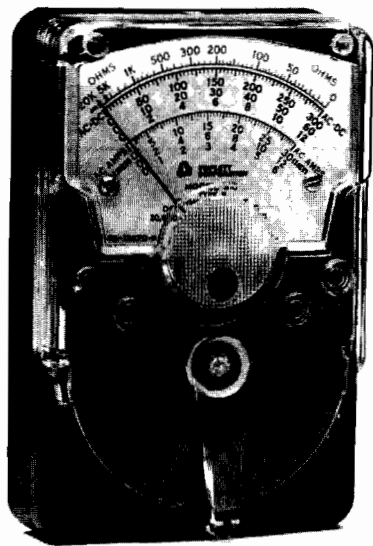


(a) VOM

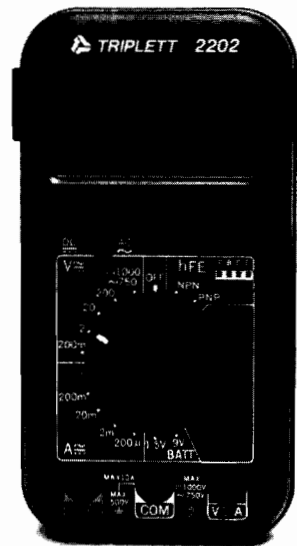

(b) DMM
(courtesy of Triplet Co.)

Figure 2-2

Electrical quantities extend from the very small to the very large. Resistance, for example, can vary from less than 1 Ω to over 1,000,000 Ω . Meters must have some means of accommodating these numbers. The position of the decimal place is determined by the *range* switch on the meter. The user selects an appropriate range to display the measured number. Some meters have **autoranging** which means they can change ranges automatically. An autoranging meter may also have an AUTO/HOLD switch which allows the meter to either operate in the autoranging mode or to hold the last range setting. To operate an autoranging meter, the meter will normally be used in the AUTO mode. The function to be measured is selected, and the meter is connected to the circuit under test. The user must be careful to connect the meter correctly for the measurement to be made. Examples of how to connect an autoranging DMM for measurement of voltage and resistance are shown in Figure 2-3.

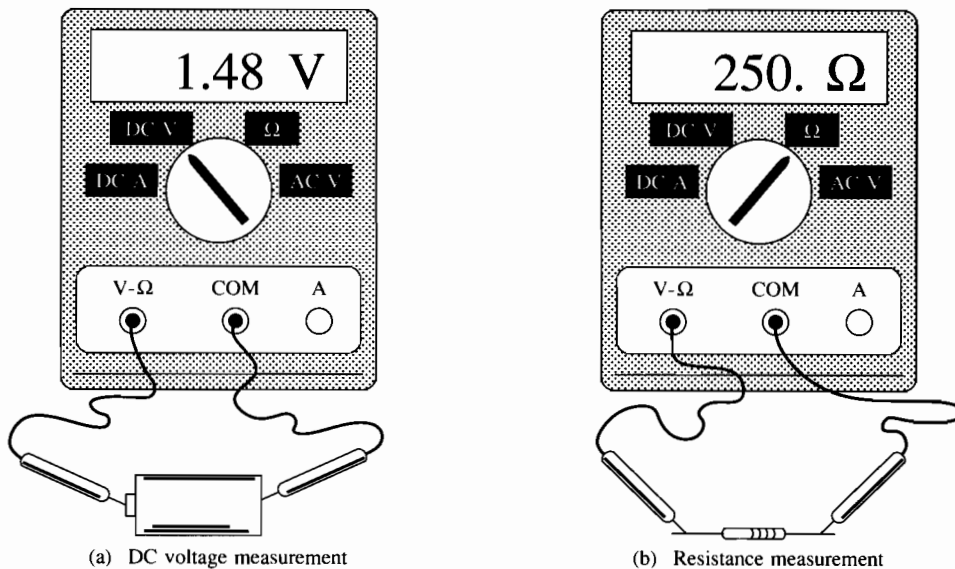

(a) DC voltage measurement

(b) Resistance measurement

Figure 2-3

Current measurements require special care to avoid damage to the meter. A *current meter must never be connected across a voltage source*. Current measurements are accomplished by selecting current (either ac or dc) with the function select switch and moving the probes to the AMPS socket. In this experiment, current will not be measured.

Many electronic measurements are made with analog meters. Analog meters can be calibrated to read almost any physical quantity, including voltage, current, power, or even nonelectrical quantities such as weight, speed, or light. The scales on analog meters may be either linear or nonlinear. They may have several scales on the same meter face. Various types of meters will be described in the Procedure section of this experiment.

Materials Needed:

None

Procedure:

1. A linear meter scale is marked in equally spaced divisions across the face of the meter. Figure 2-4 shows a linear meter scale. The major divisions, called *primary* divisions, are usually numbered. Between the primary divisions are smaller divisions called *secondary* divisions. To read this scale, note the number of secondary divisions between the numbered primary divisions and determine the value of each secondary division. The scale shown has 10 subdivisions.

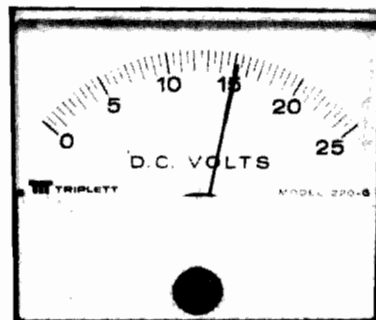


Figure 2-4

What is the value of each secondary division in Figure 2-4? _____

What is the meter reading? _____

2. Frequently a meter is used for several ranges. The meter shown in Figure 2–4 could, for example, have a 2.5 V full-scale range, a 25 V full-scale range, and a 250 V full-scale range. It is up to the user to then set the decimal place, depending on which range has been selected. If the user selects the 250 V full-scale range, then there are 50 V between each primary division.

If the meter shown in Figure 2–4 is on the 250 V range, what is the value of each secondary division? _____ What is the meter reading? _____

3. Usually, meters with more than one range have several scales called *multiple scales*. A meter with multiple scales is illustrated in Figure 2–5. Each scale can represent one or more ranges. In this case, the user must choose the appropriate scale *and* set the decimal place.

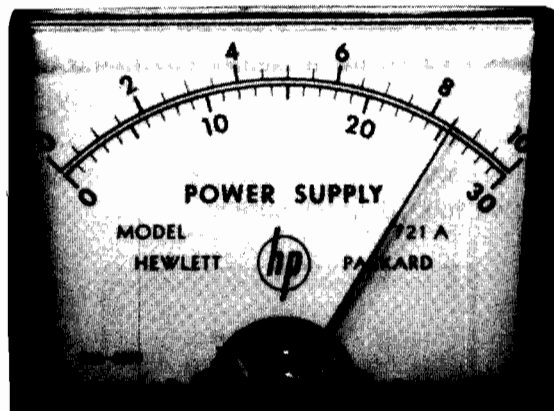


Figure 2–5

The top scale has a full-scale value of 10 V. This scale should be read if the 10 V range is selected. It is also used for any range which is a multiple of 10. For example, assume the meter shown has a 1.0 V range that has been selected. The user inserts a decimal and reads the top scale as 1.0 V full scale. The primary divisions are 0.2 V, and the secondary divisions are equal to 0.05 V. The reading on the meter is then interpreted as 0.85 V.

What is the meter reading if the range selected is the 30 V range? _____

4. VOMs and some instruments contain meters that can be used for more than one function. These scales are called *complex* scales. To read a complex scale the user chooses the appropriate scale based on the function *and* the range selected. Figure 2–6 shows a complex scale from a VOM.

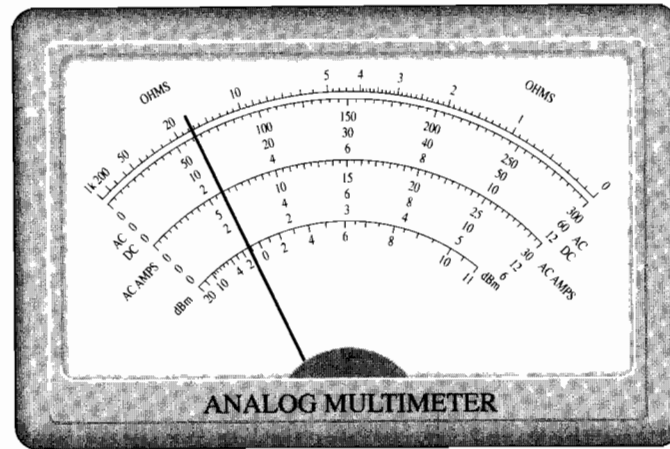


Figure 2–6

If the function selected is resistance, then the top scale is selected. This scale is nonlinear. Notice that the secondary divisions change values across the scale. To determine the reading, the primary divisions on each side of the pointer are noted. The secondary divisions can then be assigned values by counting the number of secondary divisions between the primary marks.

For the meter in Figure 2–6, assume the OHMS function is selected, and the range selected is $\times 10$ ohms. What does the meter indicate for a resistance? _____

5. Look at the meter on the power supply at your lab station. Some power supplies have meters that monitor either voltage or current. There may be more than one range or several supplies built into the same chassis, so the meter may have multiple or complex scales.

Is the meter used for more than one function? _____ If so, what determines which function is monitored? _____

Does the meter have multiple scales? _____ complex scales? _____

What is the smallest primary voltage division? _____ The smallest secondary voltage division? _____

6. Review the controls for the power supply at your lab station. The operator's manual is a good resource if you are not sure of the purpose of a control. Describe the features of your supply: (multiple outputs, current limiting, tracking, etc.)

7. In this step, you will set the power supply for a specific voltage and measure that voltage with your laboratory meter. Review the operator's manual for the DMM (or VOM) to your lab station. Review each control on the meter. Then select +DC and VOLTS on the DMM. If your DMM is not autoranging, select a range that will measure +5.0 V dc. The best choice is a range which is the *smallest* range that is larger than +5.0 V. Connect the test leads together and verify that the reading is zero. (Note: A digital meter may have a small digit in the least significant place.)

8. Turn on the power supply at your station and use the meter on the supply to set the output to +5.0 V. Then use the DMM to confirm that the setting is correct.

Reading on the power supply meter = _____ Reading on the DMM = _____

9. Set the output to +12.0 V and measure the output.

Reading on the power supply meter = _____ Reading on the DMM = _____

10. Set power supply to minimum setting and measure the output.

Reading on the power supply meter = _____ Reading on the DMM = _____

Conclusion:

Evaluation and Review Questions:

1. Compare the precision of the power supply voltmeter with the DMM or VOM at your lab station. Does one meter have an advantage for measuring 5.0 V? Explain your answer.

2. What is meant by an autoranging meter? What type is at your lab station?

3. What is the difference between a multiple scale and a complex scale?

4. What is the difference between a linear scale and a nonlinear scale?

5. Assume a scale has four secondary marks between the primary marks numbered 3.0 and 4.0. If the pointer is on the first secondary mark, what is the reading on the meter?

6. List the three basic measurements that can be made with a VOM or a DMM.

For Further Investigation:

The **sensitivity** of a panel meter is a number that describes how much current is required to obtain full-scale deflection from the meter. Meter sensitivity is easily determined with a *meter calibrator*. If you have a meter calibrator available, go over the operator's manual and learn how to measure the full-scale current in an inexpensive panel meter. Then obtain a small panel meter and measure its sensitivity. Summarize your results.

Checkup 1

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 1, and Buchla, Experiments 1 and 2

- The unit of electric current is:
(a) the volt (b) the coulomb (c) the henry (d) the ampere
- An excess of electrons in a material means that the material is:
(a) positively charged (b) negatively charged
- A meter that can be used to measure resistance is called:
(a) an ohmmeter (b) a wattmeter (c) an ammeter (d) an oscilloscope
- An ohmmeter can be damaged if:
(a) it is used in an energized circuit (c) leads are reversed
(b) it is used on the wrong range (d) it is used to measure a diode
- When using a multimeter to read an unknown voltage, you should start on the:
(a) lowest range (b) middle range (c) highest range
- The quantity $0.01 \mu\text{F}$ is the same as:
(a) 10,000 mF (b) 10,000 nF (c) 10,000 pF (d) none of these
- The number 505,000 can be expressed as:
(a) 0.505 M (b) 505 k (c) 505×10^3 (d) all of these
- The metric prefix milli multiplied by the prefix mega produces:
(a) kilo (b) milli (c) giga (d) micro
- One-fourth watt is the same as:
(a) 0.025 W (b) 250 mW (c) $250 \mu\text{W}$ (d) 2.50 W
- Engineering notation uses exponents that are multiples of:
(a) one (b) two (c) three (d) four
- What measurements can be made with a VOM?

12. Explain the difference between a primary division and a secondary division on an analog meter.
13. Why is it a good idea to check a power supply voltage setting with a laboratory meter rather than a panel meter on the supply?
14. List the unit of measurement for each:
- | | | |
|----------------|-----------------|---------------|
| (a) resistance | (b) capacitance | (c) frequency |
| (d) inductance | (e) voltage | (f) energy |
15. Show the symbol for each of the following measurement units:
- | | | |
|-----------|-------------|------------|
| (a) ohm | (b) farad | (c) watt |
| (d) hertz | (e) coulomb | (f) ampere |
16. Express the following numbers in scientific notation as a number between 1 and 10 times 10 to the appropriate power:
- | | | |
|---------------------------|------------------|-----------------------------|
| (a) 1050 | (b) 0.0575 | (c) 251×10^2 |
| (d) 89.0×10^{-5} | (e) 0.000 004 91 | (f) 0.0135×10^{-2} |
17. Express the following numbers in engineering notation:
- | | | |
|---------------------------|------------------------|------------------------------|
| (a) 0.00520 | (b) 59 200 | (c) 760×10^5 |
| (d) 19.0×10^{-4} | (e) 1.22×10^2 | (f) 0.0509×10^{-10} |
18. Change each quantity from scientific notation to a number with a metric prefix:
- | | |
|-----------------------------|--------------------------------|
| (a) 1.24×10^{-6} A | (b) 7.5×10^3 Ω |
| (c) 4.7×10^4 Hz | (d) 3.3×10^{-8} F |
| (e) 2.2×10^{-12} s | (f) 9.5×10^{-2} H |
19. Change each quantity as indicated:
- | | |
|-----------------------------|----------------------------|
| (a) 70 μ A to amps | (b) 50 MHz to hertz |
| (c) 0.010 μ F to farads | (d) 5.0 W to milliwatts |
| (e) 22 mV to volts | (f) 3300 pF to microfarads |
20. Perform the following additions. Express answers with three significant digits:
- | | |
|---|--|
| (a) $5.25 \times 10^3 + 4.97 \times 10^3$ | (b) $9.02 \times 10^4 + 1.66 \times 10^3$ |
| (c) $1.00 \times 10^{-2} + 2.25 \times 10^{-2}$ | (d) $4.15 \times 10^{-6} + 6.8 \times 10^{-7}$ |
| (e) $9.60 \times 10^{-5} + 1.95 \times 10^{-4}$ | (f) $8.79 \times 10^6 + 4.85 \times 10^7$ |

3 Measurement of Resistance

Name _____
 Date _____
 Class _____

Reading:

Floyd, Sections 2-1 through 2-5

Objectives:

After performing this experiment, you will be able to:

1. Determine the listed value of a resistor using the resistor color code.
2. Use the DMM (or VOM) to measure the value of a resistor.
3. Determine the percent difference between the measured and listed values of a resistor.
4. Measure the resistance of a potentiometer and explain its operation.



Summary of Theory:

Resistance is the opposition a substance offers to current flow. The unit for resistance is the *ohm*, symbolized with the Greek letter capital omega (Ω). A resistor is a component designed to have a specific resistance and wattage rating. Resistors limit current but, in doing so, produce heat. The physical size of a resistor is related to its ability to dissipate heat, *not* to its resistance. A physically large resistor can dissipate more heat than a small resistor, hence the larger one would have a higher wattage rating than the smaller one.

Resistors are either fixed (constant resistance) or variable. Fixed resistors are usually color coded with a four-band code that indicates the specific resistance and tolerance. Each color stands for a number, as described in Floyd's text and reprinted in Table 3-1 for convenience. Figure 3-1 shows how to read the resistance and tolerance of a four-band resistor.

Table 3-1

	Digit Color	
Resistance value, first three bands	0	Black
	1	Brown
	2	Red
	3	Orange
	4	Yellow
	5	Green
	6	Blue
	7	Violet
	8	Gray
	9	White
Tolerance, fourth band	5%	Gold
	10%	Silver
	20%	No band

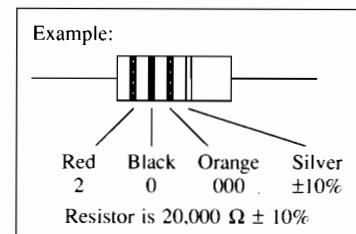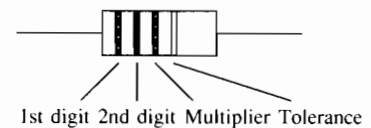

Note: In the multiplier band, Gold = X 0.1
 Silver = X 0.01

Figure 3-1

The resistance of resistors is measured using a DMM or VOM, as described in Experiment 2. If you are using a VOM, the zero reading should be checked whenever you change ranges on the meter by touching the test leads together. If you are using a nonautoranging DMM, a

suitable range needs to be selected. Resistance normally should not be measured in a circuit as other resistors in the circuit will affect the reading. The resistor to be measured is removed from the circuit, and the test leads are connected across the resistance. The resistor under test should not be held between the fingers as body resistance can affect the reading, particularly with high-value resistors. (It is okay to hold one end of the resistor under test.)

The most common form of variable resistor is the potentiometer. The potentiometer is a three-terminal device with the outer terminals having a fixed resistance between them and the center terminal connected to a moving wiper. The moving wiper is connected to a shaft that is used to vary the resistance between it and the outer terminals. Potentiometers are commonly found in applications such as volume controls.

Another type of variable resistor is the rheostat. A rheostat consists of two terminals. The control varies the resistance between the two terminals. A potentiometer can be connected as a rheostat by connecting the moving wiper and one of the outer terminals.

Materials Needed:

Resistors: Ten assorted values

One potentiometer (any value)

Procedure:

1. Obtain 10 four-band fixed resistors. Record the colors of each resistor in Table 3–2. Use the resistor color code to determine the color-code resistance of each resistor. Then measure the resistance of each resistor and record the measured value in Table 3–2. The first line has been completed as an example.
2. Compute the percent difference between the measured and color-coded values using the equation:

$$\% \text{ difference} = \frac{|R_{\text{measured}} - R_{\text{color code}}|}{R_{\text{color code}}} \times 100$$

The percent difference is shown as an absolute (positive) value for all resistors. Complete Table 3–2.

Table 3-2

Resistor	Color of Band				Color-Code Value	Measured Value	% Difference
	1st	2nd	3rd	4th			
0	brown	green	red	silver	1.5 kΩ ± 10%	1.46 kΩ	2.7%
1							
2							
3							
4							
5							
6							
7							
8							
9							
10							

3. Obtain a potentiometer. Number the terminals 1, 2, and 3 as illustrated in Figure 3-2.

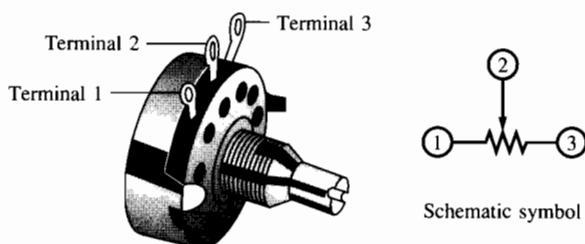


Figure 3-2

Measure and record the resistance between terminals 1 and 3 of the potentiometer (the outside terminals). $R_{1,3} =$ _____

Vary the potentiometer's shaft and monitor the resistance between terminals 1 and 3. Does the resistance change? _____ Explain: _____

4. Turn the potentiometer completely counterclockwise (CCW). Measure the resistance between terminals 1 and 2. Then measure the resistance between terminals 2 and 3. Record the measured resistance in Table 3-3. Compute the sum of the two readings and enter it into Table 3-3.
5. Turn the shaft 1/3 turn clockwise (CW) and repeat the measurements in step 4.
6. Turn the shaft 2/3 turn CW and repeat the measurements in step 4. What did you find about the sum of the resistance in steps 4, 5, and 6?

4 Voltage Measurement and Circuit Ground

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 2–6 and 2–7. (Optional: Additional information on circuit ground is found in Section 4–9.)

Objectives:

After performing this experiment, you will be able to:

1. Connect a circuit from a schematic diagram.
2. Use voltages measured with respect to ground to compute the voltage drop across a resistor.
3. Explain the meaning of circuit ground and subscripts used in voltage definitions.

Summary of Theory:

Energy is required to move a charge from a point of lower potential to one of higher potential. Voltage is a measure of this energy per charge. Energy is given up when a charge moves from a point of higher potential to one of lower potential.

Voltage is always measured with respect to some point in the circuit. For this reason, only potential *differences* have meaning. We can refer to the voltage *across* a component, in which case the reference is one side of the component. Alternatively, we can refer to the voltage at some point in the circuit. In this case the reference point is assumed to be “ground.” Circuit ground is usually called *reference ground* to differentiate it from the potential of the earth, which is called *earth ground*. Circuit or earth grounds are shown with the symbol used in Figure 4–1.

An analogy can clarify the meaning of reference ground. Assume a building has two floors below ground level. The floors in the building could be numbered from the ground floor, by numbering the lower floors with negative numbers. The reference for numbering the floors could be made the lowest floor in the basement. Then all floors would have a positive floor number. The choice of the numbering system does not change the height of the building, but it does change each floor number. Likewise, the ground reference is used in circuits as a point of reference for voltage measurements. The circuit is not changed by the ground reference chosen.

Figure 4–1 illustrates the same circuit with two different ground reference points.

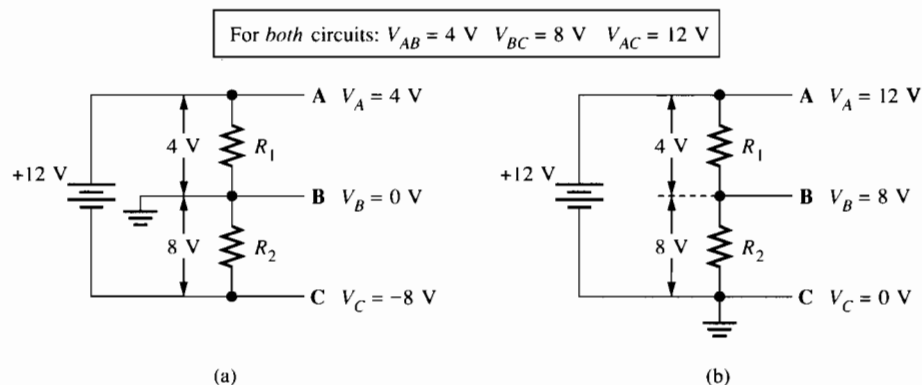


Figure 4–1

The circuit in Figure 4–1(a) has as its reference point **B**. Positive and negative voltages are shown. If the reference point is moved to point **C**, the circuit voltages are all positive, as shown in Figure 4–1(b). Voltage is always measured between two points. To define the two points, subscripts are used. The voltage difference (or simply voltage) between points **A** and **B** is written as V_{AB} where the second letter in the subscript identifies the reference point. If a single subscripted letter is shown, the voltage is defined between the lettered point and the circuit's reference ground.

Materials Needed:

Resistors:

One 330 Ω , one 680 Ω , and 1.0 k Ω

Procedure:

1. Measure three resistors with the listed values given in Table 4–1. Record the measured values in Table 4–1. You should always use the measured value in experimental work.

Table 4–1

Component	Listed Value	Measured Value
R_1	330 Ω	
R_2	680 Ω	
R_3	1.0 k Ω	

Table 4–2

	Measured Value
V_S	
V_{AB}	
V_{BC}	
V_{CD}	

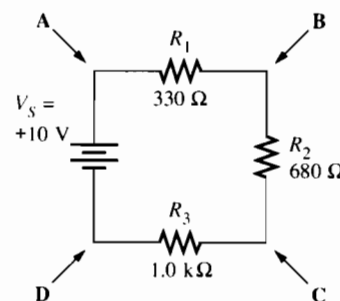


Figure 4–2

2. Construct the circuit shown in Figure 4–2. Set the power supply to +10 V. Measure the voltage across each resistor in the circuit. Enter the measured values in Table 4–2.
3. Assign point **D** as the reference ground. Measure the voltage at points **A**, **B**, and **C** with respect to point **D**. The voltage readings are made with the reference probe connected to point **D**. Enter the measured values in Table 4–3. Then use the measured voltages to compute the voltage differences V_{AB} , V_{BC} , and V_{CD} .

Table 4–3

	Measured Voltage	Voltage Difference Calculation
V_A		$V_{AB} = V_A - V_B =$
V_B		
V_C		
V_D	0.0 V (ref)	$V_{CD} = V_C - V_D =$

4. Now measure the voltages in the circuit with respect to point C. The circuit is *not changed*. Only the reference point changes. Move the reference probe of the voltmeter to point C. This point will now represent ground. The voltage at point D now has a negative value. Enter the measured voltages in Table 4-4. Compute the voltage differences as before and enter them in Table 4-4.

Table 4-4

	Measured Voltage	Voltage Difference Calculation
V_A		$V_{AB} = V_A - V_B =$
V_B		
V_C	0.0 V (ref)	$V_{BC} = V_B - V_C =$
V_D		$V_{CD} = V_C - V_D =$

5. Move the circuit reference point to point B. Again, there is no change to the circuit other than the reference ground. Repeat the measurements of the voltages with respect to circuit ground. Compute the voltage differences and enter the data in Table 4-5.

Table 4-5

	Measured Voltage	Voltage Difference Calculation
V_A		$V_{AB} = V_A - V_B =$
V_B	0.0 V (ref)	
V_C		$V_{BC} = V_B - V_C =$
V_D		$V_{CD} = V_C - V_D =$

6. Now make point A the reference point and repeat the measurements. Enter the data in Table 4-6.

Table 4-6

	Measured Voltage	Voltage Difference Calculation
V_A	0.0 V (ref)	$V_{AB} = V_A - V_B =$
V_B		
V_C		$V_{BC} = V_B - V_C =$
V_D		$V_{CD} = V_C - V_D =$

Conclusion:

Evaluation and Review Questions:

1. Compare the *voltage difference calculation* in Table 4–3 through Table 4–6. Does the circuit's reference point have any effect on the voltage differences across any of the resistors? Explain your answer.
2. Define the term *reference ground*.
3. If you measured V_{AB} as 12.0 V, what is the V_{BA} ?
4. Assume $V_M = -220$ V and $V_N = -150$ V. What is V_{MN} ?
5. If a test point in a circuit is marked +5.0 V and a second test point is marked -3.3 V, what voltage reading would you expect on a voltmeter connected between the two test points? Assume the reference lead on the meter is at the lowest potential.

For Further Investigation:

Warning: The power supplies used in this procedure must have floating output terminals. If you are not sure, check with your instructor before proceeding with this investigation.

Replace the +10 V supply used in this experiment with two +5 V supplies in series. Attach the +5 V output of one supply to the common of the second supply. Call this point the reference ground for the circuit. Measure the voltages throughout the circuit. Summarize your results.

Application Assignment 2

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 2, Section 2-8: Application Assignment

Step 1 Circuit choice and reason rejected circuits will not meet requirements:

Step 2 Wire list. (First item is given as an example.)

From	To
All lamps (pin #2)	Battery (- side)

Step 3 Fuse size selected is _____ A

Reason:

Step 4 Required battery capacity is _____ A-hr

Step 5 Test procedure for troubleshooting:

Possible faults:

Fault 1: All but one lamp can be turned on:

Fault 2: None of the lamps can be turned on:

Fault 3: Each lamp is too dim and cannot be brightened by adjusting the rheostat:

Fault 4: Each lamp is too dim; however, the amount of light can be varied with the rheostat but not to full brightness:

Related Experiment:

Materials Needed:

Six $330\ \Omega$ resistors

Six small light-emitting diodes (LEDs)

One $1\ \text{k}\Omega$ potentiometer

One 5 V power supply

Discussion:

The lamps required by Application Assignment 2 use 110 V. *It is unsafe to experiment with this voltage level*, so a low-voltage simulation can be used to verify your solution using a 5 V dc power supply. The lights you will use are called light-emitted diodes (LEDs), which use a small current to emit light. LEDs emit light only when the current flows in one direction. To limit the current to a level that is safe for the LEDs, a $330\ \Omega$ resistor is placed in series with each LED, as shown in Figure AA-2-1. The dimmer will consist of a $1\ \text{k}\Omega$ potentiometer. Be sure to check the polarity of the diodes—if they are installed backward, they will not light. A short jumper wire on your protoboard can serve as an open or closed switch to complete the circuit. Construct a working model of the application problem described in Floyd's text.

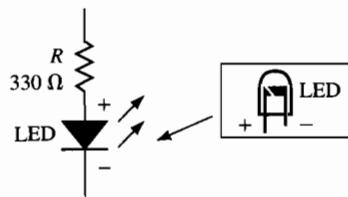


Figure AA-2-1

Checkup 2

Name _____

Date _____

Class _____

Reference:

Floyd, Chapter 2, and Buchla, Experiments 3 and 4

1. A material that is characterized by four valence electrons in its atomic structure is called:
(a) a conductor (b) an insulator (c) a semiconductor
2. The basic particle of matter that carries a negative electrical charge is the:
(a) atom (b) electron (c) proton (d) neutron
3. The unit of electrical charge is the:
(a) ampere (b) coulomb (c) joule (d) volt
4. One coulomb passing a point in one second is defined as one:
(a) ampere (b) watt (c) joule (d) volt
5. A joule per coulomb is a measure of:
(a) resistance (b) power (c) voltage (d) current
6. The unit of resistance is named in honor of:
(a) Joule (b) Watt (c) Ampere (d) Ohm
7. A resistor used to control current in a circuit is called a:
(a) circuit breaker (b) rheostat (c) potentiometer (d) choke
8. The purpose of the third band of a four-band resistor is:
(a) multiplier (b) tolerance (c) reliability (d) temperature
9. An instrument used for measuring resistance is:
(a) an ohmmeter (b) a voltmeter (c) an oscilloscope (d) an ammeter
10. In a circuit, a reference ground is always:
(a) the point with the lowest potential (b) a common point
(c) the same as earth ground (d) the negative side of the source
11. Assume a direct current of 2.0 A flows in a circuit due to electron flow. What is the number of electrons that pass a fixed point in the wire in 1 s?

12. A $5.6 \text{ k}\Omega$ resistor has a fourth band that is gold. What are the largest and smallest values of resistance that are within the tolerance rating for this resistor?
13. Calculate the minimum and maximum resistance for a $1000 \text{ }\Omega$ resistor with a tolerance of:
(a) 20% (c) 5%
(b) 10% (d) 1%
14. Determine the color-code value of resistance and the tolerance for each resistor:
(a) white-brown-red-silver:
(b) green-blue-green-gold:
(c) brown-black-black-gold:
(d) yellow-violet-orange-silver:
(e) green-brown-gold-gold:
15. Determine the color code for each of the following resistors:
(a) $470 \text{ k}\Omega \pm 10\%$
(b) $180 \text{ }\Omega \pm 5\%$
(c) $4.3 \text{ k}\Omega \pm 5\%$
(d) $1.0 \text{ }\Omega \pm 10\%$
(e) $2.7 \text{ M}\Omega \pm 5\%$
16. Explain how both positive and negative voltages can exist at the same time in a circuit but with only one voltage source.
17. Assume that a circuit contains three points labeled **A**, **B**, and **C**. Point **A** has a potential with respect to ground of 10.2 V ; point **B** has a potential of -12.4 V , and point **C** has a potential of -8.7 V . What is the potential difference between:
(a) point **A** with respect to point **B**?
(b) point **B** with respect to point **A**?
(c) point **A** with respect to point **C**?
(d) point **C** with respect to point **A**?
(e) point **B** with respect to point **C**?
(f) point **C** with respect to point **B**?
18. What is another word for potential difference?

5 Ohm's Law

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 3-1 and 3-2

Objectives:

After performing this experiment, you will be able to:

1. Measure the current-voltage curve for a resistor.
2. Construct a graph of the data from objective 1.
3. Given a graph of current-voltage for a resistor, determine the resistance.

Summary of Theory:

The flow of electrical charge in a circuit is called *current*. Current is measured in units of *amperes*, or amps for short. The ampere is defined as one coulomb of charge moving past a point in one second. Current is symbolized by the letter *I* (for *Intensity*) and is frequently shown with an arrow to indicate the direction of flow. Conventional current is defined as the direction a positive charge would move under the influence of an electric field. When electrons move, the direction is opposite to the direction defined for conventional current. To clarify the difference, the term *electron flow* is frequently applied to current in the opposite direction of conventional current flow. The experiments in this lab book work equally well with either definition.

The relationship between current and voltage is an important characteristic that defines various electronic devices. The relationship is frequently shown with a graph. Usually, the voltage is controlled (the independent variable), and the current is observed (the dependent variable). This is the basic method for this experiment, for which a series of resistors will be tested. As discussed in the *Introduction to the Student*, the independent variable is plotted along the *x*-axis and the dependent variable is plotted along the *y*-axis.

Fixed resistors have a straight-line or *linear* current-voltage curve. This linear relationship illustrates the basic relationship of Ohm's law—namely, that the current is proportional to the voltage for constant resistance. Ohm's law is the most important law of electronics. It is written in equation form as:

$$I = \frac{V}{R}$$

where *I* represents current, *V* represents voltage, and *R* represents resistance.

Materials Needed:

Resistors:

One 1.0 k Ω , one 1.5 k Ω , one 2.2 k Ω

One dc ammeter, 0–10 mA

For Further Investigation:

One 5 V zener diode

Procedure:

1. Measure three resistors with listed values of 1.0 kΩ, 1.5 kΩ, and 2.2 kΩ. Record the measured values in Table 5-1.

Table 5-1

Component	Listed Value	Measured Value
R_1	1.0 kΩ	
R_2	1.5 kΩ	
R_3	2.2 kΩ	

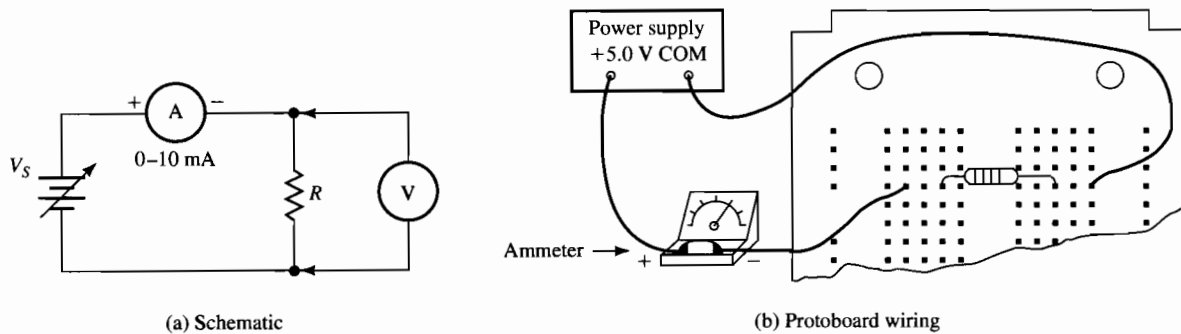


Figure 5-1

2. Connect the circuit shown in Figure 5-1(a). Notice that the ammeter is in series with the resistor and forms a single “loop” as shown in the protoboard wiring diagram in Figure 5-1(b). The voltmeter is then connected directly across the resistor.

Caution! Current meters can be easily damaged if they are incorrectly connected. Have your instructor check your connections before applying power.

3. Adjust the power supply for a voltage of 2.0 V. Read the current that is flowing through the resistor and record it in Table 5-2.
4. Adjust the power supply for 4.0 V and measure the current. Record the current in Table 5-2. Continue taking current readings for each of the voltages listed in Table 5-2.

Table 5-2 (R_1)

$V_s =$	2.0 V	4.0 V	6.0 V	8.0 V	10.0 V
$I =$					

5. Replace R_1 with R_2 and repeat steps 3 and 4. Record the data in Table 5-3.

Table 5-3 (R_2)


$V_s =$	2.0 V	4.0 V	6.0 V	8.0 V	10.0 V
$I =$					

6. Replace R_2 with R_3 and repeat steps 3 and 4. Record the data in Table 5-4.

Table 5-4 (R_3)

$V_s =$	2.0 V	4.0 V	6.0 V	8.0 V	10.0 V
$I =$					

7. On Plot 5-1, graph all three I - V curves using the data from Tables 5-2, 5-3, and 5-4. Plot the dependent variable (current) on the y -axis and the independent variable (voltage) on the x -axis. Choose a scale for the graph that spreads the data over the entire grid.

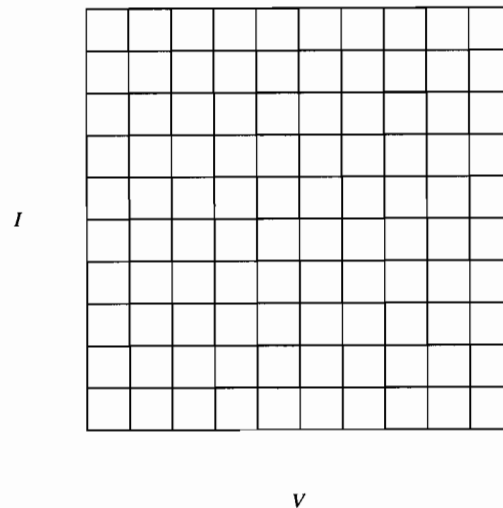


Plot 5-1

Conclusion:

Evaluation and Review Questions:

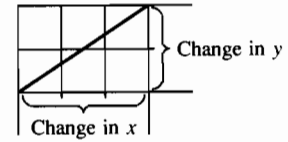1. The slope of a line is the change in the y direction divided by the change in the x direction. The definition for slope is illustrated in Figure 5–2. Find the slope for each resistor on Plot 5–1.



$$\begin{aligned}\text{Slope} &= \frac{\text{Change in } y}{\text{Change in } x} \\ &= \frac{2}{3}\end{aligned}$$

Figure 5–2

2. What happens to the slope of the I - V curve for larger resistors?
3. (a) If the resistance is halved and the voltage is not changed, what will happen to the current in a resistive circuit?
- (b) If the voltage is doubled and the resistance is not changed, what will happen to the current in a resistive circuit?
4. If the current in a resistive circuit is 24 mA and the applied voltage is 48 V, what is the resistance?
5. What current will flow through a 10Ω resistor with a 5.0 V applied?

For Further Investigation:

Not all devices have a linear current-voltage relationship. (This is what makes electronics interesting!) Investigate a zener diode I - V curve. The circuit is shown in Figure 5-3. The $1\text{ k}\Omega$ resistor is used to limit the total current in the circuit. Notice the polarity of the zener diode. The cathode is placed toward the positive side of the battery. Measure the voltage across the zener diode as the power supply is varied. The circuit is a series circuit so the zener current is the same as the current read by the ammeter. Record the voltage drop across the zener and the measured current in Table 5-5. Summarize your results with a graph of the *zener current* as a function of the *zener voltage*. (Zener diodes will be covered in Chapter 18 of the text.)


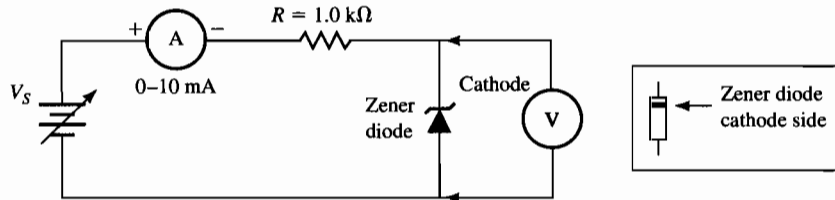


Figure 5-3

Table 5-5 (Zener Diode)

$V_s =$	2.0 V	4.0 V	6.0 V	8.0 V	10.0 V
$V_z =$					
$I_z =$					

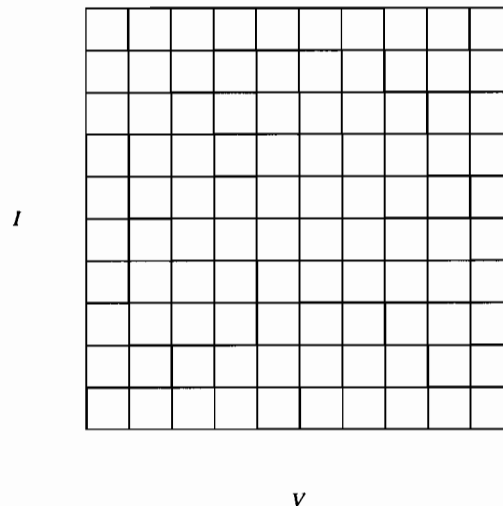

Plot 5-2

6 Power in DC Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 3-3 through 3-6

Objectives:

After performing this experiment, you will be able to:

1. Determine the power in a variable resistor at various settings of resistance.
2. Plot data for power as a function of resistance. From the plot, determine when maximum power is delivered to the variable resistor.

Summary of Theory:

When current flows through a resistor, electrical energy is converted into heat. Heat is then radiated from the resistor. The *rate* that heat is dissipated is called *power*. Power is measured in units of joules per second (J/s), which defines the unit called the watt (W). The power dissipated by a resistor is given by the power law equation:

$$P = IV$$

By applying Ohm's law to the power law equation, two more useful equations for power can be found. These are:

$$P = I^2R$$

and

$$P = \frac{V^2}{R}$$

The three power equations given above are also known as Watt's law. In this experiment, you will determine power using the last equation. Notice that if you measure the voltage in volts (V) and the resistance in kilohms (k Ω), the power will have units of milliwatts (mW).

The physical size of a resistor is related to the amount of heat it can dissipate. Therefore, larger resistors are rated for more power than smaller ones. Carbon composition resistors are available with standard power ratings ranging from 1/8 W to 2 W. For most typical low voltage applications (15 V or less and at least 1 k Ω of resistance), a 1/4 W resistor is satisfactory.

Materials Needed:

- One 2.7 k Ω resistor
- One 10 k Ω potentiometer

Procedure:

1. Measure the resistance of R_1 . The color-code value is 2.7 k Ω . $R_1 =$ _____
2. Construct the circuit shown in Figure 6–1. R_2 is a 10 k Ω potentiometer. Connect the center (variable) terminal to one of the outside terminals. Use this and the remaining terminal as a variable resistor. Adjust the potentiometer for 0.5 k Ω . (Always remove power when measuring resistance and make certain you are measuring only the potentiometer's resistance.)

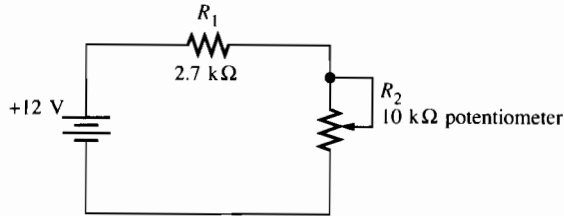


Figure 6–1

3. Measure the voltage across R_1 and the voltage across R_2 . Enter the measured voltages in Table 6–1. As a check, make sure that the sum of V_1 and V_2 is equal to 12.0 V. Then compute the power in R_2 using the equation:

$$P_2 = \frac{V_2^2}{R_2}$$


Enter the computed power, in milliwatts, in Table 6–1.

4. Disconnect the power supply and set R_2 to the next value shown in Table 6–1. Reconnect the power supply and repeat the measurements made in step 2. Continue in this manner for each of the resistance settings shown in Table 6–1.

Table 6–1

Variable Resistance Setting (R_2)	V_1 (measured)	V_2 (measured)	Power in R_2 : $P_2 = \frac{V_2^2}{R_2}$
0.5 k Ω			
1.0 k Ω			
2.0 k Ω			
3.0 k Ω			
4.0 k Ω			
5.0 k Ω			
7.5 k Ω			
10.0 k Ω			

5. Using the data in Table 6–1, graph the relationship of the power, P_2 , as a function of resistance R_2 on Plot 6–1. Since resistance is the independent variable, plot it along the x -axis and plot power along the y -axis. An *implied* data point can be plotted at the origin because there can be no power dissipated in R_2 without resistance. A smooth curve can then be drawn to the origin.

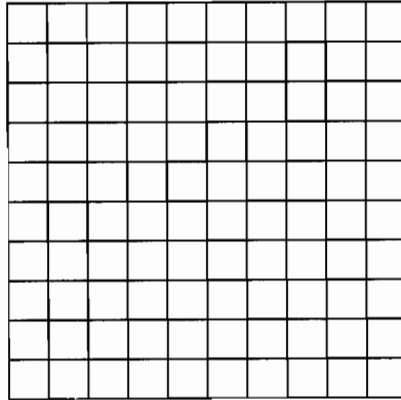

Plot 6–1

Conclusion:

Evaluation and Review Questions:

1. Observe the graph of resistance versus power for your experiment. Compare the resistance of R_1 and R_2 when power in R_2 is a maximum.
2. What was happening to the total current in the circuit as R_2 was increasing?

Application Assignment 3

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 3, Section 3–8: Application Assignment

Step 1 Inspection

Step 2 Draw the schematic of the existing resistor box. Label the resistors (R_1 through R_6).

Step 3 Modify the schematic for the resistor box to meet the new requirements. Label the resistors (R_1 through R_8) and give their power rating.

Step 4 Modify the Circuit. State the modifications that must be made.

Step 5 Test procedure:

Step 6 Troubleshooting:

Fault 1 (infinite resistance in switch position 3): _____

Fault 2 (infinite resistance in all switch positions): _____

Fault 3 (incorrect resistance in switch position 6): _____

Related Experiment:**Materials Needed:**

One LED

One resistor to be determined

Discussion:

As in the application problem, it is frequently necessary to compute the value of a current-limiting resistor. An LED must have a certain current to properly light but can be destroyed if the current is too high. Assume a current of 8 mA is required in an LED. The LED drops approximately 2 V, leaving 3 V across the dropping resistor. Determine resistance and power rating of the dropping resistor needed. Construct the circuit and verify with measurements that you have correctly calculated the dropping resistor.

Experimental Results:

Checkup 3

Reference:

Floyd, Chap. 3, and Buchla, Experiments 5 and 6

1. Ohm's law states the relationship between voltage, current, and:
(a) power (b) energy (c) resistance (d) time
2. In a given dc circuit, if the voltage were doubled and the resistance halved, the new current would be:
(a) one-fourth (b) one-half (c) unchanged (d) doubled (e) quadrupled
3. A fixed resistance is connected across a 10 V source. The current in the resistance is found to be $21.3 \mu\text{A}$. The value of the resistance is:
(a) $213 \mu\Omega$ (b) 213Ω (c) 470Ω (d) $0.470 \text{ M}\Omega$
4. A blue-gray-orange-gold resistor is connected across a 25 V source. The expected current in the resistor is:
(a) $368 \mu\text{A}$ (b) 368 mA (c) $1.7 \mu\text{A}$ (d) 1.7 mA
5. A 20 mV source is connected to a $100 \text{ k}\Omega$ load. The current in the load is:
(a) 200 nA (b) $200 \mu\text{A}$ (c) $5.0 \mu\text{A}$ (d) 5.0 mA
6. The rate at which energy is used is called:
(a) voltage (b) frequency (c) conductance (d) power
7. A megawatt is the same as:
(a) 10^{-6} W (b) 10^{-3} W (c) 10^3 W (d) 10^6 W
8. Electric utility companies charge customers for:
(a) voltage (b) current (c) power (d) energy
9. The SI unit of energy is the:
(a) joule (b) watt (c) ampere (d) kilowatt-hour
10. A 1500 W resistance heater is connected to a 115 V source. The current in the heater is:
(a) 77 mA (b) 8.8 A (c) 13 A (d) 19.6 A
11. An ammeter with an internal resistance of 0.5Ω measures a current of 10 A. What is the voltage dropped across the ammeter?

12. In Experiment 6, a fixed resistor was in series with a variable resistor. You plotted the resistance of the variable resistor as a function of the power dissipated in it.
- (a) What would you expect the graph to look like if the fixed resistor were a lower value?

 - (b) What would you expect to see if the resistance of the fixed resistor were zero?
13. A $100\ \Omega$ resistor is across a 20 V source.
- (a) Determine the current in the resistor.

 - (b) Compute the power dissipated in the resistor.
14. An insulator in a high-voltage application has a leakage current of $150\ \mu\text{A}$ when the voltage is 12 kV. Determine the insulation resistance.
15. A 10 W bulb is designed for use in a 12 V circuit.
- (a) What current is in the bulb when it is connected to a 12 V source?

 - (b) If the bulb were placed across a 6 V source, what power would it dissipate?

7 Series Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 4-1 through 4-6

Objectives:

After performing this experiment, you will be able to:

1. Use Ohm's law to find the current and voltages in a series circuit.
2. Apply Kirchoff's voltage law to a series circuit.

Summary of Theory

Consider the simple circuit illustrated in Figure 7-1. The source voltage is the total current multiplied by the total resistance as given by Ohm's law. This can be stated in equation form as:

$$V_S = I_T R_T$$

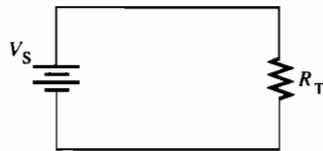


Figure 7-1

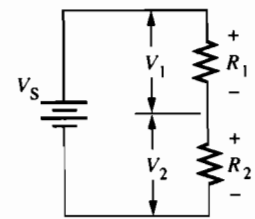


Figure 7-2

In a series circuit, the circuit elements are connected with only one path for current. For this reason, *the current is the same throughout a series circuit.*

Whenever we connect resistors in series, the total resistance increases. The total resistance of a series circuit is the sum of the individual resistors. Figure 7-2 illustrates a series circuit with two resistors. The total resistance is:

$$R_T = R_1 + R_2$$

Substituting this equation into Ohm's law for the total circuit gives:

$$V_S = I_T(R_1 + R_2)$$

Multiplying both terms by I_T results in:

$$V_S = I_T R_1 + I_T R_2$$

Since the identical current, I_T , must flow through each resistor, the voltage drops across the resistors can be found:

$$V_S = V_1 + V_2$$

This result illustrates that the source voltage is equal to the sum of the voltage drops across the resistors. This relationship is called Kirchhoff's voltage law, which is more precisely stated:

The algebraic sum of all voltage rises and drops around any single closed loop in a circuit is equal to zero.

It is important to pay attention to the polarity of the voltages. Current from the source creates a voltage drop across the resistors. The voltage drop across the resistors will have an opposite polarity to the source voltage as illustrated in Figure 7-2. We may apply Kirchhoff's voltage law by using the following rules:

1. Choose an arbitrary starting point. Go either clockwise or counterclockwise from the starting point.
2. For each voltage source or load, write down the first sign you see and the magnitude of the voltage.
3. When you arrive at the starting point, equate the algebraic sum of the voltages to zero.

Materials Needed:

Resistors:

One 330 Ω, one 1.0 kΩ, one 1.5 kΩ, one 2.2 kΩ

One dc ammeter, 0-10 mA

Procedure:

1. Obtain the resistors listed in Table 7-1. Measure each resistor and record the measured value in Table 7-1. Compute the total resistance for a series connection by adding the measured values. Enter the computed total resistance in Table 7-1 in the column for the listed value.
2. Connect the resistors in series as illustrated in Figure 7-3. Test various combinations of series resistors. Can you conclude that the total resistance of series resistors is the sum of the individual resistors? Then measure the total resistance of the series connection and verify that it agrees with your computed value. Enter your measured value in Table 7-1.

Table 7-1

Component	Listed Value	Measured Value
R_1	1.0 kΩ	
R_2	1.5 kΩ	
R_3	2.2 kΩ	
R_4	330 Ω	
$R_T =$		

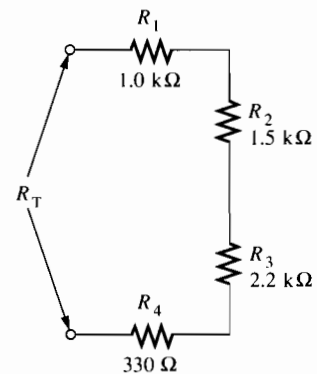


Figure 7-3

3. Complete the circuit shown in Figure 7-4. Be certain the ammeter is connected in *series*, otherwise damage to the meter may result. Before applying power, have your instructor check your circuit. Compute the current in the circuit by substituting the source voltage and the total resistance into Ohm's law. That is:

$$I_T = \frac{V_S}{R_T}$$

Record the computed current in Table 7-2. Apply power, and confirm that your computed current is within experimental uncertainty of the measured current.

Table 7-2

	Computed Value	Measured Value
I_T		
V_{AB}		
V_{BC}		
V_{CD}		
V_{DE}		

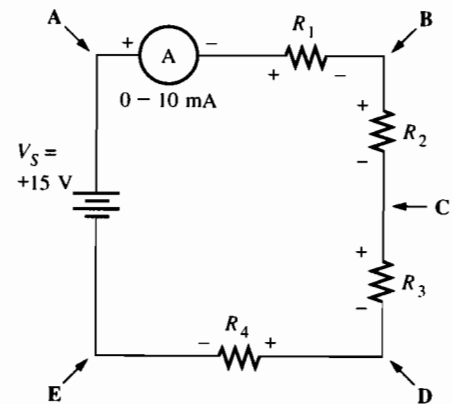


Figure 7-4

4. In a series circuit, the same current flows through all components. (Can you think of a simple proof of this?) You can use the total current measured in step 3 and Ohm's law to compute the voltage drop across each resistor. Compute V_{AB} by multiplying the total current in the circuit by the resistance between A and B. Record the results as the computed voltage in Table 7-2.
5. Repeat step 4 for the other voltages listed in Table 7-2.
6. Measure and record each of the voltages listed in Table 7-2.
7. Using the source voltage (+15 V) and the *measured voltage drops* listed in Table 7-2, prove that the algebraic sum of the voltages is zero. Do this by applying the rules listed in the Summary of Theory. The polarities of voltages are shown in Figure 7-4.
-
8. Repeat step 7 by starting at a different point in the circuit and traversing the circuit in the opposite direction.
-
9. Open the circuit at point B. Measure the voltage across the open circuit. Call this voltage V_{open} . Prove that Kirchhoff's voltage law is still valid for the open circuit.
-

Conclusion:

Evaluation and Review Questions:

1. Why doesn't the starting point for summing the voltages around a closed loop make any difference?
2. Kirchhoff's voltage law applies to any closed path, even one without current. How did the result of step 9 show that this is true?
3. Based on the result you observed in step 9, what voltage would you expect in a 110 V circuit across an open (blown) fuse?
4. Use Kirchhoff's voltage law to find V_x in Figure 7-5:

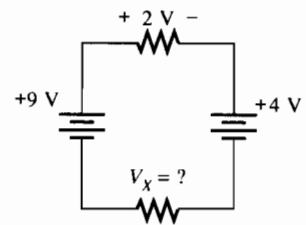


Figure 7-5

5. A 10Ω resistor is in series with a bulb and a 12 V source.
(a) If 8.0 V is across the bulb, what voltage is across the resistor?

(b) What is the current in the circuit?

(c) What is the resistance of the bulb?

For Further Investigation:

Resistors R_1 , R_2 , and R_3 used in this experiment have the same listed values as R_1 , R_2 , and R_3 from Experiment 5. Refer to your results of the current-voltage curve on Plot 1 of Experiment 5. Using the measured voltage in Table 7-2, find the current in the resistor based on Plot 5-1 of Experiment 5.

$$I_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}}$$

What observation did you make from this about the current in a series circuit?

8 The Voltage Divider

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 4-7 through 4-10

Objectives:

After performing this experiment, you will be able to:

1. Apply the voltage divider rule to series resistive circuits.
2. Design a voltage divider to meet a specific voltage output.
3. Confirm experimentally the circuit designed in step 2.
4. Determine the range of voltages available when a variable resistor is used in a voltage divider.

Summary of Theory:

A voltage divider consists of two or more resistors connected in series with a voltage source. Voltage dividers are used to obtain a smaller voltage from a larger source voltage. As you saw in Experiment 7, the voltage drops in a series circuit equal the source voltage. If you have two equal resistors in series, the voltage across each will be one-half of the source voltage. The voltage has thus been divided between the two resistors. The idea can be extended to circuits with more than two resistors and with different values.

Consider the series circuit illustrated in Figure 8-1. If the resistors are equal, the voltage across R_2 will be one-half the source voltage. But what happens if one of the resistors is larger than the other? Since both resistors must have the *same* current, Ohm's law tells us that the larger resistor must drop a larger voltage. In fact, the voltage across any resistor in a series circuit can be found by finding the *fraction* of the total resistance represented by the resistor in question. For example, if a series resistor represents one-third of the total resistance, the voltage across it will be one-third of the source voltage.

To find the voltage across R_2 , the ratio of R_2 to R_T is multiplied by the source voltage. That is:

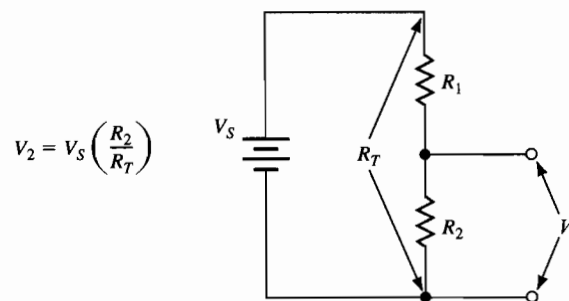


Figure 8-1

The voltage divider formula can be extended to find the voltage in a series circuit between any number of resistors. Call the resistance that is between the output terminals R_X . Then the voltage across this resistance can be written:

$$V_X = V_S \left(\frac{R_X}{R_T} \right)$$

where R_X represents the resistance between the output terminals.

This equation is a general form of the voltage divider equation. It can be stated as: “The output voltage from a voltage divider is equal to the input voltage multiplied by the ratio of the resistance between the output terminals to the total resistance.” When several resistors are used, the output is generally taken with respect to the ground reference for the divider as shown in Figure 8–2. In this case the output voltage can be found by substituting the value of R_2 and R_3 for R_X as shown.

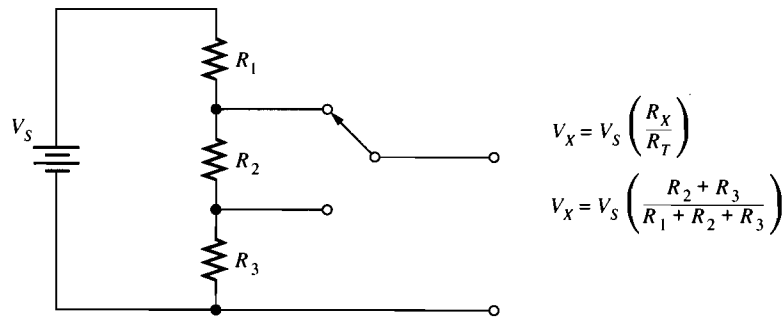


Figure 8–2

Voltage dividers can be made to obtain variable voltages by using a potentiometer. The full range of the input voltage is available at the output as illustrated in Figure 8–3(a). If one desires to limit the output voltage, this can be done by using fixed resistors in series as illustrated in Figure 8–3(b).

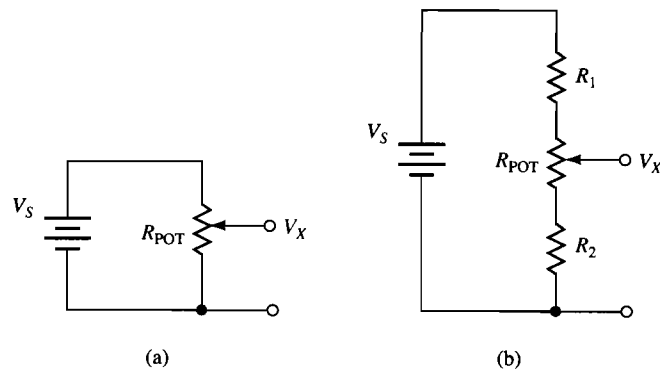


Figure 8–3

Materials Needed:

Resistors:

One 330 Ω , one 470 Ω , one 680 Ω , one 1.0 k Ω

One 1.0 k Ω potentiometer

Procedure:

1. Obtain the resistors listed in Table 8–1. Measure each resistor and record the measured value in Table 8–1, column 3. Compute the total resistance for a series

connection by adding the measured values. Enter the computed total resistance in Table 8-1.

2. Connect the resistors in the series circuit illustrated in Figure 8-4. With the power off, measure the total resistance of the series connection and verify that it agrees with your computed value.

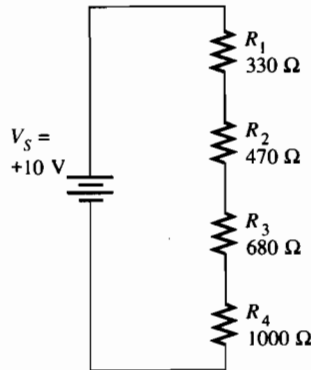


Figure 8-4



3. Apply the voltage divider rule to each resistor, one at a time, to compute the expected voltage across that resistor. Use the measured values of resistance and a source voltage of +10 V. Record the computed voltages (V_X) in Table 8-1, column 4.
4. Turn on the power and measure the voltage across each resistor. Record the measured voltage drops in Table 8-1, column 5. Your measured voltages should agree with your computed values.
5. Observe the voltages measured in step 4. In the space provided, draw the voltage divider, showing how you could obtain an output of 6.8 V.

Table 8-1

Resistor	Listed Value	Measured Value	$V_X = V_S \left(\frac{R_X}{R_T} \right)$	V_X (measured)
R_1	330 Ω			
R_2	470 Ω			
R_3	680 Ω			
R_4	1000 Ω			
Total			10.0 V	

Circuit for step 5

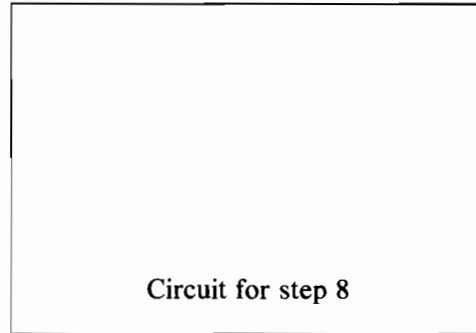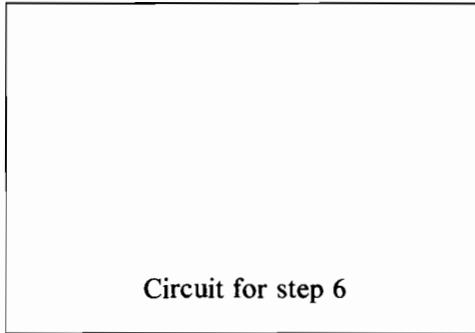6. Using the 330 Ω , 680 Ω , and 1.0 k Ω resistors, design a voltage divider with a +5.0 V output from a source voltage of +10 V. Draw your design in the space provided below.
7. Construct the circuit you designed and measure the actual output voltage. Indicate the measured value on your drawing.
8. Use two of the resistors from this experiment to design a divider with a +10 V input and a 7.5 V output. Draw your design in the space provided.



9. The circuit shown in Figure 8–3(b) uses a 1.0 k Ω potentiometer and R_1 and R_2 to limit the range of voltages. Assume V_S is +10 V. Use the voltage divider formula to compute the minimum and maximum voltages available from this circuit:

$$V_{\text{MIN}} = \underline{\hspace{2cm}}$$

$$V_{\text{MAX}} = \underline{\hspace{2cm}}$$

10. Construct the circuit computed in step 9. Measure the minimum and maximum output voltages:

$$V_{\text{MIN}} = \underline{\hspace{2cm}}$$

$$V_{\text{MAX}} = \underline{\hspace{2cm}}$$

Conclusion:

Evaluation and Review Questions:

1. (a) If all the resistors in Figure 8–4 were 10 times larger than the specified values, what would happen to the output voltage?

- (b) What would happen to the power dissipated in the voltage divider?
2. Refer to Figure 8–3(b). Assume V_S is 10.0 V.
- (a) If R_1 is open, what is the output voltage?
- (b) If R_2 is open, what is the output voltage?
3. If a student used a potentiometer in the circuit of Figure 8–3(b) that was 10 k Ω instead of 1.0 k Ω , what would happen to the range of output voltages?
4. For the circuit in Figure 8–5, compute the output voltage for each position of the switch:
- V_A _____
 V_B _____
 V_C _____
 V_D _____
5. Compute the minimum and maximum voltage available from the circuit shown in Figure 8–6:

$$V_{\text{MIN}} = \underline{\hspace{2cm}}$$

$$V_{\text{MAX}} = \underline{\hspace{2cm}}$$

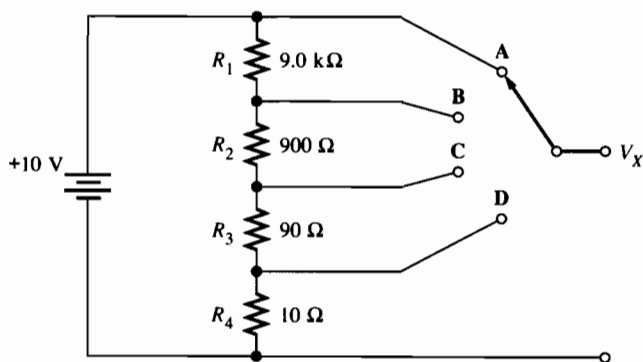


Figure 8–5

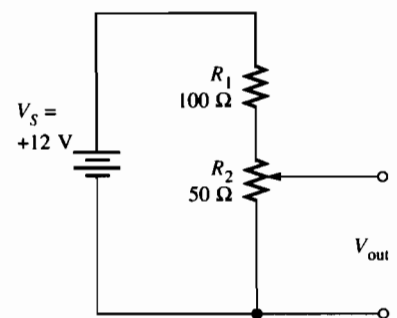


Figure 8–6

For Further Investigation

The voltage dividers in this experiment were *unloaded*—that is, they were not required to furnish current to a load. If a load is put on the output, then current is supplied to the load and the output voltage of the divider changes. Investigate this effect by placing some load resistors on the voltage divider from this experiment (Figure 8–4). What size load resistor causes a 10% or less effect? Does the size of the resistors in the divider string affect your results? Why would you choose one set of resistors over another? Summarize your findings in a short laboratory report.

Application Assignment 4

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 4, Section 4–11: Application Assignment

Step 1 Draw the schematic of the circuit:

Step 2 Determine the voltages:

	Specified (5%)	Computed
Pin 1:	0.0 V	
Pin 2:	2.7 V	
Pin 3:	12.0 V	
Pin 4:	10.4 V	
Pin 5:	8.0 V	
Pin 6:	7.3 V	
Pin 7:	6.0 V	

Step 3 Modify the existing circuit. Draw the schematic showing the changes necessary to meet the specifications.

Step 4 Determine the life of the 6.5 Ahr battery for your circuit:

Step 5 Step-by-step test procedure:

Step 6 Troubleshooting:

Fault 1 (no voltage at any pin): _____

Fault 2 (12 V at pins 3 and 4; all others have 0 V): _____

Fault 3 (12 V at all pins except 0 V at pin 1): _____

Fault 4 (12 V at pin 6 and 0 V at pin 7): _____

Fault 5 (3.3 V at pin 2): _____

Related Experiment:

Materials Needed:

Resistors:

One 3.3 k Ω , one 6.8 k Ω , two 10 k Ω

Discussion:

Voltage dividers are commonly used to set up reference voltages. For example, a logic voltage can be compared to a specified threshold level to see if it is above or below the threshold. The voltage divider circuit shown in Figure AA-4-1 provides both positive and negative reference voltages. TTL (transistor-transistor logic) uses positive voltages, whereas ECL (emitter-coupled logic) uses negative voltages. The voltages required are shown and can be obtained from a single adjustable power supply. Use the resistors listed in the materials list to design a voltage divider that produces the voltages shown. Each voltage should be within 5% of the required voltage. Set up your circuit, and measure the voltages with respect to ground. Summarize your results in a short laboratory report.

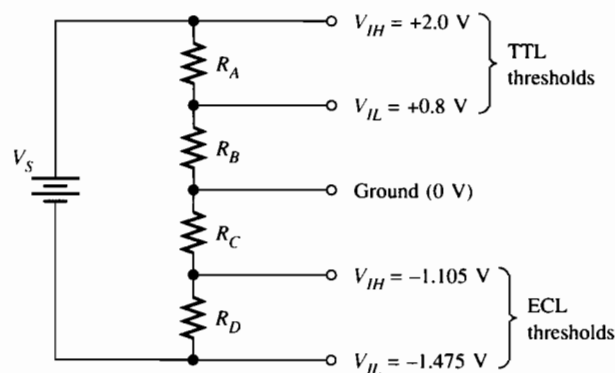


Figure AA-4-1

Checkup 4

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 4, and Buchla, Experiments 7 and 8

- In a series circuit, all components have the same:
(a) voltage drop (b) power (c) resistance (d) current
- A 50 V power supply is connected to five 1.0 k Ω resistors connected in series. The current in each resistor is:
(a) 0.1 mA (b) 10 mA (c) 50 mA (d) 250 mA
- Three equal value resistors are connected in series. If the total resistance is 10 k Ω , what is the value of each resistor?
(a) 3.3 k Ω (b) 10 k Ω (c) 20 k Ω (d) 30 k Ω
- The sum of the IR drops in a series circuit is:
(a) smaller than the applied voltage (c) greater than the applied voltage
(b) equal to the largest of the IR drops (d) equal to the applied voltage
- A voltage source of 10 V is connected to two series resistors. The voltage across the first resistor is found to be 8.0 V. The voltage across the second resistor is:
(a) 2.0 V (b) 8.0 V (c) 10 V (d) 18 V
- A 10 V supply is available to operate a dc motor that requires 6.0 V at 0.25 A. A series dropping resistor is needed to drop the voltage to the required level for the motor. The resistance should be:
(a) 1.5 Ω (b) 16 Ω (c) 24 Ω (d) 40 Ω
- Two resistors are connected in series. The first resistor is found to have 5.0 V across it, and the second resistor is found to have 10 V across it. Which resistor has the greatest resistance?
(a) the first (b) the second (c) neither (d) cannot be determined
- Two resistors are connected in series. The first resistor has 5.0 V across it, and the second resistor has 10 V across it. Which resistor dissipates the greatest power?
(a) the first (b) the second (c) neither (d) cannot be determined
- A 75 W bulb is designed to operate from a 115 V source. If two 75 W bulbs are connected in series with a 115 V source, the total power dissipated by both bulbs is:
(a) 37.5 W (b) 75 W (c) 150 W (d) 300 W
- A 75 W bulb is designed to operate from a 115 V source. If two 75 W bulbs are connected in series with a 230 V source, the total power dissipated by both bulbs is:
(a) 37.5 W (b) 75 W (c) 150 W (d) 300 W

11. Find the total resistance of the series combination of a $1.20\text{ M}\Omega$ resistor, a $620\text{ k}\Omega$ resistor, and a $150\text{ k}\Omega$ resistor.
12. Assume you need a 36 V source but have only three 12 V batteries available. Draw the connection of the batteries to provide the required voltage.
13. Assume a faulty series circuit has no current due to an open circuit. How would you use a voltmeter to locate the open circuit?
14. A series circuit consists of three $50\ \Omega$ resistors, each rated for 250 mW .
 - (a) What is the largest voltage that can be applied before exceeding the power rating of any resistor?
 - (b) What current flows in the circuit at this voltage?
15. The total resistance of a series circuit is $2.2\text{ k}\Omega$. What fraction of the input voltage will appear across a $100\ \Omega$ resistor?
16. An $8\ \Omega$ series limiting resistor is used to limit the current in a bulb to 0.375 A with 12 V applied.
 - (a) Determine the resistance of the bulb.
 - (b) If the voltage source is increased to 15 V , what additional series resistance will limit the current to the same 0.375 A ?
17. In Experiment 7 (Series Circuits), you used resistors that ranged in value from $1.0\text{ k}\Omega$ to $3.3\text{ k}\Omega$. How would your results have changed if all of the resistors were 20% larger than called for?

9 Parallel Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 5-1 through 5-9

Objectives:

After performing this experiment, you will be able to:

1. Demonstrate that the total resistance in a parallel circuit decreases as resistors are added.
2. Compute and measure resistance and currents in parallel circuits.
3. Explain how to troubleshoot parallel circuits.

Summary of Theory:

A *parallel* circuit is one in which there is more than one path for current to flow. Parallel circuits can be thought of as two parallel lines, representing conductors, with a voltage source and components connected between the lines. This idea is illustrated in Figure 9-1. The source voltage appears across each component. Each path for current is called a *branch*. The current in any branch is dependent only on the resistance of that branch and the source voltage.

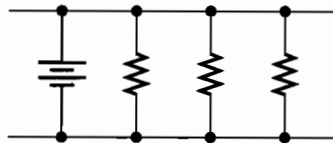


Figure 9-1

As more branches are added to a parallel circuit, the total resistance decreases. This is easy to see if you consider each added path in terms of conductance. Recall that conductance is the reciprocal of resistance. As parallel branches are added, new paths are provided for current, increasing the conductance. More total current flows in the circuit. If the total current in a circuit increases, with no change in source voltage, the total resistance must decrease according to Ohm's law. The total conductance of a parallel circuit is the sum of the individual conductances. This can be written:

$$G_T = G_1 + G_2 + G_3 + \dots + G_n$$

By substituting the definition for resistance into the formula for conductance, the reciprocal formula for resistance in parallel circuits is obtained. It is:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

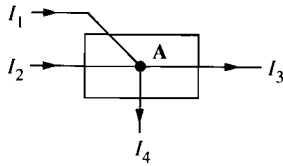


Figure 9–2

In parallel circuits, there are junctions where two or more components are connected. Figure 9–2 shows a circuit junction labeled A. Since electrical charge cannot accumulate at a point, the current flowing into the junction must be equal to the current flowing from the junction. This idea is Kirchhoff’s current law, which is stated:

The sum of the currents entering a circuit junction is equal to the sum of the currents leaving the junction.

One important idea can be seen by applying Kirchhoff’s current law to a point next to the source voltage. The current leaving the source must be equal to the sum of the individual branch currents. While Kirchhoff’s voltage law is developed in the study of series circuits, and the current law is developed in the study of parallel circuits, both laws are applicable to any circuit.

In Experiment 8, you observed how a series circuit causes voltage to be divided between the various resistances. In parallel circuits, it is the *current* that is divided between the resistances. Keep in mind that the larger the resistance, the smaller the current. The general current divider rule can be written:

$$I_X = \left(\frac{R_T}{R_X} \right) I_T$$

Notice that the fraction R_T/R_X is always less than 1.0 and represents the fraction of the total current in R_X . This equation can be simplified for the special case of exactly two resistors. The special two-resistor current divider is written:

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I_T \quad I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_T$$

Materials Needed:

Resistors:

One 3.3 kΩ, one 4.7 kΩ, one 6.8 kΩ, one 10 kΩ

One dc ammeter, 0–10 mA

Procedure:

1. Obtain the resistors listed in Table 9–1. Measure and record the value of each resistor.

Table 9-1

Component	Listed Value	Measured Value
R_1	3.3 k Ω	
R_2	4.7 k Ω	
R_3	6.8 k Ω	
R_4	10.0 k Ω	

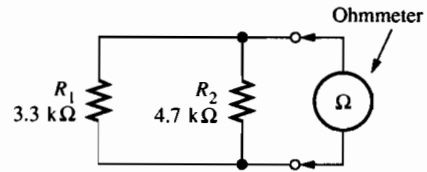


Figure 9-3

- In Table 9-2 you will tabulate the total resistance as resistors are added in parallel. (Parallel connections are indicated with two parallel lines shown between the resistors.) Enter the measured value of R_1 in the table. Then connect R_2 in parallel with R_1 and measure the total resistance as shown in Figure 9-3. Enter the measured resistance of R_1 in parallel with R_2 in Table 9-2.

Table 9-2

	R_1	$R_1 \parallel R_2$	$R_1 \parallel R_2 \parallel R_3$	$R_1 \parallel R_2 \parallel R_3 \parallel R_4$
R_T (measured)				
I_T (measured)				

- Add R_3 in parallel with R_1 and R_2 . Measure the parallel resistance of all three resistors. Then add R_4 in parallel with the other three resistors and repeat the measurement. Record your results in Table 9-2.
- Complete the parallel circuit by adding the voltage source and the ammeter as shown in Figure 9-4. Be certain that the ammeter is connected in series with the voltage source as shown. If you are not sure, have your instructor check your circuit. Measure the total current in the circuit and record it in Table 9-2.

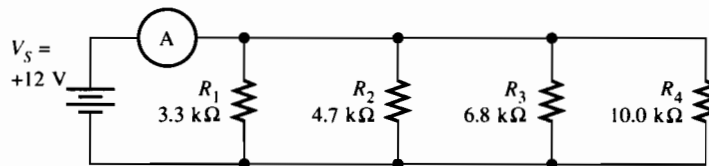


Figure 9-4

- Measure the voltage across each resistor. How does the voltage across each resistor compare to the source voltage?
-
- Use Ohm's law to compute the branch current in each resistor. Use the source voltage and the measured resistances. Tabulate the computed currents in Table 9-3.

Table 9-3

	$I_1 = \frac{V_S}{R_1}$	$I_2 = \frac{V_S}{R_2}$	$I_3 = \frac{V_S}{R_3}$	$I_4 = \frac{V_S}{R_4}$
<i>I</i> (computed)				

7. Use the general current divider rule to compute the current in each branch. Use the total current and total resistance that you recorded in Table 9-2. Compare the calculation using the current divider rule with the results using Ohm's law. Show your results in Table 9-4.

Table 9-4

	$I_1 = \frac{R_T}{R_1} I_T$	$I_2 = \frac{R_T}{R_2} I_T$	$I_3 = \frac{R_T}{R_3} I_T$	$I_4 = \frac{R_T}{R_4} I_T$
<i>I</i> (computed)				

8. Prove Kirchoff's current law for the circuit by showing that the total current is equal to the sum of the branch currents:
-

9. Simulate a burned-out resistor by removing R_4 from the circuit. What is the new total current?

$I_T =$ _____

Conclusion:

Evaluation and Review Questions:

1. In step 9, you simulated an open resistor by removing it from the circuit, and you observed that the total current dropped. Explain how the open resistor could be found in this experiment from the observed change in current and the source voltage.

2. If one of the resistors in this experiment were shorted, what would you expect to see happen? (Do not simulate this!)

3. Three resistors are connected in parallel across a 40 V source. The values of the resistors are 620Ω , 750Ω , and 820Ω .

(a) What should the total source current be?

(b) If the measured current was 118 mA, what fault could account for this?

4. The known currents for a circuit junction are shown in Figure 9–5. What is the value and direction of the unknown current, I_4 ?

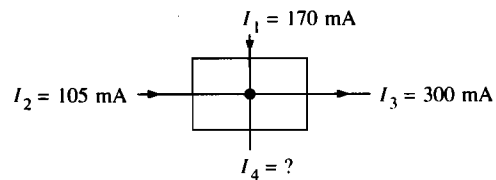


Figure 9–5

5. Could a shorted component in a parallel circuit cause an open to occur elsewhere? Explain.

For Further Investigation:

Kirchhoff's current law can be applied to any junction in a circuit. The currents in this circuit were I_1 , I_2 , I_3 , I_4 , and I_T . Apply Kirchhoff's current law to these currents by writing the numeric value of the current entering and leaving each junction circled in Figure 9-6. Then verify that you computed the correct currents by measuring them with the ammeter. The circuit must be broken, and the ammeter is inserted in series with the path you are measuring. (See Figure 5-17 of Floyd's text.) Summarize your results in a laboratory report.

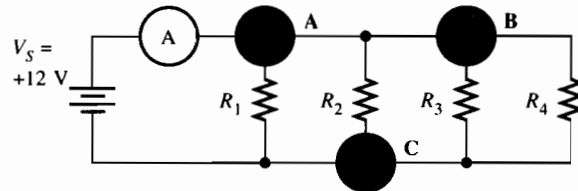


Figure 9-6

Application Assignment 5

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 5, Section 5–10: Application Assignment

Step 1 Examine the circuit:

Step 2 Compare the meter circuit to the schematic. Specify if there is a problem, and if there is, how to fix it.

Step 3 Check for additional problems.

Step 4 Analyze the circuit. Calculate the required precision resistors to correct the problem.

Related Experiment:

Materials Needed:

Resistors:

Two 1 k Ω , one 1.5 k Ω , one 1.8 k Ω , one 2.2 k Ω

Discussion:

There are several ways of finding an open resistor for the application problem; presented here is a different method that you can investigate. The method is based on the voltage divider principle. A series 1 k Ω resistor is added to the parallel resistors, as shown in Figure AA-5-1. The parallel group represents an equivalent resistance in series with the 1 k Ω resistor. The voltage dropped across the parallel resistors will change if any resistor is open. Investigate this by connecting the circuit and measuring the voltage across the parallel group. Then, open one of the parallel resistors and measure the new voltage across the remaining group. Continue like this for each of the parallel resistors. Can you use your results to determine which resistor is open?

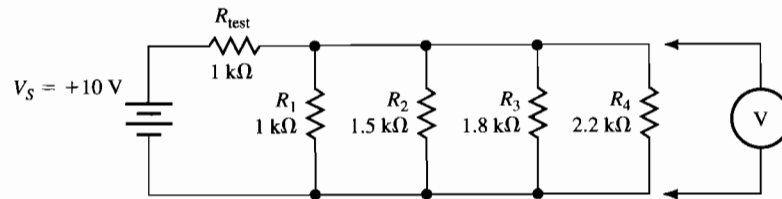


Figure AA-5-1

Experimental Results:

Checkup 5

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 5, and Buchla, Experiment 9

- In a parallel circuit, all components have the same:
(a) voltage drop (b) current (c) power (d) resistance
- A 50 V power supply is connected to five 1 k Ω resistors connected in parallel. The total current from the source is:
(a) 0.1 mA (b) 10 mA (c) 50 mA (d) 250 mA
- Three equal value resistors are connected in parallel. If the total resistance is 10 k Ω , what is the value of each resistor?
(a) 3.3 k Ω (b) 10 k Ω (c) 20 k Ω (d) 30 k Ω
- When a resistance path is added to a parallel circuit, the total resistance:
(a) decreases (b) remains the same (c) increases
- Assume a voltage of 27 V is connected across two equal parallel resistors. The current in the first resistor is 10 mA. The total resistance is:
(a) 270 Ω (b) 741 Ω (c) 1.35 k Ω (d) 2.7 k Ω
- If one resistive branch of a parallel circuit is opened, the total current will:
(a) decrease (b) remain the same (c) increase
- Three resistors are connected in parallel. The first is 1 M Ω , the second is 2 M Ω , and the third is 10 k Ω . The total resistance is approximately:
(a) 5 k Ω (b) 10 k Ω (c) 1 M Ω (d) 3 M Ω
- Three 75 W bulbs are connected in parallel across a 115 V line. The total power dissipated by the bulbs is:
(a) 25 W (b) 75 W (c) 115 W (d) 225 W
- Assume an unknown resistor is in parallel with a 68 Ω resistor. The total resistance of the combination is 40.5 Ω . The resistance of the unknown resistor is:
(a) 25 Ω (b) 34 Ω (c) 75 Ω (d) 100 Ω
- An ammeter with an internal resistance of 40 Ω and a full-scale deflection of 10 mA is needed to measure a full-scale current of 100 mA. The shunt resistor that will accomplish this has a value of:
(a) 4.0 Ω (b) 4.44 Ω (c) 400 Ω (d) 444 Ω

11. In Experiment 9 (Parallel Circuits), you were asked to find the parallel resistance of a group of resistors as new ones were placed in the circuit. What was happening to the total *conductance* of the circuit as more resistors were placed in parallel? Why?
12. Explain why electrical house wiring is done with parallel circuits.
13. A 115 V source provides 30 A into a four-branch parallel circuit. The first three branch currents are 10 A, 8 A, and 5 A.
- (a) What is the current in the fourth branch?
- (b) What is the resistance of the fourth branch?
- (c) What is the total resistance of the circuit?
14. Assume a current of $350\ \mu\text{A}$ flows into a parallel combination of two resistors, R_1 and R_2 . The resistance of R_1 is $5.6\ \text{k}\Omega$, and the resistance of R_2 is $8.2\ \text{k}\Omega$. Compute the current in each resistor.
15. Four $1\ \text{k}\Omega$ resistors are connected in parallel. The total power dissipated is 200 mW.
- (a) What power is dissipated in each resistor?
- (b) What is the source voltage?

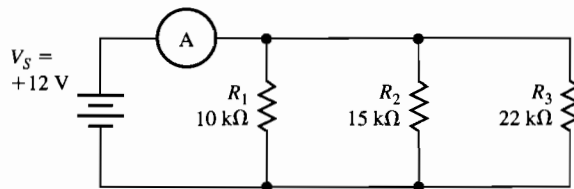


Figure C-5-1

16. For the parallel circuit shown in Figure C-5-1, assume the ammeter reads 1.75 mA. What is the likely cause of trouble? Justify your answer.

10 Series-Parallel Combination Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 6-1 through 6-4

Objectives:

After performing this experiment, you will be able to:

1. Use the concept of equivalent circuits to simplify series-parallel circuit analysis.
2. Compute the currents and voltages in a series-parallel combination circuit and verify your computation with circuit measurements.

Summary of Theory:

Most electronic circuits are not just series or just parallel circuits. Instead they may contain combinations of components. Many circuits can be analyzed by applying the ideas developed for series and parallel circuits to them. Remember that in a *series* circuit the same current flows through all components, and that the total resistance of series resistors is the sum of the individual resistors. By contrast, in *parallel* circuits, the applied voltage is the same across all branches and the total resistance is given by the reciprocals formula.

In this experiment, the circuit elements are connected in composite circuits containing both series and parallel combinations. The key to solving these circuits is to form equivalent circuits from the series or parallel elements. You need to recognize when circuit elements are connected in series or parallel in order to form the equivalent circuit. For example, in Figure 10-1(a) we see that the identical current must flow through both R_2 and R_3 . We conclude that these resistors are in series and could be replaced by an equivalent resistor equal to their sum. Figure 10-1(b) illustrates this idea. The circuit has been simplified to an equivalent parallel circuit. After finding the currents in the equivalent circuit, the results can be applied to the original circuit to complete the solution.

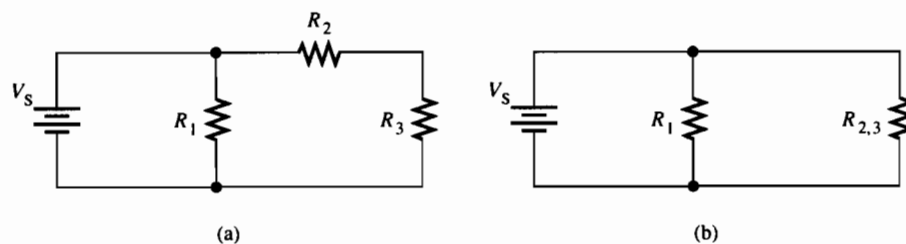


Figure 10-1

The answer to two questions will help you identify a series or parallel connection: (1) Will the *identical* current flow through both components? If the answer is yes, the components are in series. (2) Are *both ends* of the component connected directly to *both ends* of another component? If yes, the components are in parallel. The components that are in series or parallel may be replaced with an equivalent component. This process continues until the circuit is reduced to a simple series or parallel circuit. After solving the equivalent circuit,

the process is reversed in order to apply the solution to the original circuit. This idea is studied in this experiment.

Materials Needed:

Resistors:

One 2.2 kΩ, one 4.7 kΩ, one 5.6 kΩ, one 10 kΩ

Procedure:

1. Measure and record the actual values of the four resistors listed in Table 10–1.

Table 10–1

Component	Listed Value	Measured Value
R_1	2.2 kΩ	
R_2	4.7 kΩ	
R_3	5.6 kΩ	
R_4	10.0 kΩ	

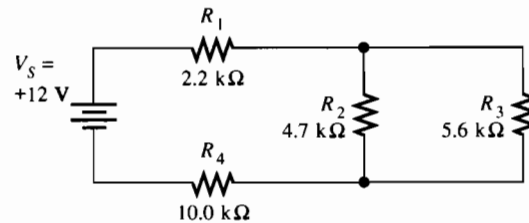


Figure 10–2

2. Connect the circuit shown in Figure 10–2. Then answer the following questions:
 - (a) Are there any resistors for which the identical current will flow through the resistors? Answer yes or no for each resistor:

R_1 _____ R_2 _____ R_3 _____ R_4 _____

- (b) Does any resistor have both ends connected directly to both ends of another resistor? Answer yes or no for each resistor:

R_1 _____ R_2 _____ R_3 _____ R_4 _____

3. The answer to these questions should clarify in your mind which resistors are in series and which resistors are in parallel. You can begin solving for the currents and voltages in the circuit by replacing resistors that are either in series or in parallel with an equivalent resistor. In this case, begin by replacing R_2 and R_3 with an equivalent resistor labeled $R_{2,3}$. Draw the equivalent circuit in the space provided. Show the value of all components including $R_{2,3}$.

Table 10–2

	Computed		Measured
	Voltage Divider	Ohm's Law	
R_T			
I_T			
V_1			
$V_{2,3}$			
V_4			
I_2			
I_3			
V_T	12.0 V	12.0 V	

4. The equivalent circuit you drew in step 3 is a simple series circuit. Compute the total resistance of this equivalent circuit and enter it in the first two columns of Table 10–2. Then disconnect the power supply and measure the total resistance to confirm your calculation.
5. The voltage divider rule can be applied directly to the series equivalent circuit to find the voltages across R_1 , $R_{2,3}$, and R_4 . Find V_1 , $V_{2,3}$, and V_4 using the voltage divider rule. Tabulate the results in Table 10–2 in the Voltage Divider column.
6. Find the total current, I_T , in the circuit by substituting the total voltage and the total resistance into Ohm's law. Enter the computed total current in Table 10–2 in the Ohm's Law column.
7. In the equivalent series circuit, the total current flows through R_1 , $R_{2,3}$, and R_4 . The voltage drop across each of these resistors can be found by applying Ohm's law to each resistor. Compute V_1 , $V_{2,3}$, and V_4 using this method. Enter the voltages in Table 10–2 in the Ohm's Law column.
8. Use $V_{2,3}$ and Ohm's law to compute the current in R_2 and R_3 of the original circuit. Enter the computed current in Table 10–2. As a check, verify that the computed sum of I_2 and I_3 is equal to the computed total current.
9. Measure the voltages V_1 , $V_{2,3}$, and V_4 . Enter the measured values in Table 10–2.

10. Change the circuit to the circuit shown in Figure 10–3. In the space provided below, draw an equivalent circuit by combining the resistors that are in series. Enter the values of the equivalent resistors on your schematic and in Table 10–3.
11. Compute the total resistance, R_T , of the equivalent circuit. Then apply Ohm's law to find the total current I_T . Enter the computed resistance and current in Table 10–3.
12. Complete the calculations of the circuit by solving for the remaining currents and voltages listed in Table 10–3. Then measure the voltages across each resistor to confirm your computation.

Table 10–3

	Computed	Measured
$R_{1,2}$		
$R_{3,4}$		
R_T		
I_T		
$I_{1,2}$		
$I_{3,4}$		
V_1		
V_2		
V_3		
V_4		

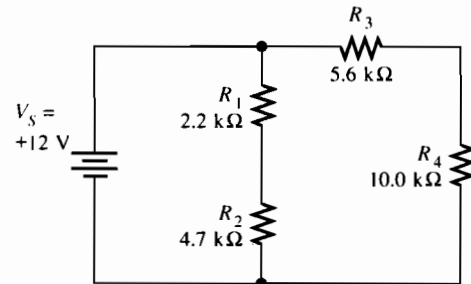


Figure 10–3

Conclusion:

Evaluation and Review Questions:

1. The voltage divider rule was developed for a series circuit, yet it was applied to the circuit in Figure 10–2.
 - (a) Explain:

- (b) Could the voltage divider rule be applied to the circuit in Figure 10–3? Explain your answer.
2. As a check on your solution of the circuit in Figure 10–3, apply Kirchhoff’s voltage law to each of two separate paths around the circuit. Show the application of the law.
3. Show the application of Kirchhoff’s current law to the junction of R_2 and R_4 of the circuit in Figure 10–3.
4. In the circuit of Figure 10–3, assume you found that I_T was the same as the current in R_3 and R_4 .
- (a) What are the possible problems?
- (b) How would you isolate the specific problem using only a voltmeter?
5. The circuit in Figure 10–4 has three equal resistors. If the voltmeter reads +8.0 V, find V_S .

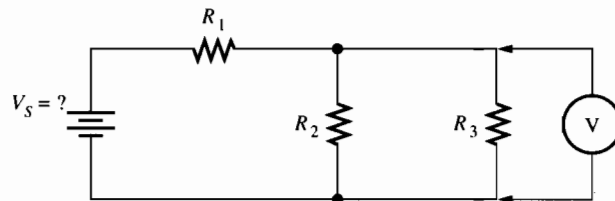


Figure 10–4

For Further Investigation:

Figure 10–5 illustrates another series-parallel circuit using the same resistors. Develop a procedure for solving the currents and voltages throughout the circuit. Summarize your procedure in a laboratory report. Confirm your method by computing and measuring the voltages in the circuit.

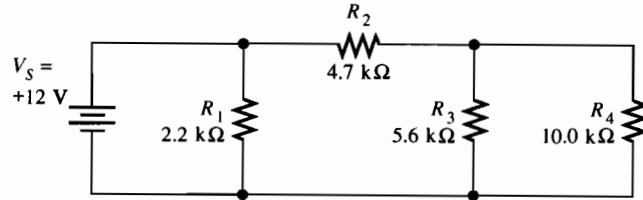


Figure 10–5

11 The Superposition Theorem

Name _____
Date _____
Class _____

Reading:

Floyd, Section 6-6

Objectives:

After performing this experiment, you will be able to:

1. Apply the superposition theorem to linear circuits with more than one voltage source.
2. Construct a circuit with two voltage sources, solve for the currents and voltages throughout the circuit, and verify your computation by measurement.

Summary of Theory:

To superimpose something means to lay one thing on top of another. The superposition theorem is a means by which we can solve circuits that have more than one independent voltage source. Each source is taken, one at a time, as if it were the only source in the circuit. All other sources are replaced with their internal resistance. (The internal resistance of a dc power supply or battery can be considered to be zero.) The currents and voltages for the first source are computed. The results are marked on the schematic, and the process is repeated for each source in the circuit. When all sources have been taken, the overall circuit can be solved. The algebraic sum of the superimposed currents and voltages is computed. Currents that are in the same direction are added; those that are in opposing directions are subtracted with the sign of the larger applied to the result. Voltages are treated in a like manner.

The superposition theorem will work for any number of sources *as long as you are consistent in accounting for the direction of currents and the polarity of voltages*. One way to keep the accounting straightforward is to assign a polarity, right or wrong, to each component. Tabulate any current which is in the same direction as the assignment as a positive current and any current which opposes the assigned direction as a negative current. When the final algebraic sum is completed, positive currents are in the assigned direction; negative currents are in the opposite direction of the assignment. In the process of replacing a voltage source with its zero internal resistance, you may completely short out a resistor in the circuit. If this occurs, there will be no current in that resistor for this part of the calculation. The final sum will still have the correct current.

Materials Needed:

Resistors:

One 4.7 k Ω , one 6.8 k Ω , one 10.0 k Ω

Procedure:

1. Obtain the resistors listed in Table 11-1. Measure each resistor and record the measured value in Table 11-1.

2. Construct the circuit shown in Figure 11–1. This circuit has two voltage sources connected to a common reference ground.

Table 11–1

	Listed Value	Measured Value
R_1	4.7 k Ω	
R_2	6.8 k Ω	

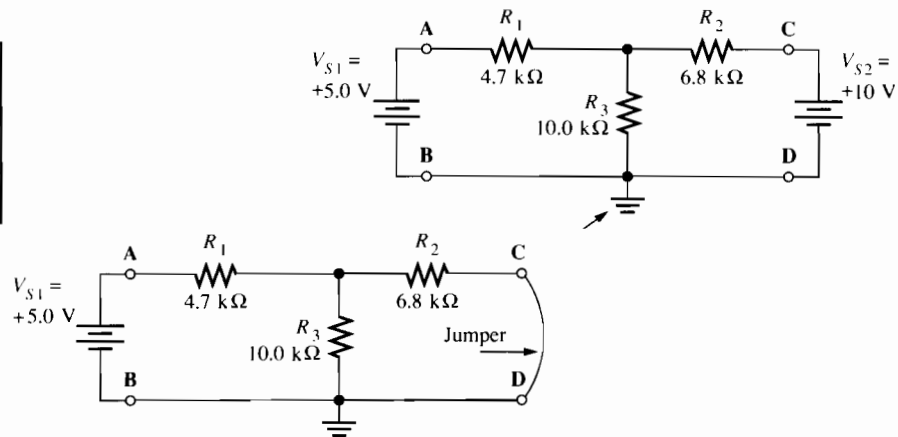


Figure 11–2

4. Compute the total resistance, R_T , seen by the +5.0 V source. Then remove the +5.0 V source and measure the resistance between points A and B to confirm your calculation. Record the computed and measured values in Table 11–2.
5. Use the source voltage, V_{S1} , and the total resistance to compute the total current, I_T , from the +5.0 V source. This current flows through R_1 so record it as I_1 in Table 11–2. Use the current divider rule to determine the currents in R_2 and R_3 . The current divider rule for I_2 and I_3 is:

$$I_2 = I_T \left(\frac{R_3}{R_2 + R_3} \right) \qquad I_3 = I_T \left(\frac{R_2}{R_2 + R_3} \right)$$

Record all three currents as *positive* values in Table 11–2. This will be the assigned direction of current flow. Mark the magnitude and direction of the current in Figure 11–2.

6. Use the currents computed in step 5 and the measured resistances to calculate the expected voltage across each resistor of Figure 11–2. Then connect the +5.0 V power supply and measure the actual voltages present in this circuit. Record the computed and measured voltages in Table 11–2. Since all currents in step 5 were considered *positive*, all voltages in this step are also *positive*.

7. Remove the +5.0 V source from the circuit and move the jumper from between points C and D to between points A and B. Compute the total resistance between points C and D. Measure the resistance to confirm your calculation. Record the computed and measured resistance in Table 11–2.

Table 11–2

	Computed Resistance	Measured Resistance	Computed Current			Computed Voltage			Measured Voltage		
			I_1	I_2	I_3	V_1	V_2	V_3	V_1	V_2	V_3
Step 4											
Step 5											
Step 6											
Step 7											
Step 8											
Step 9											
Step 10		Total→									

8. Compute the current through each resistor in Figure 11–3. Note that the total current flows through R_2 and divides each between R_1 and R_3 . Mark the magnitude and direction of the current on Figure 11–3. *Important:* Record the current as a *positive* current if it is in the same direction as recorded in step 5 and as a *negative* current if it is in the opposite direction as in step 4.

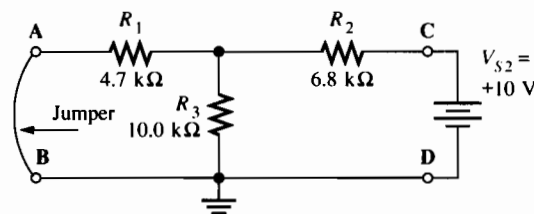


Figure 11–3

9. Use the currents computed in step 8 and the measured resistances to compute the voltage drops across each resistor. If the current through a resistor was a *positive* current, record the resistor's voltage as a *positive* voltage. If a current was a *negative* current, record the voltage as a *negative* voltage. Then connect the +10 V source as illustrated in Figure 11–3 and measure the voltages. The measured voltages should confirm your calculation.
10. Compute the algebraic sum of the currents and voltages listed in Table 11–2. Enter the computed sums in Table 11–2. Then replace the jumper between A and B with the +5.0 V source, as shown in the original circuit in Figure 11–1. Measure the voltage across each resistor in this circuit. The measured voltages should agree with the algebraic sums. Record the measured results in Table 11–2.

5. Use the superposition theorem to find the current in R_2 in Figure 11-4.

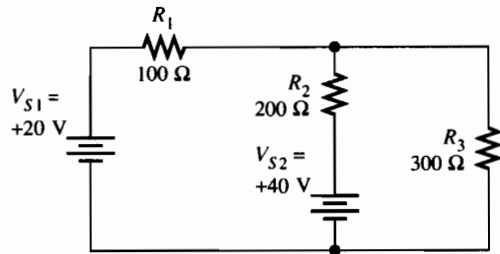


Figure 11-4

For Further Investigation:

Compute the power dissipated in each resistor in the circuits shown in Figures 11-1, 11-2, and 11-3. Using the computed results, find out if the superposition theorem is valid for power. Summarize your computations and conclusion.

12 Thevenin's Theorem

Name _____
Date _____
Class _____

Reading:

Floyd, Section 6-7

Objectives:

After performing this experiment, you will be able to:

1. Change a linear network containing several resistors into an equivalent Thevenin circuit.
2. Prove the equivalency of the network in objective 1 with the Thevenin circuit by comparing the effects of various load resistors.

Summary of Theory:

In Experiment 10, you solved series-parallel circuits by developing equivalent circuits. Equivalent circuits simplify the task of solving for current and voltage in a network. The concept of equivalent circuits is basic to solving many problems in electronics.

Thevenin's theorem provides a means of reducing a complicated, linear network into an equivalent circuit when there are two terminals of special interest (usually the output). The equivalent Thevenin circuit is composed of a voltage source and a series resistor. (In ac circuits, the resistor may be represented by opposition to ac called *impedance*.) Imagine a complicated network containing multiple voltage sources, current sources, and resistors, such as that shown in Figure 12-1(a). Thevenin's theorem can reduce this to the equivalent circuit shown in Figure 12-1(b). The circuit in Figure 12-1(b) is called a Thevenin circuit. A device connected to the output is a *load* for the Thevenin circuit. The two circuits have identical responses to any load.


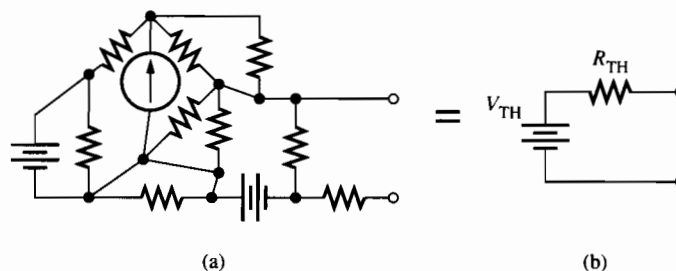


Figure 12-1

Two steps are required in order to simplify a circuit to its equivalent Thevenin circuit. The first step is to measure or compute the voltage at the output terminals with any load resistors removed. This open-circuit voltage is the Thevenin voltage. The second step is to compute the resistance seen at the same open terminals if sources are replaced with their internal resistance. For voltage sources, the internal resistance is usually taken as zero, and for current sources, the internal resistance is infinite (open circuit). An example of this process is illustrated in Figure 12-2.

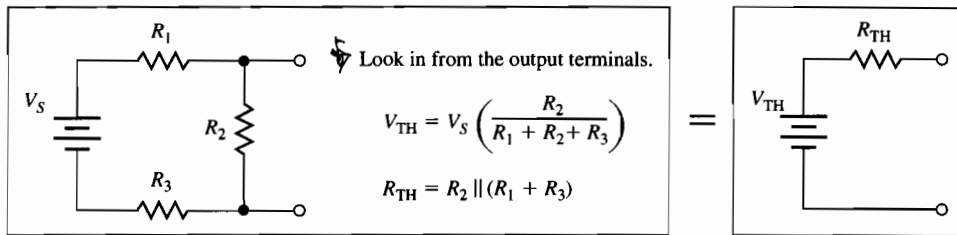

Important: The equations developed in this example are given to illustrate a *procedure* and are valid *only* for the example; they cannot be applied to other circuits, including the circuit in this experiment.

Figure 12–2

Materials Needed:

Resistors:

One 150 Ω , one 270 Ω , one 470 Ω , one 560 Ω , one 680 Ω , one 820 Ω

One 1 k Ω potentiometer

Procedure:

1. Measure and record the resistance of the 6 resistors listed in Table 12–1. The last three resistors will be used as load resistors and connected, one at a time, to the output terminals.

Table 12–1

Component	Listed Value	Measured Value
R_1	270 Ω	
R_2	560 Ω	
R_3	680 Ω	
R_{L1}	160 Ω	
R_{L2}	470 Ω	
R_{L3}	820 Ω	

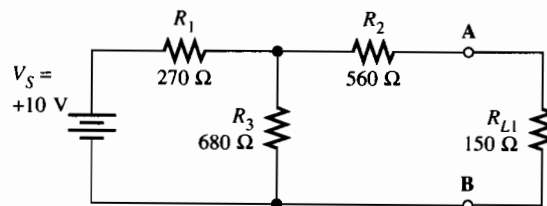


Figure 12–3

2. Construct the circuit shown in Figure 12–3. Points A and B represent the output terminals. Calculate an equivalent circuit seen by the voltage source. Figure 12–4 illustrates the procedure. Use the equivalent circuit to compute the expected voltage across the load resistor, V_{L1} . Do not use Thevenin’s theorem at this time. Show your computation of the load voltage in the space provided. For the first load resistor, your computed result should be approximately 1.19 V.

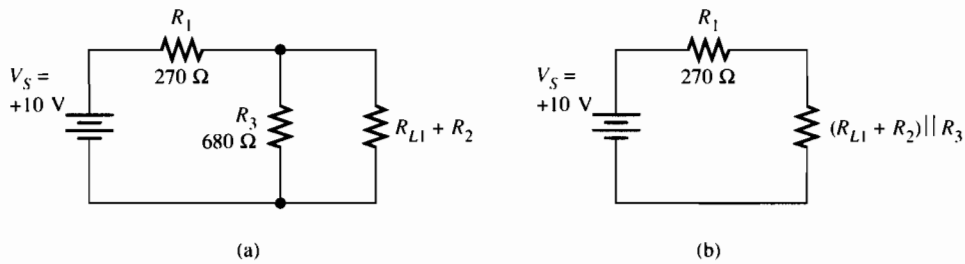


Figure 12-4

3. Measure the load voltage to verify your calculation. Enter the computed and measured load voltage in Table 12-2.

Table 12-2

	Computed	Measured
V_{L1}		
V_{L2}		
V_{L3}		
V_{TH}		
R_{TH}		

4. Replace R_{L1} with R_{L2} . Using a new equivalent circuit, compute the expected voltage, V_{L2} , across the load resistor. Then measure the actual load voltage. Enter the computed and measured voltage in Table 12-2.
5. Repeat step 4 using R_{L3} for the load resistor.
6. Remove the load resistor from the circuit. Calculate the open circuit voltage at the A-B terminals. This open circuit voltage is the *Thevenin voltage* for this circuit. Record the open circuit voltage in Table 12-2 as V_{TH} .
7. Mentally replace the voltage source with a short (zero ohms). Compute the resistance between the A-B terminals. This is the computed *Thevenin resistance* for this circuit. Then disconnect the voltage source and replace it with a jumper. Measure the actual Thevenin resistance of the circuit. Record your computed and measured Thevenin resistance in Table 12-2.
8. In the space provided, draw the Thevenin equivalent circuit. Show on your drawing the measured Thevenin voltage and resistance.

Table 12–3

	Computed	Measured
V_{L1}		
V_{L2}		
V_{L3}		
V_{TH}		
R_{TH}		

9. For the circuit you drew in step 8, compute the voltage you expect across each of the three load resistors. Since the circuit is a series circuit, the voltage divider rule will simplify the calculation. Enter the computed voltages in Table 12–3.
10. Construct the Thevenin circuit you drew in step 8. Use a 1 k Ω potentiometer to represent the Thevenin resistance. Set it for the resistance shown on your drawing. Set the voltage source for the Thevenin voltage. Place each load resistor, one at a time, on the Thevenin circuit and measure the load voltage. Enter the measured voltages in Table 12–3.
11. Remove the load resistor from the Thevenin circuit. Find the open circuit voltage with no load. Enter this voltage as the computed and measured V_{TH} in Table 12–3. Enter the measured setting of the potentiometer as R_{TH} in Table 12–3.

Conclusion:

Evaluation and Review Questions:

1. Compare the measured voltages in Tables 12–2 and 12–3. What conclusion can you draw about the two circuits?
2. Compute the load current you would expect to measure if the load resistor in Figure 12–3 were replaced with a short. Then repeat the computation for the Thevenin circuit you drew in step 8.

3. What advantage does Thevenin's theorem offer for computing the load voltage across each of the load resistors tested in this experiment?
4. Figure 12-5(a) shows a circuit, and Figure 12-5(b) shows its equivalent Thevenin circuit. Explain why R_1 has no effect on the Thevenin circuit.

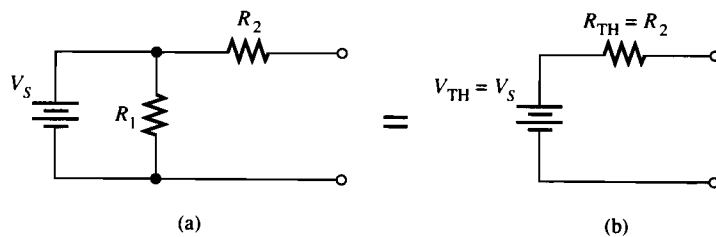


Figure 12-5

5. Draw the Thevenin circuit for the circuits shown in Figure 12-6.

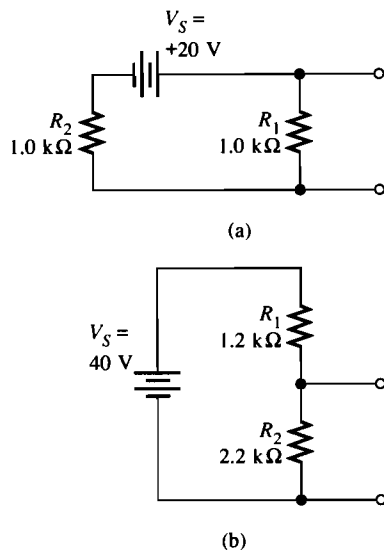


Figure 12-6

For Further Investigation:

Sometimes it is useful to compute a Thevenin equivalent circuit when it is not possible to measure the Thevenin resistance directly. The Thevenin resistance can still be determined for a source by placing a known load resistor on the output terminals and observing the loaded and unloaded output voltage. A simple method is to use a variable resistor as a load resistor and adjust it until the load voltage has dropped to one-half of the open circuit voltage. The variable load resistor and the internal Thevenin resistance of the source will then be equal. Use this method to measure the Thevenin resistance of your signal generator. Report your results and explain why this is a valid method for determining the Thevenin resistance.

13 The Wheatstone Bridge

Name _____
 Date _____
 Class _____

Reading:

Floyd, Sections 6–5 through 6–7

Objectives:

After performing this experiment, you will be able to:

1. Calculate the equivalent Thevenin circuit for a Wheatstone bridge circuit.
2. Verify that the Thevenin circuit determined in objective 1 enables you to compute the response to a load for the original circuit.
3. Balance a Wheatstone bridge and draw the Thevenin circuit for the balanced bridge.

Summary of Theory:

The Wheatstone bridge is a circuit with wide application in measurement systems. It can be used to accurately compare an unknown resistance with known precision resistors and is very sensitive to changes in the unknown resistance. The unknown resistance is frequently a transducer such as a strain gauge, in which very small changes in resistance are related to mechanical stress. The basic Wheatstone bridge is shown in Figure 13–1(a).

Thevenin’s theorem is very useful for analysis of the Wheatstone bridge, which is not a simple series-parallel combination circuit. From the perspective of the current in the load resistor, the method shown in Floyd’s text is the most straightforward analysis technique. The following alternate method is very similar but preserves the ground reference point of the voltage source. This simplifies finding *all* of the currents in the bridge and finding the voltage at point A or B with respect to ground.

Begin by splitting the bridge into two independent voltage dividers as shown in Figure 13–1(b). Thevenin’s theorem is applied between point A and ground for the left divider and between point B and ground for the right divider. V_A is the Thevenin voltage for the left divider, and V_B is the Thevenin voltage for the right divider. To find the Thevenin resistance, the source is replaced with a short, and the resistors on each side are seen to be in parallel. Two Thevenin circuits are then drawn as shown in Figure 13–1(c).

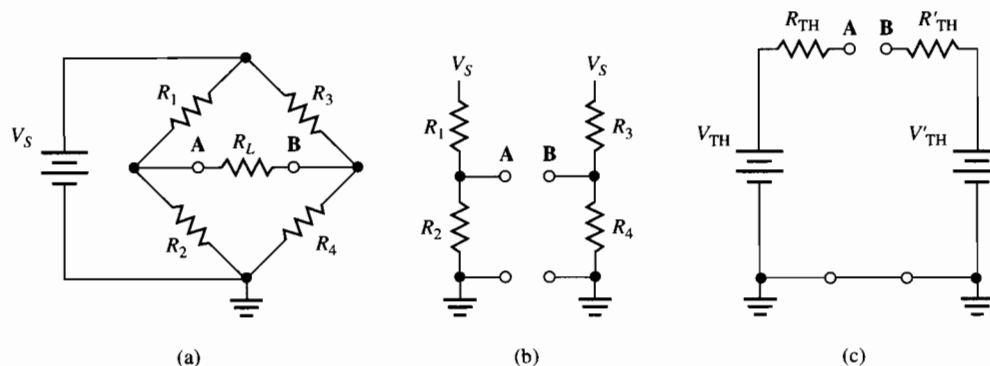


Figure 13–1

The load resistor can be added to the equivalent circuit as shown in Figure 13–2. Load current can be quickly found by the superposition theorem. The equations for the procedure are given for reference in Figure 13–2.

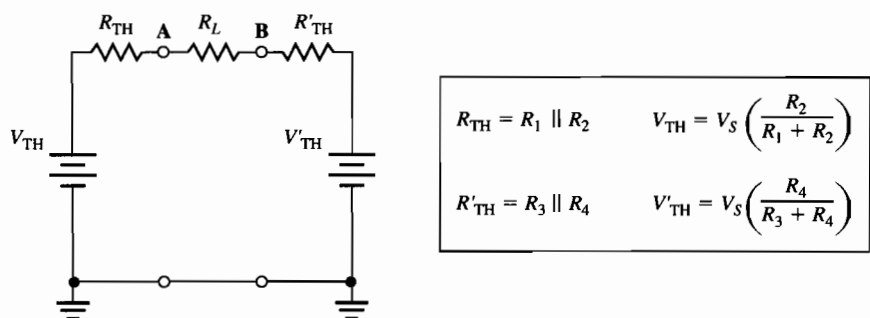


Figure 13–2

Materials Needed:

Resistors:

One 100 Ω, one 150 Ω, one 330 Ω, one 470 Ω

One 1 kΩ potentiometer

For Further Investigation:

Wheatstone bridge sensitive to 0.1 Ω

Procedure:

1. Measure and record the resistance of each of the four resistors listed in Table 13–1. R_4 is a 1 kΩ potentiometer. Set it for its maximum resistance and record this value.

Table 13–1

Component	Listed Value	Measured Value
R_1	100 Ω	
R_2	150 Ω	
R_3	330 Ω	
R_L	470 Ω	
R_4	1 kΩ pot.	

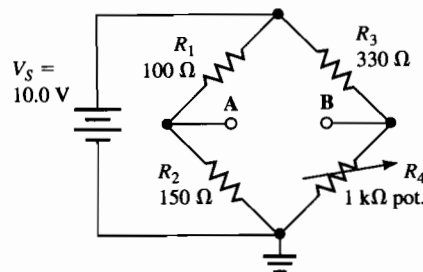


Figure 13–3

- Construct the Wheatstone bridge circuit shown in Figure 13–3. R_4 should be set to its maximum resistance. Use the voltage divider rule to compute the voltage at point **A** with respect to ground and the voltage at **B** with respect to ground. Enter the computed V_A and V_B in Table 13–2.
- Measure V_A and V_B . Because these voltages are measured with no load, they are the Thevenin voltages for the bridge using the method illustrated in Figure 13–1. Enter the measured voltages in Table 13–2 and show them on Figure 13–4.
- Compute the Thevenin resistance on the left side of the bridge in Figure 13–3 by mentally replacing V_S with a short. Notice that this causes R_1 to be in parallel with R_2 . Repeat the process for the right side of the bridge. Enter the computed Thevenin resistances, R_{TH} and R'_{TH} , in Table 13–2 and on Figure 13–4. Then replace V_S with a short and measure R_{TH} and R'_{TH} .

Table 13–2

	Computed	Measured
V_A		
V_B		
R_{TH}		
R'_{TH}		
V_L		

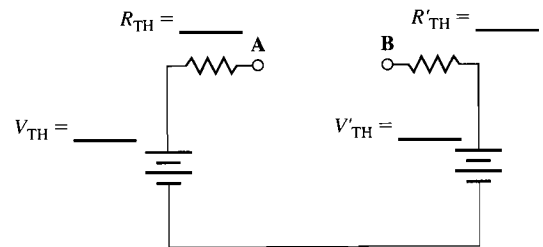


Figure 13–4

- Draw in the load resistor between the **A** and **B** terminals in the circuit of Figure 13–4. Show the value of the measured resistance of R_L . Use the superposition theorem to compute the expected voltage drop, V_L , across the load resistor. Enter the computed voltage drop in Table 13–2.
- Place the load resistor across the **A** and **B** terminals of the bridge circuit (Figure 13–3) and measure the load voltage, V_L . If the measured value does not agree with the computed value, recheck your work. Enter the measured V_L in Table 13–2.
- Monitor the voltage across the load resistor and carefully adjust R_4 until the bridge is balanced. When balance is achieved, remove the load resistor. Measure the voltage from **A** to ground and the voltage from **B** to ground. Since the load resistor has been removed, these measurements represent the Thevenin voltages of the balanced bridge. Enter the measured voltages on Figure 13–5.
- Replace the voltage source with a short. With the short in place, measure the resistance from point **A** to ground and from point **B** to ground. Enter the measured resistances on Figure 13–5.
- Use the superposition theorem to combine the two Thevenin sources into one equivalent circuit. Show the values of the single equivalent circuit on Figure 13–6.

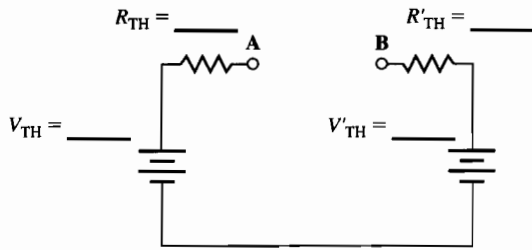


Figure 13-5 Thevenin Circuit for Balanced Bridge

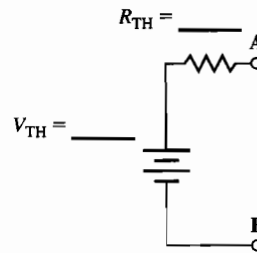


Figure 13-6 Net Thevenin Circuit for Balanced Bridge

Conclusion:

Evaluation and Review Questions:

1. If you doubled the load resistor in a Wheatstone bridge, the load current would *not* be half as much. Why not?

2. (a) Does a change in the load resistor change the currents in the arms of an *unbalanced* bridge?

- (b) Does a change in the load resistor change the currents in the arms of a *balanced* bridge? Explain.

3. (a) What would happen to the load current of an *unbalanced* bridge if all the bridge resistors were doubled in size?

- (b) What would happen to the load current of a *balanced* bridge if all the bridge resistors were doubled in size?

4. (a) What would happen to the load current of an *unbalanced* bridge if the source voltage were doubled?
- (b) What would happen to the load current of a *balanced* bridge if the source voltage were doubled?
5. How can you determine if a Wheatstone bridge is balanced?

For Further Investigation:

To do this investigation, you will need a calibrated Wheatstone bridge, capable of making resistance measurements within 0.1Ω or better. A Wheatstone bridge can determine the location of a short to ground in a multiple conductor cable. The bridge is connected to make a ratio measurement. Simulate a multiple conductor cable with two small diameter wires (#24 gauge or higher) at least 150 ft long. You will need an accurate total resistance of the wire, which you can obtain from the Wheatstone bridge or a sensitive ohmmeter. Place a short to ground at some arbitrary location along the wire. See Figure 13–7 for a diagram. The wire forms two legs of a Wheatstone bridge as illustrated.

Call the total resistance of the wire r (down and back) and the resistance of the wire to the fault a . The bridge is balanced, and the resistance a is determined by the equation shown in Figure 13–7. The fractional distance to the fault is the ratio of a to $(1/2)r$. If you know the total length of the wire, you can find the distance to the fault by setting up a proportion. Investigate this and report on your results.

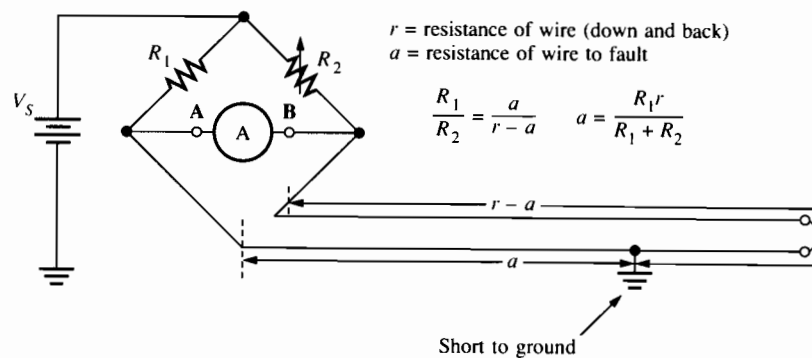


Figure 13–7



Application Assignment 6

Name _____
 Date _____
 Class _____

Reference:

Floyd, Chapter 6, Section 6-9: Application Assignment

Step 1 Draw the schematic:

Step 2 Specify how to connect the power supply so that all resistors are in series and pin 2 has the highest voltage:

Steps 3-6 Complete Table AA-6-1. Determine the unloaded output voltages, the loaded output voltages, the percent deviation between the loaded and unloaded voltages, and the load currents.

Table AA-6-1

10 MΩ Load	$V_{out (2)}$	$V_{out (3)}$	$V_{out (4)}$	% deviation	$I_{load (2)}$	$I_{load (3)}$	$I_{load (4)}$
None							
Pin 2							
Pin 3							
Pin 4							
Pins 2 and 3				2			
				3			
Pins 2 and 4				2			
				4			
Pins 3 and 4				3			
				4			
Pins 2, 3, and 4				2			
				3			
				4			

Step 7 Specify the minimum value for the fuse: _____

Step 8 Troubleshooting:
Case 1: _____
Case 2: _____
Case 3: _____
Case 4: _____
Case 5: _____
Case 6: _____
Case 7: _____
Case 8: _____

Related Experiment:

Materials Needed:

Resistors:

One 68 Ω , one 100 Ω , one 560 Ω

Discussion:

The application assignment involved determining the effects of a load on a voltage divider. Similar effects occur with a resistive matching network. A circuit is designed to match the resistance of a source and load. A circuit that performs this function is called an *attenuator pad*. The L-section shown in Figure AA-6-1 is a loaded voltage divider designed to match a higher resistance to a lower resistance. The load resistance is taken into account in the design of the divider network. The total resistance looking into the L-pad is very close to 600 Ω , the same as the source resistance.

Construct the circuit, and connect a 600 Ω source. The source can be a signal generator with an internal 600 Ω resistance set for a 1.0 kHz sine wave or a dc power supply with a series 600 Ω resistor. Set the source voltage to 5.0 V with a source open. Then connect the L-pad and load and observe V_{in} and V_{out} . What happens to V_{in} when the L-pad and load are connected? Compute and measure the attenuation (ratio of V_{out} to V_{in}). Is there a whole-number ratio between the output voltage and the input voltage? Write a short report on your results.

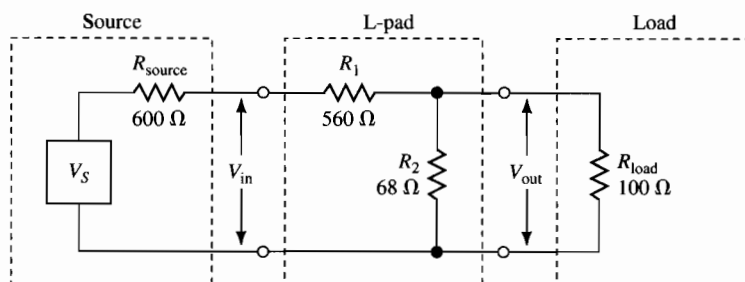


Figure AA-6-1

Checkup 6

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 6, and Buchla, Experiments 10, 11, 12, and 13

- The term that best describes the analysis of a series-parallel circuit is:
(a) one current (b) same voltage (c) equivalent circuits (d) multiple sources
- If two resistors in a series-parallel circuit are connected in series, the voltage across each will be:
(a) the same (b) proportional to the resistance (c) inversely proportional to the resistance (d) equal to the source voltage
- To minimize loading effects on a voltage divider, the load should be:
(a) much smaller than the divider resistors (b) equal to the smallest divider resistor (c) equal to the largest divider resistor (d) much larger than the divider resistors
- When a load resistor is connected to a voltage divider, the current from the source:
(a) increases (b) decreases (c) stays the same
- Assume a voltmeter has a sensitivity factor of $10,000 \Omega/V$. On the 10 V scale, the meter will have an internal resistance of:
(a) 1000Ω (b) $10,000 \Omega$ (c) $100 \text{ k}\Omega$ (d) $1.0 \text{ M}\Omega$
- For the circuit shown in Figure C-6-1, the two resistors that are in series are:
(a) R_1 and R_2 (b) R_2 and R_3 (c) R_2 and R_4 (d) R_3 and R_4
- For the circuit shown in Figure C-6-1, the equivalent Thevenin voltage is:
(a) 1.0 V (b) 3.0 V (c) 4.0 V (d) 12 V
- For the circuit shown in Figure C-6-1, the equivalent Thevenin resistance is:
(a) $6.67 \text{ k}\Omega$ (b) $10 \text{ k}\Omega$ (c) $16.7 \text{ k}\Omega$ (d) $30 \text{ k}\Omega$

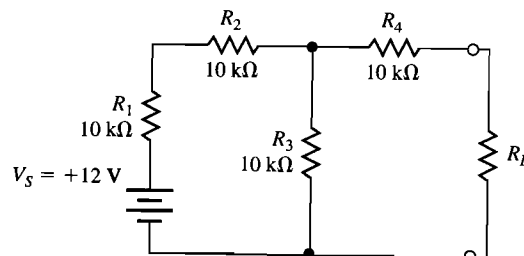


Figure C-6-1

9. To apply the superposition theorem, each source is taken one at a time, as if it were the only source in the circuit. The remaining sources are replaced with:
- (a) their internal resistance (c) a high resistance
 (b) a low resistance (d) an open circuit
10. To find the Thevenin voltage of a source, you could measure:
- (a) the voltage across the load (c) the load resistance
 (b) the current in the load (d) the open-circuit output voltage
11. Assume a $15\text{ k}\Omega$ load resistor is connected to the output terminals of the circuit shown in Figure C-6-1. Compute the voltage and current in the load.
12. Determine the total resistance between the terminals for Figure C-6-2.

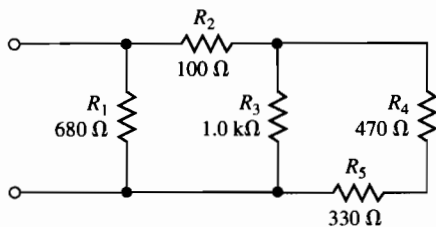


Figure C-6-2

13. The circuit shown in Figure C-6-3 contains two voltage sources. Find the current in R_2 due to both sources.

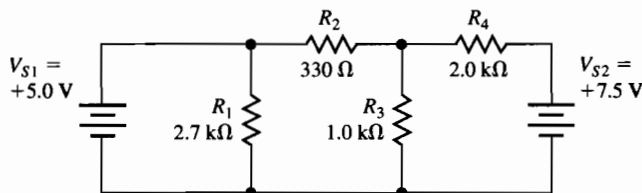


Figure C-6-3

14. Consider the Wheatstone bridge shown in Figure C-6-4. Apply Thevenin's theorem to the bridge and draw the equivalent Thevenin circuit. From the Thevenin circuit, determine the current in R_L .

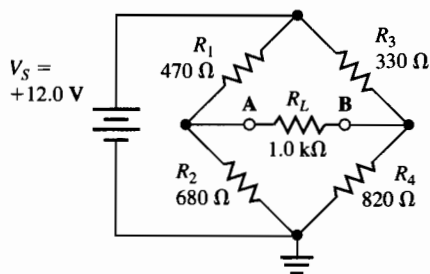


Figure C-6-4

14 Magnetic Devices

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 7-1 through 7-4

Objectives:

After performing this experiment, you will be able to:

1. Determine the pull-in voltage and release voltage for a relay.
2. Connect relay circuits including a relay latching circuit.
3. Explain the meaning of common relay terminology.

Summary of Theory:

Magnetism plays an important role in a number of electronic components and devices including inductors, transformers, relays, solenoids, and transducers. Magnetic fields are associated with the movement of electric charges. By forming a coil, the magnetic field lines are concentrated, a fact that is used in most magnetic devices. Wrapping the coil on a core material such as iron, silicon steel, or permalloy provides two additional advantages. First, the magnetic flux is increased because the *permeability* of these materials is much higher than air. Permeability is a measure of how easily magnetic field lines pass through a material. Permeability is not a constant for a material but depends on the amount of flux in the material. The second advantage of using a magnetic core material is that the flux is more concentrated.

A common magnetic device is the *relay*. The relay is an electromagnetic switch with one or more sets of contacts used for controlling large currents or voltages. The switch contacts are controlled by an electromagnet, called the coil. Contacts are specified as either *normally open* (NO) or *normally closed* (NC) when no voltage is applied to the coil. Relays are *energized* by applying the rated voltage to the coil. This causes the contacts to either close or open.

Relays, like mechanical switches, are specified in terms of the number of independent switches (called *poles*) and the number of contacts (called *throws*). Thus, a single-pole doubled-throw (SPDT) relay has a single switch with two contacts—one normally open and one normally closed. An example of such a relay in a circuit is shown in Figure 14-1. With S_1 open, the motor is off and the light is on. When S_1 is closed, coil CR_1 is energized, causing the NO contacts to close and the NC contacts to open. This applies line voltage to the motor at the same time removes line voltage from the light. Figure 14-1(a) is drawn in a manner similar to many industrial schematics, sometimes referred to as a ladder schematic. The NC contacts are indicated on this schematic with a diagonal line drawn through them. An alternative way of drawing the schematic is shown in Figure 14-1(b). In this drawing, the relay contacts are drawn as a switch.

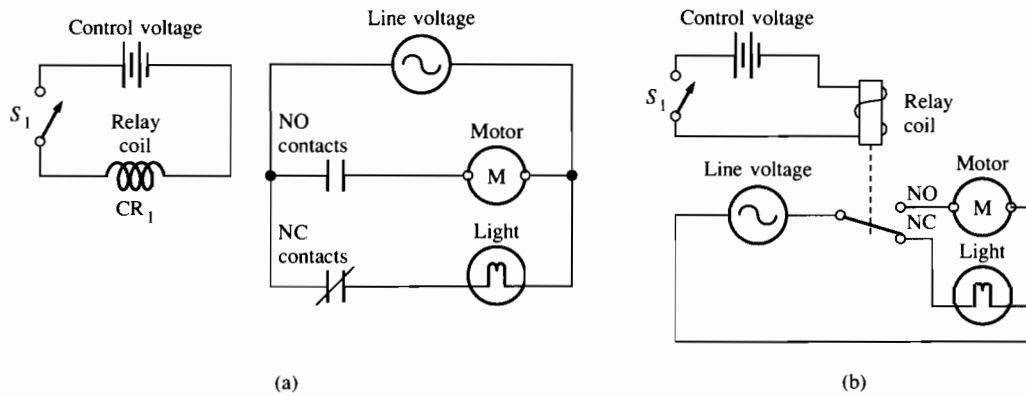


Figure 14-1

Manufacturers specify relays in terms of the ratings for the coil voltage and current, maximum contact current, operating time, and so forth. The specification sheet shows the location of contacts and coil. If these are not available, a technician can determine the electrical wiring of contacts and coil by inspection and ohmmeter tests.

Materials Needed:

- One DPDT relay with a low-voltage dc coil
- Two LEDs: one red, one green
- One SPST switch
- Two 330 Ω resistors

Procedure:

1. Obtain a double-pole double-throw (DPDT) relay with a low-voltage dc coil. The terminals should be numbered. Inspect the relay to determine which terminals are connected to the coil and which are connected to the contacts. The connection diagram is frequently drawn on the relay. Check the coil with an ohmmeter. It should indicate the coil resistance. Check contacts with the ohmmeter. NC contacts should read near zero ohms, and NO contacts should read infinite resistance. You may have difficulty determining which contact is movable until the coil is energized. In the space provided, draw a diagram of your relay, showing the coil, all contacts, and terminal numbers. Record the coil resistance on your drawing.

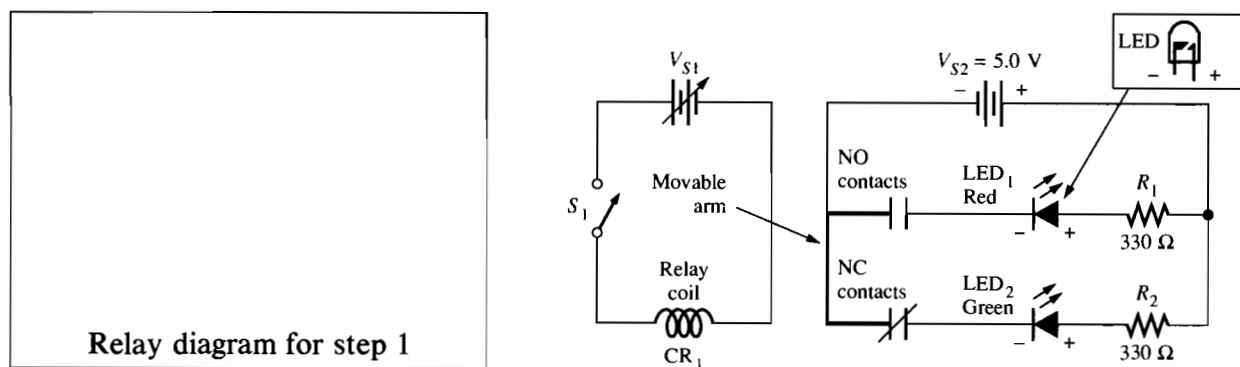


Figure 14-2

2. Connect the circuit shown in Figure 14–2. In this circuit, only one pole of the relay is used. The movable arm is connected to the negative side of V_{S2} . Note carefully the direction of the light-emitting diodes (LEDs). LEDs are polarized and must be connected in the correct direction. V_{S1} is the control voltage and should be set to the specified coil voltage for the relay. V_{S2} represents a line voltage which is being controlled. For safety, a low voltage is used. Set V_{S2} for 5.0 V. If the circuit is correctly connected, the green LED should be on with S_1 open. Close S_1 and verify that the red LED turns on and the green LED goes off.
3. In this step, you will determine the *pull-in voltage* of the relay. The *pull-in voltage* is the minimum value of coil voltage which will cause the relay to switch. Turn V_{S1} to its lowest setting. With S_1 closed, gradually raise the voltage until the relay trips as indicated with the LEDs. Record the pull-in voltage in Table 14–1.
4. The *release voltage* is the value of the coil voltage at which the contacts return to the unenergized position. Gradually lower the voltage until the relay resets to the unenergized position as indicated by the LEDs. Record the release voltage in Table 14–1.
5. Repeat steps 3 and 4 for three trials, entering the results of each trial in Table 14–1.
6. Compute the average pull-in voltage and the average release voltage. Enter the averages in Table 14–1.
7. In this step you will learn how to construct a latching relay. Connect the unused NO contacts from the other pole on the relay in parallel with S_1 as illustrated in Figure 14–3. Set V_{S1} for the rated coil voltage. Close and open S_1 . Describe your observations.

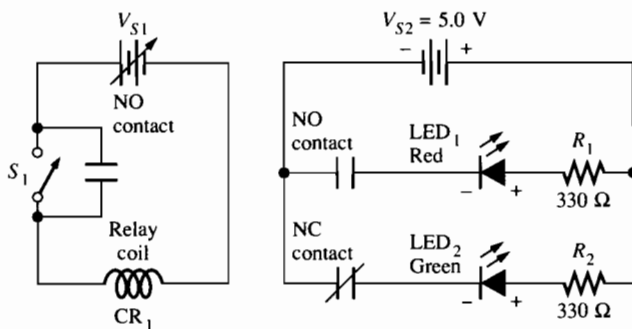


Figure 14–3

Table 14–1

	Pull-in Voltage	Release Voltage
Trial 1		
Trial 2		
Trial 3		
Average		

8. Remove the NO contact from around S_1 . Connect the NC contact in series with S_1 as shown in Figure 14–4. Explain what happens.

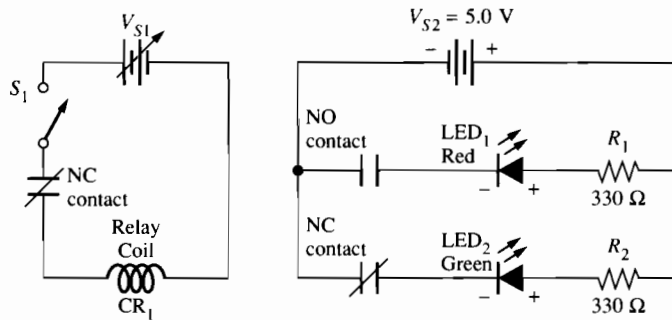


Figure 14–4

Conclusion:

Evaluation and Review Questions:

- Using the average pull-in voltage and the measured resistance of your relay coil, compute the average *pull-in current*. The pull-in current is defined as the minimum value of coil current at which the switching function is completed.
- Repeat Question 1 for the *release current* using the average of the measured release voltage and the measured resistance of the coil.
- Hysteresis can be defined as the difference in response due to an increasing or decreasing signal. For a relay, it is the difference between the pull-in and the release voltage. Compute the hysteresis of your relay.

4. (a) Explain the difference between (a) SPDT and (b) DPST.
- (b) Explain the meaning of NO and NC, as it applies to a relay.
5. For the circuit of Figure 14–1, assume that when S_1 is closed, the light stays on and the motor remains off.
- (a) Name two possible faults that could account for this.
- (b) What procedure would you suggest to isolate the fault?

For Further Investigation:

A DPDT relay can be used to reverse a voltage—such as causing a dc motor to turn in the opposite direction. Consider the problem of reversing a 5.0 V power supply with a single-pole single-throw switch and a relay, as illustrated in the partial schematic in Figure 14–5. When the switch is closed, the red LED should be ON, but when it is opened, the voltage should reverse, causing the green LED to turn on. Complete the schematic that will accomplish the problem; then build and test your circuit.

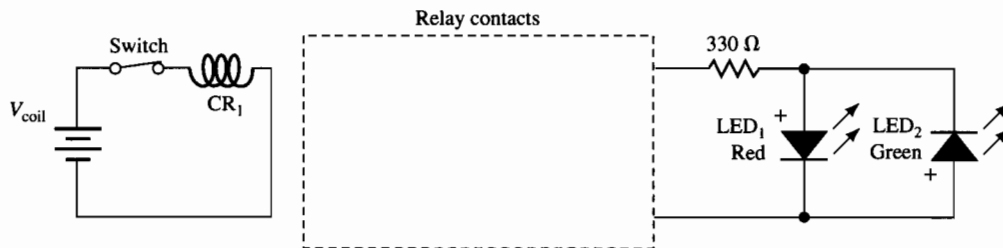


Figure 14–5




Application Assignment 7

Name _____
 Date _____
 Class _____


Reference:

Floyd, Chapter 7, Section 7-7: Application Assignment

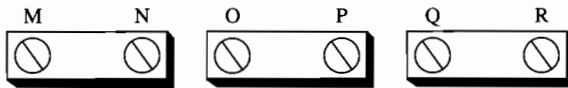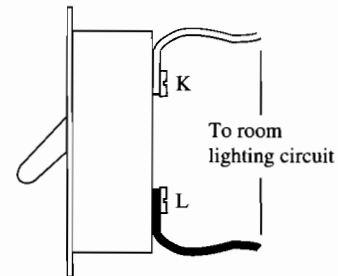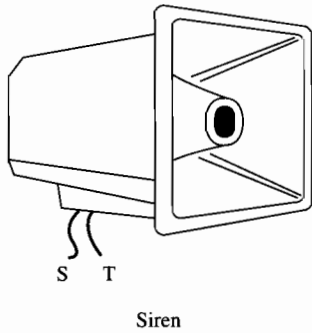
Step 1 Complete the diagram of the system and provide a wire list:




Magnetic switches

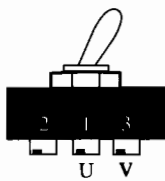

System ON/OFF toggle switch

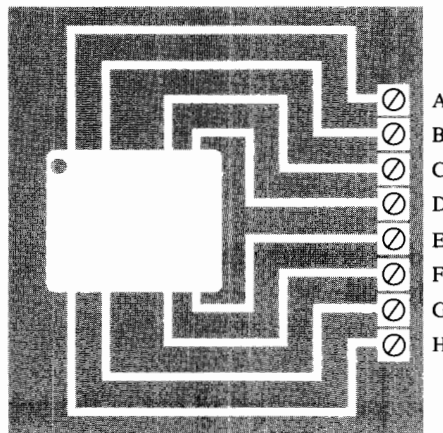

Relay terminal board

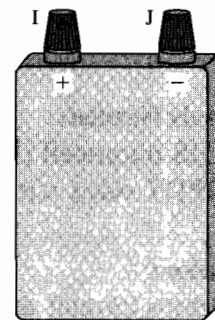

Battery

Figure AA-7-1

Wire list. (First line is given as an example.)

From	-	To	From	-	To
Relay board-A		Relay board-E	Relay board-A		Mag. SW-R

Step 2 Develop a test procedure for the alarm system:

Related Experiment:

Materials Needed:

- One CdS photocell (Radio Shack 276-116 or equivalent)
- One DPDT relay with a low-voltage dc coil

Discussion:

Sometimes burglar alarms, such as the one you figured out in the application assignment, are constructed with a light sensor acting as a switch. Detection is accomplished by breaking a beam of light that is sensed by a photocell. A cadmium sulfide (CdS) photocell is a device that changes its resistance when light strikes it. This change in resistance can be used to energize a relay. Test this idea and devise a circuit in which a CdS cell controls the energizing of a relay. Show the schematic, the measurements you made, and conclusions about your circuit in a short report.

Checkup 7

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 7, and Buchla, Experiment 14

- The magnetic field lines that surround a current-carrying wire are:
(a) parallel to the current (c) perpendicular away from the wire
(b) perpendicular toward the wire (d) concentric circles surrounding the wire
- The magnetic field strength of an electromagnet depends on:
(a) current in the coil (c) number of turns of wire
(b) type of core material (d) all of these
- The magnetic unit most like resistance in an electrical circuit is:
(a) reluctance (b) magnetic flux (c) permeability (d) magnetomotive force
- The magnetic unit most like current in an electrical circuit is:
(a) reluctance (c) permeability
(b) magnetic flux (d) magnetomotive force
- The tesla is the unit of:
(a) magnetizing force (b) flux (c) flux density (d) reluctance
- An electromagnetic device that normally is used to control contact closure in another circuit is a:
(a) solenoid (b) relay (c) switch (d) transistor
- The effect that occurs when an increase in field intensity (H) produces little change in flux density (B) is called:
(a) hysteresis (b) saturation (c) demagnetization (d) permeability
- The relative permeability of a substance is the ratio of absolute permeability to the permeability of:
(a) a vacuum (b) soft iron (c) nickel (d) glass
- The flux density in an iron core depends on the field intensity and the:
(a) area (b) length (c) permeability (d) retentivity
- Assume a coil with an mmf of 500 ampere-turns (A-t) has a flux of $100 \mu\text{Wb}$. The reluctance is:
(a) $5 \times 10^6 \text{ A-t/Wb}$ (b) 0.5 A-t/Wb
(c) $0.2 \times 10^{-6} \text{ A-t/Wb}$ (d) $5 \times 10^{-6} \text{ A-t/Wb}$

11. Show how to use one set of contacts on a DPDT relay to form a latching relay.

12. Explain why you observed that the release voltage of a relay is less than the pull-in voltage.

13.
 - (a) Compare the magnetic field strength of a 1000-turn coil that contains 100 mA of current with a 2000-turn coil that contains 50 mA of current:

 - (b) Compare the field intensity of the two coils, assuming they are both the same length:

14. Explain how Faraday's law accounts for the voltage from a basic dc generator.

15. Assume a flux of $500 \mu\text{Wb}$ is distributed evenly across a rectangular area that is $10 \text{ cm} \times 10 \text{ cm}$.
 - (a) What is the flux density?

 - (b) How much of the flux in (a) will pass through a $1 \text{ cm} \times 1 \text{ cm}$ square?

15 The Oscilloscope

Name _____
Date _____
Class _____

Reading:

Floyd, Section 8–9

Reference Guide to Laboratory Instruments, pages 4 through 10 of this manual

Objectives:

After performing this experiment, you will be able to:

1. Explain the four functional blocks on an oscilloscope and describe the major controls within each block.
2. Use an oscilloscope to measure ac and dc voltages.

Summary of Theory:

The oscilloscope is an extremely versatile instrument that lets you see a picture of the voltage in a circuit as a function of time. The voltage is converted to a visible display by a cathode-ray tube (CRT), a vacuum device similar to a television picture tube. The oscilloscope can be broken into four functional blocks, as illustrated in Figure 15–1. The input signal is coupled through a vertical section to a display section, causing the beam to move up and down as the input voltage moves up or down. A trigger section sends a signal to the horizontal section, causing the beam to move (or *sweep*) across the screen. This horizontal movement must be synchronized with the vertical signal to present a stable display.

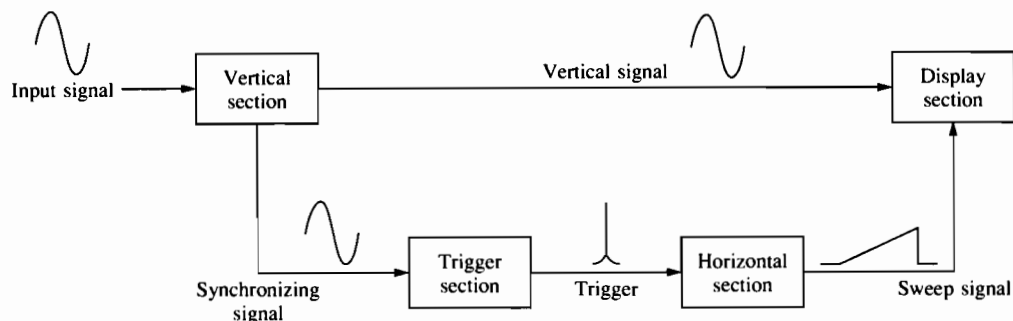


Figure 15–1

Controls for each of the functional blocks are usually grouped together. Frequently, there are color clues to help you identify groups of controls. Look for the controls for each functional group on your oscilloscope. The display controls include INTENSITY, FOCUS, and BEAM FINDER. The vertical controls include input COUPLING, VOLTS/DIV, vertical POSITION, and channel selection (CH1, CH2, DUAL, ALT, CHOP). The triggering controls include MODE, SOURCE, trigger COUPLING, trigger LEVEL, and others. The horizontal controls include the SEC/DIV, MAGNIFIER, and horizontal POSITION control. Details of these controls are explained in the Reference Guide, the text, and the operator's manual for the oscilloscope.

With all the controls to learn, you may experience difficulty obtaining a trace. If you do not see a trace, start by setting the SEC/DIV control to 1 ms/div, select AUTO triggering,

select CH1, and press the BEAM FINDER. Keep the BEAM FINDER button depressed and use the vertical and horizontal POSITION controls to center the trace. If you still have trouble, check the INTENSITY control.

Because the oscilloscope can show a voltage versus time presentation, it is easy to make ac voltage measurements with a scope. However, care must be taken to equate these measurements with meter readings. Typical multimeters show the *rms* value of an ac waveform. This value represents the effective value of an ac waveform when compared to a dc voltage when both produce the same heat in a given load. Usually the *peak-to-peak* value is easiest to read on an oscilloscope. The relationship between the ac waveform as viewed on the oscilloscope and the equivalent rms reading that a DMM will give is illustrated in Figure 15-2.

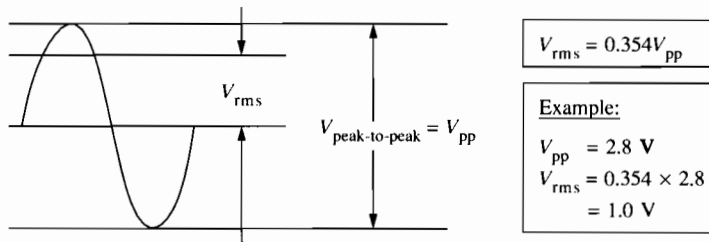


Figure 15-2

Materials Needed:

None

Procedure:

1. Review the front panel controls in each of the major groups. Then turn on the oscilloscope, select CH1, set the SEC/DIV to 0.5 ms/div, select AUTO triggering, and obtain a straight line on the CRT.

2. Turn on your power supply and use the DMM to set the output for 1.0 V. Now use the oscilloscope to measure this dc voltage from the power supply. The following steps will guide you:
 - (a) Place the input COUPLING (AC-GND-DC) in the GND position. This disconnects the input to the oscilloscope. Use the vertical POSITION control to set the ground reference level on a convenient gradicule line near the bottom of the screen.

 - (b) Set the CH1 VOLTS/DIV control to 0.2 V/div. Check that the red vernier control is in the CAL position or your measurement will not be accurate.

 - (c) Place the oscilloscope probe on the positive side of the power supply. Place the oscilloscope ground clip on the power supply common. Move the vertical coupling to the DC position. The line should jump up on the screen by 5 divisions. *Note that 5 divisions times 0.2 V per division is equal to 1.0 V (the*

supply voltage). Multiplication of the number of divisions of deflection times volts per division is equal to the voltage measurement.

3. Set the power supply to each voltage listed in Table 15–1. Measure each voltage using the preceding steps as a guide. The first line of the table has been completed as an example. To obtain accurate readings with the oscilloscope, it is necessary to select the VOLTS/DIV that gives several divisions of change between the ground reference and the voltage to be measured. The readings on the oscilloscope and meter should agree with each other within approximately 3%. When you finish this step, leave the CH1 probe connected to the power supply for the remaining part of the experiment.

Table 15–1

Power Supply Setting	VOLTS/DIV Setting	Number of Divisions of Deflection	Oscilloscope (measured voltage)	DMM (measured voltage)
1.0 V	0.2 V/DIV	5.0 DIV	1.0 V	1.0 V
2.5 V				
4.5 V				
8.3 V				

4. The trigger MODE switch allows you to select either AUTO triggering, NORMAL triggering, or TV (used to simplify looking at video signals). Compare the effect of AUTO triggering with NORMAL triggering while observing a dc level from the power supply. Notice that in NORMAL triggering, the sweep disappears. This is because there is no trigger point with a dc input signal. The oscilloscope’s trigger circuits will not start the sweep generator in NORMAL mode in the absence of a trigger; however, using AUTO triggering, a sweep will occur even without a trigger. This is why you should set up the oscilloscope in the AUTO triggering mode and switch to NORMAL mode only if it is necessary to obtain a stable display.
5. In this step, you will observe an ac waveform on the other channel of your oscilloscope. Set the function generator for an ac waveform with a frequency of 500 Hz. If the function generator has a dc offset control, set it for zero offset. Adjust the amplitude for 1.0 V_{rms} as read on your DMM. Keep the SEC/DIV control at 0.5 ms/div and set the VOLTS/DIV to 0.5 V/div. Select CH2 and connect a second oscilloscope probe and its ground to the signal generator. The CH2 input COUPLING control should be in the DC position. Locate the trigger SOURCE control and select CH2 as the trigger channel. Adjust the CH2 vertical POSITION control and the trigger LEVEL control for a stable display near the center of the screen. You should observe approximately 2.5 cycles of an ac waveform with a peak-to-peak amplitude of 2.8 V. This represents 1.0 V_{rms} as shown in Figure 15–2.
6. Use the DMM to set the signal generator amplitude to each value listed in Table 15–2. Repeat the ac voltage measurement as outlined in step 5. The first line of the table has been completed as an example. Remember, to obtain accurate readings with the

oscilloscope, you should select a VOLTS/DIV setting that gives several divisions of deflection on the screen.

Table 15-2

Signal Generator Amplitude	VOLTS/DIV Setting	Number of Divisions (peak-to-peak)	Oscilloscope Measured (peak-to-peak)	Oscilloscope Measured (rms)
1.0 V _{rms}	0.5 V/DIV	5.6 DIV	2.8 V _{pp}	1.0 V _{rms}
2.2 V _{rms}				
3.7 V _{rms}				
4.8 V _{rms}				

7. In this step, you will observe the effect of the AC-GND-DC input coupling switch. Keep the input coupling switch in the DC position and add some dc offset from your function generator to the ac signal. You should observe that the signal can be displaced from its original position using dc offset because you are adding or subtracting a dc component to the signal. While you are observing the waveform, change the input coupling switch to the AC position. Describe how this control affects the input signal.
-
-

8. In this step you will investigate the trigger LEVEL and SLOPE controls. Use the horizontal POSITION control to move the trace so you can observe the start of the sweep. While observing the beginning of the sweep, adjust the trigger LEVEL control and notice how it controls the point on the waveform that starts to draw the waveform. If it is set too high or too low, the waveform will not be stable. Now try NORMAL triggering again and observe the effect of the trigger LEVEL control. Can you obtain a stable sweep? What happens when the level adjust is outside the range of the signal? Remember to check trigger LEVEL if you are having trouble obtaining a stable sweep. Next try changing the trigger SLOPE control switch and observe what happens. This control allows you to choose either the rising or falling edge of a signal as the trigger point.

9. In this last step, you can observe both the power supply and the function generator at the same time. Select both channels (marked DUAL on some scopes). Each channel can be displayed with its own ground reference point. You will need to leave the trigger SOURCE on channel 2 because the ac waveform is connected to that channel. You can select either ALternate or CHOP mode to view the waveforms. To really see the effects of this control, slow the function generator to 10 Hz and change the horizontal SEC/DIV control to 20 ms/div. Compare the display using ALternate and CHOP. At this slow frequency, it is easier to see the waveforms using the CHOP mode; at high frequencies the ALternate mode is generally preferred.

5. If you wanted to view an ac waveform that was $20.0 V_{\text{rms}}$, what setting of the VOLTS/DIV control would be best?

6. Explain when to select ALternate and when to choose CHOP for viewing two waveforms:

For Further Investigation:

An important part of any oscilloscope measurement is the oscilloscope probe. There are a number of different types of probes for various applications. Probes must be properly compensated for frequency response. Most oscilloscopes have a square wave signal furnished for the purpose of compensating the probe. Using the operator's manual for the oscilloscope at your station and the information furnished for your probe, find out how to compensate your oscilloscope probe. Summarize the method:

16 Sine Wave Measurements

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 8-1 through 8-7

Objectives:

After performing this experiment, you will be able to:

1. Measure the period and frequency of a sine wave using an oscilloscope.
2. Measure across ungrounded components using the difference function of an oscilloscope.

Summary of Theory:

Imagine a weight suspended from a spring. If you stretch the spring and then release it, it will bob up and down with a regular motion. The distance from the rest point to the highest (or lowest) point is called the *amplitude* of the motion. As the weight moves up and down, the time for one complete cycle is called a *period*, and the number of cycles it moves in a second is called the *frequency*. This cyclic motion is called *simple harmonic motion*. A graph of simple harmonic motion as a function of time produces a sine wave, the most fundamental waveform in nature. It is generated as the natural waveform from an ac generator. Figure 16-1 illustrates these definitions.

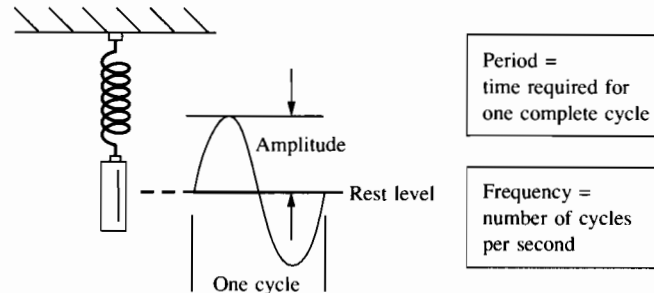


Figure 16-1

Sine waves can also be generated from uniform circular motion. Imagine a circle turning at a constant rate. The *projection* of the endpoint of the radius vector moves with simple harmonic motion. If the end point is plotted along the x -axis, the resulting curve is a sine wave, as illustrated in Floyd's text. This method is frequently used to show the phase relationship between two sine waves of the same frequency.

The sine wave has another interesting property. Different sine waves can be added together to give new waveforms. In fact, any repeating waveform such as a ramp or square wave can be made up of a group of sine waves. This property is useful in the study of the response of circuits to various waveforms.

The oscilloscope is a powerful tool for viewing any waveform in a circuit. In this experiment, you will make timing measurements on sine waves. To measure time, the oscilloscope generates an internal sawtooth waveform that is applied to the horizontal

deflection plates. This signal is the *sweep* or time base of the oscilloscope and is controlled by the SEC/DIV control on the front panel of the oscilloscope. The control generally has a vernier and a magnifier associated with it. It is important that these controls are in the calibrated positions whenever a time measurement is made.

Materials Needed:

Resistors:

One 2.7 kΩ, one 6.8 kΩ

Procedure:

1. Set the signal generator for a 1.0 V_{pp} sine wave at a frequency of 1.25 kHz. Then set the oscilloscope SEC/DIV control to 0.1 ms/div in order to show one complete cycle on the screen. *The expected time for one cycle (the period) is the reciprocal of 1.25 kHz, which is 0.8 ms.* With the SEC/DIV control at 0.1 ms/div, one cycle requires 8.0 divisions across the screen. This is presented as an example in line 1 of Table 16–1.
2. Change the signal generator to each frequency listed in Table 16–1. Complete the table by computing the expected period and then measuring the period with the oscilloscope. Adjust the SEC/DIV control to show between one and two cycles across the screen for each frequency.

Table 16–1

Signal Generator Dial Frequency	Computed Period	Oscilloscope SEC/DIV	Number of Divisions	Measured Period
1.25 kHz	0.8 ms	0.1 ms/div	8.0 div	0.8 ms
1.90 kHz				
24.5 kHz				
83.0 kHz				
600.0 kHz				

3. In this step you will need to use a two-channel oscilloscope with two probes, one connected to each channel. Frequently, a voltage measurement is needed across an ungrounded component. If the oscilloscope ground is at the same potential as the circuit ground, then the process of connecting the probe will put an undesired ground path in the circuit. Figure 16–2 illustrates this.

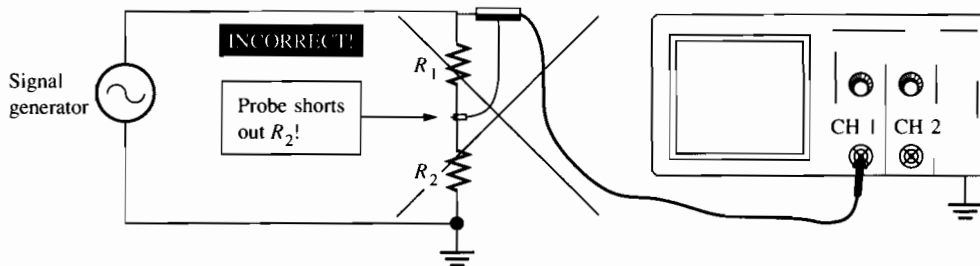


Figure 16–2

The correct way to measure the voltage across the ungrounded component is to use two channels and select the subtract mode—sometimes called the *difference function*—as illustrated in Figure 16–3. The difference function subtracts the voltage measured on channel 2 from the voltage measured on channel 1. It is important that both channels have the same vertical sensitivity—that is, that the VOLTS/DIV setting is the same on both channels and they are both calibrated.

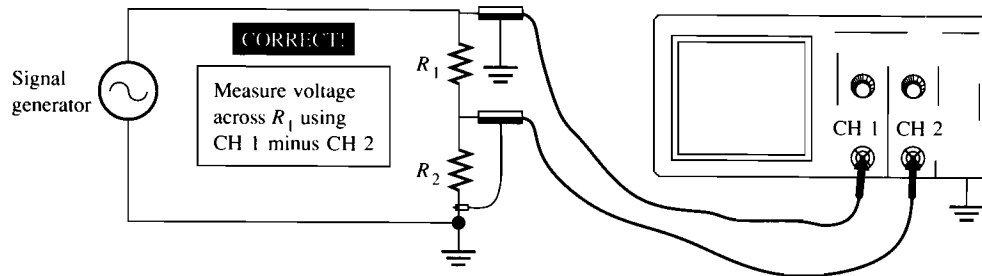


Figure 16–3

Connect the circuit shown in Figure 16–3. Use a 2.7 k Ω resistor for R_1 and a 6.8 k Ω resistor for R_2 . Set the signal generator for a 1.0 V_{pp} sine wave at 10 kHz. Channel 1 will show the voltage from the signal generator. Channel 2 will show the voltage across R_2 . The difference function (CH1 subtract CH2) will show the voltage across R_1 . Some oscilloscopes require that you ADD the channels and INVERT channel 2 in order to measure the difference in the signals.¹ Complete Table 16–2 for the voltage measurements. Use the voltage divider rule to check that your measured voltages are reasonable.

Table 16–2

	Signal Gen. Voltage	Voltage across R_1	Voltage across R_2
Measured			
Computed	1.0 V _{pp}		

Conclusion:

¹If you do not have difference channel capability, then temporarily reverse the components to put R_1 at circuit ground. This can be easily accomplished with a lab breadboard but is usually not practical in a manufactured circuit. While it is possible to isolate the oscilloscope ground and then use one channel to make the measurement, the procedure is not recommended.

17 Pulse Measurements

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 8–8 and 8–9

Objectives:

After performing this experiment, you will be able to:

1. Measure rise time, fall time, pulse repetition time, pulse width, and duty cycle for a pulse waveform.
2. Explain the limitations of instrumentation in making pulse measurements.
3. Compute the oscilloscope bandwidth necessary to make a rise time measurement with an accuracy of 3%.

Summary of Theory:

A pulse is a signal that rises from one level to another, remains at the second level for some time, and then returns to the original level. Definitions for pulses are illustrated in Figure 17–1. The time from one pulse to the next is the period, T . This is often referred to as the *pulse repetition time*. The reciprocal of period is the *frequency*. The time required for a pulse to rise from 10% to 90% of its maximum level is called the *rise time*, and the time to return from 90% to 10% of the maximum level is called the *fall time*. Pulse width, abbreviated t_w , is measured at the 50% level, as illustrated. The duty cycle is the ratio of the pulse width to the period and is usually expressed as a percentage:

$$\text{Percent duty cycle} = \frac{t_w}{T} \times 100\%$$

Actual pulses differ from the idealized model shown in Figure 17–1(a). They may have *sag*, *overshoot*, or *undershoot*, as illustrated in Figure 17–1(b). In addition, if cables are mismatched in the system, *ringing* may be observed. Ringing is the appearance of a short oscillatory transient that appears at the top and bottom of a pulse, as illustrated in Figure 17–1(c).

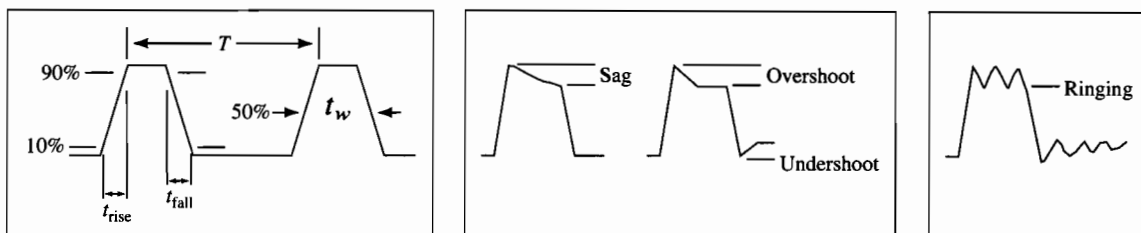


Figure 17–1

All measurements involve some error due to the limitations of the measurement instrument. Oscilloscopes can distort a pulse waveform, including the distortions illustrated in Figure 17–1. In addition, if the rise time of the oscilloscope amplifier is too slow, rise time

distortion may occur. *The oscilloscope rise time should be at least four times faster than the pulse to be measured if the observed rise time is to have less than 3% error.* If the oscilloscope rise time is only twice as fast as the measured rise time, the measurement error rises to over 12%! The oscilloscope rise time is related to the range of useful frequencies it can pass. This range of frequencies is called the *bandwidth*. To find the rise time of an oscilloscope when the bandwidth is known, the following approximate relationship is useful:

$$t_{(r)\text{scope}} = \frac{0.35}{BW}$$

where $t_{(r)\text{scope}}$ is the oscilloscope rise time in microseconds and BW is the bandwidth in megahertz. For example, an oscilloscope with a 60 MHz bandwidth has a rise time of approximately 6 ns. Measurements of pulses with rise times faster than about 24 ns on this oscilloscope will have measurable error. A correction to the measured value can be applied to obtain the actual rise time of a pulse. The correction formula is:

$$t_{(r)\text{true}} = \sqrt{t_{(r)\text{displayed}}^2 - t_{(r)\text{scope}}^2}$$

where $t_{(r)\text{true}}$ is the actual rise time of the pulse, $t_{(r)\text{displayed}}$ is the observed rise time, and $t_{(r)\text{scope}}$ is the rise time of oscilloscope. This formula can be applied to correct observed rise times by 10% or less.

Measurement of pulses normally should be done with the input signal coupled to the scope using DC coupling. This directly couples the signal to the oscilloscope and avoids causing pulse sag which can cause measurement error. Probe compensation should be checked before making pulse measurements. It is particularly important in rise time measurements to check probe compensation. This check is described in this experiment. It is also important in time and voltage measurements to be sure that the appropriate VARIABLE (VAR) controls (usually red) are in their calibrate position. Most oscilloscopes have a detent, or notched, position for these controls so the user is aware when they are calibrated.

Materials Needed:

One 1000 pF capacitor

Procedure:

1. From the manufacturer's specifications, find the bandwidth of the oscilloscope you are using. Normally the bandwidth is specified with a 10X probe connected to the input. You should make oscilloscope measurements with the 10X probe connected to avoid bandwidth reduction. Use the specific bandwidth to compute the rise time of the oscilloscope as explained in the Summary of Theory. This will give you an idea of the limitations of the oscilloscope you are using to make accurate rise time measurements. Enter the bandwidth and rise time of the scope in Table 17-1.
2. Look on your oscilloscope for a probe compensation output. This output provides an internally generated square wave, usually at a frequency of 1.0 kHz. It is a good idea to check this signal when starting with an instrument to be sure that the probe is

properly compensated. To compensate the probe, set the VOLTS/DIV control to view the square wave over several divisions of the display. An adjustment screw on the probe is used to obtain a good square wave with a flat top. An improperly compensated oscilloscope will produce inaccurate measurements. If directed by your instructor, adjust the probe compensation.

3. Set the signal generator for a square wave at a frequency of 100 kHz and an amplitude of 4.0 V. A square wave cannot be measured accurately with your meter—you will need to measure the voltage with an oscilloscope. Check the zero volt level on the oscilloscope and adjust the generator to go from zero volts to 4.0 V. Most signal generators have a separate control to adjust the dc level of the signal.
4. Measure the parameters listed in Table 17–2 for the square wave from the signal generator. Be sure the oscilloscope's SEC/DIV is in its calibrated position. If your oscilloscope has percent markers etched on the front gradicule, you may want to *uncalibrate* the VOLTS/DIV when making rise and fall time measurements. Use the vertical POSITION control and VOLTS/DIV vernier to position the waveform between 0% and 100% markers on the oscilloscope display. Then measure the time between the 10% and 90% markers.

Table 17–1
Oscilloscope

<i>BW</i>	
$t_{(r)}$	

Table 17–2
Signal Generator
(square wave output)

Rise time, $t_{(r)}$	
Fall time, $t_{(f)}$	
Period, T	
Pulse width, t_w	
Percent duty cycle	

Table 17–3
Signal Generator
(with 1000 pF capacitor
across output)

Rise time, $t_{(r)}$	
Fall time, $t_{(f)}$	

5. To obtain practice measuring rise time, place a 1000 pF capacitor across the generator output. Measure the new rise and fall times. Record your results in Table 17–3.
6. If you have a separate pulse output from your signal generator, measure the pulse characteristics listed in Table 17–4. To obtain good results with fast signals, the generator should be terminated in its characteristic impedance (typically 50 Ω). You will need to use the fastest sweep time available on your oscilloscope. Record your results in Table 17–4.

Table 17-4
Signal Generator
(pulse output)

Rise time, $t_{(r)}$	
Fall time, $t_{(f)}$	
Period, T	
Pulse width, t_w	
Percent duty cycle	

Conclusion:

Evaluation and Review Questions:

1. Were any of the measurements limited by the bandwidth of the oscilloscope? If so, which ones?
2. If you need to measure a pulse with a predicted rise time of 10 ns, what bandwidth should the oscilloscope have to measure the time within 3%?
3. The SEC/DIV control on many oscilloscopes has a $\times 10$ magnifier. When the magnifier is ON, the time scale must be divided by 10. Explain.
4. An oscilloscope presentation has the SEC/DIV control set to 2.0 ms/DIV and the $\times 10$ magnifier is OFF. Determine the rise time of the pulse shown in Figure 17-2.

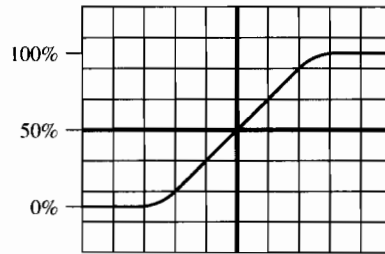


Figure 17-2

5. Repeat Question 4 for the $\times 10$ magnifier ON.

For Further Investigation:

In many applications, it is important to measure time differences. One important technique for doing this is to use *delayed sweep* measurements. If your scope is equipped with delayed sweep, you can trigger from a signal and view a magnified portion of the signal at a later time. With dual time base oscilloscopes, delayed sweep offers increased timing accuracy. If you have a *calibrated* DELAY TIME POSITION dial, you can make differential delay time measurements between two different signals. Most delayed sweep oscilloscopes will have a HORIZONTAL MODE switch which allows you to view either the A sweep, the B sweep, or A intensified by B. The sweep speeds for A and B can be separately controlled, often by concentric rings on the SEC/DIV control. Consult the operator's manual for your oscilloscope to determine the exact procedure.¹ Then practice by measuring the rise time of the pulse generator using delayed sweep. Summarize your procedure and results.

¹An excellent source of information is *The XYZs of Using an Oscilloscope*, Tektronix, Inc., P.O. Box 500, Beaverton, OR 97077.

Application Assignment 8

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 8, Section 8–10: Application Assignment

- Step 1** Review the operation and controls of the function generator.
- Step 2** Review the operation and controls of the oscilloscope.
- Step 3** Measure the sinusoidal output of the function generator.
From Figure 8–65(a)
minimum amplitude: peak: _____ rms: _____
minimum frequency _____
Comparison of frequency with generator setting: _____
From Figure 8–65(b)
maximum amplitude: peak: _____ rms: _____
maximum frequency _____
Comparison of frequency with generator setting: _____
- Step 4** Measure the DC offset of the function generator.
From Figure 8–66(a)
maximum positive dc offset: _____
From Figure 8–66(b)
maximum negative dc offset: _____
- Step 5** Measure the triangular output of the function generator.
From Figure 8–67(a)
minimum amplitude: _____ minimum frequency _____
From Figure 8–67(b)
maximum amplitude: _____ maximum frequency _____
- Step 6** Measure the pulse output of the function generator.
From Figure 8–68(a)
minimum amplitude: _____ minimum frequency _____
duty cycle: _____
From Figure 8–68(b)
maximum amplitude: _____ maximum frequency _____
duty cycle: _____


Related Experiment:

This application requires you to set up the oscilloscope for optimum settings to measure the period and amplitude of different waveforms. When you measure the period of a signal, choose the lowest SEC/DIV setting that shows at least one full cycle on the display. When measuring amplitude, use the lowest VOLT/DIV setting that shows the entire vertical portion of the waveform. Table AA-8-1 lists waveforms to measure. Before making the measurement, consider the best settings of the controls, and enter the settings in the predicted columns. Set up each signal, measure it, and enter the measured values in the table. Then sketch each waveform on the plots shown, showing the oscilloscope display.


Experimental Results:

Table AA-8-1


Function Generator Waveform	Required Amplitude	Required Frequency	VOLTS/DIV Setting (predicted)	SEC/DIV Setting (predicted)	Measured Values of Signal:		
					Horizontal Divisions	Vertical Divisions	Plot Number
Sine wave	1.0 V _{rms}	30 Hz					See Plot AA
Sine wave	5.0 V _{pp}	30 kHz					See Plot AA
Pulse	4.0 V	2.5 kHz					See Plot AA
Pulse	0.5 V	75 kHz					See Plot AA
Sawtooth	2.0 V _{pp}	400 Hz					See Plot AA
Sawtooth	9.0 V _{pp}	10 kHz					See Plot AA

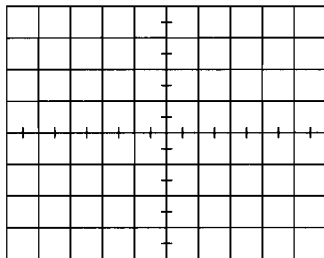


Plot AA-8-1

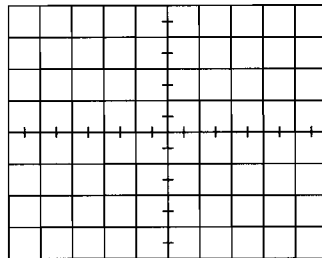


Plot AA-8-2

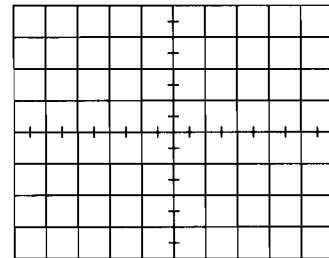


Plot AA-8-3

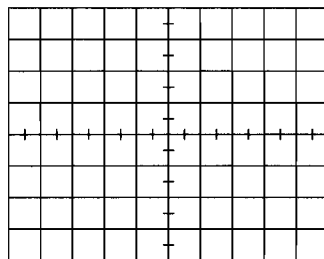

Plot AA-8-4

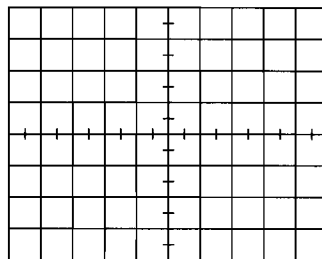

Plot AA-8-5

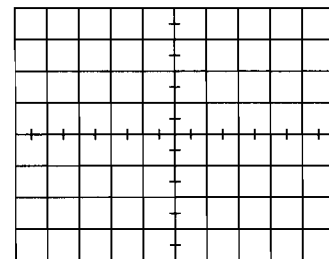

Plot AA-8-6

Name _____
Date _____
Class _____

Checkup 8

Reference:

Floyd, Chap. 8, and Buchla, Experiments 15, 16, and 17

1. A sine wave has a peak-to-peak voltage of 25 V. The rms voltage is:
(a) 8.83 V (b) 12.5 V (c) 17.7 V (d) 35.4 V
2. The number of radians in one-fourth cycle is:
(a) 57.3 (b) $\pi/2$ (c) π (d) 2π
3. Assume a sine wave has 100 complete cycles in 10 s. The period is:
(a) 0.1 s (b) 1 s (c) 10 s (d) 100 s
4. Assume a series resistive circuit contains three equal resistors. The source voltage is a sinusoidal waveform of 30 V_{pp}. What is the rms voltage drop across each resistor?
(a) 3.54 V (b) 5.0 V (c) 10 V (d) 21.2 V
5. Pulse width is normally measured at the:
(a) 10% level (b) 50% level (c) 90% level (d) baseline
6. A waveform characterized by positive and negative ramps of equal slope is called a:
(a) triangle (b) sawtooth (c) sweep (d) step
7. A repetitive pulse train has a pulse width of 2.5 μ s and a frequency of 100 kHz. The duty cycle is:
(a) 2.5% (b) 10% (c) 25% (d) 40%
8. The oscilloscope section that determines when it begins to trace a waveform is:
(a) horizontal (b) vertical (c) trigger (d) display
9. The oscilloscope control that determines how fast the electron beam moves along the x-axis is:
(a) SLOPE (b) HOLDOFF (c) VOLTS/DIV (d) SEC/DIV
10. The oscilloscope control that determines if a rising or falling edge is used to trigger the sweep is:
(a) MODE (b) SLOPE (c) LEVEL (d) COUPLING

11. A standard utility voltage is 115 V at a frequency of 60 Hz.
 (a) What is the peak-to-peak voltage?
 (b) What is the period?
12. How many cycles of a 40 MHz sine wave occur in 0.2 ms?
13. A sinusoidal waveform is represented by the equation $v = 40 \sin(\theta - 35^\circ)$.
 (a) What is the peak voltage?
 (b) What is the phase shift?
14. Figure C-8-1 illustrates an oscilloscope display showing the time relationship between two sine waves. Assume the VOLTS/DIV control is set to 1.0 V/div. Draw a phasor diagram showing the relationship between the two waves.

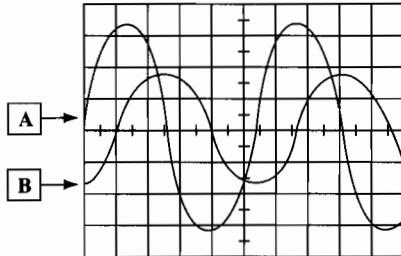


Figure C-8-1

15. Assume the oscilloscope display shown in Figure C-8-1 has the SEC/DIV control set to $5.0 \mu\text{s}/\text{div}$. Determine the frequency of the waveforms.
16. An oscilloscope with a bandwidth of 60 MHz is used to measure a pulse with a rise time of 8 ns.
 (a) What is the equivalent rise time of the scope?
 (b) What is the approximate displayed rise time?

18 Capacitors

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 9–1 through 9–5, Section 9–8

Objectives:

After performing this experiment, you will be able to:

1. Compare total capacitance, charge, and voltage drop for capacitors connected in series and in parallel.
2. Test capacitors with an ohmmeter and a voltmeter.

Summary of Theory:

A capacitor is formed whenever two conductors are separated by an insulating material. When a voltage exists between the conductors, there will be an electric charge between the conductors. The ability to store an electric charge is a fundamental property of capacitors and affects both dc and ac circuits. Capacitors are made with large flat conductors called *plates*. The plates are separated with an insulating material called a *dielectric*. The ability to store charge increases with larger plate size and closer separation.

When a voltage is connected across a capacitor, charge will flow in the external circuit until the voltage across the capacitor is equal to the applied voltage. The charge that flows is proportional to the size of the capacitor and the applied voltage. This is a fundamental concept for capacitors and is given by the equation

$$Q = CV$$

where Q is the charge in coulombs, C is the capacitance in farads, and V is the applied voltage. An analogous situation is that of putting compressed air into a bottle. The quantity of air is directly proportional to the capacity of the bottle and the applied pressure.

Recall that current is defined as charge per time. That is,

$$I = \frac{Q}{t}$$

where I is the current in amperes, Q is the charge in coulombs, and t is the time in seconds. This equation can be rearranged as

$$Q = It$$

If we connect two capacitors in series with a voltage source, the same charging current flows through both capacitors. Since this current flows for the same amount of time, the total charge, Q_T , must be the same as the charge on each capacitor. That is,

$$Q_T = Q_1 = Q_2$$

Charging capacitors in series causes the same charge to be across each capacitor; however, as shown in Floyd's text, the total capacitance *decreases*. In a series circuit, the total capacitance is given by the formula:

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_i}$$

Now consider capacitors in parallel. In a parallel circuit, the total current is equal to the sum of the currents in each branch as stated by Kirchhoff's current law. If this current flows for the same amount of time, the total charge leaving the voltage source will equal the sum of the charges which flow in each branch. Mathematically:

$$Q_T = Q_1 + Q_2 + \dots + Q_i$$

Capacitors connected in parallel will raise the total capacitance because more charge is stored at the same voltage. The equation for the total capacitance of parallel capacitors is:

$$C_T = C_1 + C_2 + \dots + C_i$$

There are two quick tests you can make to check capacitors. The first is an ohmmeter test, useful for capacitors larger than 0.01 μF . This test is best done with an analog ohmmeter rather than a digital meter. The test will sometimes indicate a faulty capacitor is good; however, you can be sure that if a capacitor fails the test, it is bad. The test is done as follows:

- (a) Remove one end of the capacitor from the circuit and discharge it by placing a short across its terminals.
- (b) Set the ohmmeter on a high-resistance scale and place the negative lead from an ohmmeter on the negative terminal of the capacitor. You must connect the ohmmeter with the proper polarity. *Do not assume the common lead from the ohmmeter is the negative side!*
- (c) Touch the other lead of the ohmmeter onto the remaining terminal of the capacitor. The meter should indicate very low resistance and then gradually increase resistance. If you put the meter in a higher range, the ohmmeter charges the capacitor slower and the capacitance "kick" will be emphasized. For small capacitors (under 0.01 μF), this charge may not be seen. Large electrolytic capacitors require more time to charge, so use a lower range on your ohmmeter. Capacitors should never remain near zero resistance, as this indicates a short. An immediate high resistance reading indicates an open for larger capacitors.

A capacitor that passes the ohmmeter test may fail when working voltage is applied. A voltmeter can be used to check a capacitor with voltage applied. The voltmeter is connected in *series* with the capacitor, as indicated in Figure 18–1. When voltage is first applied, the capacitor charges making it appear shorted. As it charges, voltage will appear across it, and

the voltmeter indication should be a very small voltage. Large electrolytic capacitors may have leakage current that makes them appear bad, especially with a very high impedance voltmeter. In this case, use the test as a relative test, comparing the reading with a similar capacitor that you know is good.

Materials Needed:

Two LEDs

Resistors:

Two 1.0 kΩ

Capacitors:

One of each : 100 μF, 47 μF, 1.0 μF, 0.1 μF, 0.01 μF (35 WV or greater)

Procedure:

1. Obtain five capacitors as listed in Table 18–1. Check each capacitor using the ohmmeter test described in the Summary of Theory. Record the results of the test in Table 18–1.
2. Test each capacitor using the voltmeter test as illustrated in Figure 18–1. Large electrolytic capacitors may appear to fail this test. Check the voltage rating on the capacitor to be sure it is not exceeded. The working voltage is the maximum voltage that can safely be applied to the capacitor. Record your results in Table 18–1.

Table 18–1

Capacitor	Listed Value	Ohmmeter Test Pass/Fail	Voltmeter Test Pass/Fail
C ₁	100 μF		
C ₂	47 μF		
C ₃	1.0 μF		
C ₄	0.1 μF		
C ₅	0.01 μF		

3. Connect the circuit shown in Figure 18–2. The switches can be made from wire. Leave both switches open. The light-emitting diodes (LEDs) and the capacitor are both polarized components—they must be connected in the correct direction in order to work properly.

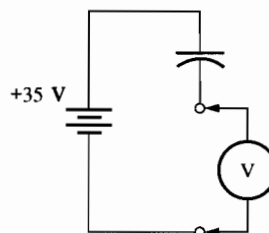


Figure 18–1

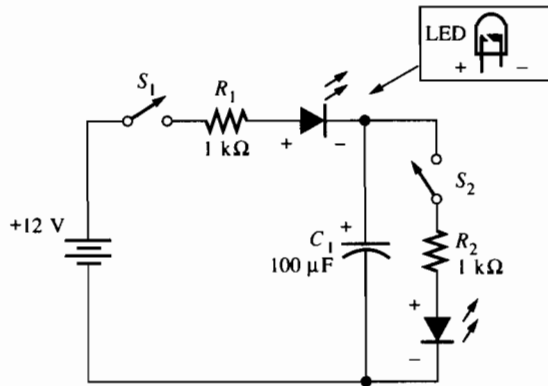


Figure 18-2

4. Close S_1 and observe the LEDs. Describe your observation.

5. Open S_1 and close S_2 . What happens?

6. Now connect C_2 in series with C_1 . Open S_2 . Make certain the capacitors are fully discharged by shorting them with a piece of wire; then close S_1 . Measure the voltage across each capacitor. Do this quickly to prevent the meter from causing the capacitors to discharge. Record the voltages and describe your observations.

$V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$

Observations:

7. Using the measured voltage, compute the charge on each capacitor.

$Q_1 = \underline{\hspace{2cm}}$ $Q_2 = \underline{\hspace{2cm}}$

Then open S_1 and close S_2 . Observe the result.

8. Change the capacitors from series to parallel. Ensure that the capacitors are fully discharged. Open S_2 and close S_1 . Repeat steps 4 and 5 for the parallel connection.

$$V_1 = \underline{\hspace{2cm}} \quad V_2 = \underline{\hspace{2cm}}$$

Observations:

$$Q_1 = \underline{\hspace{2cm}} \quad Q_2 = \underline{\hspace{2cm}}$$

9. Replace the 12 V dc source with a signal generator. Close both S_1 and S_2 . Set the signal generator to a square wave and set the amplitude to $12 V_{pp}$. Set the frequency to 10 Hz. Notice the difference in the LED pulses. This demonstrates one of the principal applications of large capacitors—that of filtering. Explain your observations.

Conclusion:

Evaluation and Review Questions:

1. Why did the LEDs flash for a shorter time in step 6 than in steps 4 and 5?


2. What would happen if you added more series capacitance in step 6?

3. (a) What is the total capacitance when a $1.0 \mu\text{F}$ capacitor is connected in parallel with a $2.0 \mu\text{F}$ capacitor?
- (b) If the capacitors are connected in series, what is the total capacitance?
- (c) In the previous series connection, which capacitor has the greater voltage across it?
4. A $3.0 \mu\text{F}$ capacitor is charged to 100 V . If it is then connected in parallel with a $10 \mu\text{F}$ capacitor, what voltage will be across the capacitors?
5. Two capacitors, labeled *A* and *B*, have the same charge, but *A* has twice the voltage across it than *B*. Which capacitor has the greater capacitance? Prove your answer.

For Further Investigation:


Use the oscilloscope to measure the waveforms across the capacitors and the LEDs in step 9. Try speeding up the signal generator and observe the waveforms. Use the two-channel difference measurement explained in Experiment 16 to see the waveform across the ungrounded LED. Draw and label the waveforms.

Capacitor waveform:

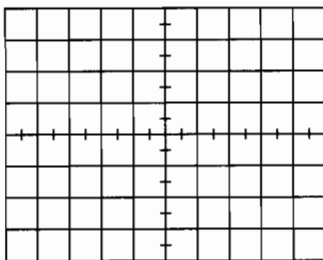

Plot 18-1

LED waveform:

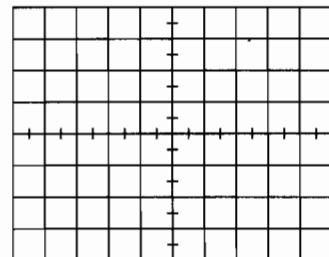

Plot 18-2

19 Capacitive Reactance

Name _____

Date _____

Class _____

Reading:

Floyd, Sections 9-6 through 9-7

Objectives:

After performing this experiment, you will be able to:

1. Measure the capacitive reactance of a capacitor at a specified frequency.
2. Compare the reactance of capacitors connected in series and parallel.

Summary of Theory:

If a resistor is connected across a sine wave generator, a current flows that is *in phase* with the applied voltage. If, instead of a resistor, we connect a capacitor across the generator, the current is not in phase with the voltage. This is illustrated in Figure 19-1. Note that the current and voltage have exactly the same frequency, but the current is *leading* the voltage by 1/4 cycle.

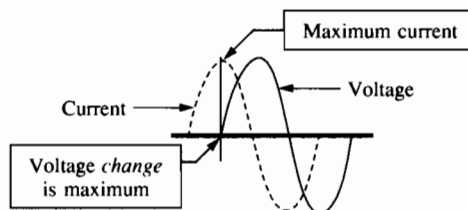


Figure 19-1

Current flow in the capacitor is directly proportional to the capacitance and the rate of change of voltage. The largest current flows when the voltage *change* is a maximum. If the capacitance is increased or the frequency is increased, more current will flow. This is why a capacitor is sometimes thought of as a high-frequency short.

Reactance is the opposition to ac current flow and is measured in ohms, like resistance. Capacitive reactance is written with the symbol X_C . It can be defined as:

$$X_C = \frac{1}{2\pi fC}$$

where f is the generator frequency in hertz and C is the capacitance in farads.

Ohm's law can be generalized to ac circuits. For a capacitor, we can find the voltage across the capacitor using the current and the capacitive reactance. Ohm's law for the voltage across a capacitor is written

$$V_C = IX_C$$

Materials Needed:

Capacitors:

One of each: 0.1 μF , 0.047 μF , 1.0 μF

Resistors:

One of each: 1.0 $\text{k}\Omega$, 4.7 $\text{k}\Omega$, 10 $\text{k}\Omega$

For Further Investigation:

Two 100 μF capacitors, two LEDs, one 100 $\text{k}\Omega$ resistor

Procedure:

1. Obtain two capacitors with the values shown in Table 19–1. If you have a capacitance bridge available, measure their capacitance and record in Table 19–1; otherwise, record the listed value of the capacitors. Measure and record the value of resistor R_1 .
2. Set up the circuit shown in Figure 19–2. Set the generator for a 1.0 kHz sine wave with a 1.0 V rms output. Measure the rms voltage with your DMM while it is connected to the circuit.¹ Check the frequency and voltage with the oscilloscope.
Note: $1.0 \text{ V}_{\text{rms}} = 2.828 \text{ V}_{\text{pp}}$.

Table 19–1

Component	Listed Value	Measured Value
C_1	0.1 μF	
C_2	0.047 μF	
R_1	1.0 $\text{k}\Omega$	

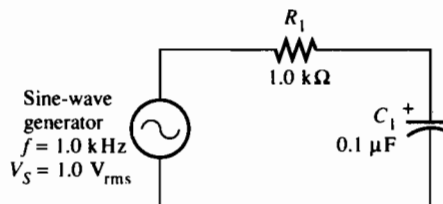


Figure 19–2

3. The circuit is a series circuit, so the current in the resistor is the identical current seen by the capacitor. You can find this current easily by applying Ohm's law to the resistor. Measure the voltage across the resistor, V_R , using the DMM. Record the measured voltage in Table 19–2 in the column labeled Capacitor C_1 . Compute the current in the circuit by dividing the measured voltage by the resistance of R_1 and enter in Table 19–2.
4. Measure the rms voltage across the capacitor, V_C . Record this voltage in Table 19–2. Then use this voltage to compute the capacitive reactance using Ohm's law:

$$X_C = \frac{V_C}{I}$$

Enter this value as the capacitive reactance in Table 19–2.

¹DMMs have a relatively low bandwidth, although most can measure 1.0 kHz. Verify that the DMM you are using has at least a 1.0 kHz bandwidth; if it does not, use the oscilloscope for all voltage measurements.

Table 19–2

	Capacitor C_1	Capacitor C_2
Voltage across R_1 , V_R		
Total current, I		
Voltage across C , V_C		
Capacitive reactance, X_C		
Computed capacitance, C		

5. Using the capacitive reactance found in step 4, compute the capacitance using the equation

$$C = \frac{1}{2\pi f X_C}$$

Enter the computed capacitance in Table 19–2. This value should agree with the value marked on the capacitor and measured in step 1 within experimental tolerances.

6. Repeat steps 3, 4, and 5 using capacitor C_2 . Enter the data in Table 19–2 in the column labeled Capacitor C_2 .
7. Now connect C_1 in series with C_2 . The equivalent capacitive reactance and capacitance can be found for the series connection by measuring across both capacitors as if they were one capacitor. Enter the data in Table 19–3 in the column labeled Series Capacitors. The following steps will guide you:
- Check that the generator is set to 1.0 V rms. Find the current in the circuit by measuring the voltage across the resistor as before and dividing by the resistance. Enter the measured voltage and the current you found in Table 19–3.
 - Measure the voltage across *both* capacitors. Enter this voltage in Table 19–3.
 - Use Ohm's law to find the capacitive reactance of both capacitors. Use the voltage measured in step (b) and the current measured in step (a).
 - Compute the total capacitance by using the equation

$$C_T = \frac{1}{2\pi f X_{CT}}$$

8. Connect the capacitors in parallel and repeat step 7. Assume the parallel capacitors are one equivalent capacitor for the measurements. Enter the data in Table 19–3 in the column labeled Parallel Capacitors.

Table 19–3

Step		Series Capacitors	Parallel Capacitors
(a)	Voltage across R_1 , V_R		
	Total current, I		
(b)	Voltage across capacitors, V_C		
(c)	Capacitive reactance, X_{CT}		
(d)	Computed capacitance, C_T		

Conclusion:

Evaluation and Review Questions:

1. Compare the capacitive reactance of the series capacitors with the capacitive reactance of the parallel capacitors. Use your data in Table 19–3.
2. Compare the total capacitance of the series capacitors with the total capacitance of the parallel capacitors.
3. If someone had mistakenly used too small a capacitor in a circuit, what would happen to the capacitive reactance?
4. How could you apply the method used in this experiment to find the value of the unknown capacitor?

5. Compute the capacitive reactance for an 800 pF capacitor at a frequency of 250 kHz.

For Further Investigation:

A voltage multiplier is a circuit that uses diodes and capacitors to increase the peak value of a sine wave. Voltage multipliers can produce high voltages without requiring a high-voltage transformer. The circuit illustrated in Figure 19–3 is a full-wave voltage doubler. The circuit is drawn as a bridge with diodes in two arms and capacitors in two arms. The diodes allow current to flow in only one direction, charging the capacitors to near the peak voltage of the sine wave. Generally, voltage doublers are used with 60 Hz power line frequencies and with ordinary diodes, but in order to clarify the operation of this circuit, you can use the LEDs that were used in this experiment. (Note that this causes the output voltage to be reduced slightly.) Connect the circuit, setting the function generator to 20 V_{pp} sine wave at a frequency of 1.0 Hz. (If you cannot obtain a 20 V_{pp} signal, use the largest signal you can obtain from your generator.) Observe the operation of the circuit, then try speeding up the generator. Look at the waveform across the load resistor with your oscilloscope using the two-channel difference method. What is the dc voltage across the load resistor? What happens to the output as the generator is speeded up? Try a smaller load resistor. Can you explain your observations?

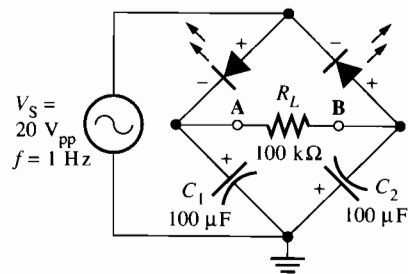


Figure 19–3



Application Assignment 9

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 9, Section 9–9: Application Assignment

Step 1 Compare the PC board with the schematic. Do they agree?

Step 2 Test the input to amplifier board 1. If incorrect, specify the likely fault:

Step 3 Test the input to amplifier board 2. If incorrect, specify the likely fault:

Step 4 Test the input to amplifier board 3. If incorrect, specify the likely fault:

Related Experiment:

Materials Needed:

Resistors:

One 1.0 k Ω , two 10 k Ω

Capacitors:

One 0.1 μ F, 1.0 μ F

Discussion:

The capacitor tests described in Experiment 18 can be conducted only on a capacitor that has been removed from the circuit under test. Usually there are other components that could account for a circuit failure; you need to have an idea of the reason for the failure before you randomly check parts. If a capacitor fails because it is open, it has no effect on the dc voltages but will not pass ac. If it fails because it is shorted, both dc and ac paths are affected. Other failures (such as the wrong size component) may produce a partial failure.

The circuit shown in Figure AA–9–1 is similar to the problem presented in the text. Capacitor C_1 represents a coupling capacitor and R_1 and R_2 set up the bias conditions needed

for an amplifier. R_3 represents additional source resistance. Start by investigating the circuit when it is operating normally. Find the ac and dc voltage drops across each component. Then open C_1 and check circuit operation. Are there any changes to the dc voltages with the open capacitor? Then test the circuit with a short across C_1 (use a jumper). Finally, assume a capacitor that is too small was accidentally put in the circuit. Replace C_1 with a $0.1 \mu\text{F}$ capacitor and test the circuit. Table AA-9-1 is set up to record your data. Write a conclusion for your observations.

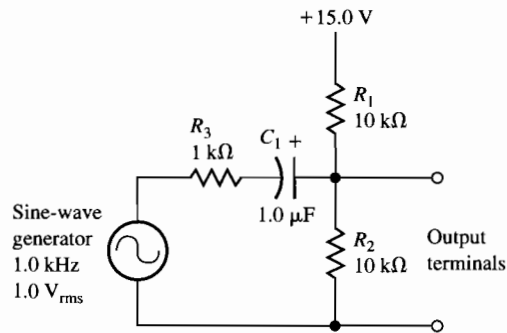


Figure AA-9-1

Table AA-9-1

Condition	Measured Voltages							
	V_{R1}		V_{R2}		V_{R3}		V_{C1}	
	dc	ac	dc	ac	dc	ac	dc	ac
Normal								
C_1 Open								
C_1 Shorted								
C_1 Wrong value								

Experimental Results:

Checkup 9

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 9, and Buchla, Experiments 18 and 19

- Assume two capacitors have the same voltage across them but capacitor *A* has twice the charge of capacitor *B*. From this we can conclude that:
(a) *A* is larger. (c) *B* is larger.
(b) They are equal. (d) No conclusion can be made.
- Assume two capacitors have equal capacitances, but capacitor *A* has twice the voltage of capacitor *B*. From this we can conclude that:
(a) *A* has larger plates. (c) *A* has a greater charge.
(b) *A* has smaller plates. (d) *A* has less charge.
- Assume capacitor *A* is larger than capacitor *B*. If they are connected in series, the total capacitance will be:
(a) larger than *A* (c) larger than *B*
(b) smaller than *B* (d) between *A* and *B*
- Compared to any one capacitor, the total capacitance of three equal parallel capacitors is:
(a) one-third (b) the same (c) double (d) three times
- Assume a 100 μF capacitor is charged to 10 V. The stored charge is:
(a) 10 μC (b) 100 μC (c) 110 μC (d) 1000 μC
- In a series *RC* circuit, the time required for a capacitor to go from no charge to full charge (99%) is:
(a) one time constant (c) five time constants
(b) three time constants (d) 100 ms
- A sinusoidal voltage waveform is applied to a capacitor. The amount of current is inversely proportional to the:
(a) reactance (b) capacitance (c) frequency (d) resistance
- A sinusoidal voltage waveform is applied to a capacitor. If the frequency of the waveform is increased, the capacitance:
(a) increases (b) does not change (c) decreases
- The unit of measurement for capacitive reactance is the:
(a) volt (b) ohm (c) farad (d) coulomb

10. The power that is stored or returned to the circuit from a capacitor is called:
 (a) stored power (c) true power
 (b) apparent power (d) reactive power
11. The time constant of an RC circuit is measured with an oscilloscope and found to require 7.6 divisions to change from 0 to 63% of the final value. The SEC/DIV control is set to $20 \mu\text{s}/\text{div}$.
 (a) If the resistance is $4.7 \text{ k}\Omega$, what is the measured value of the capacitance?
 (b) How long after charging begins does it take the capacitor to reach full charge?
12. Assume you want to check a $100 \mu\text{F}$ capacitor to see if it is capable of storing a charge. What simple test would you perform?

13. Consider the circuit shown in Figure C-9-1.
 (a) Compute the capacitive reactance of each capacitor.

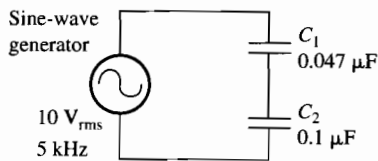


Figure C-9-1

- (b) Determine the voltage across each capacitor.
14. Consider the circuit shown in Figure C-9-2. C_1 is known to be $0.047 \mu\text{F}$, but the value of C_2 is unknown. Assume you measure $6.8 \text{ V}_{\text{rms}}$ across C_2 . What is its capacitance?

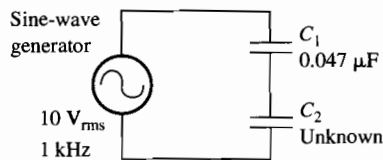


Figure C-9-2

20 Inductors

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 10–1 through 10–5

Objectives:

After performing this experiment, you will be able to:

1. Describe the effect of Lenz's law in a circuit.
2. Measure the time constant of an LR circuit and test the effects of series and parallel inductances on the time constant.

Summary of Theory:

When a current flows through a coil of wire, a magnetic field is created around the wire. This electromagnetic field accompanies any moving electric charge and is proportional to the magnitude of the current. If the current changes, the electromagnetic field causes a voltage to be induced across the coil, which opposes the change. This property, which causes a voltage to oppose a **change** in current, is called *inductance*.

Inductance is the electrical equivalent of inertia in a mechanical system. It opposes a change in *current* in a manner similar to the way capacitance opposed a change in *voltage*. This property of inductance is described by Lenz's law. According to Lenz's law, an inductor develops a voltage across it that counters the effect of a *change* in current in the circuit. The induced voltage is equal to the inductance times the rate of change of current. Inductance is measured in *henries*. *One henry is defined as the quantity of inductance present when one volt is generated as a result of a current changing at the rate of one ampere per second.* Coils that are made to provide a specific amount of inductance are called *inductors*.

When inductors are connected in series, the total inductance is the sum of the individual inductors. This is similar to resistors connected in series. Likewise, the formula for parallel inductors is similar to the formula for parallel resistors. Unlike resistors, an additional effect can appear in inductive circuits. This effect is called *mutual inductance* and is caused by interaction of the magnetic fields. The total inductance can be either increased or decreased due to mutual inductance.

Inductive circuits have a time constant associated with them, just as capacitive circuits do, except the rising exponential curve is a picture of the *current* in the circuit rather than the *voltage* as in the case of the capacitive circuit. Unlike the capacitive circuit, if the resistance is greater, the time constant is shorter. The time constant is found from the equation

$$\tau = \frac{L}{R}$$

where τ represents the time constant in seconds when L is in henries and R is in ohms.

Materials Needed:

Two 7 H inductors (approximate value)
(second inductor may be shared from another experiment)

One neon bulb (NE-2 or equivalent)

One 33 k Ω resistor

For Further Investigation:

One unknown inductor

Procedure:

1. In this step, you can observe the effect of Lenz's law. Connect the circuit shown in Figure 20–1 with a neon bulb in parallel with a large inductor. Neon bulbs contain two insulated electrodes in a glass envelope containing neon gas. The gas will not conduct unless the voltage reaches approximately 70 V. When the gas conducts, the bulb will glow. When the switch is closed, dc current in the inductor is determined by the inductor's winding resistance. Close and open S_1 several times and observe the results.

Observations:

2. Find out if the neon bulb will fire if the voltage is lowered. How low can you reduce the voltage source and still observe the bulb to glow? _____

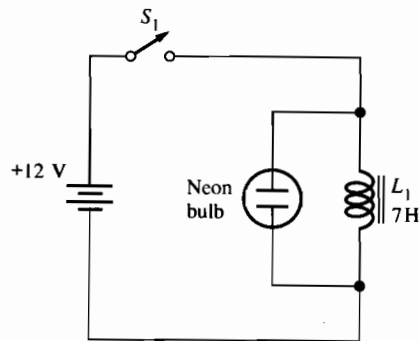


Figure 20–1


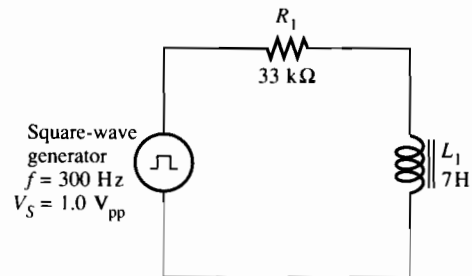


Figure 20–2

3. Connect the circuit shown in Figure 20–2. This circuit will be used to view the waveforms from a square wave generator. Set the generator, V_S , for a 1.0 V_{pp} square wave at a frequency of 300 Hz. This frequency is chosen to allow sufficient time to see the effects of the time constant. View the generator voltage on CH1 of a two-channel oscilloscope and the inductor waveform on CH2. If both channels are calibrated and have the VOLTS/DIV controls set to the same setting, you will be able to see the voltage across the resistor using the difference channel. Set the oscilloscope SEC/DIV control to 0.5 ms/div. Sketch the waveforms you see on Plot 20–1.

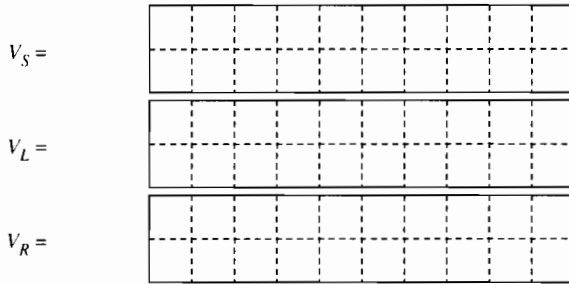

Plot 20–1

Table 20–1

	Computed Time	Measured Time
Time constant, τ		

4. Compute the time constant for the circuit. Enter the computed value in Table 20–1. Now measure the time constant by viewing the waveform across the resistor. The resistor voltage has the same shape as the current in the circuit, so you can measure the time constant by finding the time required for the resistor voltage to change from 0 to 63% of its final value. Stretch the waveform across the oscilloscope screen to make an accurate time measurement. Enter the measured time constant in Table 20–1.
5. When inductors are connected in series, the total inductance increases. When they are connected in parallel, the total inductance decreases. You can see the effect of decreasing the inductance by connecting a second 7 H inductor in parallel with the first. Note what happens to the voltage waveforms across the resistor and the inductor. Then connect the inductors in series and compare the effect on the waveforms. Describe your observations.

Conclusion:

Evaluation and Review Questions:

1. The ionizing voltage for a neon bulb is approximately 70 V. Explain how a 12 V source was able to cause the neon bulb to conduct.

2. When a circuit containing an inductor is opened suddenly, an arc may occur across the switch. How does Lenz's law explain this?

3. What is the total inductance when two 100 mH inductors are connected in series?
_____ in parallel? _____

4. What would happen to the time constant in Figure 20–2 if a 3.3 k Ω resistor were used instead of the 33 k Ω resistor?

5. What effect does an increase in the frequency of the square wave generator have on the waveforms observed in Figure 20–2?

For Further Investigation:

Suggest a method in which you could use a square wave generator and a known resistor to determine the inductance of an unknown inductor. Then obtain an unknown inductor from your instructor and measure its inductance. Report on your method, results, and how your result compares to the accepted value for the inductor.

21 Inductive Reactance

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 10–6 through 10–8

Objectives:

After performing this experiment, you will be able to:

1. Measure the inductive reactance of an inductor at a specified frequency.
2. Compare the reactance of inductors connected in series and parallel.

Summary of Theory:

When a sine wave is applied to an inductor, a voltage is induced across the inductor as given by Lenz's law. When the *change* in current is a maximum, the largest induced voltage appears across the inductor. This is illustrated in Figure 21–1. Notice that when the current is not changing (at the peaks), the induced voltage is zero. For this reason, the voltage that appears across an inductor leads the current in the inductor by 1/4 cycle.

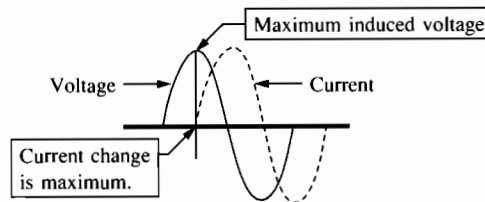


Figure 21–1

If we *raise* the frequency of the sine wave, the rate of change of current is increased and the value of the opposing voltage is increased. This results in a net *decrease* in the amount of current that flows. Thus, the inductive reactance is increased by an increase in frequency. The inductive reactance is given by the equation

$$X_L = 2\pi fL$$

This equation reveals that a linear relationship exists between the inductance and the reactance at a constant frequency. Recall that in series, the total inductance is the sum of individual inductors (ignoring mutual inductance). The reactance of a series inductors is, therefore, also the sum of the individual reactances. Likewise, in parallel, the reciprocal formula which applies to parallel resistors can be applied to both the inductance and the inductive reactance.

Ohm's law can be applied to inductive circuits. The reactance of an inductor can be found by dividing the voltage across the inductor by the current in it. That is,

$$X_L = \frac{V_L}{I_L}$$

Materials Needed:

Two 100 mH inductors

One 1 kΩ resistor

For Further Investigation:


One 12.6 V center-tapped transformer

Procedure:

1. Measure the inductance of each of two 100 mH inductors and record their measured values in Table 21–1. Measure and record the value of a 1.0 kΩ resistor. Use the listed values if you cannot measure the inductors.
2. Connect the circuit shown in Figure 21–2. Set the generator for a 1.0 kHz sine wave with a 1.0 V_{rms}. Measure the generator voltage with your DMM while it is connected to the circuit.¹ Check the frequency and voltage with the oscilloscope. Remember to convert the oscilloscope voltage reading to rms voltage to compare it to the DMM.

Table 21–1

Component	Listed Value	Measured Value
L_1	100 mH	
L_2	100 mH	
R_1	1.0 kΩ	

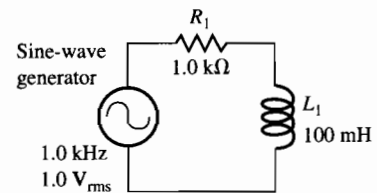**Figure 21–2**

3. The circuit is a series circuit, so the current in the resistor is the identical current that flows through the inductor. First, find the voltage across the resistor with the DMM. Then apply Ohm's law to the resistor to find the current in the circuit. Record the measured voltage and the computed current in Table 21–2 in the column labeled Inductor L_1 .
4. Measure the voltage across the inductor with the DMM. Then find the inductive reactance by Ohm's law. Enter the values in Table 21–2.
5. Now compute the inductance based on the equation

$$L = \frac{X_L}{2\pi f}$$

Enter the computed inductance in Table 21–2.

¹DMMs have a relatively low bandwidth, although most can measure 1.0 kHz. Verify that the DMM you are using has at least a 1.0 kHz bandwidth; if it does not, use the oscilloscope for all voltage measurements.

Table 21–2

	Inductor L_1	Inductor L_2
Voltage across R_1 , V_R		
Total current, I		
Voltage across L , V_L		
Inductive reactance, X_L		
Computed inductance, L		

6. Replace L_1 with L_2 and repeat steps 3, 4, and 5. Enter the data in Table 21–2 in the column labeled Inductor L_2 .

7. Place L_2 in series with L_1 . Then find the inductive reactance for the series combination of the inductors as if they were one inductor. Enter the data in Table 21–3 in the column labeled Series Inductors. The following steps will guide you:
 - (a) Check that the generator is set to 1.0 V rms. Find the current in the circuit by measuring the voltage across the resistor as before and dividing by the resistance.

 - (b) Measure the voltage across *both* inductors.

 - (c) Use Ohm’s law to find the inductive reactance of both inductors. Use the voltage measured in step (b) and the current found in step (a).

 - (d) Compute the total inductance by using the equation

$$L = \frac{X_L}{2\pi f}$$

Table 21–3

Step		Series Inductors	Parallel Inductors
(a)	Voltage across R_1 , V_R		
	Total current, I		
(b)	Voltage across inductors, V_L		
(c)	Inductive reactance, X_L		
(d)	Computed inductance, L		

8. Connect the inductors in parallel and repeat step 7. Assume the parallel inductors are one equivalent inductor for the measurements. Enter the data in Table 21–3 in the column labeled Parallel Inductors.

Conclusion:

Evaluation and Review Questions:

1. (a) Using the data in Table 21–2, compute the sum of the inductive reactances of the two inductors:

$$X_{L1} + X_{L1} =$$

- (b) Using the data in Table 21–2, compute the product-over-sum of the inductive reactances of the two inductors:

$$\frac{(X_{L1})(X_{L2})}{X_{L1} + X_{L2}} =$$

- (c) Compare the results from (a) and (b) with the reactances for the series and parallel connections listed in Table 21–3. What conclusion can you draw from these data?

2. Repeat Question 1 using the data for the inductance, L . Compare the inductance of series and parallel inductors.

3. What effect would an error in the frequency of the generator have on the data for this experiment?

4. How could you apply the method used in this experiment to find the value of an unknown inductor?

5. Compute the inductive reactance of a $50\ \mu\text{H}$ inductor at a frequency of 50 MHz.

For Further Investigation:

A transformer consists of two or more coils wound on a common iron core. Frequently, one or more windings has a *center tap*, which splits a winding into two equal inductors. Because the windings are on the same core, mutual inductance exists between the windings. Obtain a small power transformer that has a low-voltage center-tapped secondary winding. Determine the inductance of each half of the winding using the method in this experiment. Then investigate what happens if the windings are connected in series. Keep the output of the signal generator constant for the measurements. Summarize your results.

Application Assignment 10

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 10, Section 10–9: Application Assignment

- Step 1* Measure the coil resistance and select a series resistor.
- Step 2* Determine the time constant and the approximate inductance of coil 1.
- Step 3* Determine the time constant and the approximate inductance of coil 2.
- Step 4* Discuss how you could find the approximate inductance of the coils using a sinusoidal input instead of a square wave.

Related Experiment:

Materials Needed:

- Two decade boxes
- One 0.1 μF capacitor (for a standard)
- One 1.0 k Ω resistor
- One 100 mH inductor (or other value from about 1 mH to 100 mH)

Discussion:

A Maxwell bridge is commonly used to measure inductors that do not have a very high Q . It employs a fixed capacitor and two resistors as standards. The circuit for a Maxwell bridge is shown in Figure AA-10-1. Construct the bridge using two decade resistance boxes for R_1 and R_2 and a measured capacitor of $0.1 \mu\text{F}$ for C_1 . A 100 mH inductor from Experiment 21 (or any unknown from about 1 mH to 100 mH) can be used for the unknown. R_3 is a fixed $1.0 \text{ k}\Omega$ resistor. Measure the output voltage between terminals A and B with your DMM. Adjust both decade boxes for the minimum voltage observed on the DMM.

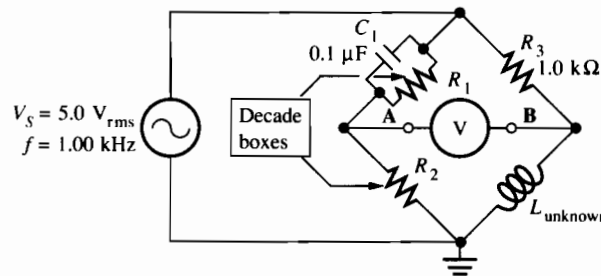


Figure AA-10-1

After you have adjusted the decade boxes for minimum voltage across the A and B terminals, the circuit is a balanced ac bridge. The bridge is balanced when the product of the impedance of the diagonal elements is equal. The equations for the Maxwell bridge, given without proof, are

$$L_{\text{unknown}} = R_2 R_3 C_1$$

$$Q = 2\pi f C_1 R_1$$

Measure the unknown inductor with your Maxwell bridge. Compare your measurement with a laboratory bridge. What measurement errors account for the differences in the two measurements?

Experimental Results:

Checkup 10

Name _____

Date _____

Class _____

Reference:

Floyd, Chap. 10, and Buchla, Experiments 20 and 21

1. The voltage induced across an inductor by a changing magnetic field tends to:
(a) oppose the current in the inductor (c) oppose the voltage across the inductor
(b) oppose a change in the current (d) oppose a change in the voltage
2. Assume a neon bulb is in parallel with a large inductor. When current is interrupted by opening a switch, the neon bulb glows for a short time. This is due to:
(a) the rapid change in resistance (c) collapsing electric field
(b) the time constant of the circuit (d) induced voltage across the inductor
3. The total inductance of parallel inductors is always:
(a) less than the smallest inductor (c) greater than the smallest inductor
(b) less than the largest inductor (d) greater than the largest inductor
4. Assume two inductors have the same physical size and core material but inductor A has twice the number of windings of inductor B. From this we can conclude that the:
(a) inductance of A is one-fourth that of B (c) inductance of A is twice that of B
(b) inductances are equal (d) inductance of A is four times that of B
5. The time constant for a series *RL* circuit consisting of a 10 k Ω resistor and a 30 mH inductor is:
(a) 3 μ s (b) 15 μ s (c) 30 μ s (d) 300 μ s
6. The instant after the switch is closed in a series *RL* circuit, the voltage across the inductor is:
(a) zero (b) equal to the voltage across the resistor
(c) 63% of the source voltage (d) equal and opposite to the source voltage
7. The instant after the switch is closed in a series *RL* circuit, the voltage across the resistor is:
(a) zero (b) equal to the voltage across the inductor
(c) 63% of the source voltage (d) equal and opposite to the source voltage
8. One time constant after a switch is closed in a series *RL* circuit, the current will be:
(a) 37% of its final value (c) 63% of its final value
(b) 50% of its final value (d) 100% of its final value
9. The unit of inductive reactance is the:
(a) farad (b) henry (c) ohm (d) second

10. An inductor is connected across a sinusoidal generator. If the generator frequency is increased, the inductance:
 (a) decreases (b) stays the same (c) increases
11. Name four factors that affect the inductance of a coil.
12. Compare the waveforms you observed for the pulse response of an RC circuit with the waveforms observed in an RL circuit.
13. For a sinusoidal input, compare the phase difference between voltage and current for an RC circuit with that of an RL circuit.
14. The total inductance of two series inductors is $900\ \mu\text{H}$.
 (a) If one of the inductors is $350\ \mu\text{H}$, what is the inductance of the other?
 (b) Assume a $10\ \text{V}$ sinusoidal waveform is applied to the two series inductors. What is the voltage across the $350\ \mu\text{H}$ inductor?
15. In Experiment 20 (Figure 20–2), the frequency of the generator was set to $300\ \text{Hz}$. Could a higher frequency have been specified for this experiment? Why or why not?
16. For the circuit in Figure C–10–1, assume the voltage across the resistor is $2.1\ \text{V}$, and the voltage across the inductor is $4.0\ \text{V}$. If the source frequency is $100\ \text{kHz}$, determine the inductive reactance and the inductance of the unknown.

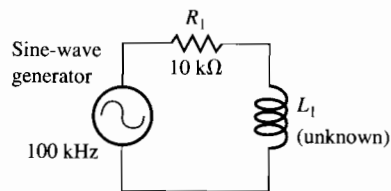


Figure C–10–1

22 Transformers

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 11–1 through 11–11

Objectives:

After performing this experiment, you will be able to:

1. Determine the turns ratio for a transformer.
2. Show the phase relationships between the primary and secondary of a center-tapped transformer.
3. Compute the turns ratio required for matching a signal generator to a speaker.
4. Demonstrate how an impedance matching transformer can increase the power transferred to a load.

Summary of Theory:

A transformer consists of two (or more) closely coupled coils that share a common magnetic field. When an ac voltage is applied to the first coil, called the *primary*, a voltage is induced in the second coil, called the *secondary*. The voltage that appears across the secondary is proportional to the transformer turns ratio. The turns ratio is found by dividing the number of turns in the secondary winding by the number of turns in the primary winding. The turns ratio, n , is directly proportional to the primary and secondary voltages. That is,

$$n = \frac{N_S}{N_P} = \frac{V_S}{V_P}$$

For most work, we can assume that a transformer has no internal power dissipation and that all the magnetic flux lines in the primary also cut through the secondary—that is, we can assume the transformer is *ideal*. The ideal transformer delivers to the load 100% of the applied power. Actual transformers have losses due to magnetizing current, eddy currents, coil resistance, and so forth. In typical power applications, transformers are used to change the ac line voltage from one voltage to another or to isolate ac grounds. For the ideal transformer, the secondary voltage is found by multiplying the turns ratio by the applied primary voltage. That is,

$$V_S = nV_P$$

Since the ideal transformer has no internal losses, we can equate the power delivered to the primary to the power delivered by the secondary. Since $P = IV$, we can write:

$$\text{Power} = I_P V_P = I_S V_S$$

This equation shows that if the transformer causes the secondary voltage to be higher than the primary voltage, the secondary current must be less than the primary current. Also, if the transformer has no load, then no primary or secondary current will flow in the ideal transformer.

In addition to their ability to change voltages and isolate grounds, transformers are useful to change the resistance (or *impedance*) of a load as viewed from the primary side. (Impedance is a more generalized word meaning opposition to ac current.) The load resistance appears to increase by the turns ratio squared (n^2) when viewed from the primary side. Transformers used to change impedance are designed differently from power transformers. They need to transform voltages over a band of frequencies with low distortion. Special transformers called *audio*, or *wideband*, transformers are designed for this. To find the correct turns ratio needed to match a load impedance to a source impedance, use the following equation:

$$n = \sqrt{\frac{R_{\text{load}}}{R_{\text{source}}}}$$

In this experiment, you will examine both a power transformer and an impedance matching transformer and calculate parameters for each.

Materials Needed:

One 12.6 V center-tapped transformer

One small impedance matching transformer (approximately 600 Ω to 800 Ω)

One small speaker (4 or 8 Ω)

For Further Investigation:

One 100 Ω resistor

Procedure:

1. Obtain a low-voltage power transformer with a center-tapped secondary (12.6 V secondary). Using an ohmmeter, measure the primary and secondary resistance. Record in Table 22–1.
2. Compute the turns ratio based on the normal line voltage (V_p) of 115 V and the specified secondary voltage of 12.6 V. Record this as the computed turns ratio, n , in Table 22–1.
3. For safety, we will use an audio generator in place of ac line voltages. Connect the circuit illustrated in Figure 22–1. Power transformers are designed to operate at a specific frequency (generally 60 Hz). Set the generator to a 60 Hz sine wave at 5.0 V_{rms} on the primary. Measure the secondary voltage. From the measured voltages, compute the turns ratio for the transformer. Enter this value as the measured turns ratio in Table 22–1.
4. Compute the percent difference between the computed and measured turns ratio and enter the result in Table 22–1. The percent difference is found from the equation:

$$\%diff = \frac{n(meas.) - n(comp.)}{n(comp.)} \times 100\%$$

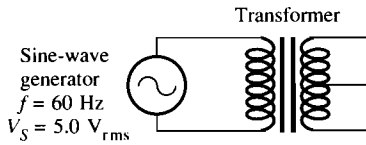


Figure 22-1

Table 22-1

Primary winding resistance, R_P	
Secondary winding resistance, R_S	
Turns ratio, n (computed)	
Turns ratio, n (measured)	
% difference	

- Connect a two-channel oscilloscope to the secondary, as illustrated in Figure 22-2(a). Trigger the oscilloscope from channel 1. Do not use compromise triggering. Compare the phase of the primary side viewed on channel 1 with the phase of the secondary side viewed on channel 2. Then reverse the leads on the secondary side. Describe your observations.
- Connect the oscilloscope ground to the center tap of the transformer and view the signals on each side at the center tap at the same time as illustrated in Figure 22-2(b). Sketch the waveforms beside the figures showing measured voltages.

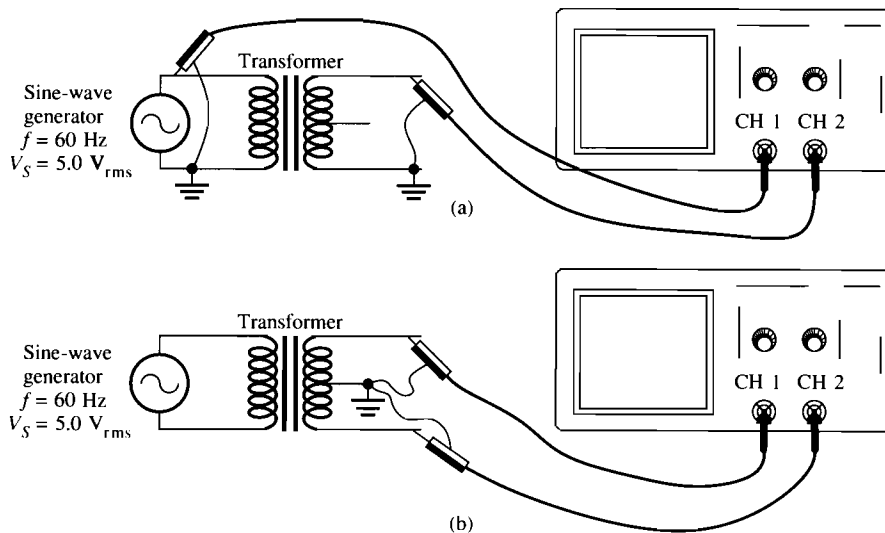


Figure 22-2

- In this step, a transformer will be used to match a source impedance to a load impedance. A small speaker represents a low impedance (typically 4 or 8 Ω), whereas a signal generator is typically 600 Ω of Thevenin impedance. An impedance matching transformer can make the load appear to have the same impedance as the source. This

allows maximum power to be transferred to the load. Connect a small speaker directly to your signal generator and set the frequency to approximately 2 kHz. Note the volume of the sound from the speaker. Measure the voltage across the speaker.

$$V_{\text{SPKR}} = \underline{\hspace{2cm}}$$

8. Using the specified Thevenin impedance of the generator and the specified speaker impedance, compute the turns ratio required to match the speaker with your signal generator.

$$n = \underline{\hspace{2cm}}$$

9. Connect a small impedance matching transformer into the circuit. It is not necessary to obtain the precise turns ratio required to note the improvement in the power delivered to the speaker. You can find the correct leads to the primary and secondary of the impedance matching transformer using an ohmmeter. Since the required transformer is a step down type, the primary resistance will be higher than the secondary resistance. Often, the primary winding will have a center tap for push-pull amplifiers. Again measure the voltage across the speaker.

$$V_{\text{SPKR}} = \underline{\hspace{2cm}}$$

Conclusion:

Evaluation and Review Questions:

1. (a) Using the data from step 1, compute a resistance ratio between the secondary and primary coils by dividing the measured secondary resistance by the measured primary resistance.

$$\text{Resistance ratio} = \underline{\hspace{2cm}}$$

- (b) What factors could cause the computed resistance ratio to differ from the turns ratio?

2. What factors might cause a difference between the measured and computed turns ratio in steps 2 and 3?

3. Compare the voltage across the speaker as measured in step 7 and in step 9. Explain why there is a difference.
4. The power supplied to an ideal transformer should be zero if there is no load. Why?
5. (a) If an ideal transformer has 115 V across the primary and draws 200 mA of current, what power is dissipated in the load?
 - (b) If the secondary voltage in the transformer of part (a) is 24 V, what is the secondary current?
 - (c) What is the turns ratio?

For Further Investigation:

The ideal transformer model neglects a small current that flows in the primary independent of secondary load current. This current, called the *magnetizing* current, is required to produce the magnetic flux and is added to the current that is present due to the load. The magnetizing current appears to be flowing through an equivalent inductor parallel to the ideal transformer. Investigate this current by connecting the circuit in Figure 22–3 using the impedance matching transformer. Calculate the magnetizing current, I_M , in the primary by measuring the voltage across a series resistor with no load and applying Ohm's law:

$$I_M = \frac{V_R}{R}$$

Find out if the magnetizing current changes as frequency is changed. Be sure to keep the generator at a constant 5.0 V_{rms}.

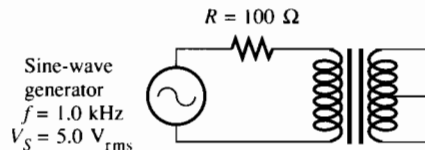


Figure 22–3

Name _____
 Date _____
 Class _____

Application Assignment 11

Reference:

Floyd, Chapter 11, Section 11–12: Application Assignment

Step 1 Familiarization with the power supply.

Step 2 Measure voltages on power supply unit 1. Determine from the readings whether or not the unit is working properly. If not, isolate the problem to one of the items in Table AA–11–1.

Table AA–11–1

Unit 1 is:
A) working properly B) has the following problem: a) rectifier, filter, or regulator b) transformer c) fuse d) power source

Step 3 Measure voltages on power supply units 2, 3, 4. Determine from the readings whether or not the unit is working properly. If not, isolate the problem to one of the items in Table AA–11–2.

Table AA–11–2

Unit 2 is:	Unit 3 is:	Unit 4 is:
A) working properly B) has the following problem: a) rectifier, filter, or regulator b) transformer c) fuse d) power source	A) working properly B) has the following problem: a) rectifier, filter, or regulator b) transformer c) fuse d) power source	A) working properly B) has the following problem: a) rectifier, filter, or regulator b) transformer c) fuse d) power source

Related Experiment:

Materials Needed:

- One small speaker (4 or 8 Ω)
- One 20 Ω variable resistor

Discussion:

To match the impedance of a speaker to an amplifier, you need to know the impedance of the speaker. You can measure the impedance of a speaker by the circuit shown in Figure

AA-11-1. Set the scope controls as follows: CH 1, 0.1 V/div; CH 2, 50 mV/div (this is a 2:1 ratio); and SEC/DIV, 0.5 ms/div. The variable controls should be in the calibrated position. Adjust the peak-to-peak amplitude of the function generator to about 300 mV_{pp} (actual value is not critical) and center both traces. Then adjust the potentiometer until the two signals appear as one—they should appear superimposed on each other. At this point, the impedance of the speaker is the same as the impedance of the potentiometer. (Why?) Remove the potentiometer and measure its resistance.

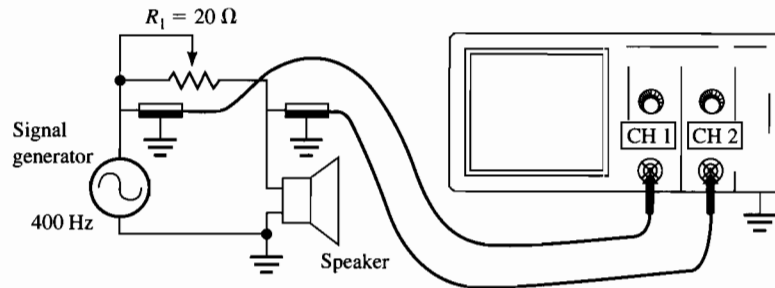


Figure AA-11-1

A variation of the method is to observe the waveform using the XY mode. Switch to XY mode but do not change the vertical sensitivity of the channels. At 400 Hz, the speaker impedance is primarily resistive, and a straight line at a 45° slope should be observed. Note how changing the potentiometer affects the line. Now try raising the frequency. Does the impedance of the speaker change? Try 20 kHz and see what happens. Summarize your findings.

Experimental Results:

Checkup 11

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 11, and Buchla, Experiment 22

- Transformers work by the principle of:
(a) self-inductance (c) hysteresis
(b) mutual inductance (d) coupled electric fields
- The efficiency of an ideal transformer is:
(a) 90% (b) 95% (c) 100% (d) dependent on the transformer
- Air core transformers are primarily used for:
(a) impedance matching (c) power
(b) isolation (d) radio frequencies
- The impedance seen on the primary side of an impedance matching transformer is called:
(a) load resistance (c) reflected resistance
(b) primary resistance (d) winding resistance
- A transformer with a single winding that can be adjusted with a sliding mechanism is known as a(n):
(a) variac (b) rheostat (c) isolation transformer (d) tapped transformer
- If a transformer has a much lower secondary voltage than primary voltage, which of the following is true?
(a) $P_S > P_P$ (b) $N_S > N_P$ (c) $I_S > I_P$ (d) efficiency is very poor
- A transformer with a turns ratio of 2 has a primary voltage of 110 V. The secondary voltage is:
(a) 55 V (b) 110 V (c) 220 V (d) 440 V
- An ideal transformer with a turns ratio of 5 has a primary voltage of 110 V and a secondary load consisting of a 100 Ω resistor. The primary current is:
(a) 0.22 A (b) 1.1 A (c) 5.5 A (d) 27.5 A
- An impedance matching transformer is needed to match an 8 Ω load to a 600 Ω source. The ideal reflected resistance is:
(a) 8 Ω (b) 16 Ω (c) 600 Ω (d) 1200 Ω
- The turns ratio for the transformer in Question 9 is:
(a) 0.0133 (b) 0.115 (c) 8.66 (d) 75

23 Series RC Circuits

Name _____
 Date _____
 Class _____

Reading:

Floyd, Sections 12–1 through 12–3

Objectives:

After performing this experiment, you will be able to:

1. Compute the capacitive reactance of a capacitor from voltage measurements in a series RC circuit.
2. Draw the impedance and voltage phasor diagrams for a series RC circuit.
3. Explain how frequency affects the impedance and voltage phasors in a series RC circuit.

Summary of Theory:

When a sine wave at some frequency drives a circuit that contains only linear elements (resistors, capacitors, and inductors), the waveforms throughout the circuit are also sine waves at that same frequency. To understand the relationship between the sinusoidal voltages and currents, we can represent ac waveforms as phasor quantities. A *phasor* is a complex number used to represent a sine wave's amplitude and phase. A graphical representation of the phasors in a circuit is a useful tool for visualizing the amplitude and phase relationship of the various waveforms. The algebra of complex numbers can then be used to perform arithmetic operations on sine waves.

Figure 23–1(a) shows an RC circuit with its impedance phasor diagram plotted in Figure 23–1(b). The total impedance is $5\text{ k}\Omega$, producing a current in this example of 1.0 mA . In any series circuit, the same current flows throughout the circuit. By multiplying each of the phasors in the impedance diagram by the current in the circuit, we arrive at the voltage phasor diagram illustrated in Figure 23–1(c). It is convenient to use current as the reference for comparing voltage phasors because the current is the same throughout. Notice the direction of current. The voltage and the current are in the same direction across the resistor because they are in phase, but the voltage across the capacitor lags the current by 90° . The generator voltage is the phasor sum of the voltage across the resistor and the voltage across the capacitor.

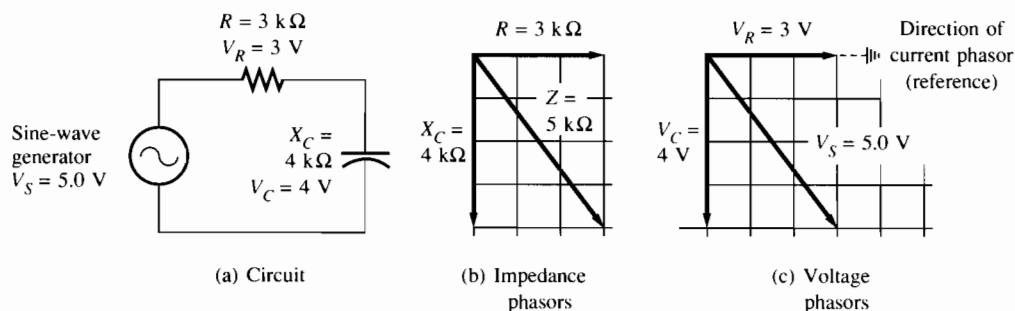


Figure 23–1

The phasor diagram illustrated by Figure 23–1 is correct only at one frequency. This is because the reactance of a capacitor is frequency dependent as given by the equation:

$$X_C = \frac{1}{2\pi fC}$$

As the frequency is raised, the reactance (X_C) of the capacitor decreases. This changes the phase angle and voltages across the components. These changes are investigated in this experiment.

Materials Needed:

- One 6.8 kΩ resistor
- One 0.01 μF capacitor

Procedure:

1. Measure the actual capacitance of a 0.01 μF capacitor and a 6.8 kΩ resistor. Enter the measured values in Table 23–1. If you cannot measure the capacitor, use the listed value.
2. Connect the series RC circuit shown in Figure 23–2. Set the signal generator for a 500 Hz sine wave at 3.0 V_{pp}. The voltage should be measured with the circuit connected. Set the voltage with a voltmeter, and check both voltage and frequency with the oscilloscope. Record all voltages and currents throughout this experiment as peak-to-peak values.

Table 23–1

Component	Listed Value	Measured Value
C_1	0.01 μF	
R_1	6.8 kΩ	

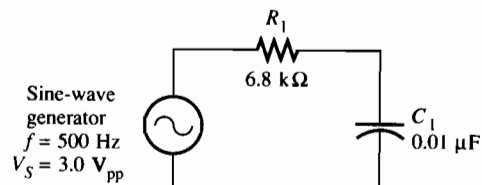


Figure 23–2

3. Using the two-channel-difference technique described in Experiment 16, measure the peak-to-peak voltage across the resistor (V_R). Then measure the peak-to-peak voltage across the capacitor (V_C). Record the voltage readings on the first line of Table 23–2.
4. Compute the peak-to-peak current in the circuit by applying Ohm’s law to the measured value of the resistor:

$$I = \frac{V_R}{R}$$


Since the current is the same throughout a series circuit, this is a simple method for finding the current in both the resistor and the capacitor. Enter this computed current in Table 23–2.

5. Compute the capacitive reactance, X_C , by applying Ohm's law to the capacitor. The reactance is found by dividing the voltage across the capacitor (step 3) by the current in the circuit (step 4). Enter the capacitive reactance in Table 23–2.
6. Compute the total impedance of the circuit by applying Ohm's law to the entire circuit. Use the generator voltage set in step 2 and the current determined in step 4. Enter the computed impedance in Table 23–2.


Table 23–2

Frequency	V_R	V_C	I	X_C	Z
500 Hz					
1000 Hz					
1500 Hz					
2000 Hz					
4000 Hz					
8000 Hz					

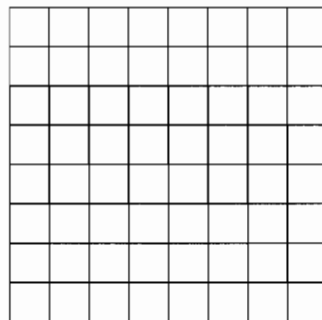7. Change the frequency of the generator to 1000 Hz. Check the generator voltage and reset it to $3.0 V_{pp}$ if necessary. Repeat steps 3 through 6, entering the data in Table 23–2. Continue in this manner for each frequency listed in Table 23–2.
8. From the data in Table 23–2 and the measured value of R_1 , draw the impedance phasors for the circuit at a frequency of 1000 Hz on Plot 23–1(a) and the voltage phasors on Plot 23–1(b).




(a)

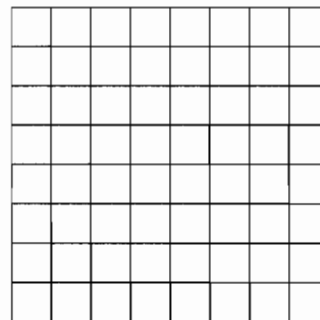


(b)

Plot 23–1

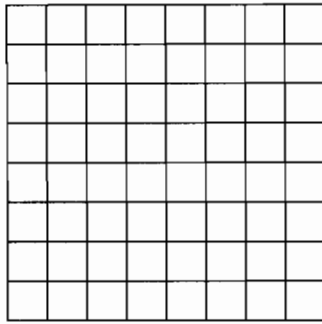9. Repeat step 8 for a frequency of 4000 Hz. Draw the impedance phasors on Plot 23–2(a) and the voltage phasors on Plot 23–2(b).




(a)

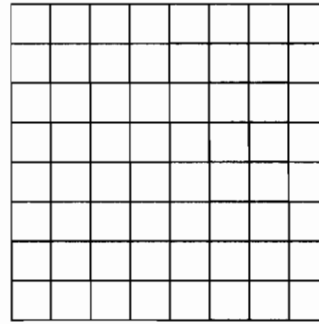

(b)

Plot 23–2

10. The phasor drawings reveal how the impedance and voltage phasors change with frequency. Investigate the frequency effect further by graphing both the voltage across the capacitor and the voltage across the resistor as a function of frequency. Label each curve. Use Plot 23–3 for your graph.

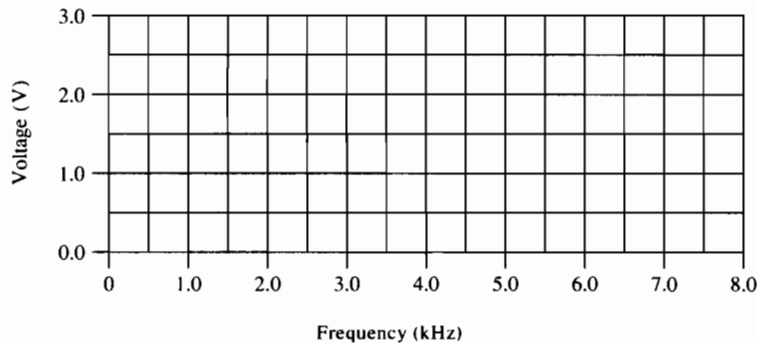

Plot 23–3

Conclusion:

Evaluation and Review Questions:

1. The Pythagorean theorem can be applied to the phasors drawn in Plots 23–1 and 23–2. Show that the data in both plots satisfy the equations

$$Z = \sqrt{R^2 + X_C^2}$$

$$V_S = \sqrt{V_R^2 + V_C^2}$$

2. Assume you needed to pass high frequencies through an RC filter but block low frequencies. From the data in Plot 23–3, should you connect the output across the capacitor or across the resistor? Explain your answer.

3.
 - (a) What happens to the total impedance of a series RC circuit as the frequency is increased?


 - (b) Explain why the phase angle between the generator voltage and the resistor voltage decreases as the frequency is increased.

4. A student accidentally used a capacitor that was ten times larger than required in the experiment. Predict what happens to the frequency response shown in Plot 23–3 with the larger capacitor.

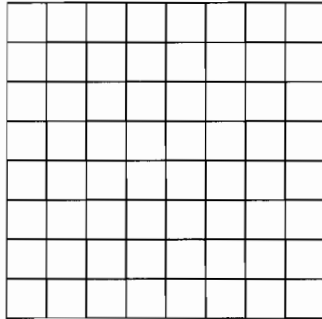
5. Assume no current flowed in the series RC circuit because of an open circuit. How could you quickly determine if the resistor or the capacitor were open?

For Further Investigation:

This experiment showed that the voltage phasor diagram can be obtained by multiplying each quantity on the impedance phasor diagram by the current in the circuit. In turn, if each of the voltage phasors is multiplied by the current, the resulting diagram is the power phasor diagram. Using the data from Table 23–2, convert the current and source voltage to an rms value. Then determine the true power, the reactive power, and the apparent power in the *RC* circuit at a frequency of 1000 Hz and a frequency of 4000 Hz. On Plot 23–4, draw the power phasor diagrams. (See Section 12–7 of Floyd’s text for further discussion of the power phasors.)



$f = 1000 \text{ Hz}$

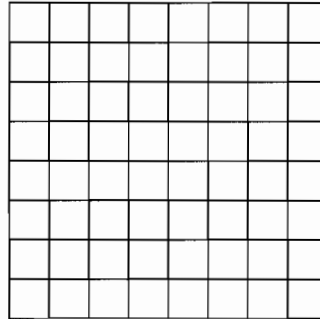

$f = 4000 \text{ Hz}$

Plot 23–4

24 Parallel RC Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 12–4 through 12–9

Objectives:

After performing this experiment, you will be able to:

1. Measure the current phasors for a parallel RC circuit.
2. Explain how the current phasors and phase angle are affected by a change in frequency for parallel RC circuits.

Summary of Theory:

In a series circuit, the same *current* is in all components. For this reason, current is generally used as the reference. By contrast, in parallel, the same *voltage* is across all components. The voltage is therefore the reference. Current in each branch is compared to the circuit voltage. In parallel circuits, Kirchhoff's current law applies to any junction but care must be taken to add the currents as phasors. The current entering a junction is always equal to the current leaving the junction.

Figure 24–1 illustrates a parallel RC circuit. If the impedance of each branch is known, the current in that branch can be determined directly from Ohm's law. The current phasor diagram can then be constructed. The total current can be found as the phasor sum of the currents in each branch. The current in the capacitor is shown at $+90^\circ$ from the voltage reference because the current leads the voltage in a capacitor. The current in the resistor is along the x -axis because current and voltage are in phase in a resistor. The Pythagorean theorem can be applied to the current phasors, resulting in the equation

$$I_T = \sqrt{I_R^2 + I_C^2}$$

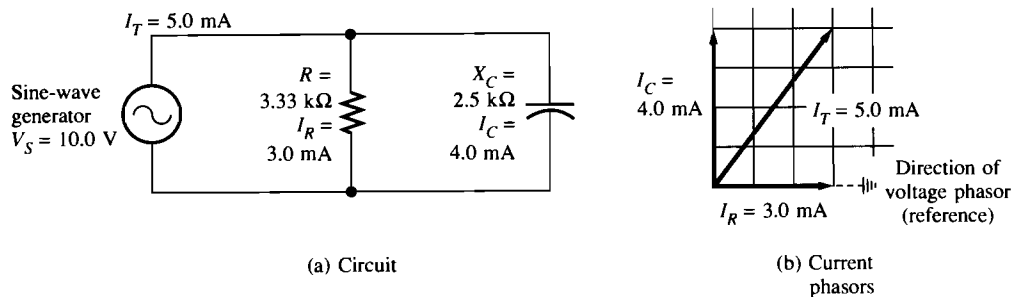


Figure 24–1

In this experiment, two extra 1.0 kΩ resistors are added to “sense” current and provide a small voltage drop that can be measured. These resistors are much smaller than the parallel branch impedance, so their resistance can be ignored in the computation of circuit impedance.

Materials Needed:

Resistors:

One 100 kΩ, two 1.0 kΩ

Capacitors:

One 1000 pF

Procedure:

1. Measure a resistor with a color-code value of 100 kΩ and each of two current-sense resistors (R_{S1} and R_{S2}) with color-code values of 1.0 kΩ. Measure the capacitance of a 1000 pF capacitor. Use the listed value if a measurement cannot be made. Record the measured values in Table 24–1.

Table 24–1 ($f = 1.0$ kHz)

	Listed Value	Measured Value	Voltage Drop	Computed Current
R_1	100 kΩ			
R_{S1}	1.0 kΩ			
R_{S2}	1.0 kΩ			
C_1	1000 pF			


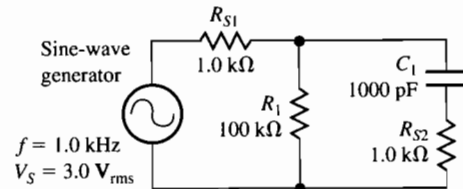


Figure 24–2

2. Construct the circuit shown in Figure 24–2. Set the generator to a voltage of 3.0 V_{rms} at 1.0 kHz. Check the voltage and frequency with your oscilloscope.
3. Using a voltmeter, measure the voltage drop across each resistor. The voltage drops are small, so measure as accurately as possible. You should keep three significant figures in your measurement. Record the voltage drops in Table 24–1.
4. Compute the current in each resistor using Ohm’s law. Record the computed current in Table 24–1.
5. Draw the current phasors I_{R1} , I_{C1} , and the total current I_T on Plot 24–1. The total current flows through sense resistor R_{S1} . The current I_{C1} flows through sense resistor R_{S2} . Ignore the small effect of the sense resistors on the phasor diagram. Note carefully the direction of the phasors. Label each of the current phasors.

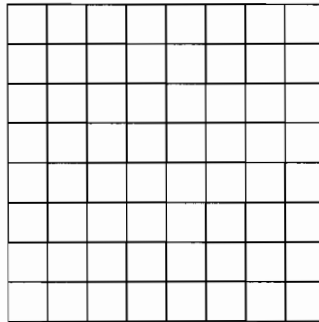

Plot 24-1

6. Compute X_{C1} for the 1.0 kHz frequency. Then, using this value and the measured resistance of R_1 , find the total impedance, Z_T , of the circuit using the product-over-sum rule. The sense resistors can be ignored for this calculation.

$$X_{C1} = \underline{\hspace{2cm}} \quad Z_T = \frac{R_1 X_C}{\sqrt{R_1^2 + X_C^2}} = \underline{\hspace{2cm}}$$


7. Using Z_T from step 6 and the applied voltage, V_S , compute the total current, I_T . The total current should basically agree with the value determined in step 4.

$$I_T = \underline{\hspace{2cm}}$$

8. Change the frequency of the generator to 2.0 kHz. Check that generator voltage is still 3.0 V. Repeat steps 1-5 for the 2.0 kHz frequency. Enter the data in Table 24-2 and draw the current phasors on Plot 24-2.

Table 24-2 ($f = 2.0$ kHz)

	Listed Value	Measured Value	Voltage Drop	Computed Current
R_1	100 k Ω			
R_{S1}	1.0 k Ω			
R_{S2}	1.0 k Ω			
C_1	1000 pF			

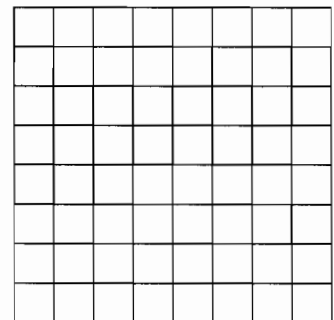

Plot 24-2

Conclusion:

Evaluation and Review Questions:

1. Explain how increasing the frequency affects:
 - (a) the total impedance of the circuit

 - (b) the phase angle between the generator voltage and the generator current

2. Assume the frequency had been set to 5.0 kHz in this experiment. Compute:
 - (a) the current in the resistor

 - (b) the current in the capacitor

 - (c) the total current

3. If a smaller capacitor had been substituted in the experiment, what would happen to the current phasor diagrams?

4. (a) The high-frequency response of a transistor amplifier is limited by stray capacitance, as illustrated in Figure 24–3. The upper *cutoff* frequency is defined as the frequency at which the resistance R_{IN} is equal to the capacitive reactance X_C of the stray capacitance. An equivalent parallel RC circuit can simplify the problem. Compute the cutoff frequency for the circuit shown by setting $R_{IN} = X_C$ and solving for f_c


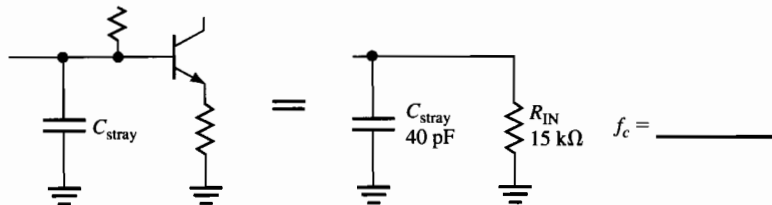


Figure 24–3

- (b) How do the branch currents compare at the cutoff frequency?
 - (c) Explain what happens above this frequency to the current in the equivalent parallel RC circuit.
5. If the stray capacitance in Figure 24–3 is increased, what happens to the cutoff frequency?

For Further Investigation:

In a series RC circuit, the impedance phasor is the sum of the resistance and reactance phasors as shown in Experiment 23. In a parallel circuit, the admittance phasor is the sum of the conductance and the susceptance phasors. On Plot 24–3, draw the admittance, conductance, and susceptance phasors for the experiment at a frequency of 1.0 kHz. Hint: The admittance phasor diagram can be obtained directly from the current phasor diagram by dividing the current phasors by the applied voltage.

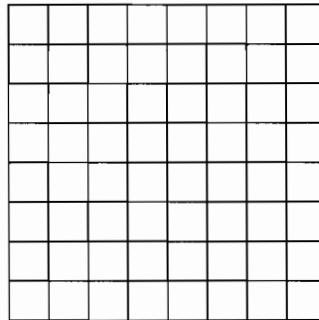

Plot 24–3


Application Assignment 12

Name _____
 Date _____
 Class _____


Reference:

Floyd, Chapter 12, Section 12-10: Application Assignment


- Step 1** Evaluate the amplifier input circuit. Determine the equivalent resistance:
 Equivalent resistance = _____
- Step 2** Measure the response at frequency f_1 . Sketch the waveform for channel 2 on Plot AA-12-1.
- Step 3** Measure the response at frequency f_2 . Sketch the waveform for channel 2 on Plot AA-12-2. Explain why the response is different than in step 2:
- Step 4** Measure the response at frequency f_3 . Sketch the waveform for channel 2 on Plot AA-12-3. Explain why the response is different from that in steps 2 and 3:
- Step 5** Plot a response curve for the amplifier input circuit on Plot AA-12-4

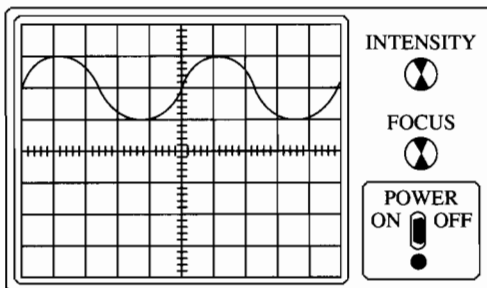


Plot AA-12-1

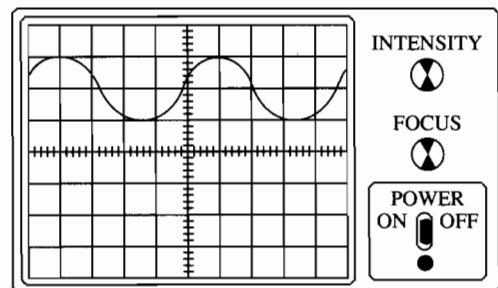

Plot AA-12-2

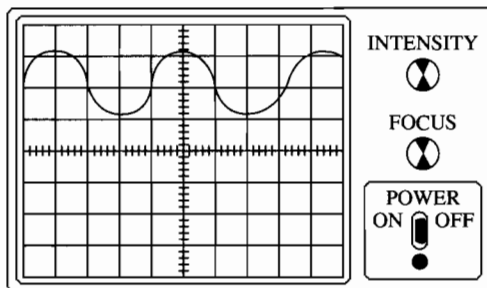

Plot AA-12-3

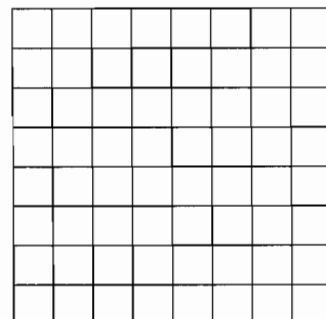

Plot AA-12-4

Related Experiment

Materials Needed:

One 100 k Ω resistor

One capacitor (value to be determined by student)

Discussion:

The application assignment requires you to consider the frequency response of a coupling capacitor. A circuit using a coupling capacitor was introduced in Application Assignment 9. The capacitor should look nearly like a short to the ac signal but appear open to the dc voltage. A simplified coupling circuit, with the dc portion removed, is illustrated in Figure AA-12-1. R_{input} represents the input resistance of an amplifier and C_{coupling} is the coupling capacitor.

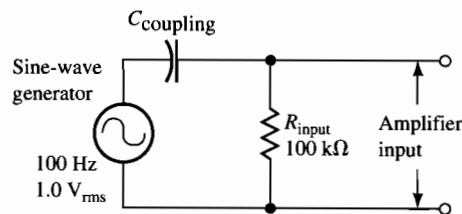


Figure AA-12-1

In this application, you need to find a capacitor that will allow a minimum of 90% of the generator signal to appear across R_{input} at a frequency of 100 Hz. Compute the value of a capacitor that will meet this requirement. Construct your circuit and test it by measuring the generator voltage, the voltage drop across the capacitor, and the voltage drop across the resistor using a 100 Hz signal from the generator. Summarize your calculations and measurements.

Experimental Results:

Checkup 12


Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 12, and Buchla, Experiments 23 and 24

- If a sinusoidal voltage wave is applied to a capacitor, the current in the capacitor:
(a) leads the voltage by 45° (c) lags the voltage by 45°
(b) leads the voltage by 90° (d) lags the voltage by 90°
- If a $0.1 \mu\text{F}$ capacitor is connected across a $50 \text{ V}_{\text{rms}}$, 1 kHz source, the current in the capacitor will be:
(a) 2.00 nA (b) $3.14 \mu\text{A}$ (c) 0.795 mA (d) 31.4 mA
- In a series RC circuit in which $X_C = R$, the generator current:
(a) leads the generator voltage by 45° (c) lags the generator voltage by 45°
(b) leads the generator voltage by 90° (d) lags the generator voltage by 90°
- In a parallel RC circuit in which $X_C = R$, the generator current:
(a) leads the generator voltage by 45° (c) lags the generator voltage by 45°
(b) leads the generator voltage by 90° (d) lags the generator voltage by 90°
- If the frequency is raised in a series RC circuit and nothing else changes, the current in the circuit will:
(a) increase (b) stay the same (c) decrease
- If the frequency is raised in a parallel RC circuit and nothing else changes, the current in the circuit will:
(a) increase (b) stay the same (c) decrease
- The reciprocal of reactance is:
(a) conductance (b) susceptance (c) admittance (d) impedance
- If the phase angle between the voltage and current in a series RC circuit is 30° , what is the power factor?
(a) 0.5 (b) 0.707 (c) 0.866 (d) 1.0
- In a purely capacitive circuit, the power factor is:
(a) 0.0 (b) 0.5 (c) 0.707 (d) 1.0
- To use a series RC circuit as a high-pass filter, the output should be taken from:
(a) the resistor (b) the capacitor (c) the generator

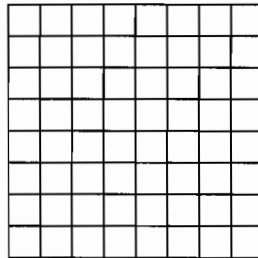11. In a series circuit, the generator current is frequently used as the reference (see Experiment 23), but in a parallel circuit, the generator voltage is almost always used as the reference (see Experiment 24). Explain.
12. An RC circuit uses a $10\text{ k}\Omega$ resistor in series with a $0.047\text{ }\mu\text{F}$ capacitor and is connected to a generator set to 10 V_{rms} .
- (a) Determine the frequency at which $X_C = R$.
- (b) At this frequency, what is the current in the circuit?
- (c) At this frequency, what is the voltage across the resistor?
13. In a certain parallel RC circuit, the generator current leads the generator voltage by 60° . Assume the generator is set to 10 V_{rms} and the resistor has a value of $12.5\text{ k}\Omega$. Sketch the current phasor diagram on the Plot C-12-1. Label the values of currents on your diagram.



Plot C-12-1

14. In Experiment 24, two $1\text{ k}\Omega$ sense resistors were used to determine quickly the total current and the current in the capacitor. Would it be reasonable to use these same sense resistors for the problem circuit described in Question 13? Justify your answer.

25 Series *RL* Circuits

Name _____
 Date _____
 Class _____

Reading:

Floyd, Sections 13–1 through 13–3

Objectives:

After performing this experiment, you will be able to:

1. Compute the inductive reactance of an inductor from voltage measurements in a series *RL* circuit.
2. Draw the impedance and voltage phasor diagram for the series *RL* circuit.
3. Measure the phase angle in a series circuit using either of two methods.

Summary of Theory:

When a sine wave drives a linear series circuit, the phase relationships between the current and the voltage are determined by the components in the circuit. The current and voltage are always in phase across resistors. In capacitors, the current is always leading the voltage by 90° , but for inductors, the voltage always leads the current by 90° . (A simple memory aid for this is *ELI the ICE man*, where *E* stands for voltage, *I* for current, and *L* and *C* for inductance and capacitance.)

Figure 25–1(a) illustrates a series *RL* circuit. The graphical representation of the phasors for this circuit is shown in Figure 25–1(b) and (c). As in the series *RC* circuit, the total impedance is obtained by adding the resistance and inductive reactance using the algebra for complex numbers. In this example, the current is 1.0 mA, and the total impedance is 5 k Ω . The current is the same in all components of a series circuit, so the current is drawn as a reference in the direction of the *x*-axis. If the current is multiplied by the impedance phasors, the voltage phasors are obtained as shown in Figure 25–1(c).

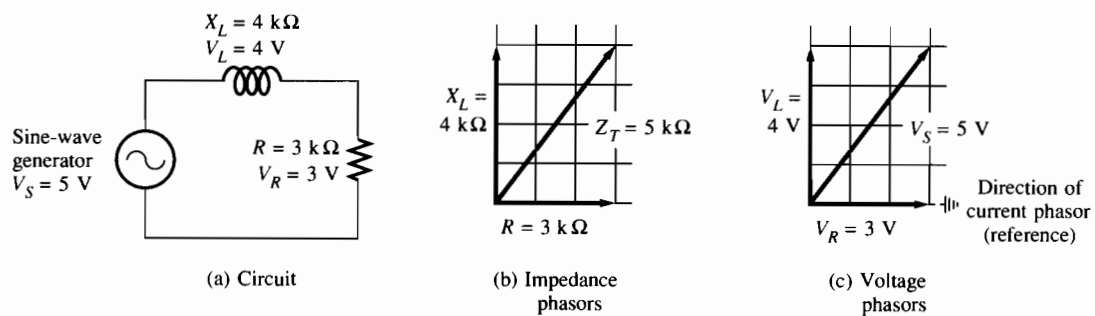


Figure 25–1

In this experiment, you learn how to make measurements of the phase angle. Actual inductors may have enough resistance to affect the phase angle in the circuit. You will use a series resistor that is large compared to the inductor’s resistance to avoid this error.

Materials Needed:

- One 10 kΩ resistor
- One 100 mH inductor

Procedure:

1. Measure the actual resistance of a 10 kΩ resistor and the inductance of a 100 mH inductor. If the inductor cannot be measured, record the listed value. Record the measured values in Table 25–1.
2. Connect the circuit shown in Figure 25–2. Set the generator voltage with the circuit connected to 3.0 V_{pp} at a frequency of 25 kHz. The generator should have no dc offset. Measure the generator voltage and frequency with the oscilloscope as most meters cannot respond to the 25 kHz frequency. Use peak-to-peak readings for all voltage and current measurements in this experiment.

Table 25–1

Component	Listed Value	Measured Value
L_1	100 mH	
R_1	10 kΩ	

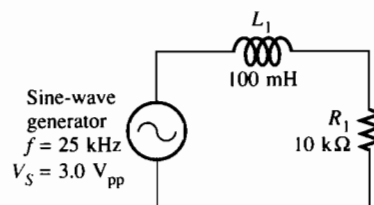


Figure 25–2

3. Using a two-channel oscilloscope, measure the peak-to-peak voltage across the resistor (V_R) and the peak-to-peak voltage across the inductor (V_L). (See Figure 25–3 for the setup.) Measure the voltage across the inductor using the difference technique described in Experiment 16. Record the voltage readings in Table 25–2.
4. Compute the peak-to-peak current in the circuit by applying Ohm’s law to the resistor. That is,

$$I = \frac{V_R}{R}$$

Enter the computed current in Table 25–2.

5. Compute the inductive reactance, X_L , by applying Ohm’s law to the inductor. The reactance is


$$X_L = \frac{V_L}{I}$$

Table 25–2 ($f = 25 \text{ kHz}$)

V_R	V_L	I	X_L	Z_T

Enter the computed reactance in Table 25–2.

6. Calculate the total impedance (Z_T) by applying Ohm's law to the entire circuit. Use the generator voltage set in step 2 (V_S), and the current determined in step 4. Enter the computed impedance in Table 25-2.
7. Using the values listed in Tables 25-1 and 25-2, draw the impedance phasors on Plot 25-1(a) and the voltage phasors on Plot 25-1(b) for the circuit at a frequency of 25 kHz.

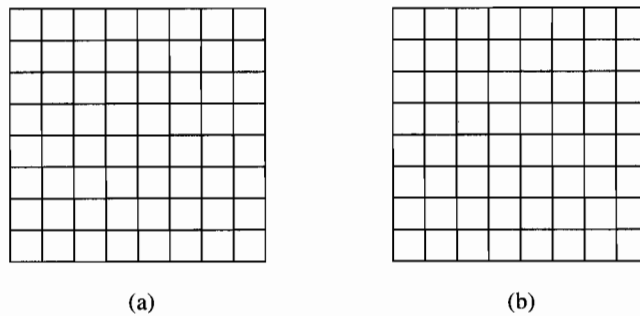

Plot 25-1

8. Compute the phase angle between V_R and V_S using the trigonometric relation

$$\theta = \tan^{-1} \left(\frac{V_L}{V_R} \right)$$

Enter the computed phase angle in Table 25-3.

9. Two methods for measuring phase angle will be explained. Measure the phase angle between V_R and V_S using each method. The measured phase angle will be recorded in Table 25-3.

Phase Angle Measurement—Method 1

- (a) Connect the oscilloscope so that channel 1 is across the generator and channel 2 is across the resistor. (See Figure 25-3.) Obtain a stable display showing between one and two cycles while viewing channel 1 (V_S). The scope should *not* be triggered using composite (vertical mode) triggering.

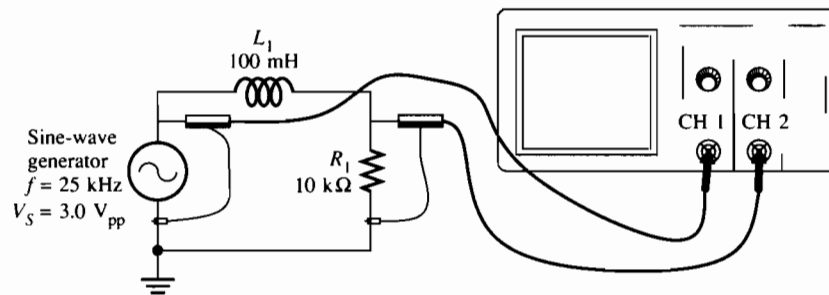


Figure 25-3

- (b) Measure the period, T , of the generator. Record it in Table 25–3. You will use this time in step (e).
- (c) Set the oscilloscope to view both channels. (Do not have channel 2 inverted.) Adjust the amplitudes of the signals using the VOLTS/DIV, VERT POSITION, and the red vernier controls until both channels appear to have the same amplitude as seen on the scope face.
- (d) Spread the signal horizontally using the SEC/DIV control until both signals are just visible across the screen. The SEC/DIV control must remain calibrated. Measure the time between the two signals, Δt , by counting the number of divisions along a horizontal graticule of the oscilloscope and multiplying by the SEC/DIV setting. (See Figure 25–4.) Record the measured Δt in Table 25–3.

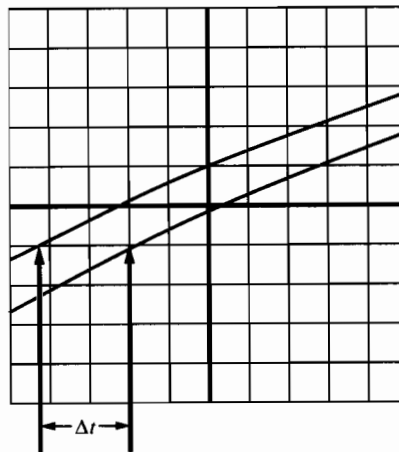


Figure 25–4

- (e) The phase angle may now be computed from the equation

$$\theta = \left(\frac{\Delta t}{T} \right) \times 360^\circ$$

Enter the measured phase angle in Table 25–3 under Phase Angle—Method 1.

Phase Angle Measurement—Method 2

- (a) In this method the oscilloscope face will represent degrees, and the phase angle can be measured directly. The probes are connected as before. View channel 1 and obtain a stable display. Then adjust the SEC/DIV control and its vernier until you have exactly one cycle across the scope face. This is equivalent to 360° in 10 divisions, so each division is worth 36° .¹

¹For even better resolution, you can set one-half cycle across the screen, making each division worth 18° . Care must be taken to center the waveform.

- (b) Now switch the scope to view both channels. As before, adjust the amplitudes of the signals using the VOLTS/DIV, VERT POSITION, and the red vernier controls until both channels appear to have the same amplitude.
- (c) Measure the number of divisions between the signals and multiply by 36° per division. Record the measured phase angle in Table 25–3 under Phase Angle—Method 2.

Table 25–3

Computed Phase Angle θ	Measured Period T	Time Difference Δt	Phase Angle	
			Method 1 θ	Method 2 θ

Conclusion:

Evaluation and Review Questions:

1.
 - (a) What will happen to the impedance in this experiment if the frequency increases?
 - (b) What would happen to the impedance if the inductance were larger?
2.
 - (a) What will happen to the phase angle in this experiment if the frequency increases?

- (b) What would happen to the phase angle if the inductance were larger?
3. (a) Compute the percent difference between the computed phase angle and the method 1 phase angle measurement.
- (b) Compute the percent difference between the computed phase angle and the method 2 measurement.
- (c) Which method was most accurate?
4. The critical frequency for an RL circuit occurs at the frequency at which the resistance is equal to the inductive reactance. That is, $R = X_L$. Since $X_L = 2\pi fL$ for an inductor, it can easily be shown that the circuit frequency for an RL circuit is

$$f_{\text{crit}} = \frac{R}{2\pi L}$$

Compute the critical frequency for this experiment. What is the phase angle between V_R and V_S at the critical frequency?

$$f_{\text{crit}} = \text{_____} \quad \theta = \text{_____}$$

5. A series RL circuit contains a $100\ \Omega$ resistor and a $1.0\ \text{H}$ inductor and is operating at a frequency of $60\ \text{Hz}$. If $3.0\ \text{V}$ are across the resistor, compute:
- the current in the inductor _____
 - the inductive reactance X_L _____
 - the voltage across the inductor, V_L _____
 - the source voltage, V_S _____
 - the phase angle between V_R and V_S _____

For Further Investigation:

An older method for measuring phase angles involved interpreting Lissajous figures. A Lissajous figure is the pattern formed by the application of a sinusoidal waveform to both the x - and y -axes of an oscilloscope. Two signals of equal amplitude and exactly in phase will produce a 45° line on the scope face. If the signals are the same amplitude and exactly 90° apart, the waveform will appear as a circle. Other phase angles can be determined by applying the formula

$$\theta = \arcsin \frac{OA}{OB}$$

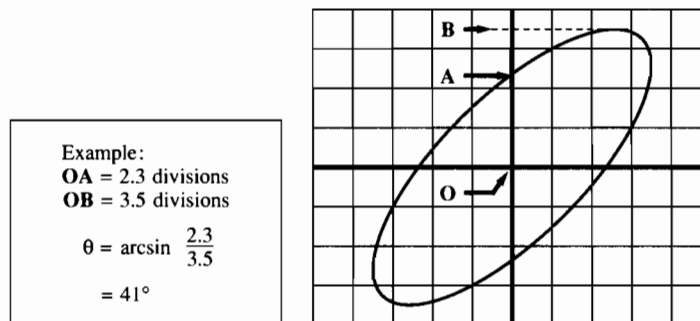


Figure 25-5

Figure 25-5 illustrates a Lissajous figure phase measurement. The measurement of OA and OB is along the y -axis. Try measuring the phase angle in this experiment using a Lissajous figure. You will have to have the signals the same amplitude and centered on the oscilloscope face. Then switch the time base of the oscilloscope to the XY mode.

26 Parallel *RL* Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 13–4 through 13–9

Objectives:

After performing this experiment, you will be able to:

1. Determine the current phasor diagram for a parallel *RL* circuit.
2. Measure the phase angle between the current and voltage for a parallel *RL* circuit.
3. Explain how an actual circuit differs from the ideal model of a circuit.

Summary of Theory:

The parallel *RC* circuit was investigated in Experiment 24. Recall that the circuit phasor diagram was drawn with current phasors and the voltage phasor was used as a reference, since voltage is the same across parallel components. In a parallel *RL* circuit, the current phasors will again be drawn with reference to the voltage phasor. The direction of the current phasor in a resistor is always in the direction of the voltage. Since current lags the voltage in an inductor, the current phasor is drawn at an angle of -90° from the voltage reference. A parallel *RL* circuit and the associated phasors are shown in Figure 26–1.

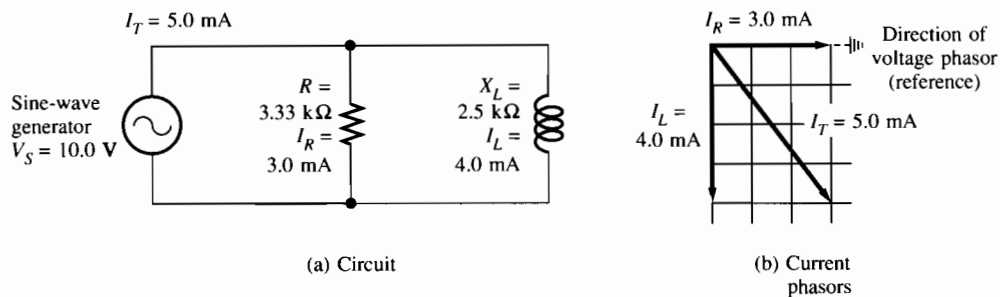


Figure 26–1

Practical inductors contain resistance that frequently is large enough to affect the purely reactive inductor phasor drawn in Figure 26–1. The resistance of an inductor can be thought of as a resistor in series with a pure inductor. The effect on the phasor diagram is to reduce an angle between I_L and I_R . In a practical circuit this angle will be slightly less than the 90° shown in Figure 26–1. This experiment illustrates the difference between the approximations of circuit performance based on ideal components and the actual measured values.

Recall that in Experiment 25, the phase angle between the source voltage, V_S , and the resistor voltage, V_R , in a series circuit were measured. The oscilloscope is a voltage-sensitive device, so comparing these voltages is straightforward. In parallel circuits, the phase angle of interest is usually between the total current, I_T , and one of the branch currents. To use the oscilloscope to measure the phase angle in a parallel circuit, we must convert the current to a

voltage. This was done by inserting a small resistor in the branch where the current is to be measured. The resistor must be small enough not to have a major effect on the circuit.

Materials Needed:

Resistors:

One 3.3 kΩ, two 47 Ω

One 100 mH inductor

Procedure:

1. Measure the actual resistance of a resistor with a color-code value of 3.3 kΩ and the resistance of two current-sensing resistors of 47 Ω each. Measure the inductance of a 100 mH inductor. Use the listed value if you cannot measure the inductor. Record the measured values in Table 26–1.
2. Measure the coil resistance of the inductor with an ohmmeter. Record the resistance in Table 26–1.
3. Construct the circuit shown in Figure 26–2. Notice that the reference ground connection is at the low side of the generator. This connection will enable you to use a generator that does not have a “floating” common connection. Using your oscilloscope, set the generator to a voltage of 6.0 V_{pp} at 5.0 kHz. Check both the voltage and frequency with your oscilloscope. Record all voltages and currents in this experiment as peak-to-peak values.

Table 26–1

	Listed Value	Measured Value	Voltage Drop	Computed Current
R_1	3.3 kΩ			
R_{S1}	47 Ω			
R_{S2}	47 Ω			
L_1	100 mH			
L_1	Resistance			


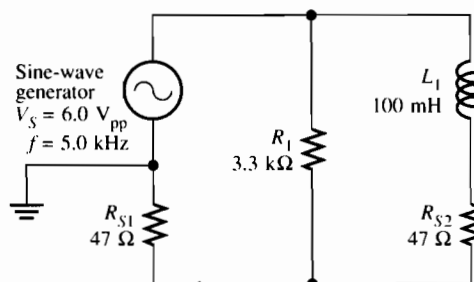


Figure 26–2

4. Using the oscilloscope, measure the peak-to-peak voltages across R_1 , R_{S1} , and R_{S2} . Use the two-channel difference method (described in Experiment 16) to measure the voltage across the ungrounded resistors. Apply Ohm’s law to compute the current in each branch. Record the measured voltage drops and the computed currents in Table 26–1. Since L_1 is in series with R_{S2} , enter the same current for both.
5. The currents measured indirectly in step 4 are phasors because the current in the inductor is lagging the current in R_1 by 90°. The current in the inductor is the same as the current in R_{S2} , and the total current flows through R_{S1} . Using the computed peak-to-peak currents from Table 26–1, draw the current phasors for the circuit on Plot 26–1. (Ignore the effects of the sense resistors.)

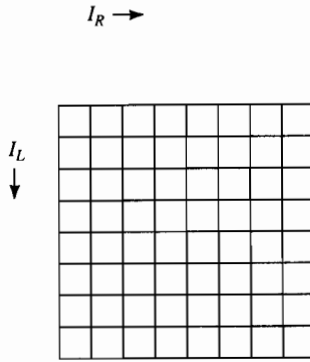

Plot 26-1

Table 26-2

Phase Angle Between:	Computed	Measured
I_T and I_R		
I_R and I_L	90°	
I_T and I_L		

- The phasor diagram illustrates the relationship between the total current and the current in each branch. Using the measured currents, compute the phase angle between the total current (I_T) and the current in R_1 (I_R). Then compute the phase angle between the total current (I_T), and the current in L_1 (I_L). Enter the computed phase angles in Table 26-2. (Note that the computed angles should add up to 90°, the angle between I_R and I_L .)
- In this step, you will measure the phase angle between the generator voltage and current. This angle is approximately equal to the angle between I_T and I_R as shown in Figure 26-1. (Why?) Connect the oscilloscope probes as shown in Figure 26-3. Measure the phase angle using one of the methods in Experiment 25. The signal amplitudes in each channel are quite different, so the vertical sensitivity controls should be adjusted to make each signal appear to have the same amplitude on the scope. Record the measured angle between I_T and I_R in Table 26-2.

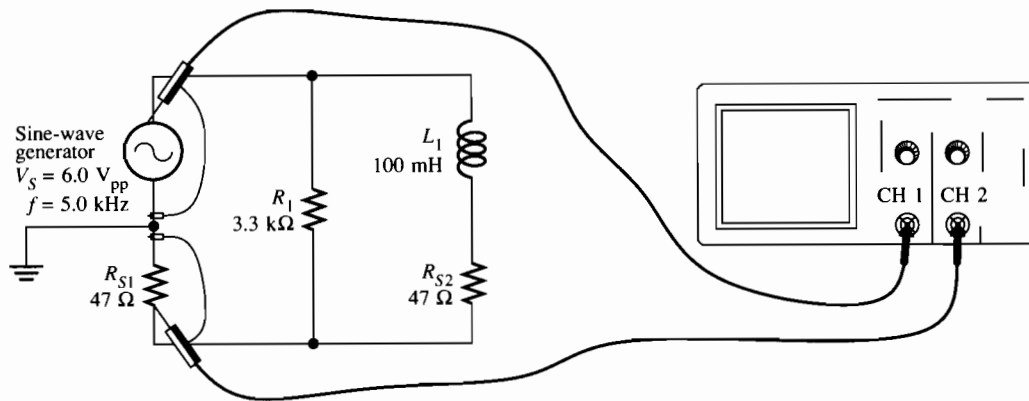


Figure 26-3

- Replace R_{S1} with a jumper. This procedure enables you to reference the low side of R_1 and R_{S2} . Measure the angle between I_L and I_R by connecting the probes as shown in Figure 26-4. Ideally, this measurement should be 90°, but because of the coil resistance, you will likely find a smaller value. Adjust both channels for the same apparent amplitude on the scope face. Record your measured result in the second line in Table 26-2.

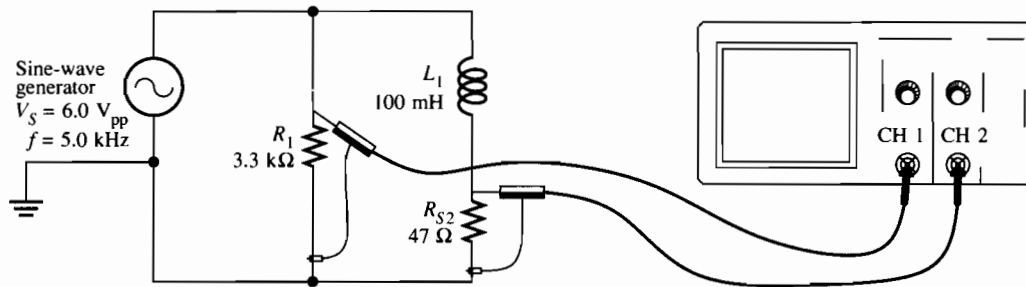


Figure 26-4

9. By subtracting the angle measured in step 7 from the angle measured step 8, you can find the phase angle between the I_T and I_L . Record this as the measured value on the third line of Table 26-2.

Conclusions:

Evaluation and Review Questions:

1. If we assume that the currents determined in step 4 are 90° apart, the magnitude of the total current can be computed by applying the Pythagorean theorem to the current phasors. That is

$$I_T = \sqrt{I_{R1}^2 + I_{L1}^2}$$

- (a) Compare the total current measured in R_{S1} (Table 26-1) with the current found by applying the Pythagorean theorem to the current phasors.
- (b) What factors account for differences between the two currents?
2. How does the coil resistance measured in step 2 affect the angle between the current in the resistor and the current in the inductor?

For Further Investigation:

We could find the *magnitude* of the total current by observing the loading effect of the circuit on a signal generator. Consider the signal generator as a Thevenin circuit consisting of a zero impedance signal generator driving an internal series resistor consisting of the Thevenin source impedance. (See Figure 26–5.) When current flows to the external circuit, there is a voltage drop across the Thevenin resistance. The voltage drop across the Thevenin resistor, when divided by the Thevenin resistance, represents the total current in the circuit. To find the voltage drop across the Thevenin resistance, simply measure the difference in the generator voltage with the generator connected and disconnected from the circuit.

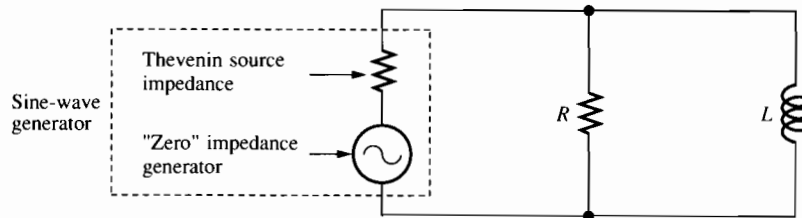


Figure 26–5

In addition to loading effects, the generator impedance also changes the phase angles in the circuit connected to it. If the impedance is smaller, the effect is greater. Investigate the loading effects for this experiment. Try finding the total current by the difference in loaded and unloaded voltage from the generator. What effect does the generator's impedance have on the phase angle?

Discussion:

A circuit will transfer maximum power to a load when the power factor is equal to 1. Maximum power factor is useful in certain impedance matching networks.

You can easily detect when the power factor is not maximum by observing a Lissajous figure on an oscilloscope. (See Experiment 25—For Further Investigation.) The phase angle is zero (power factor of 1) when the Lissajous figure shows a straight line on the oscilloscope display.

Construct the circuit shown in Figure AA-13-1. The oscilloscope is connected as shown. Adjust the VOLTS/DIV, VERT POSITION, and the red vernier controls until both channels appear to have the same amplitude. Then, switch the oscilloscope to the XY mode. Measure and record the phase shift using the Lissajous figure as described in Experiment 25.

The results of the preceding measurement clearly show that the power factor is not 1. Add a variable capacitor of approximately 12–100 pF in series with the inductor, as shown in Figure AA-13-2. Observe the Lissajous figure and adjust the capacitor until the power factor is 1. Then, remove the capacitor and measure its value. Compare the reactance of the capacitor with the reactance of the inductor when the power factor is 1. What conclusion can you draw from this?

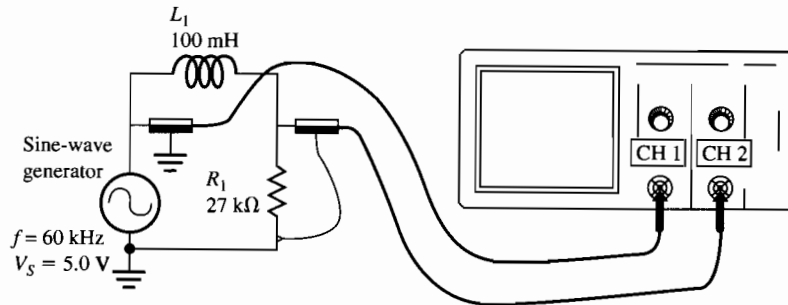


Figure AA-13-1

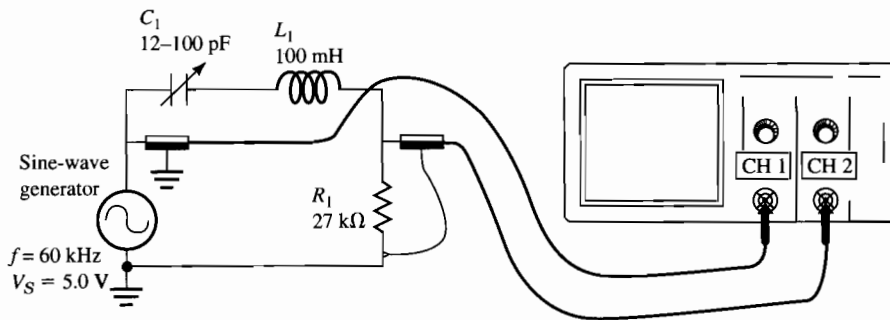


Figure AA-13-2

Experimental Results:

Checkup 13

Name _____
Date _____
Class _____


Reference:

Floyd, Chap. 13, and Buchla, Experiments 25 and 26

- If a sinusoidal voltage wave is applied to an inductor, the current in the inductor:
(a) leads the voltage by 45° (c) lags the voltage by 45°
(b) leads the voltage by 90° (d) lags the voltage by 90°
- A $191 \mu\text{H}$ inductor is connected across a $20 \text{ V}_{\text{rms}}$, 50 MHz source. The current in the inductor will be approximately:
(a) $333 \mu\text{A}$ (b) 3.3 mA (c) 33 mA (d) 333 mA
- In a series RL circuit in which $X_L = R$, the generator current:
(a) leads the generator voltage by 45° (c) lags the generator voltage by 45°
(b) leads the generator voltage by 90° (d) lags the generator voltage by 90°
- In a parallel RL circuit in which $X_L = R$, the generator current:
(a) leads the generator voltage by 45° (c) lags the generator voltage by 45°
(b) leads the generator voltage by 90° (d) lags the generator voltage by 90°
- If the frequency is raised in a series RL circuit and nothing else changes, the current in the circuit:
(a) increases (b) stays the same (c) decreases
- If the frequency is raised in a parallel RL circuit and nothing else changes, the current in the circuit:
(a) increases (b) stays the same (c) decreases
- The admittance of a parallel RL circuit is $200 \mu\text{S}$. If the total current is $400 \mu\text{A}$, the applied voltage is:
(a) 0.5 (b) 2.0 V (c) 6.0 V (d) 8.0 V
- A series RL circuit contains a 300Ω resistor and an inductor with a reactance of 400Ω . The total impedance of the circuit is:
(a) 171Ω (b) 350Ω (c) 500Ω (d) 700Ω
- A parallel RL circuit is connected to a 500 kHz voltage source of 16 V . The current in the inductor is 0.5 mA . The inductance is approximately:
(a) $64 \mu\text{H}$ (b) $640 \mu\text{H}$ (c) 1.0 mH (d) 10 mH

10. In a certain series RL circuit, the phase angle is measured at 60° between the generator current and voltage. If the voltage across the inductor is 10 V, the voltage across the resistor is:
 (a) 5 V (b) 5.8 V (c) 8.66 V (d) 17.3 V
11. In Experiment 25 (step 9a), you were directed *not* to trigger the oscilloscope using composite triggering. Why was this important?
12. In Experiment 26 (step 7), the statement is made that the phase angle between the generator voltage and current is approximately equal to the angle between I_T and I_R . Explain.
13. A parallel RL circuit is connected to a 10 V source. The current in the inductor has twice the magnitude of the current in the resistor. The total current is 7.0 mA.
 (a) What is the phase angle between the generator current and voltage?

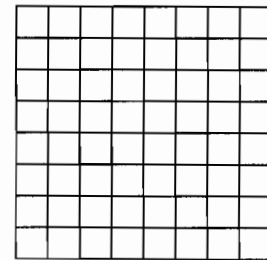(b) Draw the current phasor diagram on Plot C-13-1.



Plot C-13-1

14. For the circuit shown in Figure C-13-1, compute:
 (a) the impedance seen by the generator
 (b) total current from the generator
 (c) voltage across L_1
 (d) phase angle between generator voltage and voltage across L_1

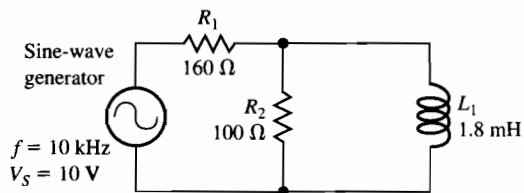


Figure C-13-1

27 Series Resonance

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 14–1 through 14–4

Objectives:

After performing this experiment, you will be able to:

1. Compute the resonant frequency, Q , and bandwidth of a series resonant circuit.
2. Measure the parameters listed in objective 1.
3. Explain the factors affecting the selectivity of a series resonant circuit.

Summary of Theory:

The reactance of inductors increases with frequency according to the equation

$$X_L = 2\pi fL$$

On the other hand, the reactance of capacitors decreases with frequency according to the equation

$$X_C = \frac{1}{2\pi fC}$$

In any LC circuit, there is a frequency at which the inductive reactance is equal to the capacitive reactance. The point at which there is equal and opposite reactance is called *resonance*. By setting $X_L = X_C$, substituting the relations given above, and solving for f , it is easy to show that the resonant frequency of an LC circuit is:

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

where f_r is the resonant frequency. Recall that reactance phasors for inductors and capacitors are drawn in opposite directions because of the opposite phase shift that occurs between inductors and capacitors. At series resonance these two phasors are added and cancel each other. This is illustrated in Figure 27–1(b). The current in the circuit is limited only by the total resistance of the circuit. The current in this example is 5.0 mA. If each of the impedance phasors is multiplied by this current, the result is the voltage phasor diagram as shown in Figure 27–1(c). Notice that the voltage across the inductor and the capacitor can be *greater* than the applied voltage!

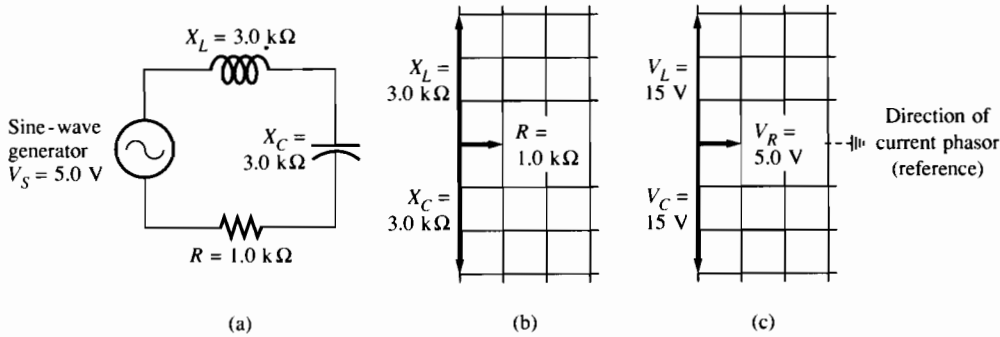


Figure 27-1

At the resonant frequency, the cancellation of the inductive and capacitive phasors leaves only the resistive phasor to limit the current in the circuit. Therefore, at resonance, the impedance of the circuit is a *minimum* and the current is a *maximum* and equal to V_S/R . The phase angle between the source voltage and current is zero. If the frequency is lowered, the inductive reactance will be smaller and the capacitive reactance will be larger. The circuit is said to be capacitive because the source current leads the source voltage. If the frequency is raised, the inductive reactance increases, and the capacitive reactance decreases. The circuit is said to be inductive.

The *selectivity* of a resonant circuit describes how the circuit responds to a group of frequencies. A highly selective circuit responds to a narrow group of frequencies and rejects other frequencies. The *bandwidth* of a resonant circuit is the frequency range at which the current is 70.7% of the maximum current. A highly selective circuit thus has a narrow bandwidth. The sharpness of the response to the frequencies is determined by the circuit Q . The Q for a series resonant circuit is the reactive power in either the coil or capacitor divided by the true power, which is dissipated in the total resistance of the circuit. The bandwidth and resonant frequency can be shown to be related to the circuit Q by the equation

$$Q = \frac{f_r}{BW}$$

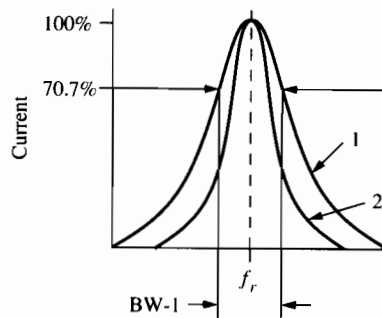


Figure 27-2

Figure 27-2 illustrates how the bandwidth can change with Q . Responses 1 and 2 have the same resonant frequency but different bandwidths. The bandwidth for curve 1 is shown.

Response curve 2 has a higher Q and a smaller BW . A useful equation that relates the circuit resistance, capacitance, and inductance to Q is

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

The value of R in this equation is the total equivalent series resistance in the circuit. Using this equation, the circuit response can be tailored to the application. For a highly selective circuit, the circuit resistance is held to a minimum and the L/C ratio is made high.

The Q of a resonant circuit can also be computed from the equation

$$Q = \frac{X_L}{R}$$

where X_L is the inductive reactance and R is again the total equivalent series resistance of the circuit. The result is the same if X_C is used in the equation, since the values are the same at resonance, but usually X_L is shown because the resistance of the inductor is frequently the dominant resistance of the circuit.

Materials Needed:

Resistors:

One 100 Ω , one 47 Ω

One 0.01 μF capacitor

One 100 mH inductor

Procedure:

1. Measure the value of a 100 mH inductor, a 0.01 μF capacitor, a 100 Ω resistor, and a 47 Ω resistor. Enter the measured values in Table 27-1. If it is not possible to measure the inductor or capacitor, use the listed values.
2. Measure the winding resistance of the inductor, R_w . Enter the measured inductor resistance in Table 27-1.
3. Construct the circuit shown in Figure 27-3. The purpose of the parallel 100 Ω resistor is to reduce the Thevenin driving impedance of the generator and, therefore, the total equivalent series resistance of the circuit.¹ Compute the total resistance of the equivalent series circuit. Note that looking back to the generator, R_{TH} is in parallel with R_1 . In equation form, the equivalent series resistance, R_T , is

$$R_T = (R_{\text{TH}} \parallel R_1) + R_w + R_{S1}$$

Enter the computed total resistance in Table 27-2.

¹Some high-quality generators have a Thevenin resistance of 50 Ω . If you are using a 50 Ω generator, it is not necessary to include R_1 .

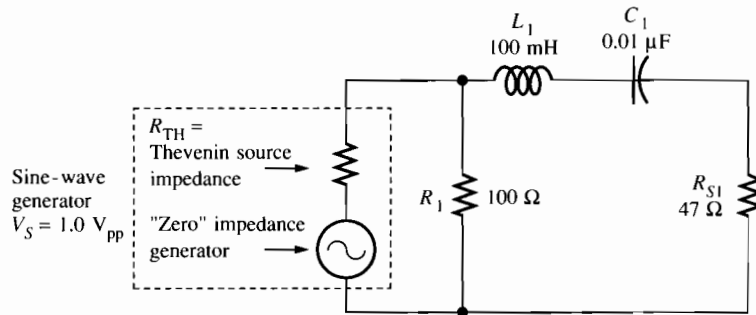


Figure 27-3

- Using the measured values from Table 27-1, compute the resonant frequency of the circuit from the equation

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Record the computed resonant frequency in Table 27-2.

- Use the total resistance computed in step 3 and the measured values of L and C to compute the approximate Q of the circuit from the equation:

$$Q = \frac{1}{R_T} \sqrt{\frac{L}{C}}$$

Enter the computed Q in Table 27-2.

- Compute the bandwidth from the equation

$$BW = \frac{f_r}{Q}$$

Enter this as the computed BW in Table 27-2.

- Using your oscilloscope, tune for resonance by observing the voltage across the sense resistor, R_{S1} . As explained in Floyd's text, the current in the circuit rises to a maximum at resonance. The sense resistor will have the highest voltage across it at resonance. Measure the resonant frequency with the oscilloscope. Record the measured resonant frequency in Table 27-2.

Table 27-1

	Listed Value	Measured Value
L_1	100 mH	
C_1	0.01 μ F	
R_1	100 Ω	
R_{S1}	47 Ω	
R_w (L_1 resistance)		

Table 27-2

	Computed	Measured
R_T		
f_r		
Q		
V_{RS1}		
f_2		
f_1		
BW		

8. Check that the voltage across R_1 is 1.0 V_{pp} . Measure the peak-to-peak voltage across the sense resistor at resonance. The voltage across R_{S1} is directly proportional to the current in the series LC branch, so it is not necessary to compute the current. Record in Table 27-2 the measured peak-to-peak voltage across R_{S1} (V_{RS1}).
9. Raise the frequency of the generator until the voltage across R_{S1} falls to 70.7% of the value read in step 7. Do not readjust the generator's amplitude in this step; this means that the Thevenin resistance of the generator is included in the measurement of the bandwidth. Measure and record this frequency as f_2 in Table 27-2.
10. Lower the frequency to below resonance until the voltage across R_{S1} falls to 70.7% of the value read in step 6. Again, do not adjust the generator amplitude. Measure and record this frequency as f_1 in Table 27-2.
11. Compute the bandwidth by subtracting f_1 from f_2 . Enter this result in Table 27-2 as the measured bandwidth.
12. At resonance, the current in the circuit, the voltage across the capacitor, and the voltage across the inductor are all at a maximum value. Tune across resonance by observing the voltage across the capacitor, then try it on the inductor. Use the oscilloscope difference function technique described in Experiment 16. What is the maximum voltage observed on the capacitor? Is it the same or different than the maximum voltage across the inductor?


V_C (max) = _____

V_L (max) = _____

4. (a) What happens to the resonant frequency, if the inductor is twice as large and the capacitor is half as large?
- (b) What happens to the bandwidth?
5. (a) Compute the resonant frequency for a circuit consisting of a $50\ \mu\text{H}$ inductor in series with a $1000\ \text{pF}$ capacitor.
- (b) If the total resistance of the above circuit is $10\ \Omega$, what are Q and the bandwidth?

For Further Investigation:

In this experiment, you measured three points on the response curve similar to Figure 27-1. Using the technique of measuring the voltage across R_{S1} , find several more points on the response curve. Graph your results on Plot 27-1.

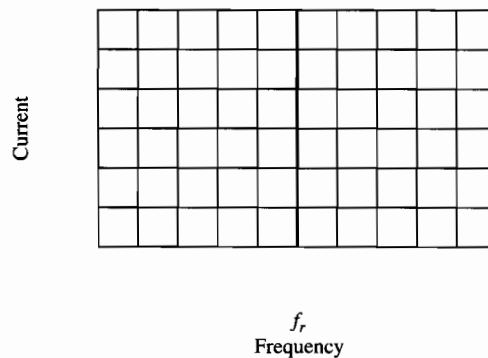

Plot 27-1

28 Parallel Resonance

Name _____
 Date _____
 Class _____

Reading:

Floyd, Sections 14–5 through 14–8

Objectives:

After performing this experiment, you will be able to:

1. Compute the resonant frequency, Q , and bandwidth of a parallel resonant circuit.
2. Measure the frequency response of a parallel resonant circuit.
3. Use the frequency response to determine the bandwidth of a parallel resonant circuit.

Summary of Theory:

In an RLC parallel circuit, the current in each branch is determined by the applied voltage and the impedance of that branch. For an “ideal” inductor (no resistance), the branch impedance is X_L , and for a capacitor the branch impedance is X_C . Since X_L and X_C are functions of frequency, it is apparent that the currents in each branch are also dependent on the frequency. For any given L and C , there is a frequency at which the currents in each are equal and of opposite phase. This frequency is the resonant frequency and is found using the same equation as was used for series resonance:

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

The circuit and phasor diagram for an ideal parallel RLC circuit at resonance is illustrated in Figure 28–1. Some interesting points to observe are: The total source current at resonance is equal to the current in the resistor. The total current is actually less than the current in either the inductor or the capacitor. This is because of the opposite phase shift which occurs between inductors and capacitors, causing the addition of the currents to cancel. Also, the impedance of the circuit is solely determined by R , as the inductor and capacitor appear to be open. In a two-branch circuit consisting of only L and C , the source current would be zero, causing the impedance to be infinite! Of course, this does not happen with actual components that do have resistance and other effects.

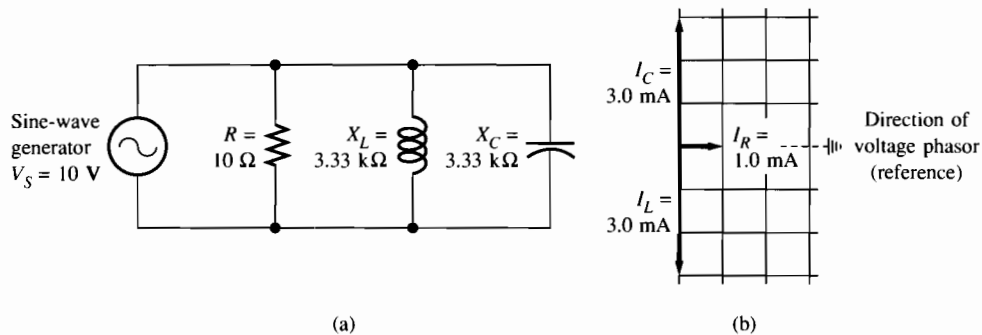


Figure 28–1

In a practical two-branch parallel circuit consisting of an inductor and a capacitor, the only significant resistance is the winding resistance of the inductor. Figure 28–2(a) illustrates a practical parallel LC circuit containing winding resistance. By network theorems, the practical LC circuit can be converted to an equivalent parallel RLC circuit, as shown in Figure 28–2(b). The equivalent circuit is easier to analyze. The phasor diagram for the ideal parallel RLC circuit can then be applied to the equivalent circuit as was illustrated in Figure 28–1. The equations to convert the inductance and its winding resistance to an equivalent parallel circuit are

$$L_{\text{eq}} = L \left(\frac{Q^2 + 1}{Q^2} \right) \quad R_{\text{p(eq)}} = R_W (Q^2 + 1)$$

where $R_{\text{p(eq)}}$ represents the parallel equivalent resistance, Q represents the Q of the inductor, and R_W represents the winding resistance of the inductor.

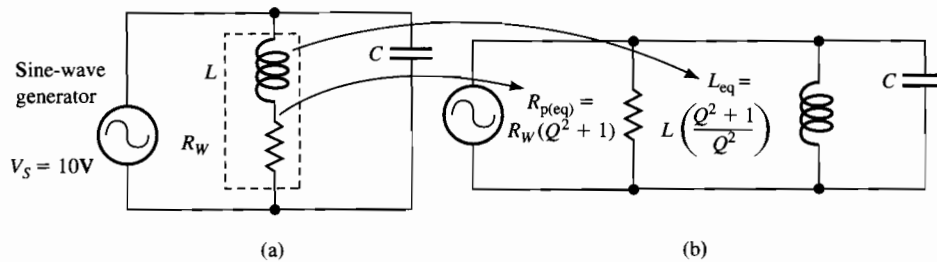


Figure 28–2

The Q used in the conversion equation is the Q for the inductor:

$$Q = \frac{X_L}{R_W}$$

The *selectivity* of series circuits was discussed in Experiment 27. Parallel resonant circuits also respond to a group of frequencies. In parallel resonant circuits, the impedance as a function of frequency has the same shape as the current versus frequency curve for series resonant circuits. The *bandwidth* of a parallel resonant circuit is the frequency range at which the circuit impedance is 70.7% of the maximum impedance. The sharpness of the response to frequencies is again measured by the circuit Q . The circuit Q will be different from the Q of the inductor if there is additional resistance in the circuit. If there is no additional resistance in parallel with L and C , then the Q for a parallel resonant circuit is equal to the Q of the inductor.

Materials Needed:

- One 100 mH inductor
- One 0.047 μF capacitor
- One 1.0 k Ω resistor

Procedure:

1. Measure the value of a 100 mH inductor, a 0.047 μF capacitor, and a 1.0 k Ω resistor. Enter the measured values in Table 28–1. If it is not possible to measure the inductor or capacitor, use the listed values.
2. Measure the resistance of the inductor. Enter the measured inductor resistance in Table 28–1.
3. Construct the circuit shown in Figure 28–3. The purpose of R_{S1} is to develop a voltage that can be used to sense the total current in the circuit. Compute the resonant frequency of the circuit using the equation

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Enter the computed resonant frequency in Table 28–2. Set the generator to the f_r at 1.0 V_{pp} output, as measured with your oscilloscope. Use peak-to-peak values for all voltage measurements in this experiment.

Table 28–1

	Listed Value	Measured Value
L_1	100 mH	
C_1	0.047 μF	
R_{S1}	1.0 k Ω	
R_w (L_1 resistance)		

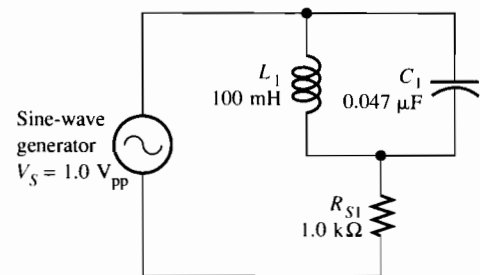


Figure 28–3

4. The Q of a parallel LC circuit with no resistance other than the inductor winding resistance is equal to the Q of the inductor. Compute the approximate Q of the parallel LC circuit from

$$Q = \frac{X_L}{R_w}$$

Enter the computed Q in Table 28–2.

5. Compute the bandwidth from the equation

$$BW = \frac{f_r}{Q}$$

Enter this as the computed BW in Table 28–2.

- Connect your oscilloscope across R_{S1} and tune for resonance by observing the voltage across the sense resistor, R_{S1} . Resonance occurs when the voltage across R_{S1} is a minimum, since the impedance of the parallel LC circuit is highest. Measure the resonant frequency (f_r) and record the measured result in Table 28–2.
- Compute a frequency increment (f_i) by dividing the computed bandwidth by 4. That is,

$$f_i = \frac{BW}{4}$$

Enter the computed f_i in Table 28–2.

- Use the measured resonant frequency (f_r) and the frequency increment (f_i) from Table 28–2 to compute 11 frequencies according to the Computed Frequency column of Table 28–3. Enter the 11 frequencies in column 1 of Table 28–3.

Table 28–2


	Computed	Measured
f_r		
Q		
BW		
$f_i = \frac{BW}{4}$		

Table 28–3

Computed Frequency	V_{RS1}	I	Z
$f_r - 5f_i =$			
$f_r - 4f_i =$			
$f_r - 3f_i =$			
$f_r - 2f_i =$			
$f_r - 1f_i =$			
$f_r =$			
$f_r + 1f_i =$			
$f_r + 2f_i =$			
$f_r + 3f_i =$			
$f_r + 4f_i =$			
$f_r + 5f_i =$			

- Tune the generator to each of the computed frequencies listed in Table 28–3. At each frequency, check that the generator voltage is still at $1.0 V_{pp}$; then measure the peak-to-peak voltage across R_{S1} . Record the voltage in column 2 of Table 28–3.
- Compute the total peak-to-peak current, I , at each frequency by applying Ohm's law to the sense resistor R_{S1} . (That is, $I = V_{RS1}/R_{S1}$.) Record the current in column 3 of Table 28–3.
- Use Ohm's law with the measured source voltage ($1.0 V_{pp}$) and source current at each frequency to compute the impedance at each frequency. Complete Table 28–3 by listing the computed impedances.

12. On Plot 28–1, draw the impedance versus frequency curve. From your curve determine the bandwidth. Complete Table 28–2 with the measured bandwidth.

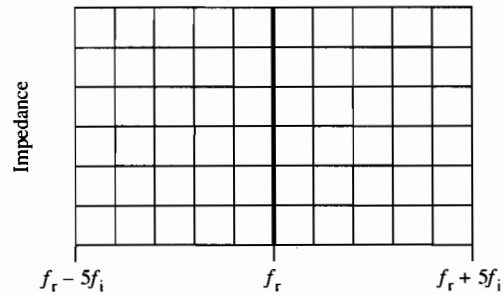

Plot 28–1

Conclusion:

Evaluation and Review Questions:

1. (a) Compare the impedance as a function of frequency for series and parallel resonance.

- (b) Compare the current as a function of frequency for series and parallel resonance.

2. What was the phase shift between the total current and voltage at resonance?

3. At resonance the total current was a minimum, but the branch currents were not. How could you find the value of the current in each branch?

4. What factors affect the Q of a parallel resonant circuit?
5. In the circuit of Figure 28–2(a), assume the inductor is 100 mH with 120 Ω of winding resistance and the capacitor is 0.01 μF . Compute:
- the resonant frequency _____
 - the reactance, X_L , of the inductor at resonance _____
 - the Q of the circuit _____
 - the bandwidth, BW _____

For Further Investigation:

The oscilloscope can be used to display the resonant dip in current by connecting a sweep generator to the circuit. This converts the time base on the oscilloscope to a frequency base. The sweep generator produces an FM (frequency modulated) signal, which is connected in place of the signal generator. In addition, the sweep generator has a synchronous sweep output that should be connected to the oscilloscope on the X channel input. The Y channel input is connected across the 1.0 k Ω sense resistor. The oscilloscope is placed in the XY mode. A diagram of the setup is shown in Figure 28–4. Build the circuit shown, determine a method to calibrate the frequency base, and summarize your procedure in a report.

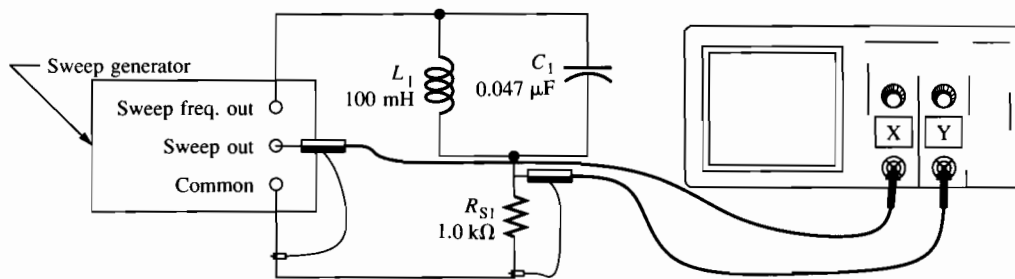


Figure 28–4

29 Passive Filters

Name _____
 Date _____
 Class _____

Reading:

Floyd, Sections 14-4 through 14-7


Objectives:

After performing this experiment, you will be able to:

1. Compare the characteristics and responses of low-pass, high-pass, bandpass, and notch filters.
2. Construct a T filter, a pi filter, and a resonant filter circuit and measure their frequency responses.

Summary of Theory:

In many circuits, different frequencies are present. If some frequencies are not desired, they can be rejected with special circuits called *filters*. Filters can be designed to pass either low or high frequencies. For example, in communication circuits, an audio frequency (AF) signal may be present with a radio frequency (RF) signal. The AF signal could be retained and the RF signal rejected with a *low-pass* filter. A *high-pass* filter will do the opposite: it will pass the RF signal and reject the AF signal. Sometimes the frequencies of interest are between other frequencies that are not desired. This is the case for a radio or television receiver, for example. The desired frequencies are present along with many other frequencies coming into the receiver. A resonant circuit is used to select the desired frequencies from the band of frequencies present. A circuit that passes only selected frequencies from a band is called a *bandpass* filter. The opposite of a bandpass filter is a *band reject* or *notch* filter. A typical application of a notch filter is to eliminate a specific interfering frequency from a band of desired frequencies. Figure 29-1 illustrates representative circuits and the frequency responses of various types of filters.

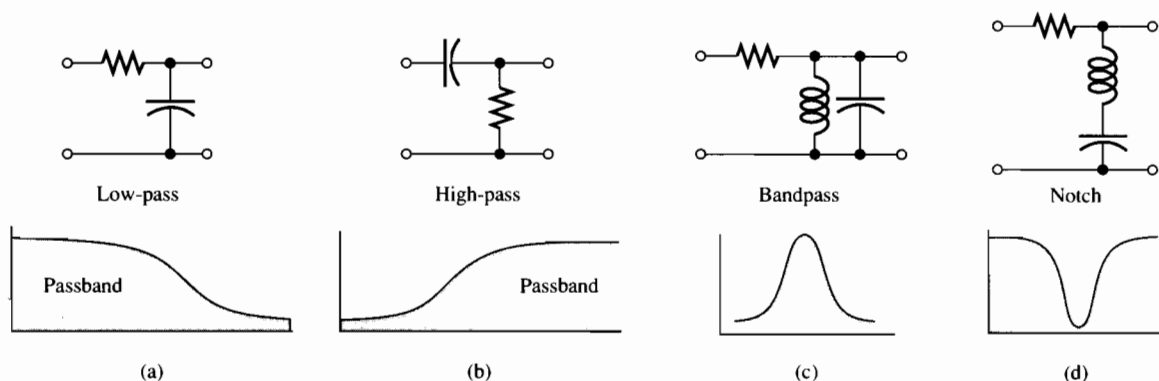

Filter 29-1 Frequency Response of Filters

The simplest filters are *RC* and *RL* series circuits studied in Experiments 23 and 25. These circuits can be used as either high-pass or low-pass filters, depending on where the input and output voltages are applied and removed. A problem with simple *RC* and *RL* filters

is that they change gradually from the passband to the stop band. You illustrated this characteristic on Plot 23–3 of Experiment 23.

Improved filter characteristics can be obtained by combining several filter sections. Unfortunately, you cannot simply stack identical sections together to improve the response as there are loading effects that must be taken into account. Two common improved filters are the *T* and the *pi* filters, so named because of the placement of the components in the circuit. Example of *T* and *pi* filters are shown in Figure 29–2. Notice that the low-pass filters have an inductor in series with the load and a capacitor in parallel with the load. The high-pass filter is the opposite.

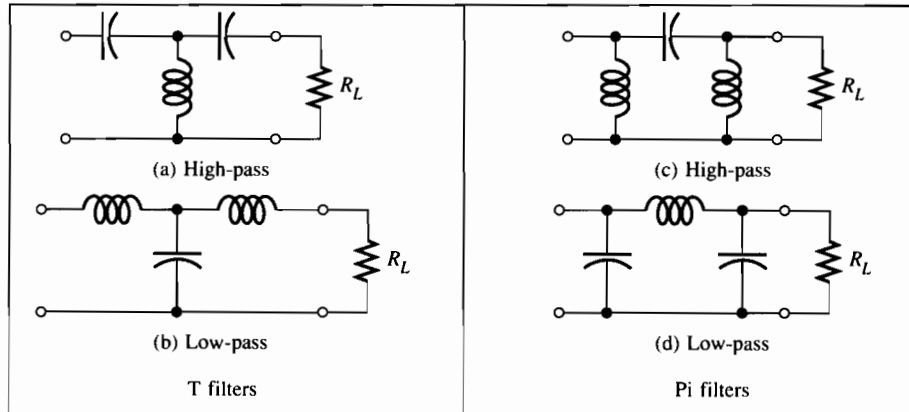


Figure 29–2

The choice of using a *T* or *pi* filter is determined by the load resistor and source impedance. If the load resistor is much larger than the source impedance, then the *T*-type filter is best. If the load resistor is much lower than the source impedance, then the *pi* filter is best.

Materials Needed:

Resistors:

One 680 Ω, one 1.6 kΩ

Capacitors:

One 0.033 μF, two 0.1 μF

One 100 mH inductor

Procedure:

1. Obtain the components listed in Table 29–1. For this experiment, it is important to have values that are close to the listed ones. Measure all components and record the measured values in Table 29–1. Use listed values for those components that you cannot measure.
2. Construct the *pi* filter circuit illustrated in Figure 29–3. Set the signal generator for a 500 Hz sine wave at 3.0 V_{rms}. The voltage should be measured at the generator with the circuit connected. Set the voltage with a voltmeter and check both voltage and frequency with the oscilloscope.

Table 29-1

	Listed Value	Measured Value
L_1	100 mH	
C_1	0.1 μF	
C_2	0.1 μF	
C_3	0.033 μF	
R_{L1}	680 Ω	
R_{L2}	1.6 k Ω	


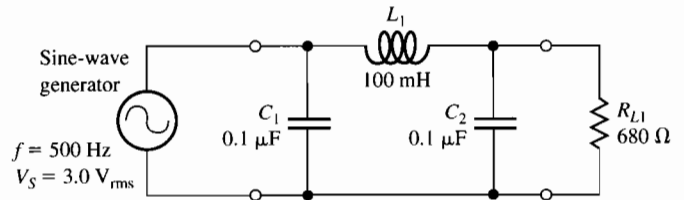


Figure 29-3

3. Measure and record the rms voltage across the load resistor (V_{RL1}) at 500 Hz. Record the measured voltage in Table 29-2.
4. Change the frequencies of the generator to 1000 Hz. Readjust the generator's amplitude to 3.0 V_{rms} . Measure V_{RL1} , entering the data in Table 29-2. Continue in this manner for each frequency listed in Table 29-2. (Note: You may be unable to obtain 3.0 V from the generator at 8.0 kHz.)

Table 29-2

Frequency	V_{RL1}
500 Hz	
1000 Hz	
1500 Hz	
2000 Hz	
3000 Hz	
4000 Hz	
8000 Hz	

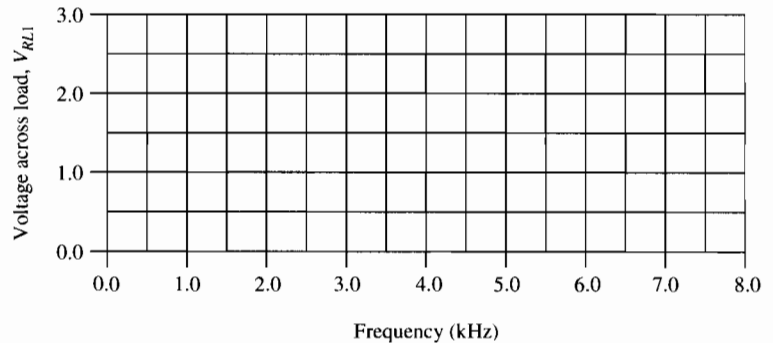

Plot 29-1

5. Graph the voltage across the load resistor (V_{RL1}) as a function of frequency on Plot 29-1.
6. Construct the T filter circuit illustrated in Figure 29-4. Set the signal generator for a 500 Hz sine wave at 3.0 V_{rms} . The voltage should be measured with the circuit connected. Set the voltage with a voltmeter and check both voltage and frequency with the oscilloscope as before.


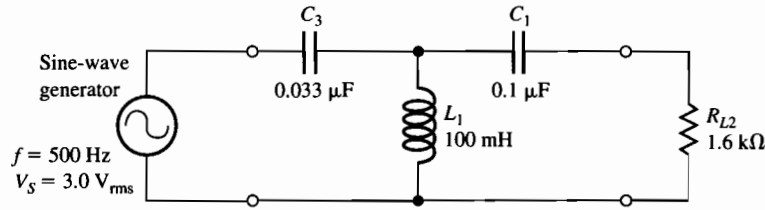


Figure 29-4

7. Measure and record the voltage across the load resistor (V_{RL2}) for each frequency listed in Table 29-3. Keep the generator voltage at $3.0 V_{rms}$. Graph the voltage across the load resistor (V_{RL2}) as a function of frequency on Plot 29-2.

Table 29-3

Frequency	V_{RL2}
500 Hz	
1000 Hz	
1500 Hz	
2000 Hz	
3000 Hz	
4000 Hz	
8000 Hz	

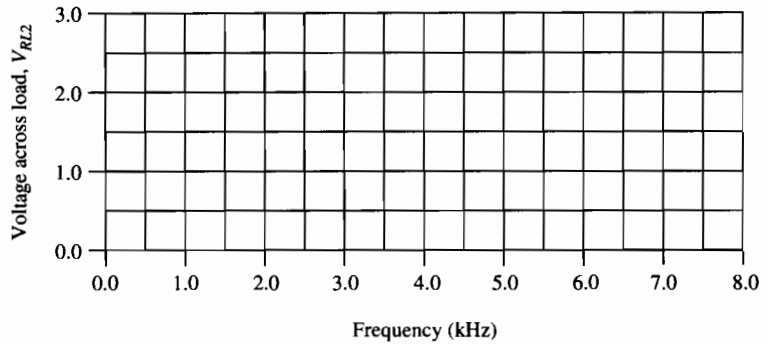

Plot 29-2

8. Construct the series resonant filter circuit illustrated in Figure 29-5. Set the generator for $3.0 V_{rms}$ at 500 Hz.


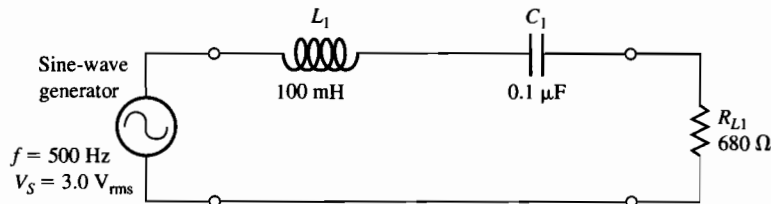


Figure 29-5

9. Measure and record the voltage across the load resistor (V_{RL1}) for each frequency listed in Table 29-4. Graph the voltage across the load resistor as a function of frequency on Plot 29-3.

Table 29–4

Frequency	V_{RL1}
500 Hz	
1000 Hz	
1500 Hz	
2000 Hz	
3000 Hz	
4000 Hz	
8000 Hz	

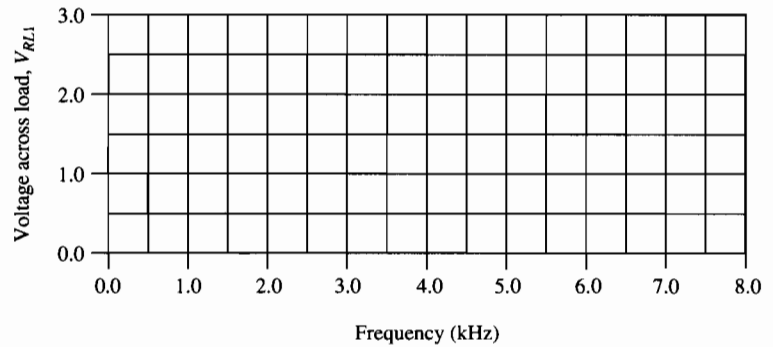

Plot 29–3

Conclusion:

Evaluation and Review Questions:

1. The cutoff frequency for each filter in this experiment is that frequency at which the output is 70.7% of its maximum value. From the frequency response curves in Plots 29–1 and 29–2, estimate the cutoff frequency for the high- and low-pass filters.
Pi filter cutoff frequency = _____
T filter cutoff frequency = _____
2. Compare the response curve of the high and low filters in this experiment with the response curve from the simple *RC* filter in Experiment 23.
3. For each filter constructed in this experiment, identify it as a low-pass, high-pass, bandpass, or notch filter:
(a) Plot 29–1 (pi filter): _____
(b) Plot 29–2 (T filter): _____
(c) Plot 29–3 (resonant filter): _____
4. Explain what would happen to the response curve from the series resonant filter if the output were taken across the inductor and capacitor instead of the load resistor.

5. (a) Sketch the circuit for a parallel resonant filter used as a bandpass filter.
- (b) Sketch the circuit for a parallel resonant filter used as a notch filter.

For Further Investigation:

Using the components from this experiment, construct a parallel resonant notch filter. Measure the frequency response with a sufficient number of points to determine the bandwidth accurately. The bandwidth (BW) of a resonant filter is the difference in the two frequencies at which the response is 70.7% of the maximum output. From your data, determine the BW of the parallel notch resonant filter.

Summarize your results, including the notch frequency, BW , and response curve in a lab report.


Application Assignment 14

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 14, Section 14-9: Application Assignment

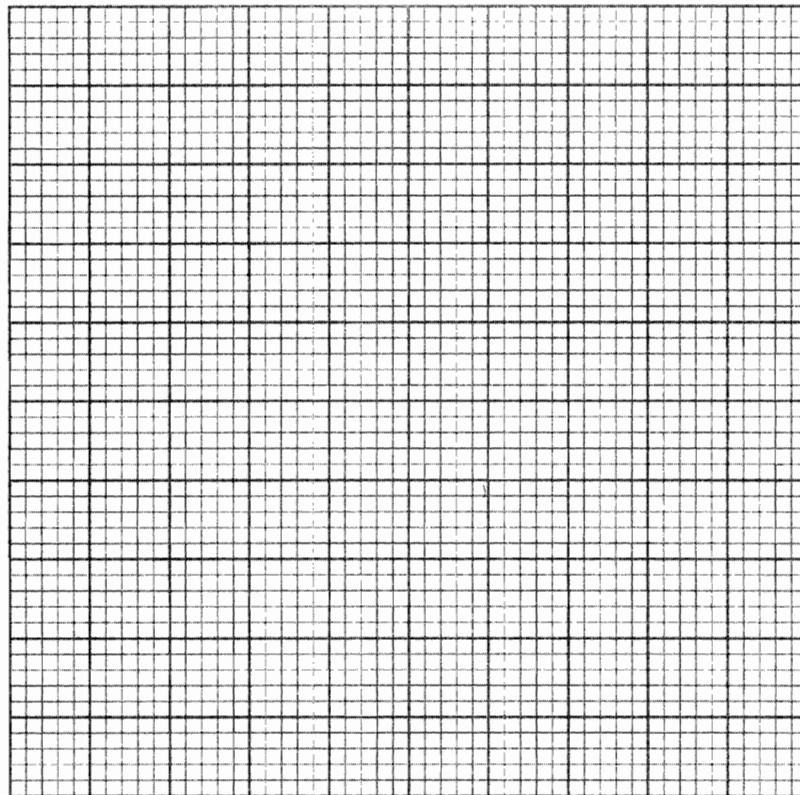Step 1 From the oscilloscope displays shown in Floyd's text, plot the frequency response of the filter.



Plot AA-14-1

Step 2 Specify the type of filter and determine the resonant frequency and the bandwidth.

Type of filter is _____

Resonant frequency = _____ Bandwidth = _____

Related Experiment:

Materials Needed:

Resistors:

Two 10 kΩ, one 5.1 kΩ

Four 1000 pF capacitors

Discussion:

A bandstop, or notch, filter, as described in the text, is capable of removing certain undesired frequencies from a signal. Another application of a notch filter is the twin-T oscillator shown in Figure AA-14-1(a). It oscillates at the notch frequency, which is given by the equation

$$f_r = \frac{1}{2\pi RC}$$

Test the filter portion of the oscillator by constructing the circuit shown in Figure AA-14-1(b). Use two 1000 pF capacitors in parallel for 2C. Connect a signal generator to the input and set it for a sine wave at 3.0 V_{pp} near the computed notch frequency. Vary the frequency of the generator and observe the output. Graph the response by plotting the voltage out as a function of the frequency for several points around the notch frequency.

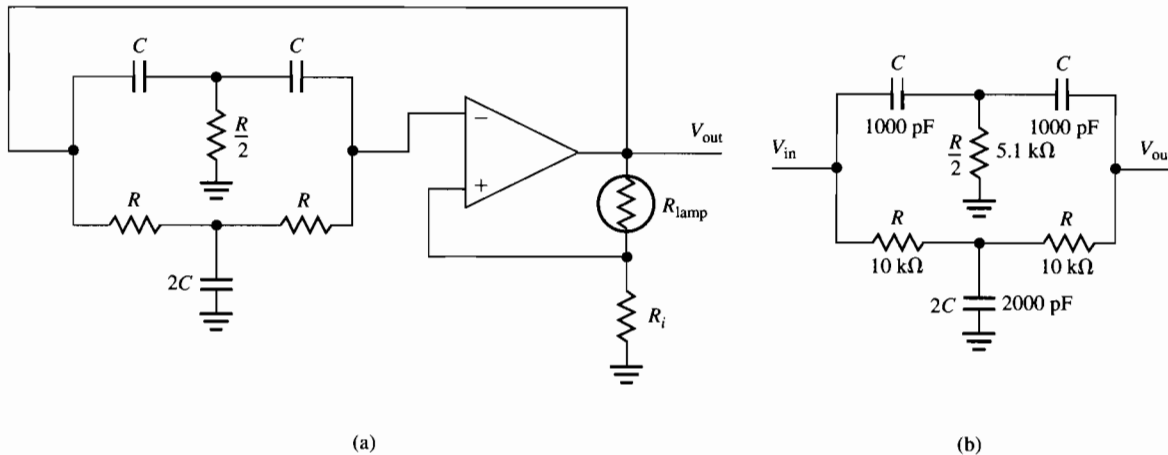


Figure AA-14-1

Experimental Results:

Checkup 14

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 14, and Buchla, Experiments 27, 28, and 29

- In a series resonant circuit at resonance:
 - current is a maximum
 - total impedance is zero
 - inductive reactance is larger than capacitive reactance
 - capacitive reactance is larger than inductive reactance
- In a series *RLC* circuit, the phase angle between the capacitor voltage and inductor voltage is:
 - 0°
 - 90°
 - 180°
 - dependent on the frequency
- In a resonant circuit, if *L* is halved and *C* is doubled, the resonant frequency will:
 - remain the same
 - double
 - quadruple
 - be halved
- In a resonant circuit, if *L* is halved and *C* is doubled, *Q* will:
 - remain the same
 - double
 - be halved
 - be one-fourth
- In a parallel resonant circuit, if the frequency is higher than resonance, the circuit is said to be:
 - purely resistive
 - inductive
 - capacitive
 - cutoff
- At the cutoff frequency of a filter, the output voltage is approximately:
 - 10% of the input voltage
 - 50% of the input voltage
 - 71% of the input voltage
 - 100% of the input voltage
- A bandstop filter can be made with a series resonant circuit and a resistor. The output is taken across:
 - the capacitor and the inductor
 - the capacitor and resistor
 - the inductor and resistor
 - the resistor
- If the inductor in a resonant circuit is replaced with an identical inductor but the replacement inductor has higher coil resistance, the new bandwidth will be:
 - unchanged
 - larger
 - smaller
- If a load is connected to a parallel resonant circuit, the selectivity will:
 - decrease
 - remain the same
 - increase
- Assume a series *RLC* circuit is connected across a dc source. The dc voltage will be across:
 - the inductor
 - the capacitor
 - the resistor

11. A series *RLC* circuit has a 200 pF capacitor and a 100 μ H inductor. If the inductor has a winding resistance of 20 Ω , calculate:
- the resonant frequency
 - the impedance of the circuit at resonance
 - the Q of the coil
12. The series resonant circuit in Experiment 27 used a 100 Ω resistor in parallel with the source. Explain how this resistor affected the Q of the circuit.
13. A tank circuit is constructed using a 200 μ H inductor and a variable capacitor. The circuit is required to tune the frequency range from 535 to 1605 kHz (AM radio band).
- Compute the range of capacitance required to cause resonance over the range of frequencies.
 - Assuming the inductor has a resistance of 10 Ω , compute the Q of the circuit at each end of the tuning range.
 - Using the Q value found in (b), determine the bandwidth at each end of the tuning range.
14. Observe the parallel resonant circuit shown in Figure C-14-1. Assume the inductor has a winding resistance of 25 Ω . At resonance, calculate:
- the inductive reactance
 - the Q of the coil

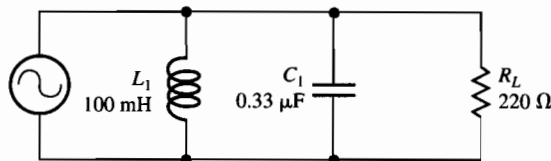


Figure C-14-1

30 Integrating and Differentiating Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 15–1 through 15–9

Objectives:

After performing this experiment, you will be able to:

1. Explain how an *RC* or *RL* series circuit can integrate or differentiate a signal.
2. Compare the waveforms for *RC* and *RL* circuits driven by a square wave generator.
3. Determine the effect of a frequency change for pulsed *RC* and *RL* circuits.

Summary of Theory:

In mathematics, the word *integrate* means to sum. If we kept a running sum of the area under a horizontal straight line, the area would increase linearly. An example is the speed of a car. Let's say the car is traveling a constant 40 miles per hour. In 1/2 hour the car has traveled 20 miles. In 1 hour the car has traveled 40 miles, and so forth. The car's rate is illustrated in Figure 30–1(a). Each of the three areas shown under the rate curve represents 20 miles. The area increases linearly with time and is shown in Figure 30–1(b). This graph represents the integral of the rate curve.

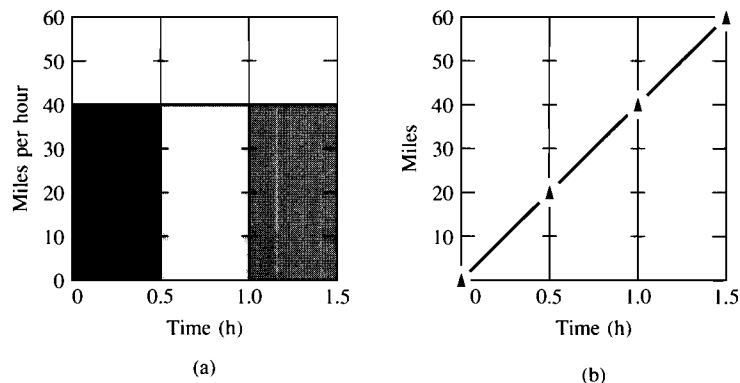


Figure 30–1

A similar situation exists when a capacitor starts to charge. If the applied voltage is a constant, the voltage on the capacitor rises exponentially. However, if we examine the beginning of this exponential rise, it appears to rise in a linear fashion. As long as the voltage change across the capacitor is small compared to the final voltage, the output will represent integration. An *integrator* is any circuit in which the output is proportional to the integral of the input signal. *If the RC time constant of the circuit is long compared to the period of the input waveform, then the waveform across the capacitor is integrated.*

The opposite of integration is *differentiation*. Differentiation means rate of change. *If the RC time constant of the circuit is short compared to the period of the input waveform,*

then the waveform across the resistor is differentiated. A pulse waveform that is differentiated produces spikes at the leading and trailing edge as shown in Figure 30–2. Differentiator circuits can be used to detect the leading or trailing edge of a pulse. Diodes can be used to remove either the positive or negative spike.

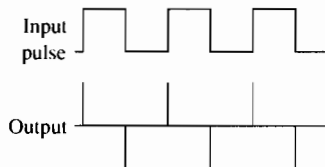


Figure 30–2

An *RL* circuit can also be used as an integrator or differentiator. As in the *RC* circuit, the time constant for the *RL* integrating circuit must be long compared to the period of the input waveform, and the time constant for the differentiator circuit must be short compared to the input waveform. The *RL* circuit will have similar waveforms to the *RC* circuit except that the output signal is taken across the inductor for the differentiating circuit and across the resistor for the integrating circuit.

Materials Needed:

One 10 kΩ resistor

Capacitors:

One 0.01 μF, one 1000 pF

One 100 mH inductor

Procedure:

1. Measure the value of a 100 mH inductor, a 0.01 μF and a 1000 pF capacitor, and a 10 kΩ resistor. Record their values in Table 30–1. If it is not possible to measure the inductor or capacitors, use the listed values.

Table 30–1

	Listed Value	Measured Value
L_1	100 mH	
C_1	0.01 μF	
C_2	1000 pF	
R_1	10 kΩ	

Table 30–2

	Computed	Measured
<i>RC</i> time constant		

2. Construct the circuit shown in Figure 30–3. The $10\text{ k}\Omega$ resistor is large compared to the Thevenin impedance of the generator. Set the generator for a 1.0 V_{pp} square wave with no load at a frequency of 1.0 kHz . You should observe that the capacitor fully charges and discharges at this frequency because the RC time constant is short compared to the period. On Plot 30–1, sketch the waveforms for the generator, the capacitor, and the resistor. Label voltage and time on your sketch. To look at the voltage across the resistor, use the difference function technique described in Experiment 16. The scope should be dc coupled for those measurements.


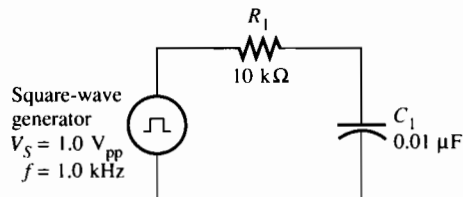


Figure 30–3

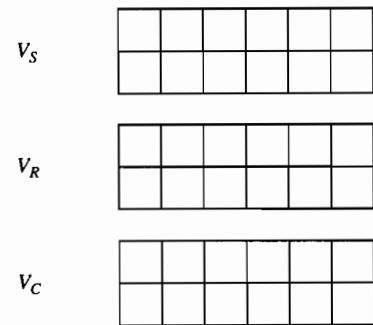

Plot 30–1

3. Compute the RC time constant for the circuit. Include the generator's Thevenin impedance as part of the resistance in the computation. Enter the computed time constant in Table 30–2.
4. Measure the RC time constant using the following procedure:
- With the generator disconnected from the circuit, set the output square wave on the oscilloscope to cover 5 vertical divisions (0 to 100%).
 - Connect the generator to the circuit. Adjust the SEC/DIV and trigger controls to stretch the capacitor-charging waveform across the scope face to obtain best resolution.
 - Count the number of horizontal divisions from the start of the rise to the point where the waveform crosses 3.15 vertical divisions (63% of the final level). Multiply the number of horizontal divisions that you counted by the setting of the SEC/DIV control.


Enter the measured RC time constant in Table 30–2.

5. Observe the capacitor waveform while you increase the generator frequency to 10 kHz . On Plot 30–2, sketch the waveforms for the generator, the capacitor, and the resistor at 10 kHz . Label the voltage and time on your sketch.


6. Temporarily, change the generator from a square wave to a triangle waveform. Describe the waveform across the capacitor.

7. Change back to a square wave at 10 kHz. Replace the capacitor with a 1000 pF capacitor. Using the difference channel, observe the waveform across the resistor. If the output were taken across the resistor, what would this circuit be called?

8. Replace the 1000 pF capacitor with a 100 mH inductor. Using the 10 kHz square wave, look at the signal across the generator, the inductor, and the resistor. On Plot 30–3, sketch the waveforms for each. Label the voltage and time on your sketch.

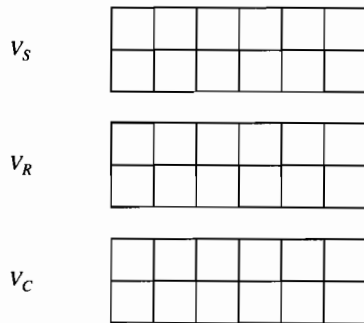

Plot 30–2

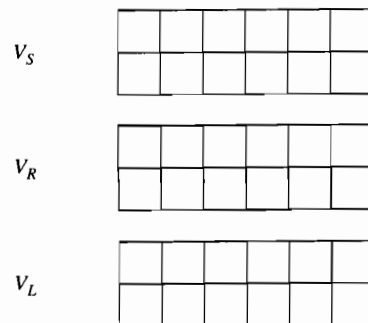

Plot 30–3

Conclusion:

Evaluation and Review Questions

1. (a) Explain why the Thevenin impedance of the generator was included in the calculated RC time constant measurement in step 3.

- (b) Suggest how you might find the value of an unknown capacitor using the RC time constant.
2. (a) Compute the percent difference between the measured and computed RC time constant.
- (b) List some factors that affect the accuracy of the measured result.
3. What accounts for the change in the capacitor voltage waveform as the frequency was raised in step 5?
4. (a) Draw an RC integrating circuit and an RC differentiating circuit.
- (b) Draw an RL integrating circuit and an RL differentiating circuit.
5. Assume you had connected a square wave to an oscilloscope but saw a signal that was differentiated as illustrated in Figure 30–2. What could account for this effect?

For Further Investigation:

The rate at which a capacitor charges is determined by the RC time constant of the equivalent series resistance and capacitance. The RC time constant for the circuit illustrated in Figure 30–4 can be determined by applying Thevenin’s theorem to the left of points **A–A**. The Thevenin resistance of the generator is part of the charging path and *should* be included. The capacitor is not charging to the generator voltage but to a voltage determined by the voltage divider consisting of R_1 and R_2 . Predict the time constant and the waveforms across each resistor. Investigate carefully the waveforms across each of the components.

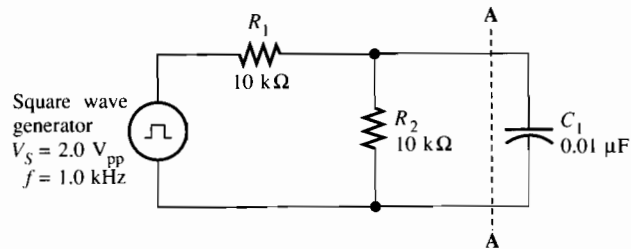


Figure 30–4

Application Assignment 15

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 15, Section 15–10: Application Assignment

Step 1 From the list of standard capacitors, specify the five capacitors for the integrator delay circuit.

$C_1 =$ _____ $C_2 =$ _____ $C_3 =$ _____
 $C_4 =$ _____ $C_5 =$ _____

Step 2 Complete the wire list for the breadboard using the circled numbers.

From	To	From	To	From	To
1					

Step 3 Specify the amplitude, frequency, and duty cycle settings for the function generator in order to test the delay times. Amplitude = _____

Frequencies for each delay time:

$f_1 =$ _____ $f_2 =$ _____
 $f_3 =$ _____ $f_4 =$ _____ $f_5 =$ _____

Develop a test procedure.

Step 4 Explain how you will verify that each switch setting produces the proper output delay time.

Related Experiment:

Materials Needed:

- One 7414 hex inverter (Schmitt trigger)
- One 10 k Ω potentiometer
- One 0.01 μ F capacitor

Discussion:

An interesting variation of the application assignment uses a Schmitt trigger as a switching device. A Schmitt trigger is a circuit with two thresholds for change. The switching level is dependent on whether the input signal is rising or falling. Consider the circuit shown in Figure AA-15-1. The charging and discharging of the capacitor is determined by the switching points of the Schmitt trigger. The input voltage is initially low and the output voltage is high (near 5.0 V). The capacitor begins to charge toward the higher output voltage. As the capacitor charges, the input voltage passes a trip point, causing the input voltage to go high and the output voltage to go low. The capacitor begins to discharge toward the lower output voltage until it passes the lower trip point causing the process to repeat.

Construct the circuit and measure the output waveform and the waveform across the capacitor. Try varying R as you observe the capacitor voltage. What is the output waveshape and frequency? Can you determine the threshold voltages of the Schmitt trigger by observing the output?

Experimental Results:

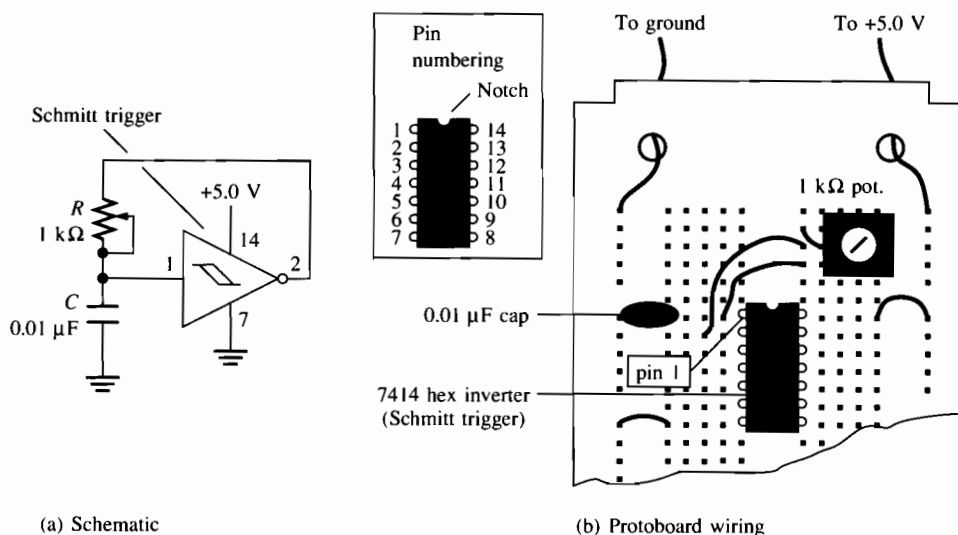


Figure AA-15-1

Checkup 15

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 15, and Buchla, Experiment 30

1. A circuit that can be used to change a square wave into a triangle wave is:
(a) a tuned circuit (b) a ladder circuit (c) an integrator (d) a differentiator
2. For an RC circuit driven by a pulse, the capacitor will fully charge in:
(a) one time constant (c) five time constants
(b) 1 s (d) a time depending on the amplitude of the pulse
3. An RC integrator circuit is driven by a square wave that goes from 0 V to 10 V. The time constant is very short compared to the input square wave. The output will be:
(a) a 5 V dc level (c) an exponentially rising and falling waveform
(b) a triangle waveform (d) a series of positive and negative spikes
4. Assume an RC differentiator circuit is driven by a square wave. The output is a square wave with a slight droop and overshoot. The time constant of the circuit (τ) is:
(a) much longer than the pulse width (c) equal to the pulse width
(b) much shorter than the pulse width
5. A $4.7\text{ k}\Omega$ resistor is connected in series with a $0.1\ \mu\text{F}$ capacitor. The time constant is:
(a) $0.47\ \mu\text{s}$ (b) $0.47\ \text{ms}$ (c) $21.3\ \text{ns}$ (d) $21.3\ \mu\text{s}$
6. A $4.7\text{ k}\Omega$ resistor is connected in series with a $10\ \text{mH}$ inductor. The time constant is:
(a) $0.47\ \mu\text{s}$ (b) $47\ \text{ms}$ (c) $4.7\ \text{s}$ (d) $2.13\ \mu\text{s}$
7. Assume that a switch is closed in a series RC circuit that has a time constant of 10 ms. The current in the circuit will be 37% of its initial value in:
(a) 1.0 ms (b) 3.7 ms (c) 6.3 ms (d) 10 ms
8. When a single pulse is applied to a series RL circuit, the greatest *change* in current occurs:
(a) at the beginning (b) at the 50% point (c) after one time constant
(d) at the end
9. A 1.0 kHz square wave is applied to an RL differentiator circuit. The current in the circuit will reach steady-state conditions if the time constant is equal to:
(a) $100\ \mu\text{s}$ (b) 1.0 ms (c) 6.3 ms (d) 10 ms

31 Diode Characteristics

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 16-1 through 16-7

Objectives:

After performing this experiment, you will be able to:

1. Measure and plot the forward- and reverse-biased IV characteristics for a diode.
2. Test the effect of heat on a diode's response.
3. Measure the ac resistance of a diode.

Summary of Theory:

Semiconductors are certain crystalline materials that can be altered with impurities to radically change their electrical characteristics. The impurity can be an electron donor or an electron acceptor. Donor impurities provide an "extra" electron that is free to move through the crystal at normal temperatures. The total crystal is electrically neutral, but the availability of free electrons in the material causes the material to be classified as an N-type (for negative) semiconductor. Acceptor impurities leave a "hole" (the absence of an electron) in the crystal structure. These materials are called P-type (for positive) semiconductors. They conduct by the motion of shared valence bond electrons moving between the atoms of the crystal. This motion is referred to as hole motion because the absence of an electron from the crystal structure can be thought of as a hole.

When a P-type and an N-type material are effectively made on the same crystal base, a *diode* is formed. The PN junction has unique electrical characteristics. Electrons and holes diffuse across the junction, creating a *barrier potential*, which prevents further current without an external voltage source. If a dc voltage source is connected to the diode, the direction it is connected has the effect of either increasing or decreasing the barrier potential. The effect is to allow the diode to either conduct readily or to become a poor conductor. If the negative terminal of the source is connected to the N-type material and the positive terminal is connected to P-type material, the diode is said to be forward-biased, and it conducts. If the positive terminal of the source is connected to the N-type material and the negative terminal is connected to P-type material, the diode is said to be reverse-biased, and the diode is a poor conductor.

While the actual processes that occur in a diode are rather complex, diode operation can be simplified with three approximations. The first approximation is to consider the diode as a switch. If it is forward-biased, the switch is closed. If it is reverse-biased, the switch is open. The second approximation is the same as the first except it takes into account the barrier potential. For a silicon diode, this is approximately 0.7 V. A forward-biased silicon diode will drop approximately 0.7 V across the diode. The third approximation includes the first and second approximations and adds the small forward (*bulk*) resistance that is present when the diode is forward-biased.

Materials Needed:

Resistors:

One 330 Ω , one 1.0 M Ω

One signal diode (1N914 or equivalent)

Procedure:

1. Measure and record the resistance of the resistors listed in Table 31–1. Then check your diode with the ohmmeter. Select a low ohm range and measure the forward and reverse resistance by reversing the diode. The diode is good on this test if the resistance is significantly different between the forward and the reverse directions. If you are using an autoranging meter, the meter may not produce enough voltage to overcome the barrier potential. You should select a low ohm range and hold that range. Consult the operator’s manual for specific instructions. Record the data in Table 31–1.

Table 31–1

Component	Listed Value	Measured Value
R_1	330 Ω	
R_2	1.0 M Ω	
D_1 forward resistance		
D_1 reverse resistance		

2. Construct the forward-biased circuit shown in Figure 31–1. The line on the diode indicates the cathode side of the diode. Set the power supply for zero volts.

Table 31–2

V_{FOR} (measured)	V_{R1} (measured)	I_{FOR} (computed)
0.45 V		
0.50 V		
0.55 V		
0.60 V		
0.65 V		
0.70 V		
0.75 V		

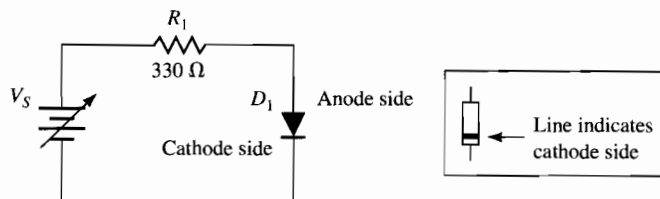


Figure 31–1

3. Monitor the forward voltage drop, V_{FOR} , across the diode. Slowly increase V_S to establish 0.45 V across the diode. Measure the voltage across the resistor, V_{R1} , and record it in Table 31–2.

4. The diode forward current, I_{FOR} , can be found by applying Ohm's law to R_1 . Compute I_{FOR} and enter the computed current in Table 31-2.
5. Repeat steps 3 and 4 for each voltage listed in Table 31-2.
6. With the power supply set to the voltage that causes 0.75 V to drop across the diode, bring a hot soldering iron near the diode. Do *not* touch the diode with the iron. Observe the effect of heat on the voltage and current in a forward-biased diode. If you have freeze spray available, test the effect of freeze spray on the diode's operation. Describe your observations.
7. The data in this step will be accurate only if your voltmeter has a very high input impedance. You can find out if your meter is high impedance by measuring the power supply voltage through a series 1.0 M Ω resistor. If the meter reads the supply voltage accurately, it has high input impedance. Connect the reverse-biased circuit shown in Figure 31-2. Set the power supply to each voltage listed in Table 31-3. Apply Ohm's law to the resistor and compute the reverse current in each case. Enter the computed current in Table 31-3.

Table 31-3

V_{R2} (measured)	V_{REV} (measured)	I_{REV} (computed)
5.0 V		
10.0 V		
15.0 V		


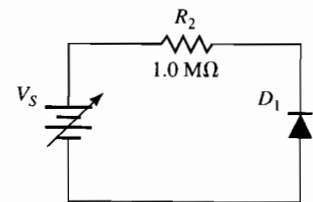


Figure 31-2

8. Graph the forward- and reverse-biased diode curves on Plot 31-1. The different voltage scale factors for the forward and reverse curves are chosen to allow the data to cover more of the graph. You need to choose an appropriate current scale factor that will put the largest current recorded near the top of the graph.

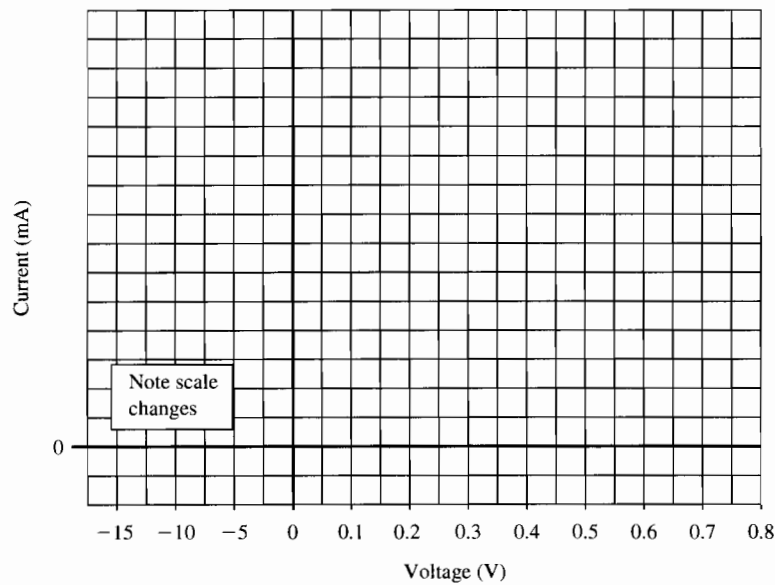

Plot 31-1

9. With the power supply set to 15 V, bring a hot soldering iron near the diode. Do *not* touch the diode with the iron. Observe the effect of heat on the voltage and current in the reverse-biased diode. If you have freeze spray available, test the effect of freeze spray on the diode's operation. Describe your observations.

Conclusion:

Evaluation and Review Questions:

1. Compute the diode's forward resistance at three points on the forward-biased curve. Apply Ohm's law to the curve in Plot 31-1 at 0.5 V, 0.6 V, and 0.7 V by dividing a small change in voltage by a small change in current, as illustrated in Figure 31-3. This result is called the ac resistance (r_{ac}) of the diode.

r_{ac} (0.5 V) = _____

r_{ac} (0.6 V) = _____

r_{ac} (0.7 V) = _____

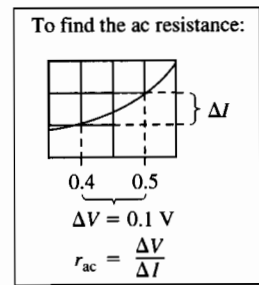


Figure 31-3

2. Does the diode's reverse resistance stay constant? Explain your answer.

3. From the data in Table 31-2, compute the maximum power dissipated in the diode.


4. Based on your observations of the heating and cooling of a diode, what does heat do to the forward and reverse resistance of a diode?

5. Explain how you could use an ohmmeter to identify the cathode of an unmarked diode. Why is it necessary to know the *actual* polarity of the ohmmeter leads?

6. A student measures the resistance of an unmarked diode with an ohmmeter. When the (+) lead of the ohmmeter is connected to lead 1 of the diode and the (-) lead of the ohmmeter is connected to lead 2 of the diode, the reading is 400Ω . When the ohmmeter leads are reversed, the reading is ∞ . Which lead on the diode is the anode?

For Further Investigation

The theoretical equation for a diode's I - V curve shows that the current is an exponential function of the bias voltage.¹ This means that the theoretical forward diode curve will plot as a straight line on semilog paper. Semilog paper contains a logarithmic scale on one axis and a linear scale on the other axis. Graph your data from this experiment (Table 31-2) onto Plot 31-2. What conclusion can you make from the data you recorded?

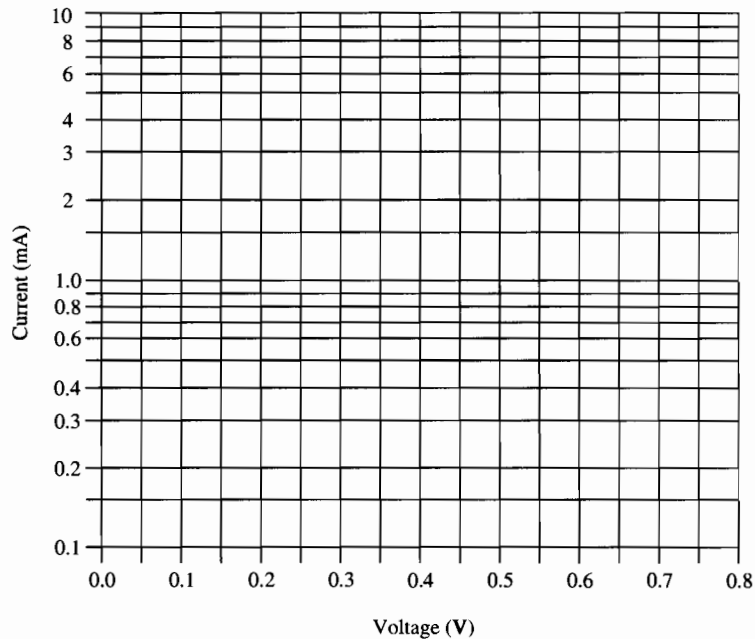

Plot 31-2

¹A complete discussion of the diode equation can be found in Bogart, *Electronic Devices and Circuits*, 3d edition, 1993, Merrill/Macmillan Publishing Co., Columbus, Ohio.

Application Assignment 16

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 16, Section 16–8: Application Assignment

- Step 1** Identify the fuse, transformer, and diodes. For each diode, determine the anode and the cathode end.
- Step 2** Basic Information. Review the measurements of the diode and transformer.
- Step 3** Troubleshooting. From the measurements shown, determine the likely problem with each power supply and complete Table AA–16–1. (Hint: If a diode is open, the resistance reading across the open diode is determined by other paths in the circuit. For example, if diode 4 is open, the meter can forward bias diode 1 through the secondary winding of the transformer.)

Table AA–16–1

Power Supply	Likely Fault
PS #1	
PS #2	
PS #3	
PS #4	

Related Experiment:

Materials Needed:

One 12.6 V_{rms} transformer
Four 1N4001 rectifier diodes (or equivalent)
One 100 μ F capacitor, one 10 μ F capacitor
One 7809 or 78L09 regulator. (Small regulators are preferred for protoboards. For this application assignment, any three-terminal regulator can be substituted.)

Discussion:

The faults in the power supplies described in the application assignment can be simulated in the laboratory. Construct the circuit shown in Figure AA–16–1. Do not apply power to the circuit. Simulate each fault you found in Table AA–16–1, then measure the resistance between the test points listed in Table AA–16–2. Resistance readings are relative; you will likely measure different values from those shown in the text due to differences in meters.

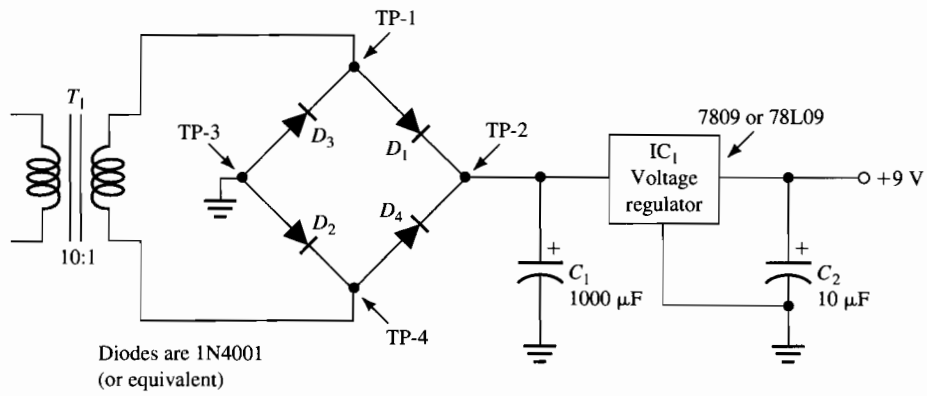


Figure AA-16-1

Table AA-16-2

Ohmmeter Readings for Simulated Faults				
Test Points	PS #1	PS #2	PS #3	PS #4
1 2				
2 1				
1 3				
3 1				
2 4				
4 2				
3 4				
4 3				
1 4				

Checkup 16

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 16, and Buchla, Experiment 31

1. A P-type material is a semiconductor containing:
(a) only pure material (b) extra electrons
(c) donor impurities (d) acceptor impurities
2. The number of valence electrons in the outer shell of a donor impurity is:
(a) 1 (b) 3 (c) 4 (d) 5
3. An example of an acceptor impurity is:
(a) aluminum (b) germanium (c) arsenic (d) phosphorus
4. The ac resistance of a silicon diode is highest:
(a) in the reverse direction (b) at 0.5 V
(c) at 0.6 V (d) at 0.7 V
5. When a PN junction is formed in silicon, carriers move across the junction, forming a potential barrier of approximately:
(a) 0.1 V (b) 0.3 V (c) 0.7 V (d) 1.5 V
6. When a forward-bias voltage is applied to a PN junction, the barrier voltage is
(a) reduced (b) unchanged (c) increased
7. When a diode is forward-biased, its internal resistance is typically:
(a) less than 100 Ω (b) between 100 Ω and 1000 Ω (c) greater than 1000 Ω
8. A germanium diode and 100 Ω series resistor are connected to a source of voltage. If the voltage measured across the resistor is 3 V, you know that:
(a) the diode is reverse-biased (b) the diode is shorted
(c) the diode is open (d) the current in the diode is 30 mA
9. The voltage for the source in Question 8 is approximately:
(a) 2.7 V (b) 3.0 V (c) 3.3 V (d) 3.7 V
10. The power dissipated in the diode in Question 8 is:
(a) zero (b) 9 mW (c) 21 mW (d) 3 W

11. A crystal set was one of the first radio receivers because it did not require power. It used a crystal, which was basically a diode detector. If you were choosing a modern diode to use in a crystal set, would you select a silicon or germanium diode? Why?
12. If you check the forward resistance of a diode with an ohmmeter, it will change depending on the range setting of the meter. Explain.
13. Compare the I - V curve between germanium and silicon.
 - (a) How does the barrier potential difference show up in the two curves?
 - (b) How does the I - V curve change as the temperature is increased?
14. Assume you are measuring the voltage across a forward-biased diode that is at room temperature. How can you determine if the diode is a silicon or germanium diode?
15. For the circuit shown in Figure C-16-1, determine if there is a fault for each of the following conditions. If so, state what the most likely problem is.
 - (a) The voltmeter reads zero; the ammeter reads 3.0 mA.
 - (b) The voltmeter reads +10 V; the ammeter reads zero.
 - (c) The voltmeter reads 0.7 V; the ammeter reads 2.8 mA.
 - (d) Both the voltmeter and the ammeter read zero.

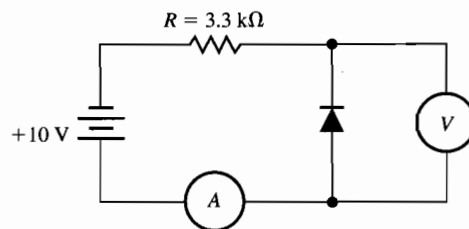


Figure C-16-1

32 Rectifier Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 17-1 through 17-3

Objectives:

After performing this experiment, you will be able to:

1. Construct half-wave, full-wave, and bridge rectifier circuits, and compare the input and output voltage for each.
2. Connect a filter capacitor to each circuit in objective 1 and measure the ripple voltage and ripple frequency.

Summary of Theory:

Rectifiers are diodes used to change ac to dc. They work like a one-way valve, allowing current to flow in only one direction, as illustrated in Figure 32-1. The diode is forward-biased for one-half cycle of the applied voltage and reverse-biased for the other half-cycle. The output waveform is a pulsating dc wave. This waveform can then be filtered to remove the unwanted variations.

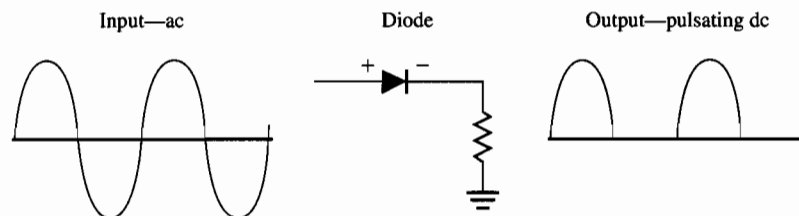


Figure 32-1

Rectifiers are widely used in power supplies that provide the dc voltage necessary for almost all active devices to work. The three basic rectifier circuits are the half-wave, the center-tapped full-wave, and the full-wave bridge rectifier circuits. The most important parameters for choosing diodes for these circuits are the maximum forward current, I_F , and the peak inverse voltage rating (PIV) of the diode. The peak inverse voltage is the maximum voltage the diode can withstand when it is reverse-biased. The amount of reverse voltage that appears across a diode depends on the type of circuit in which it is connected. Some characteristics of the three rectifier circuits are investigated in this experiment.

Rectifier circuits are generally connected through a transformer, as shown in Figure 32-2. Notice the ground on the primary side of the transformer is not the same as the ground on the secondary side of the transformer. This is because transformers isolate the ground connection of the 3-wire service connection. The oscilloscope chassis is normally connected to earth ground through the 3-prong service cord, causing the ground to be common; however, you cannot be certain of this. If there is no connection between the grounds, the reference ground is said to be a *floating* ground. You can determine if the ground is floating by testing the voltage difference between the grounds.

Materials Needed:

One 12.6 V_{rms} center-tapped transformer with fused line cord

Four diodes 1N4001 (or equivalent)

Two 2.2 kΩ resistors

One 100 μF capacitor

For Further Investigation:

One 0.01 μF capacitor


One 7812 or 78L12 regulator

Procedure:

Do this experiment only under supervision.

Caution! In this experiment, you are instructed to connect a low-voltage (12.6 V ac) transformer to the ac line. Be certain that you are using a properly fused and grounded transformer that has no exposed primary leads. Do not touch any connection in the circuit. At no time will you make a measurement on the primary side of the transformer. Have your connections checked by your instructor before applying power to the circuit.

1. Connect the half-wave rectifier circuit shown in Figure 32–2. Notice the polarity of the diode. Connect the oscilloscope so that channel 1 is across the transformer secondary and channel 2 is across the load resistor. The oscilloscope should be set for LINE triggering since all waveforms are synchronized with the ac line voltage. View the secondary voltage, V_{SEC} and load voltage, V_{LOAD} , for this circuit and sketch them on Plot 32–1. Label voltages on your sketch.

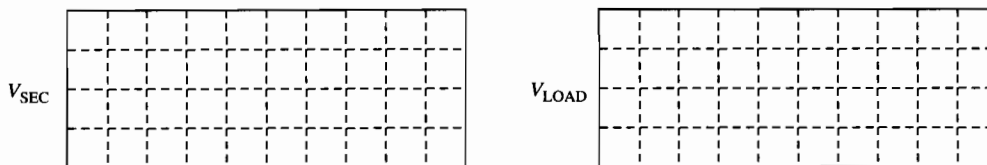

Plot 32–1

Measure the rms input voltage to the diode, V_{SEC} , and the output peak voltage, V_{LOAD} . Remember to convert the oscilloscope reading of V_{SEC} to rms. Record the data in Table 32–1.

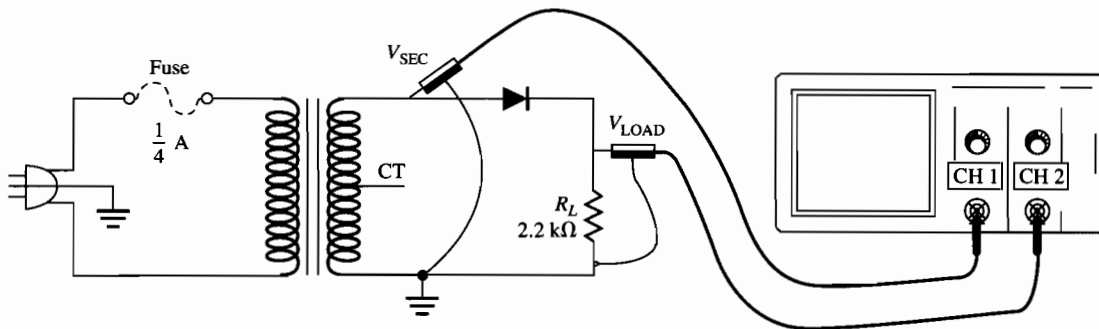



Figure 32–2

2. The output isn't very useful as a dc source because of the variations in the output waveform. Connect a $100\ \mu\text{F}$ capacitor (C_1) in parallel with the load resistor (R_L). *Note the polarity of the capacitor.* Measure the dc load voltage, V_{LOAD} , and the peak-to-peak ripple voltage, V_{RIPPLE} , in the output. To measure the ripple voltage, switch the oscilloscope vertical input to AC COUPLING. This allows you to magnify the small ac ripple voltage without including the much larger dc level. Measure the peak-to-peak ripple voltage and the ripple frequency. The ripple frequency is the frequency at which the waveform repeats. Record all data in Table 32-1.

Table 32-1 Half-Wave Rectifier Circuit

Without Filter Capacitor				With Filter Capacitor		
Computed	Measured	Computed	Measured	Measured		Ripple Frequency
V_{IN} (rms)	V_{SEC} (rms)	V_{LOAD} (peak)	V_{LOAD} (peak)	V_{LOAD} (dc)	V_{RIPPLE}	
12.6 V ac						

3. Disconnect power and change the circuit to the full-wave rectifier circuit shown in Figure 32-3. Notice that the ground for the circuit has changed. The oscilloscope ground needs to be connected as shown. *Check your circuit carefully before applying power.* Compute the expected peak output voltage. Then apply power and view the V_{SEC} and V_{LOAD} waveforms. Sketch the observed waveforms on Plot 32-2.

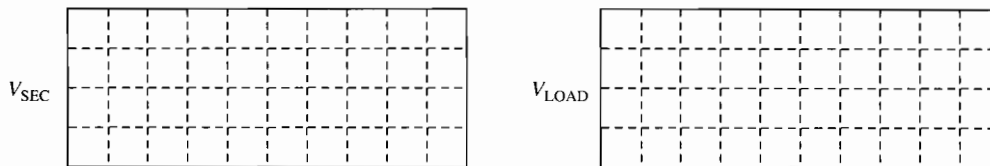

Plot 32-2

Measure V_{SEC} (rms) and the peak output voltage (V_{LOAD}) without a filter capacitor. Record the data in Table 32-2.

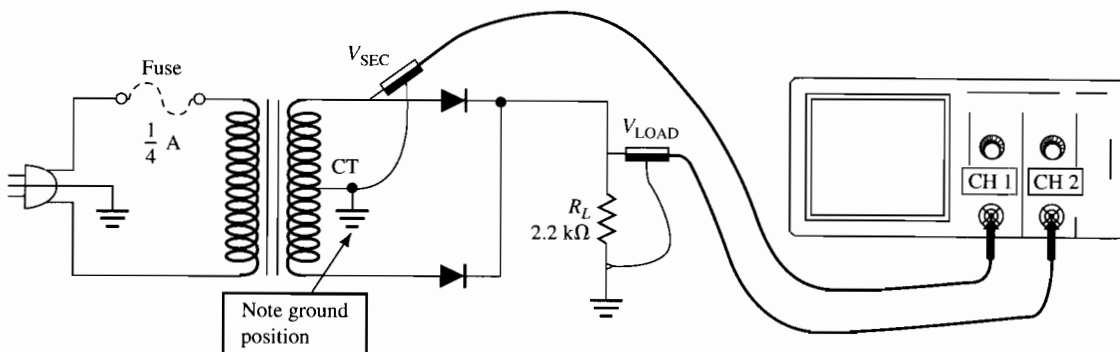


Figure 32-3

4. Connect the $100\ \mu\text{F}$ capacitor in parallel with the load resistor. Measure V_{LOAD} , the peak-to-peak ripple voltage, and the ripple frequency as before. Record the data in Table 32-2.

Table 32–2 Full-Wave Rectifier Circuit

Without Filter Capacitor				With Filter Capacitor		
Computed	Measured	Computed	Measured	Measured		Ripple Frequency
V_{SEC} (rms)	V_{SEC} (rms)	V_{LOAD} (peak)	V_{LOAD} (peak)	V_{LOAD} (dc)	V_{RIPPLE}	
6.3 V ac						

- Investigate the effect of the load resistor on the ripple voltage by connecting a second 2.2 k Ω load resistor in parallel with R_L and C_1 in the full-wave circuit in Figure 32–3. Measure the ripple voltage. What can you conclude about the effect of additional load current on the ripple voltage?

- Disconnect power and change the circuit to the bridge rectifier circuit shown in Figure 32–4. Notice that *no* terminal of the transformer secondary is at ground potential. The input voltage to the bridge, V_{SEC} , is not referenced to ground. *The oscilloscope cannot be used to view both the input voltage and the load voltage at the same time.* Check your circuit carefully before applying power. Compute the expected peak output voltage. Then apply power and *use a voltmeter* to measure V_{SEC} (rms). Use the oscilloscope to measure the peak output voltage (V_{LOAD}) without a filter capacitor. Record the data in Table 32–3.

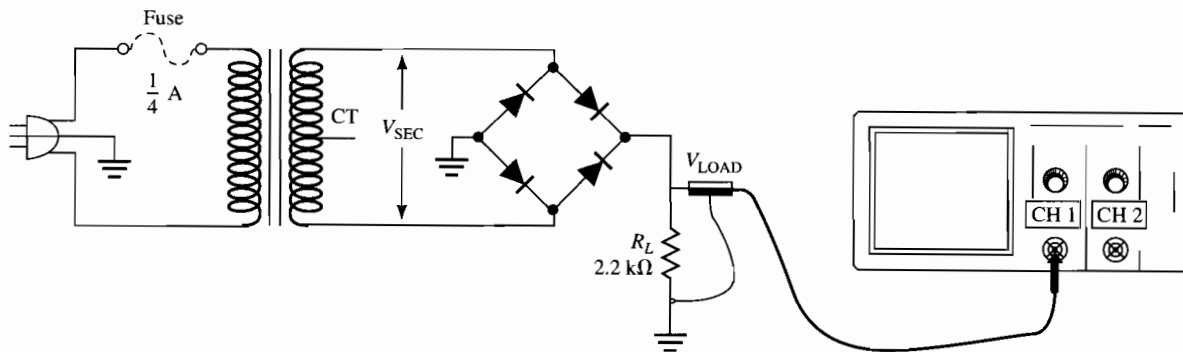


Figure 32–4

- Connect the 100 μ F capacitor in parallel with the load resistor. Measure V_{LOAD} , the peak-to-peak ripple voltage, and the ripple frequency as before. Record the data in Table 32–3.

Table 32–3 Bridge Rectifier Circuit

Without Filter Capacitor				With Filter Capacitor		
Computed	Measured	Computed	Measured	Measured		Ripple Frequency
V_{SEC} (rms)	V_{SEC} (rms)	V_{LOAD} (peak)	V_{LOAD} (peak)	V_{LOAD} (dc)	V_{RIPPLE}	
12.6 V ac						

8. Simulate an open diode in the bridge by removing one diode from the circuit. What happens to the output voltage? The ripple voltage? The ripple frequency?

Conclusion:

Evaluation and Review Questions:

1. What advantage does a full-wave rectifier circuit have over a half-wave rectifier circuit?
2. Compare a bridge rectifier circuit with a full-wave rectifier circuit. Which has the higher output voltage? Which has the greater current in the diodes?
3. Explain how you could measure the ripple frequency to determine if a diode were open in a bridge rectifier circuit.

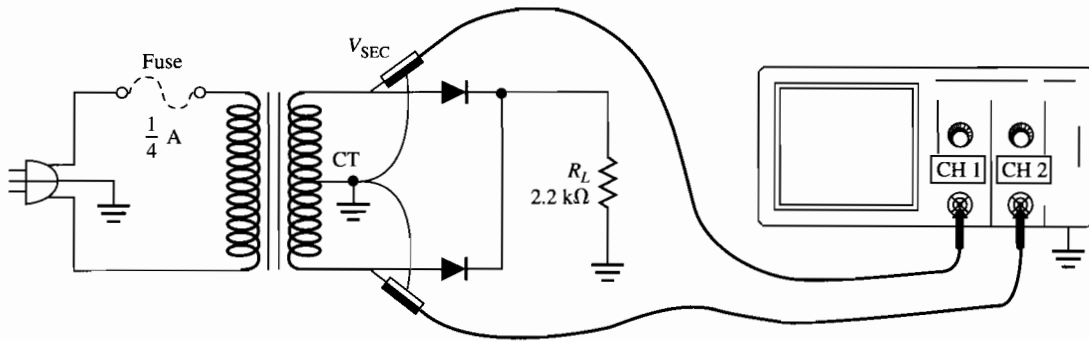


Figure 32-5

4. In step 3, you moved the ground reference to the center-tap of the transformer. If you wanted to look at the voltage across the entire secondary, you would need to connect the oscilloscope as shown in Figure 32-5 and *subtract* channel 2 from channel 1. (Some oscilloscopes do not have this capability.) Why is it necessary to use *two* channels to view the entire secondary voltage?
5. (a) What is the maximum dc voltage you could expect to obtain from a transformer with an 18 V_{rms} secondary using a bridge circuit with a filter capacitor?
- (b) What is the maximum dc voltage you could expect to obtain from the same transformer connected in a full-wave rectifier circuit with a filter capacitor?

For Further Investigation:

The bridge rectifier circuit shown in Figure 32-4 can be changed to a +12 V regulated power supply with the addition of a 7812 or 78L12 three-terminal regulator. The 7812 can deliver over 1.0 A of current, whereas the 78L12 can deliver over 100 mA. Add one of the regulators to your bridge rectifier circuit as shown in Figure 32-6. Measure the output ripple from the circuit with the regulator. Compare your results with the unregulated circuit in step 7.

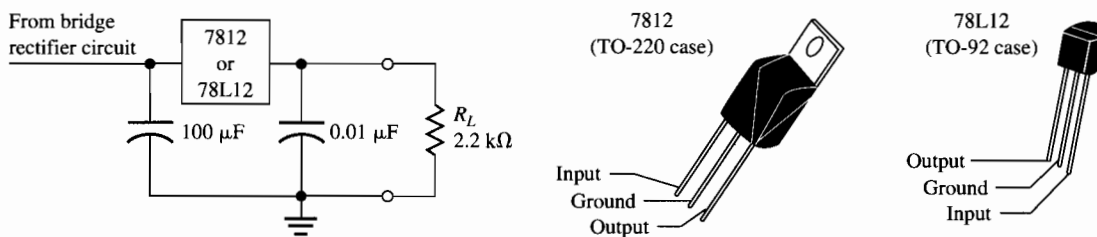


Figure 32-6

33 Diode Limiting and Clamping Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 17-4 through 17-8

Objectives:

After performing this experiment, you will be able to:

1. Explain the difference between clipping and clamping circuits.
2. Calculate and measure the voltage limits of both biased and unbiased clipping circuits.
3. Predict and measure the effect of a dc bias voltage on a clamping circuit.

Summary of Theory:

In addition to the use of diodes as rectifiers, there are a number of other interesting applications. For example, diodes are frequently used in applications such as waveshaping, mixers, detectors, protection circuits, and switching circuits. In this experiment, you will investigate two widely used applications of diode circuits, diode *limiter* circuits (also called *clippers*) and diode *clamping* circuits. Diode clipping circuits are used to prevent a waveform from exceeding some particular limit, either negative or positive. For example, assume it is desired to remove the portion of sine wave that exceeds +5.0 V. The bias voltage, V_B , is set to a voltage 0.7 V less than the desired clipping level. The circuit in Figure 33-1 will limit the waveform because the diode will be forward-biased whenever the signal exceeds +5.0 V. This places V_B in parallel with R_L and prevents the input voltage from going above +5.0 V. When the signal is less than +5.0 V, the diode is reverse-biased and appears to be an open circuit. If, instead, it was desired to clip the waveform below some specified level, the diode can be reversed and V_B is set to 0.7 V greater than the desired clipping level.

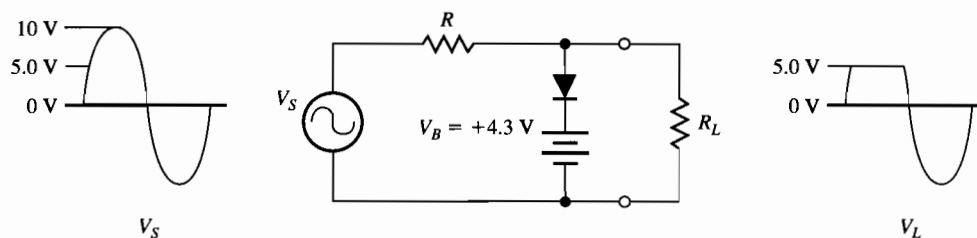


Figure 33-1

Diode clamping circuits are used to shift the dc level of a waveform. When a signal is passed through a capacitor, the dc component is blocked. A clamping circuit can restore the dc level. For this reason these circuits are sometimes called *dc restorers*. Diode clamping action is illustrated in Figure 33-2 for both positive and negative clamping circuits. The diode causes the series capacitor to have a low-resistance charging path and a high resistance discharge path through R_L . As long as the RC time constant is long compared to the period of the waveform, the capacitor will be charged to the peak value of the input waveform. This action requires several cycles of the input signal to charge the capacitor. The output load resistor sees the sum of the dc level on the capacitor and the input voltage.

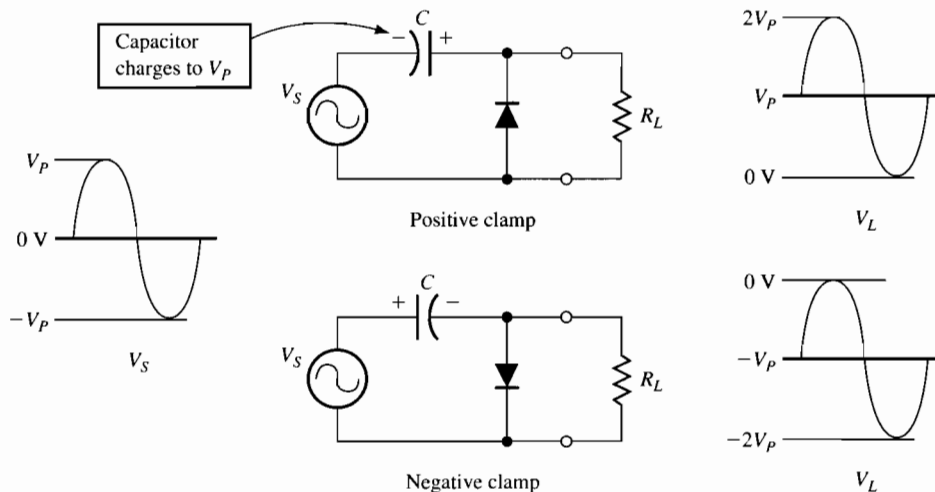


Figure 33-2

Materials Needed:

Resistors:

Two 10 k Ω , one 47 k Ω

Two signal diodes (1N914 or equivalent)

One 47 μ F capacitor

For Further Investigation:

One 10 k Ω potentiometer

One 1.0 k Ω resistor

Procedure:

1. Connect the circuit shown in Figure 33-3. Connect the signal generator to the circuit and set it for a 6.0 V_{pp} sine wave at a frequency of 1.0 kHz with no dc offset. Observe the input and output waveforms on the oscilloscope by connecting it as shown. Notice that R_2 and R_L form a voltage divider, causing the load voltage to be less than the source voltage. R_1 will provide a dc return path in case the signal generator is capacitively coupled.

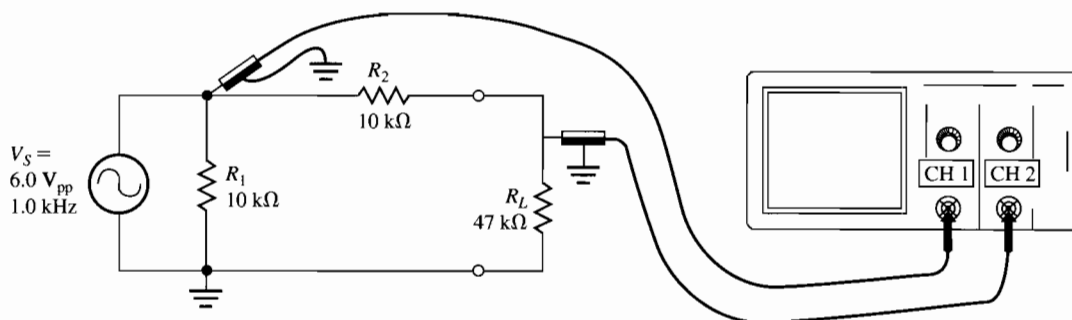


Figure 33-3

2. Now add the diode to the circuit as shown in Figure 33-4. Look carefully at the output waveform. Note the zero volt level. Sketch the input and output waveforms in the space provided. Then use the difference function technique (described in

Experiment 16) to measure the waveform across R_2 . Sketch the observed waveforms on Plot 33-1.


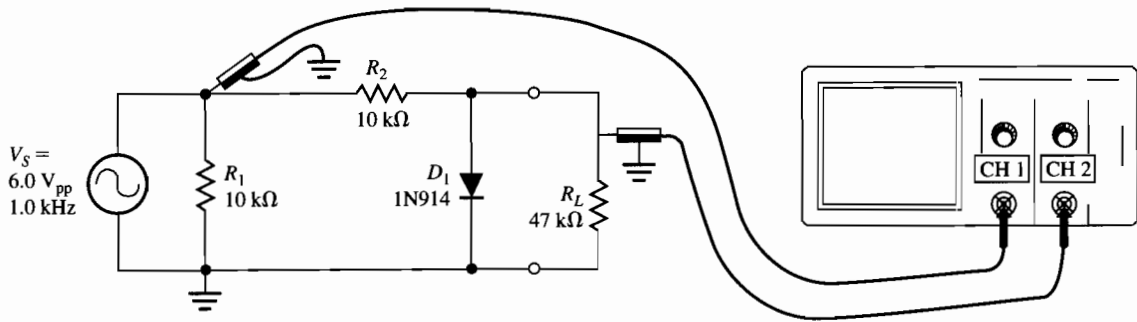


Figure 33-4

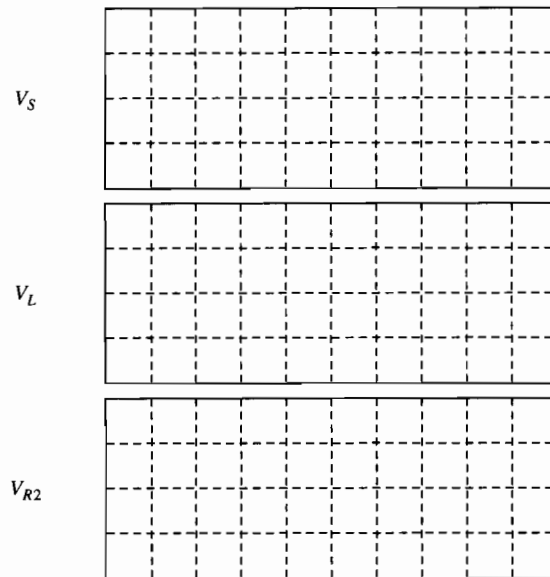

Plot 33-1

- Remove the cathode of the diode from ground and connect it to the power supply as shown in Figure 33-5. Vary the voltage from the supply and describe the results:

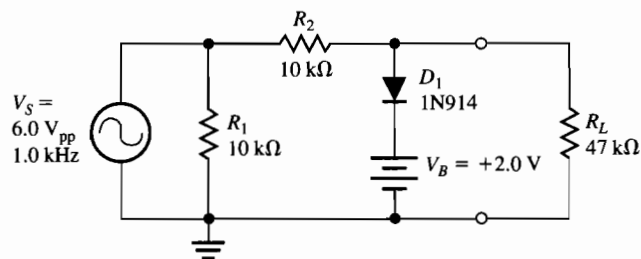


Figure 33-5

4. Reverse the diode in the circuit of Figure 33–5. Vary the dc voltage and describe the results:

5. Replace the positive power supply with a negative supply. Again, vary the dc voltage and describe the results:

6. If you have freeze spray available, test the effect on the clipping level when the diode is cooled.
Observations:

7. Connect the clamp circuit shown in Figure 33–6. Couple the oscilloscope with dc coupling and observe the output voltage. Vary the input voltage and observe the result.
Observations:

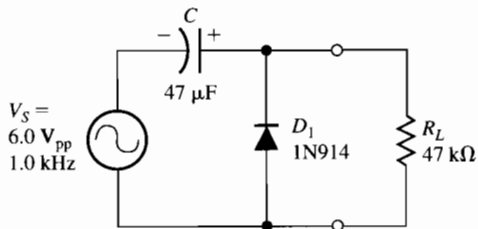


Figure 33–6


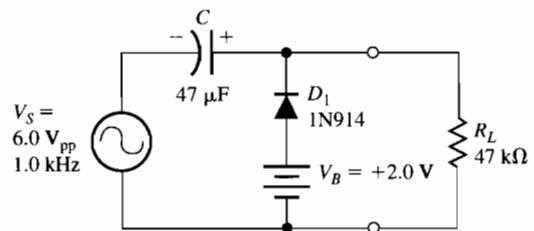


Figure 33–7

8. Add a dc voltage to the diode by connecting the power supply as shown in Figure 33–7. Sketch the output waveform on Plot 33–2 below. Show the dc level on your sketch:

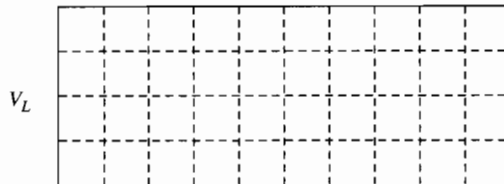

Plot 33–2

9. Find out what happens if the positive dc voltage is replaced with a negative dc source.
Observations:

Conclusion:

Evaluation and Review Questions:

1. In step 2, you observed the voltage waveform across the series resistor, R_2 . The waveform observed across R_2 could have been predicted by applying Kirchhoff's voltage law to V_S and V_L . Explain.
2. For the circuit of Figure 33–6, describe what would happen to the output voltage if the capacitor were shorted.
3. For the circuit of Figure 33–7, what change would you expect in the output if the diode were reversed?
4. Explain the difference between a limiting and a clamping circuit:

5. Predict the maximum and minimum output voltage for the clipping circuit shown in Figure 33–8.

$V_{\min} =$ _____

$V_{\max} =$ _____

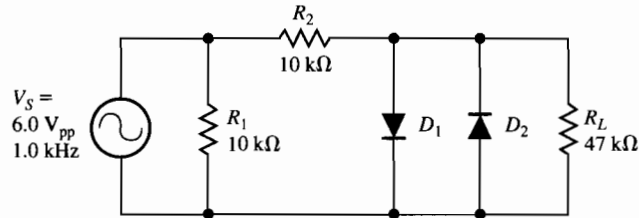


Figure 33–8

For Further Investigation:

A variable clipping level is possible from a fixed power supply by setting the reference voltage with a voltage divider as shown in Figure 33–9. Connect the circuit and determine the maximum and minimum clipping levels by measuring the output voltage as the potentiometer is varied.

Minimum clipping level = _____

Maximum clipping level = _____

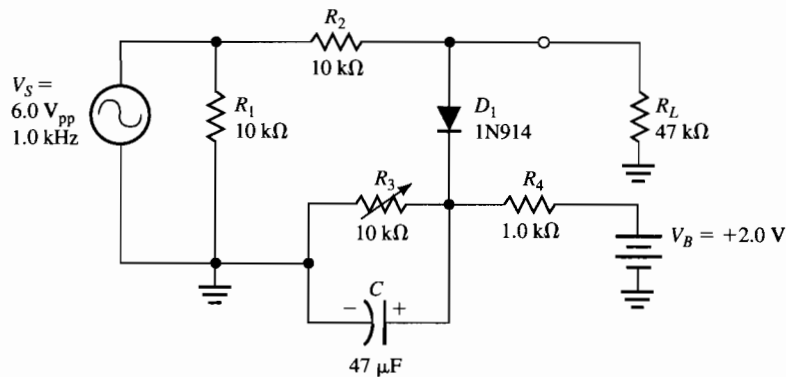


Figure 33–9

Application Assignment 17

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 17, Section 17–10: Application Assignment

Step 1 Identify the components.

Step 2 Relate the PC boards to the schematics

Step 3 Analyze the power supply/IR emitter board. Determine the voltages that are at points 1, 2, and 3. Assume the boards are operating correctly.

$$V_1 = \text{_____} \quad V_2 = \text{_____} \quad V_3 = \text{_____}$$

Step 4 Analyze the IR detector board. Determine the voltage at point 4 with no light. (Neglect the small dark current and current into the digital circuit.)

$$V_4 = \text{_____} \text{ (with no incident light)}$$

Step 5 Determine the voltage at point 4 with incident light. Assume a reverse current of $10 \mu\text{A}$ flows through the photodiode.

$$V_4 = \text{_____} \text{ (with incident light)}$$

Step 6 Troubleshoot the system. Give the probable cause of each fault listed in the text. Complete Table AA–17–1.

Table AA–17–1

Fault	Probable Cause
1	
2	
3	
4	
5	
6	
7	
8	

Related Experiment:

Materials Needed:

One opto-coupler (4N35 or equivalent)

One 10 μF capacitor

Resistors:

One 220 Ω , one 1.0 k Ω , one 2.0 k Ω

Discussion:

The test circuit shows an infrared LED and photodiode combination used to count objects. This combination of light source and receiver are also used when it is necessary to achieve a high degree of electrical isolation. (An electrocardiogram machine is an example.) Devices are available in packages called an opto-coupler (or opto-isolator) containing an LED light source and a sensor (a phototransistor or photodiode) in an opaque enclosure. In this application assignment, an audio signal will be transmitted by light in an optical isolator to a phototransistor connected as a photodiode. Normally, an opto-coupler is used to isolate two circuits, but in order to simplify the test circuit, common grounds and supply voltages are used here. Set up the test circuit shown in Figure AA-17-1. Set the function generator for a 1.0 V_{pp} sine wave at 1.0 kHz. This causes the LED to vary in brightness at a rate determined by the function generator. Compare the input and output signals on a two-channel oscilloscope. Compare the phase of the input and output signal and note the amplitude of the received signal. Summarize your observations.

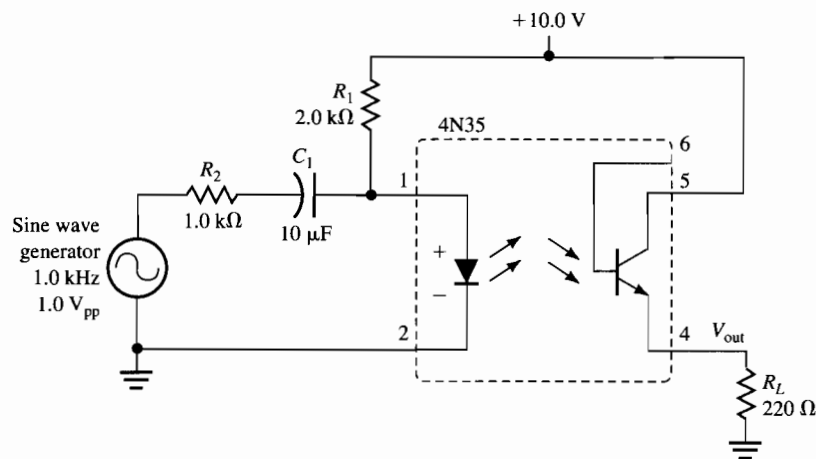


Figure AA-17-1

Checkup 17

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 17, and Buchla, Experiments 32 and 33

1. An advantage of a full-wave bridge rectifier is:
(a) it uses four diodes (b) two diodes are in series with the load
(c) diodes carry a smaller current (d) a center-tapped transformer is not needed
2. A half-wave rectified sine wave has an average voltage of 25 V. The peak voltage is approximately:
(a) 8 V (b) 16 V (c) 39 V (d) 79 V
3. A full-wave rectifier supply contains a capacitor input filter. The amount of the ripple voltage is dependent on the size of:
(a) the capacitor (b) the load resistor
(c) the capacitor and load resistor (d) neither the capacitor nor load resistor
4. If one diode in a full-wave rectifier is open, the output:
(a) ripple voltage and frequency will both increase
(b) ripple voltage will increase, but frequency will decrease
(c) ripple voltage and frequency will both decrease
(d) ripple voltage will decrease, but frequency will increase
5. A half-wave rectifier is connected to a 60 Hz source. The ripple frequency of the output should be:
(a) 30 Hz (b) 60 Hz (c) 120 Hz (d) 240 Hz
6. A full-wave bridge rectifier is across the $12.6 V_{\text{rms}}$ secondary of a transformer. The output is filtered with a capacitor input filter. The dc voltage is about:
(a) 9 V (b) 12 V (c) 17 V (d) 25 V
7. Each diode in a certain bridge rectifier circuit is rated for 1 A dc current. This means that the dc output current can have a maximum value of:
(a) 0.5 A (b) 1.0 A (c) 2.0 A (d) 4.0 A
8. A circuit that uses a series capacitor charged to the peak value of a waveform is a:
(a) clipping circuit (b) regulator (c) filter (d) dc restorer
9. In order to hold a load voltage constant, a zener diode needs to operate:
(a) with zero bias (b) with forward bias
(c) before the breakdown region (d) in the breakdown region

10. A diode that can be used to vary the frequency in a resonant circuit is a:
 (a) varactor (b) zener (c) rectifier (d) photodiode
11. (a) Explain how a measurement of the ripple frequency can help determine if all diodes are working in a bridge circuit.
- (b) Assume that you discovered from the ripple measurement that a diode was open, how would you locate which diode was bad?
12. A transformer with a $12.6 \text{ V}_{\text{rms}}$ secondary supplies the ac voltage for a full-wave bridge circuit. The output is connected to a $1000 \mu\text{F}$ capacitor in parallel with a $4.7 \text{ k}\Omega$ resistive load.
- (a) Compute the dc voltage on the load.
- (b) Compute the dc load current.
13. For the circuit in Figure C-17-1, assume the zener current is 5 mA .
- (a) What is the resistance of R_1 ?
- (b) If R_L were open, what current would flow in the zener diode?

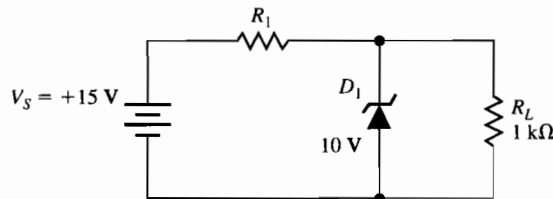


Figure C-17-1

14. A power supply, rated for 1 A of output current, changes from 5.00 V with no load to 4.92 V with a 5Ω resistive load. Calculate the percent load regulation.

34 Bipolar Transistors

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 18–1 through 18–5

Objectives:

After performing this experiment, you will be able to:

1. Measure and graph the collector characteristic curves for a bipolar junction transistor.
2. Use the characteristic curves to determine the β_{dc} of the transistor at a given point.

Summary of Theory:

A bipolar junction transistor (BJT) is a three-terminal device capable of amplifying an ac signal. The three terminals are called the base, emitter, and the collector. BJTs consist of a very thin base material sandwiched in between two of the opposite type materials. They are available in two forms, either NPN or PNP. The middle letter indicates the type of material used for the base, while the outer letters indicate the emitter and collector material. Two PN junctions are formed when a transistor is made, the junction between the base and emitter and the junction between the base and collector. These two junctions form two diodes, the emitter-base diode and the base-collector diode.

BJTs are current amplifiers. A small base current is amplified to a larger current in the collector-emitter circuit. An important characteristic is the dc current gain, which is the ratio of collector current to base current. This is called the dc beta (β_{dc}) of the transistor. Another useful characteristic is the dc alpha (α_{dc}). The dc alpha is the ratio of the collector current to the emitter current and is always less than 1.

For a transistor to amplify, power is required from dc sources. The dc voltages required for proper operation are referred to as bias voltages. The purpose of bias is to establish and maintain the required operating conditions despite variations between transistors or circuit parameters. For normal operation, the base-emitter junction is forward-biased and the base-collector junction is reverse-biased. Since the base-emitter junction is forward-biased, it has characteristics of a forward-biased diode. A silicon bipolar transistor requires approximately 0.7 V of voltage across the base-emitter junction to cause base current to flow.

Materials Needed:

Resistors:

One 100 Ω , one 33 k Ω

One 2N3904 NPN transistor (or equivalent)

For Further Investigation:

Transistor curve tracer

Procedure:

1. Measure and record the resistance of the resistors listed in Table 34–1.

Table 34–1

	Listed Value	Measured Value
R_1	33 k Ω	
R_2	100 Ω	

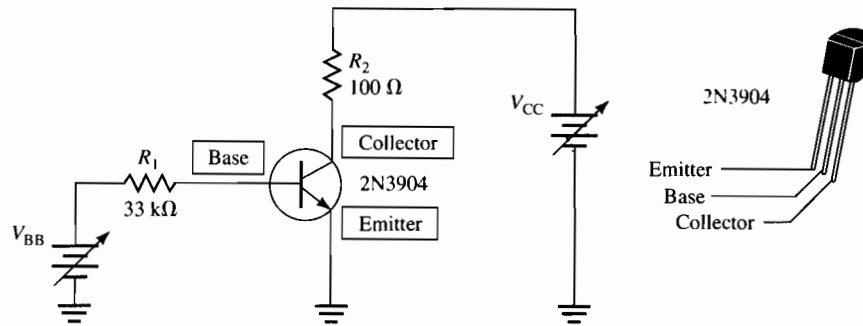


Figure 34–1


2. Connect the common emitter configuration illustrated in Figure 34–1. Start with both power supplies set to 0 V. The purpose of R_1 is to limit base current and allow determination of the base current. Slowly increase V_{BB} until V_{R1} is 1.65 V. This sets up a base current of 50 μA , which can be shown by applying Ohm's law to R_1 .
3. Without disturbing the setting of V_{BB} , slowly increase V_{CC} until 2.0 V is measured between the transistor's collector and emitter. This voltage is called V_{CE} . Then measure and record V_{R2} for this setting. Record V_{R2} in Table 34–2 under the columns labeled Base Current = 50 μA .

Table 34–2

V_{CE} (measured)	Base Current = 50 μA		Base Current = 100 μA		Base Current = 150 μA	
	V_{R2} (measured)	I_C (computed)	V_{R2} (measured)	I_C (computed)	V_{R2} (measured)	I_C (computed)
2.0 V						
4.0 V						
6.0 V						
8.0 V						

4. Compute the collector current, I_C , by applying Ohm's law to R_2 . Use the measured voltage, V_{R2} , and the measured resistance, R_2 , to determine the current. Note that the current in R_2 is the same as I_C for the transistor. Enter the computed collector current in Table 34–2 under the columns labeled Base Current = 50 μA .
5. Without disturbing the setting of V_{BB} , increase V_{CC} until 4.0 V is measured across the transistor's collector to emitter. Measure and record V_{R2} for this setting. Compute the collector current by applying Ohm's law as in step 4. Continue in this manner for each of the values of V_{CE} listed in Table 34–2.
6. Reset V_{CC} for 0 V and adjust V_{BB} until V_{R1} is 3.3 V. The base current is now 100 μA .

7. Without disturbing the setting of V_{BB} , slowly increase V_{CC} until V_{CE} is 2.0 V. Then measure and record V_{R2} for this setting in Table 34-2 under columns labeled Base Current = 100 μA . Compute I_C for this setting by applying Ohm's law to R_2 . Enter the computed collector current in Table 34-2.
8. Increase V_{CC} until V_{CE} is equal to 4.0 V. Measure and record V_{R2} for this setting. Compute I_C as before. Continue in this manner for each value of V_{CE} listed in Table 34-2.
9. Reset V_{CC} for 0 V and adjust V_{BB} until V_{R1} is 4.95 V. The base current is now 150 μA .
10. Complete Table 34-2 by repeating steps 7 and 8 for 150 μA of base current.
11. Plot three collector characteristic curves using the data tabulated in Table 34-2. The collector characteristic curve is a graph of V_{CE} versus I_C for a constant base current. Choose a scale for I_C that allows the largest current observed to fit on the graph. Label each curve with the base current it represents. Graph the data on Plot 34-1.

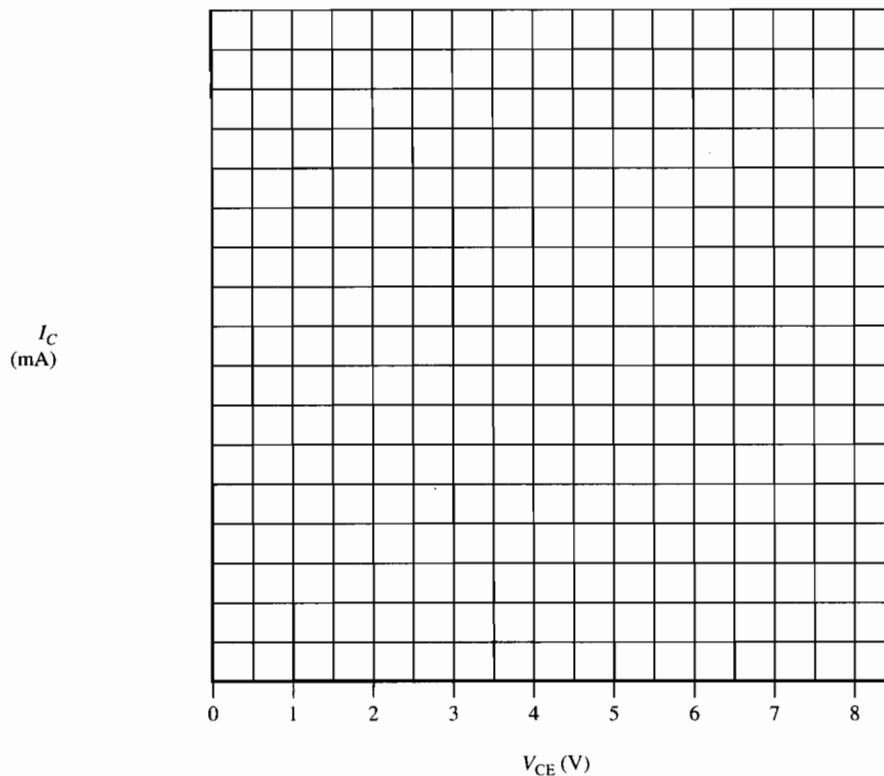

Plot 34-1

12. Use the characteristic curve you plotted to determine the β_{dc} for the transistor at a V_{CE} of 3.0 V and a base current of 50, 100, and 150 μA . Then repeat the procedure for a β_{dc} at a V_{CE} of 5.0 V. Tabulate your results in Table 34–3.

Table 34–3

V_{CE}	Current Gain, β_{dc}		
	$I_B = 50 \mu\text{A}$	$I_B = 100 \mu\text{A}$	$I_B = 150 \mu\text{A}$
3.0 V			
5.0 V			

Conclusion:

Evaluation and Review Questions:

- Do the experimental data indicate that β_{dc} is a constant at all points? Does this have any effect on the linearity of the transistor?
- What effect would a higher β_{dc} have on the characteristic curves you measured?
- What is the maximum power dissipated in the transistor for the data taken in the experiment?
- (a) The dc alpha of a bipolar transistor is the collector current I_C , divided by the emitter current, I_E . Using this definition and $I_E = I_C + I_B$, show that dc alpha can be written

$$\alpha_{dc} = \frac{\beta_{dc}}{\beta_{dc} + 1}$$

- (b) Compute the dc alpha for your transistor at $V_{CE} = 4.0 \text{ V}$ and $I_B = 100 \mu\text{A}$.
5. What value of V_{CE} would you expect if the base terminal of a transistor were open? Explain your answer.

For Further Investigation:

If you have a transistor curve tracer available, use it to check the data taken in this experiment. A transistor curve tracer has a step generator that generates a staircase set of current or voltage steps. Set the step generator to $50 \mu\text{A}$ per step. Select positive steps to apply to the base with the emitter grounded. Select a positive sweep voltage of approximately $+20 \text{ V}$ with a series limiting resistance of several hundred ohms. Select a horizontal display of 1 V/div and a vertical display of about 10 mA/div . (If your transistor has a very high or low β_{dc} , you may need to change these settings.) The curve tracer will show the collector characteristic curves. Test the effect of heating or cooling the transistor on β_{dc} .

35 Field-Effect Transistors

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 18–6 through 18–9

Objectives:

After performing this experiment, you will be able to:

1. Measure and graph the drain characteristic curves for a junction field-effect transistor (JFET).
2. Use the characteristic drain curves to determine the transconductance of the JFET.
3. Explain how a JFET can be used as a two-terminal constant current source.

Summary of Theory:

The field-effect transistor (FET) is a voltage-controlled transistor that uses an electrostatic field to control current flow rather than a base current. Instead of a sandwich of materials as in the bipolar transistor, the FET begins with a doped piece of silicon called a *channel*. On one end of the channel is a terminal called the *source* and on the other end of the channel is a terminal called the *drain*. Current flow in the channel is controlled by a voltage applied to a third terminal called the *gate*. Field-effect transistors are classified as either junction-gate (JFET) or insulated-gate (IGFET) devices. Insulated gate devices are also called MOSFETs (for *Metal Oxide Semiconductor* FETs). The major difference between bipolar and field-effect transistors is that bipolar transistors use a small base *current* to control a larger current, but the FET uses a gate *voltage* to control the current. Since the input of an FET draws virtually no current, the input impedance is extremely high; however, the sensitivity to input voltage change is much greater in the bipolar transistor than in the FET. Both the JFET and MOSFET have similar ac characteristics; however, in this experiment, we will concentrate on the JFET to simplify the discussion.

The gate of a JFET is made of the opposite type of material from that of the channel, forming a PN diode between the gate and channel. Application of a reverse bias on this junction decreases the conductivity of the channel, reducing the source-drain current. The gate diode is never forward-biased and hence draws almost no current. The JFET comes in two forms, N-channel and P-channel. The N-channel is distinguished on drawings by an inward drawn arrow on the gate connection, while the P-channel has an outward pointing arrow on the gate.

The characteristic drain curves for a JFET exhibit several important differences from the BJT. Besides being a voltage-controlled device, the JFET is a normally ON device. In other words, a reverse-bias voltage must be applied to the gate-source diode in order to close off the channel and stop drain-source current. When the gate is shorted to the source, maximum allowable drain-source current flows. This current is called I_{DSS} for *Drain-Source current with gate Shorted*. The JFET exhibits a region on its characteristic curve where drain current is proportional to the drain-source voltage. This region, called the ohmic region, has important applications as a voltage-controlled resistance.

A useful specification for estimating the gain of a JFET is called the *transconductance*, which is abbreviated g_m . Recall that conductance is the reciprocal of resistance. Since the output current is controlled by an input voltage, it is useful to think of FETs as transconductance amplifiers. The transconductance can be found by dividing a small change in the *output current* by a small change in the *input voltage*; that is,

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Materials Needed:

Resistors:

One 100 Ω , one 33 k Ω

One 2N5458 N-channel JFET transistor (or equivalent)

Procedure:

1. Measure and record the resistance of the resistors listed in Table 35–1.
2. Construct the circuit shown in Figure 35–1. Start with V_{GG} and V_{DD} at zero volts. Connect a voltmeter between the drain and source of the transistor. Keep V_{CC} at 0 V and slowly increase V_{DD} until V_{DS} is 1.0 V. (V_{DS} is the voltage between the transistor’s drain and source.)

Table 35–1

	Listed Value	Measured Value
R_1	33 k Ω	
R_2	100 Ω	

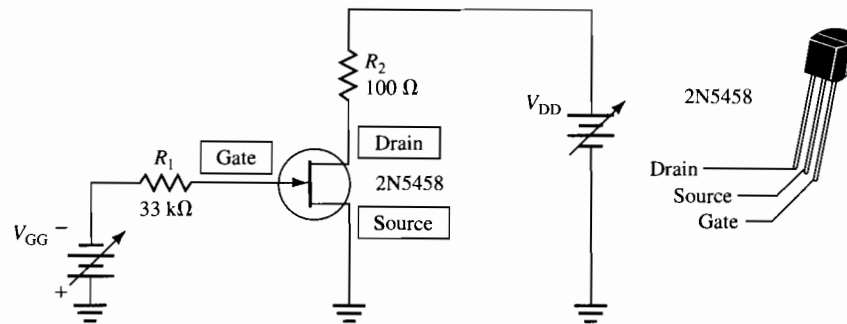


Figure 35–1


3. With V_{DS} at 1.0 V, measure the voltage across R_2 (V_{R2}). Compute the drain current, I_D , by applying Ohm’s law to R_2 . Note that the current in R_2 is the same as I_D for the transistor. Enter the computed I_D in Table 35–2 under the columns labeled Gate Voltage = 0 V.
4. Without disturbing the setting of V_{GG} , slowly increase V_{DD} until V_{DS} is 2.0 V. Then measure and record V_{R2} for this setting. Compute I_D as before and enter the computed current in Table 35–2 under the columns labeled Gate Voltage = 0 V.

Table 35-2

V_{DS} (measured)	Gate Voltage = 0 V		Gate Voltage = -1.0 V		Gate Voltage = -2.0V	
	V_{R2} (measured)	I_D (computed)	V_{R2} (measured)	I_D (computed)	V_{R2} (measured)	I_D (computed)
1.0 V						
2.0 V						
3.0 V						
4.0 V						
6.0 V						
8.0 V						

- Repeat step 4 for each value of V_{DS} listed in Table 35-2.
- Adjust V_{GG} for -1.0 V. This applies -1.0 V between the gate and source because there is almost no gate current into the JFET and almost no voltage drop across R_1 . Reset V_{DD} until $V_{DS} = 1.0$ V. Measure V_{R2} and enter it in Table 35-2. Compute I_D and enter the computed current in Table 35-2 under the columns labeled Gate Voltage = -1.0 V.
- Without changing the setting of V_{GG} , adjust V_{DD} for each value of V_{GS} listed in Table 35-2 as before. Compute the drain current at each setting and enter it in Table 35-2 under the columns labeled Gate Voltage = -1.0 V.
- Adjust V_{GG} for -2.0 V.¹ Repeat steps 6 and 7, entering the data under the columns labeled Gate Voltage = -2.0 V.
- The data in Table 35-2 represent three drain characteristic curves for your JFET. The drain characteristic curve is a graph of V_{DS} versus I_D for a constant gate voltage. Plot the three drain characteristic curves on Plot 35-1. Choose a scale for I_D that allows the largest current observed to fit on the graph. Label each curve with the gate voltage it represents.

¹The gate-source cutoff voltage for the 2N5458 can vary from -1.0 V to -7.0 V. You may find that -2.0 V turns off the transistor. If the transistor is turned off, try testing it with a gate voltage of -0.5 V.

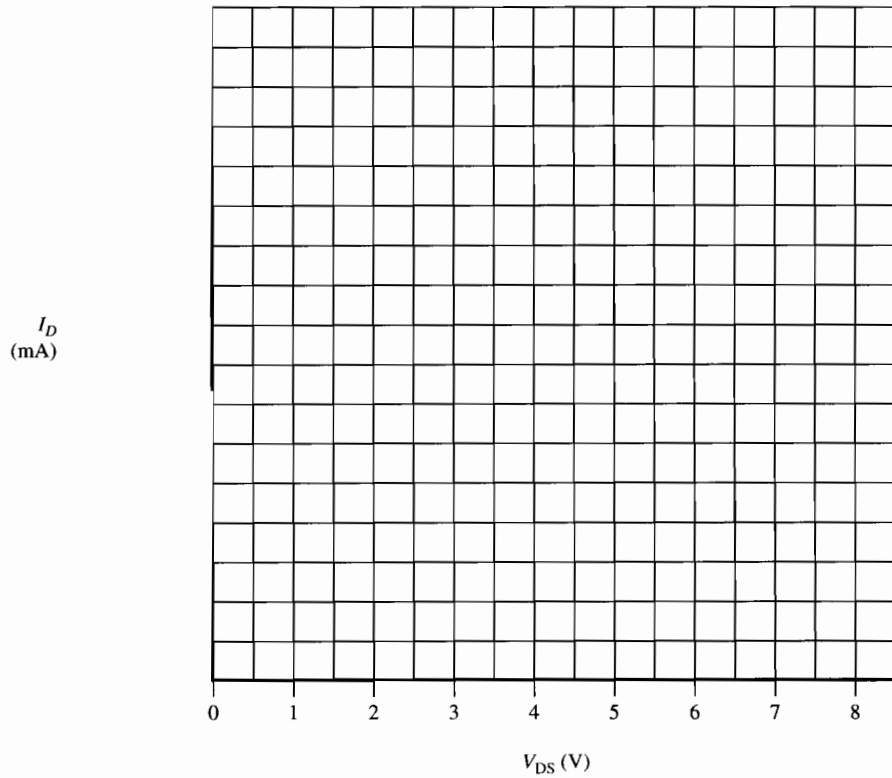

Plot 35-1

10. Determine the approximate transconductance (g_m) of your JFET at $V_{DS} = 6$ V. Do this by observing the change in drain current between two of the characteristic curves at $V_{DS} = 6$ V and dividing it by a change in the gate-source voltage. Note that the change in the gate-source voltage is 1.0 V between each plotted curve. You should be able to find a transconductance that agrees with the specified range for the JFET you are using, typically $1000 \mu\text{S}$ to several thousand μS .

$g_m =$ _____

Conclusion:

Evaluation and Review Questions:

1. (a) Explain how to find I_{DSS} from the characteristic curves of a JFET.

- (b) From your data, what is the I_{DSS} for your JFET?
2. Using the data when the gate voltage is 0, explain how you could use your JFET as a two-terminal current source that gives a current of I_{DSS} .
3. (a) Does the experimental data indicate that the transconductance is a constant at all points?
- (b) From your experimental data, what evidence indicates that a JFET is a nonlinear device?
4. Look up the meaning of pinch-off voltage when $V_{GS} = 0$. Note that the *magnitude* of V_{GS} is equal to the *magnitude* of V_p , so we can use the characteristic curve for $V_{GS} = 0$ to determine V_p . Using the data from this experiment, determine the pinch-off voltage for your JFET.
5. Why should a JFET be operated with only reverse bias on the gate source?

For Further Investigation:


Using the test circuit shown in Figure 35–1, test the effect of varying V_{GS} with V_{DD} held at a constant +10 V. Tabulate a set of data of I_D as a function of V_{GS} . Start with $V_{GS} = 0.0$ V and take data every -5.0 V until there is no appreciable drain current. Then graph the data

on Plot 35-2. This curve is the transconductance curve for your JFET. The data you obtain are nonlinear because the gate-source voltage is proportional to the square root of the drain current. To illustrate this, compute the square root of I_D and plot the square root of the drain current as a function of the gate-source voltage on Plot 35-3.

Table 35-3


V_{GS} (measured)	I_D (measured)	$\sqrt{I_D}$ (computed)
0.0 V		
-0.5 V		
-1.0 V		
-1.5 V		
-2.0 V		
-2.5 V		
-3.0 V		
-3.5 V		
-4.0 V		
-4.5 V		
-5.0 V		

I_D
(mA)

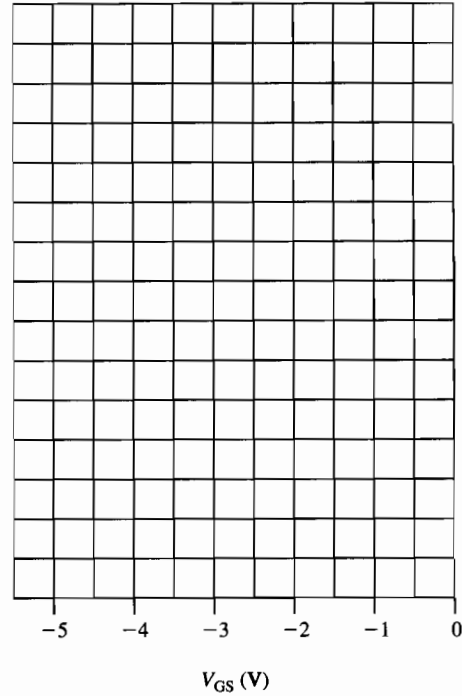

Plot 35-2

$\sqrt{I_D}$

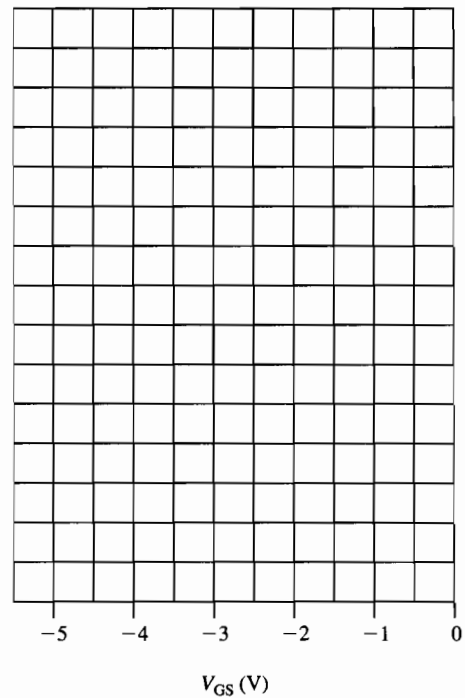

Plot 35-3

36 The SCR

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 18–10 through 18–12

Objectives:

After performing this experiment, you will be able to:

1. Measure the gate trigger voltage and holding current for an SCR.
2. Compare a transistor latch circuit with an SCR.
3. Explain the effect of varying the gate control on the voltage waveforms in an ac SCR circuit.

Summary of Theory:

Thyristors are a class of semiconductor devices consisting of multiple layers of alternating P and N material. They are bistable devices that use either two, three, or four terminals to control either ac or dc. Thyristors are primarily used in power-control and switching applications. A variety of geometry and gate arrangements are available, leading to various types of thyristors such as the diac, triac, and silicon-controlled rectifier (SCR). In this experiment, you will investigate an SCR. It is one of the oldest and most popular thyristor. It is a four-layer device and can be represented as equivalent PNP and NPN transistors, as shown in Figure 36–1.

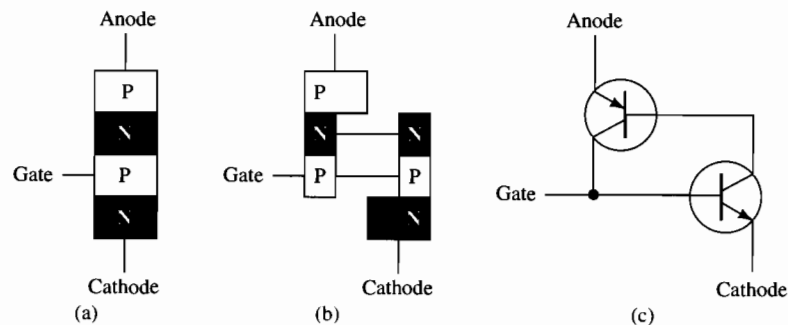


Figure 36–1

The SCR is a thyristor that operates as a latching switch controlled by a sensitive gate. If the anode is negative with respect to the cathode, the SCR is reverse-biased and will be off. When the anode is made more positive than the cathode, the SCR is forward-biased, but without a gate signal, it remains off. The application of a small positive gate pulse causes the SCR to go rapidly into conduction. Once it begins conduction, control is lost by the gate. Conduction ceases only when the anode current is brought below a value called the *holding current*.

SCRs have specific requirements for proper triggering. A number of special thyristors and other solid-state devices, such as the unijunction transistor (UJT), are used for trigger circuits. The primary requirement of any triggering circuit is to provide adequate gate current and voltage at a precise time. The triggering device provides a precise control signal to a

thyristor power device. Applications include dc switching, motor control, electronic ignition, battery chargers, and lamp drivers.

Materials Needed:

Resistors:

- One 160 Ω, two 1.0 kΩ, one 10 kΩ
- One 10 kΩ potentiometer
- One 0.1 μF capacitor
- One LED
- One 2N3904 NPN transistor (or equivalent)
- One 2N3906 PNP transistor (or equivalent)
- One SK3950 SCR (or equivalent)
- One 12.6 V power transformer

For Further Investigation:

- One photocell (Radio Shack 276-116 or equivalent)

Procedure:

1. Measure and record the resistance of the resistors listed in Table 36–1. R_2 is a 10 kΩ variable resistor, so it is not listed.

Table 36–1

Resistor	Listed Value	Measured Value
R_1	1.0 kΩ	
R_3	160 Ω	
R_4	1.0 kΩ	
R_5	10 kΩ	

Table 36–2

	Transistor Latch	SCR
V_{AK} (off state)		
V_{AK} (on state)		
V_{Gate} Trigger		
V_{R4}		
$I_{Holding}$ (min)		

2. Construct the transistor latch shown in Figure 36–2. The purpose of C_1 is to prevent noise from triggering the latch. The switch can be made from a piece of wire. Set R_2 for the maximum resistance and close S_1 . The LED should be off. Measure the voltage across the latch shown as V_{AK} (off state). (V_{AK} refers to the voltage from the anode to cathode.) Enter the measured voltage in Table 36–2 under Transistor Latch.

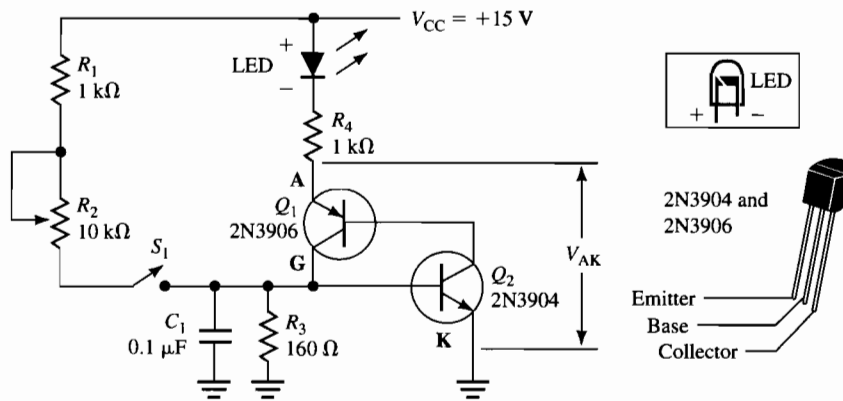


Figure 36-2

3. Slowly decrease the resistance of R_2 until the LED comes on. Measure V_{AK} with the LED on (latch closed). Record this value as V_{AK} (on state) in Table 36-2. Measure the voltage across R_3 . Record this as the gate trigger voltage in Table 36-2.
4. Open S_1 . The LED should stay on because of latching action. Connect a voltmeter across R_4 . Monitor the voltage while *slowly* decreasing V_{CC} . Record the smallest voltage you can obtain across R_4 with the LED on. Then apply Ohm's law using the measured V_{R4} and the measured resistance of R_4 to compute the current through R_4 . This current is the minimum holding current for the latch. Record this as $I_{\text{Holding (min)}}$ in Table 36-2.
5. Replace the transistor latch with an SCR as shown in Figure 36-3. Repeat steps 2, 3, and 4 for the SCR. Enter the data in Table 36-2 under SCR.

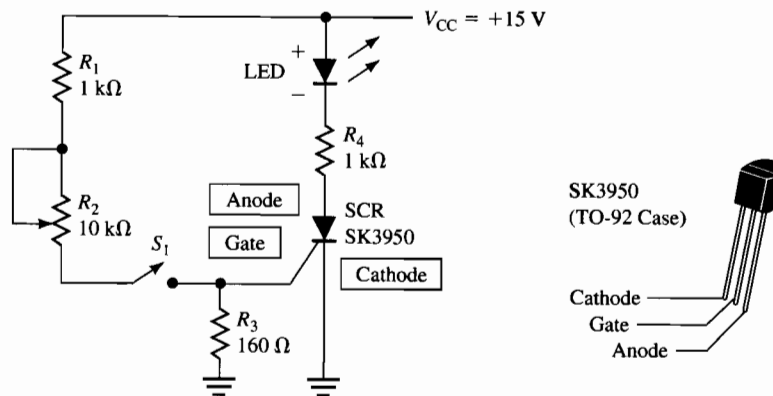


Figure 36-3

6. As you have seen, the only way to turn off an SCR is to drop the conduction to a value below the holding current. A circuit that can do this for dc operation is shown in Figure 36-4. In this circuit, the capacitor is charged to approximately V_{CC} . When S_2 is momentarily pressed, the capacitor is connected in reverse across the SCR, causing the SCR to drop out of conduction. This is called *capacitor commutation*. Add the commutation circuit to the SCR circuit.

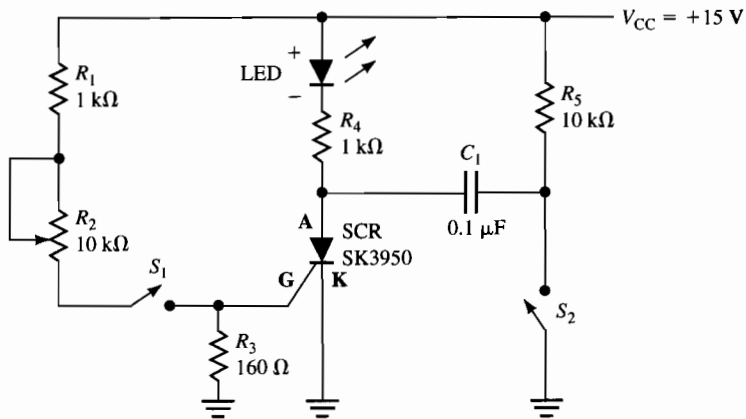


Figure 36-4


7. Test the commutation circuit by *momentarily* closing S_1 and then *momentarily* closing S_2 . Describe your observations.

8. *Do this procedure only under supervision.*

Caution! In this procedure, you are instructed to connect a low-voltage (12.6 V ac) transformer to the ac line. Be certain that you are using a properly fused and grounded transformer that has no exposed primary leads. Do not touch any connection in the circuit. At no time will you make a measurement on the primary side of the transformer. Have your connections checked by your instructor before applying power to the circuit.

A typical application of SCRs is in ac circuits such as motor speed controls. The ac voltage is rectified by the SCR and applied to a dc motor. Control is obtained by triggering the gate during the positive alteration of the ac voltage. The SCR drops out of conduction on each negative half-cycle; therefore, a commutation circuit is unnecessary. Remove the commutation circuit and replace V_{CC} with a 12.6 V_{rms} voltage from a low-voltage power transformer.¹ Observe the voltage waveform across R_4 by connecting one channel of your oscilloscope on each side of R_4 and using the difference function as illustrated in Experiment 16. Compare this waveform with the voltage waveform across the SCR anode to cathode. Vary R_2 and observe the effect on the waveforms. On Plot 36-1, sketch representative waveforms across R_4 and across the SCR. Show the measured voltage on your sketch.

¹A signal generator can be used instead. Set the generator for a 15 V peak signal at 60 Hz.

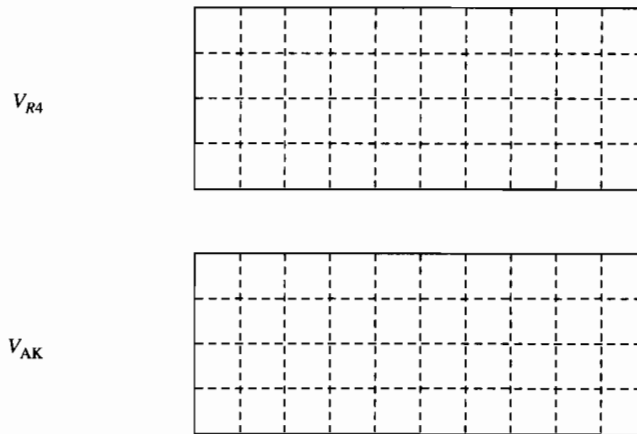

Plot 36-1

Conclusion:

Evaluation and Review Questions:

1. Explain how to turn off a conducting SCR in a dc circuit.

2. To what does commutation in an SCR circuit refer?

3. Explain why a short from V_{CC} to the anode of the SCR in Figure 36-3 could cause the SCR to burn out.

4. What symptom would you expect to see if the SCR in the circuit of Figure 36-4 had an anode-to-cathode short?

5. For the circuit of Figure 36–4, what effect on the voltage waveform measured across R_4 would you expect if the holding current for the SCR were higher?

For Further Investigation:

The trigger control circuit of an SCR can be controlled by a light-sensitive detector such as a photocell. Operate the circuit shown in Figure 36–3 from a sine wave source. Replace R_3 with a photocell (Radio Shack 276-116 or equivalent). Then put R_3 back and replace R_2 with the photocell. Summarize your findings in a laboratory report. There are various resistive sensors on the market for temperature, moisture, and so forth. Can you think of other potential applications for this circuit?

37 The UJT

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 18–10 and 18–11

Objectives:

After performing this experiment, you will be able to:

1. Connect a UJT as a relaxation oscillator.
2. Determine the effect of varying resistance on the waveshape and the output frequency.
3. Show how to trigger an SCR with a UJT.

Summary of Theory:

The unijunction transistor, or UJT, is a 3-terminal device, so named because it contains a single PN junction joined to a silicon bar. The bar of silicon has connections at each end for base leads (base 1 and base 2). The remaining lead, on the other side of the PN junction, is called the emitter. The symbol for a UJT is shown in Figure 37–1(a). The emitter terminal is shown with an arrow drawn at a slant. It points inward to indicate a P-type of emitter and N-type of base material.

The operating principle for a UJT is quite different from that for bipolar or field effect transistors. The base leads can be thought of as connected to the ends of a voltage divider consisting of the two base resistances as shown in Figure 37–1(b). When a dc voltage is applied between the bases, a portion of the voltage appears across the base 1 resistance, as given by the voltage divider rule. This voltage can be written

$$V_k = \eta V_{BB}$$

where V_k = voltage at point k in the equivalent circuit, $\eta = R_{B1}/(R_{B1} + R_{B2})$, the intrinsic standoff ratio, and V_{BB} = voltage between the bases.

If the emitter is brought to a voltage that is approximately one diode drop higher than V_k , emitter current will flow. This occurs at a peak voltage point, illustrated in the emitter characteristic curve shown in Figure 37–2. As a result of this emitter current, the base 1 resistance drops dramatically and the emitter current increases rapidly. This implies a region of negative resistance—that is, once emitter current begins, current will increase even though the input emitter voltage decreases! This negative resistance region is unstable, and the device quickly reaches saturation. Current between the bases is limited only by the external resistors and the interbase resistance.

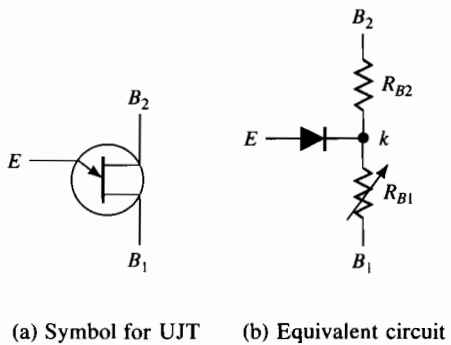


Figure 37-1

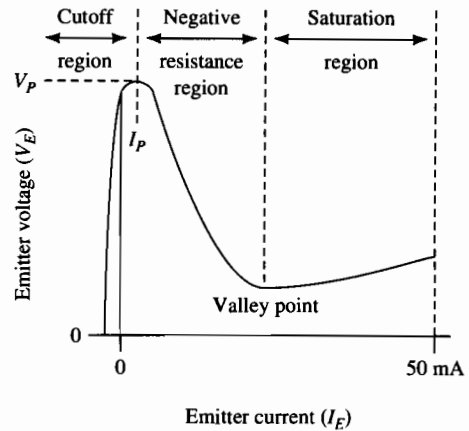


Figure 37-2

Devices that have a negative resistance characteristic are frequently used as relaxation oscillators, an application that will be investigated in this experiment. In addition to its application as an oscillator, the negative resistance characteristic makes a UJT useful as a trigger device for thyristors such as SCRs.

The basic circuit for this experiment is shown in Figure 37-3. When power is applied, the capacitor is uncharged, and the emitter current is approximately zero. The current in between the bases is determined by the interbase resistance and the supply voltage. As the capacitor charges, the junction becomes forward-biased and the emitter-base 1 conductivity increases, turning on the UJT rapidly. The capacitor supplies the current to maintain conduction. Eventually, the capacitor discharges through the PN junction, and the emitter voltage is insufficient to maintain forward bias. The cycle then repeats. The concept is extended in the section For Further Investigation by using the oscillator to drive an SCR.

Materials Needed:

One 2N2646 UJT (or equivalent)

Resistors:

One 47 Ω , one 220 Ω , one 1.0 k Ω , one 15 k Ω

One 100 k Ω potentiometer

One 0.1 μ F capacitor

For Further Investigation:

One transformer with 12.6 V ac output, one 5 V zener, one SK3950 SCR, one #44 bulb

Procedure:

1. Measure and record the resistance of the resistors listed in Table 37-1.

Table 37-1

Resistor	Listed Value	Measured Value
R_1	47 Ω	
R_2	220 Ω	
R_3	15 k Ω	


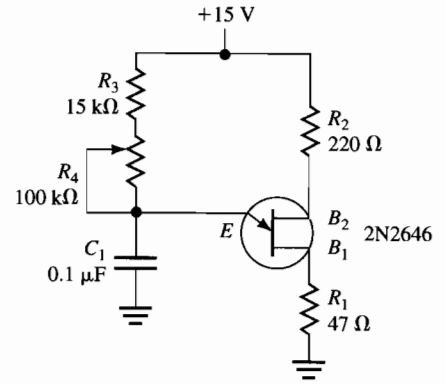


Figure 37-3

2. Construct the circuit shown in Figure 37-3. Set R_4 for zero resistance. Observe the waveforms at the emitter, base 1 and base 2. Sketch the observed waveforms in the proper time relationship on Plot 37-1. Label the scales with the time and amplitude.

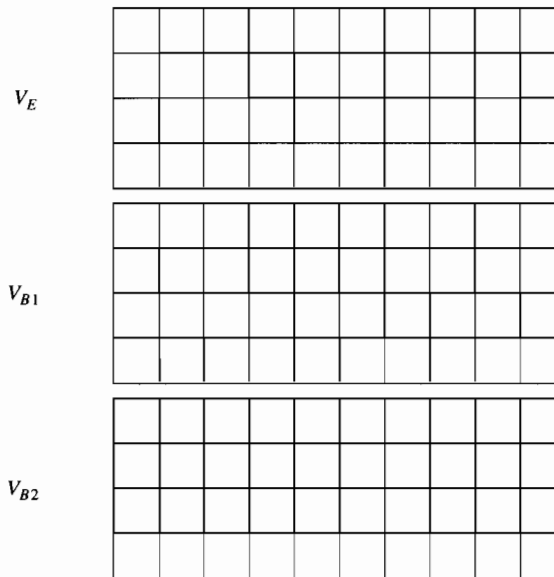


Plot 37-1

3. Set the potentiometer for each resistance listed in Table 37-2. You will need to remove power from the circuit and disconnect one end of the potentiometer to do this. Add the measured value of R_3 to determine the total resistance at each setting. Then measure the frequency at each resistance setting and record it in Table 37-2.

Table 37-2

Resistance Setting of R_4	Total Resistance	Measured Frequency
5 k Ω		
25 k Ω		
45 k Ω		
65 k Ω		
85 k Ω		

Frequency

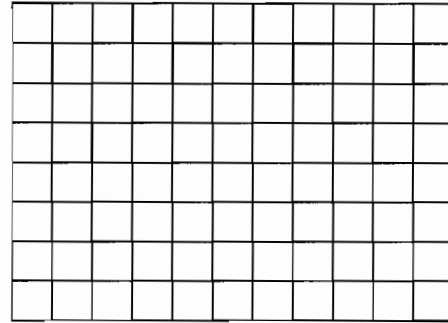

Total resistance

Plot 37-2

4. Graph the frequency as a function of the total resistance in Plot 37-2. What conclusion can you draw from these data?
5. Describe the effect on the waveform at the emitter terminal as the potentiometer is varied.
6. Try reducing the power supply voltage while you observe the waveform at the emitter. Does this affect the frequency? The amplitude?

Conclusion:

Evaluation and Review Questions:

1. Use one (or more) of your measured values from the experiment to determine the intrinsic standoff ratio (discussed in the text). It is given by the equation

$$\eta = 1 - e^{-T/RC}$$

where η = intrinsic standoff ratio, e = the base of natural logarithms which is 2.718, T = period of the signal(s), R = total resistance between V_{CC} and the emitter (Ω), and C = capacitance of C_1 (F).

Intrinsic standoff ratio = _____

2. Compute the percent difference between your answer and the manufacturer's specified typical value. For the 2N2646, the typical value is 0.69.
3. Explain what conditions must be satisfied before the UJT can turn on.
4. Assume a UJT has an intrinsic standoff ratio of 0.6 and V_{BB} is 10 V. What value of V_E will just turn on the UJT?
5. In the circuit in Figure 37-3, what would you expect if:
 - (a) R_2 were shorted?
 - (b) The capacitor were ten times larger?
 - (c) The UJT were to have a higher intrinsic standoff ratio than the one used?

For Further Investigation:

Caution! In this investigation, you are instructed to connect a low voltage (12.6 V ac) transformer to the ac line. Be certain that you are using a properly fused and grounded transformer that has no exposed primary leads. Do not touch any connection in the circuit. At no time will you make a measurement on the primary side of the transformer. Have your connections checked by your instructor before applying power to the circuit.

One of the important applications of UJT's is as a trigger device for an SCR. Unlike the trigger circuit you investigated in the last experiment, a UJT will enable you to trigger an SCR along either the front or back of the positive half-cycle of the sine wave. The UJT oscillator constructed in this experiment can be used to trigger an SCR, as shown in Figure 37-4. The purpose of the zener diode is to provide a relatively constant charging voltage during the positive half cycle. The oscillator then triggers the SCR at a time determined by the RC time constant.

Construct the circuit and observe the waveform across the bulb as you vary the potentiometer. (Use the two-channel difference technique described in Experiment 16 to observe the waveform across any ungrounded component.) Also observe the waveforms across the zener diode and at the emitter terminal of the UJT. Can you explain your observations? Summarize your findings in a short laboratory report.

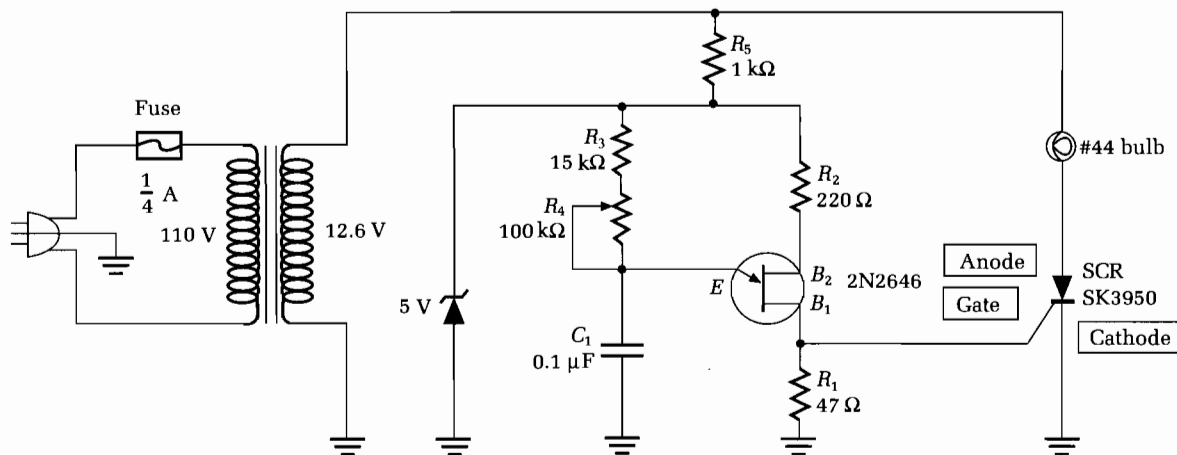


Figure 37-4

Application Assignment 18

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 18, Section 18–14: Application Assignment

Step 1 Develop a schematic of the circuit from the PC board layout and identify the type of biasing. Draw the schematic in the space provided.

Step 2 Analyze the circuit in the controlled range. With $V_{CC} = +15\text{ V}$, determine the output for each temperature listed in Table AA–18–1.

Table AA–18–1

Temperature	Thermistor Resistance	V_{out} (computed)
50° C	2.75 k Ω	
49° C	3.10 k Ω	
51° C	2.50 k Ω	

Step 3 Analyze the circuit in the range from 30°C to 110°C. With $V_{CC} = +15\text{ V}$, determine the output for each temperature listed in Table AA–18–2. You will need to determine the thermistor resistance from the graph.

Table AA–18–2

Temperature	Thermistor Resistance	V_{out} (computed)
30° C		
50° C	2.75 k Ω	
70° C		
90° C		
110° C		

Step 4

Troubleshoot the circuit. Give the likely problem(s) for each symptom. Describe how you will isolate the problem.

1. V_{CE} is approximately 0.1V and V_C is 3.8V.

2. Collector of Q_1 remains at approximately +15 V.

Related Experiment:

Materials Needed:

One small-signal NPN transistor: 2N3904 (or equivalent)

Resistors:

One 330 Ω , one 1.0 k Ω , one 22.0 k Ω

One 10 k Ω potentiometer

Discussion:

Assume you needed to test the circuit given in the text application assignment. Temperature changes can be simulated by replacing the thermistor with a 10 k Ω potentiometer. Connect the circuit on a breadboard and set the potentiometer to each resistance listed in Tables AA-18-1 and AA-18-2. Add a column to each table for the measured output voltage and record your data. Write a conclusion summarizing your observations.

Checkup 18

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 18, and Buchla, Experiments 34 through 37

- To bias a PNP transistor, the polarity of the bias voltage with respect to the emitter is:
(a) negative on both the base and collector
(b) negative on the base, positive on the collector
(c) positive on both the base and collector
(d) positive on the base, negative on the collector
- When a bipolar transistor is in saturation, the voltage between the collector and emitter is closest to:
(a) 0.1 V (b) 0.7 V (c) 15 V (d) equal to the supply voltage
- In order to saturate a bipolar transistor, the base current must be:
(a) 0 (b) 0.1 mA (c) greater than I_C (d) greater than I_C divided by β
- The β_{dc} of a bipolar transistor is found by dividing the collector current by the:
(a) emitter current (b) collector voltage
(c) base current (d) emitter voltage
- A common-collector amplifier does not have:
(a) voltage gain (b) current gain (c) power gain (d) an emitter resistor
- The transconductance of a JFET is found by dividing a change in drain current by a:
(a) change in source voltage (b) change in gate voltage
(c) change in drain voltage (d) change in gate current
- Assume an N-channel JFET is operated above pinch-off with V_{GS} equal to zero volts. The drain current is:
(a) zero (b) equal to the supply voltage divided by R_D
(c) I_{DSS} (d) not able to be determined
- A device that can be operated with either a negative or positive gate-source voltage is:
(a) an N-channel JFET (b) a P-channel JFET
(c) an E MOSFET (d) a DE MOSFET
- A device that has a negative resistance characteristic is:
(a) a zener diode (b) a UJT
(c) an SCR (d) a diac

10. An SCR is normally triggered:
- (a) when a positive gate voltage is applied (b) when a negative gate voltage is applied
- (c) by exceeding the breakover voltage (d) whenever the anode is positive
11. Assume the ac collector voltage of a common-emitter amplifier shows a sinusoidal waveform that is clipped on top. Is this saturation clipping or cutoff clipping? Explain your answer.
12. For the circuit shown in Figure C-18-1, determine the dc voltage at the:
- (a) base (b) emitter (c) collector
13. Assume that the symptoms of troubles listed below are present in the circuit in Figure C-18-1. What are the possible problems with the circuit?

Symptom

Possible Problems

- (a) emitter = +5.7 V, collector = +5.8 V: _____
- (b) emitter = 0 V, collector = +15 V: _____

14. For the circuit shown in Figure C-18-2, assume that $V_S = +1.4$ V.
- (a) What is the drain voltage? (b) What is the drain-source voltage?
- (c) What type of bias is this?

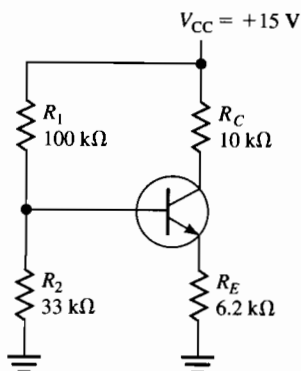


Figure C-18-1

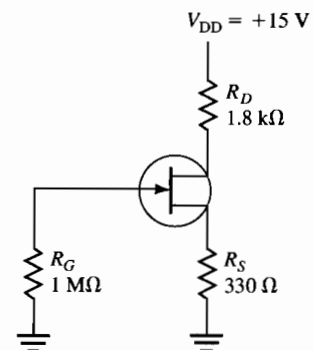


Figure C-18-2

38 The Common-Emitter Amplifier

Name _____
Date _____
Class _____

Reading:

Floyd, Section 19-1

Objectives:

After performing this experiment, you will be able to:

1. Compute the dc parameters, r_e , and the voltage gain of a common-emitter amplifier with voltage divider bias.
2. Build a common-emitter amplifier and measure the dc and ac parameters.
3. Predict the result of faults in a common-emitter amplifier.

Summary of Theory:

In a common-emitter (CE) amplifier, the input signal is applied between the base and emitter, and the output signal is developed between the collector and emitter. The transistor's *emitter* is common to both the input and output circuit; hence, the term common emitter. Do not confuse the term common emitter with grounded emitter. The emitter terminal of a CE amplifier may or may not be at circuit ground.

To make any transistor circuit amplify ac signals, the base-emitter junction must be forward-biased, and the base-collector junction must be reverse-biased. The purpose of bias circuits is to establish and maintain the proper dc operating conditions for the transistor. The bias circuit must provide these conditions for wide variations between transistors that may occur as a result of mass production.

There are several ways to apply dc bias. The simplest method, called base bias or fixed bias, is frequently unsatisfactory due to manufacturing variations between transistors and sensitivity to temperature changes. Base bias is recognized by a single resistor connected from V_{CC} to the transistor base. A much more widely used bias circuit is called voltage divider bias. Voltage divider bias is not as sensitive to transistor variations and temperature changes. Voltage divider bias is shown in Figure 38-1(a).

There are many variations in transistor amplifiers. The purpose of the example shown is to develop a *method for analysis* rather than a set of equations. The equations for each configuration of amplifier are necessarily different, depending on the circuit. You should not attempt to memorize a set of equations for analysis, but rather observe the application of analysis methods.

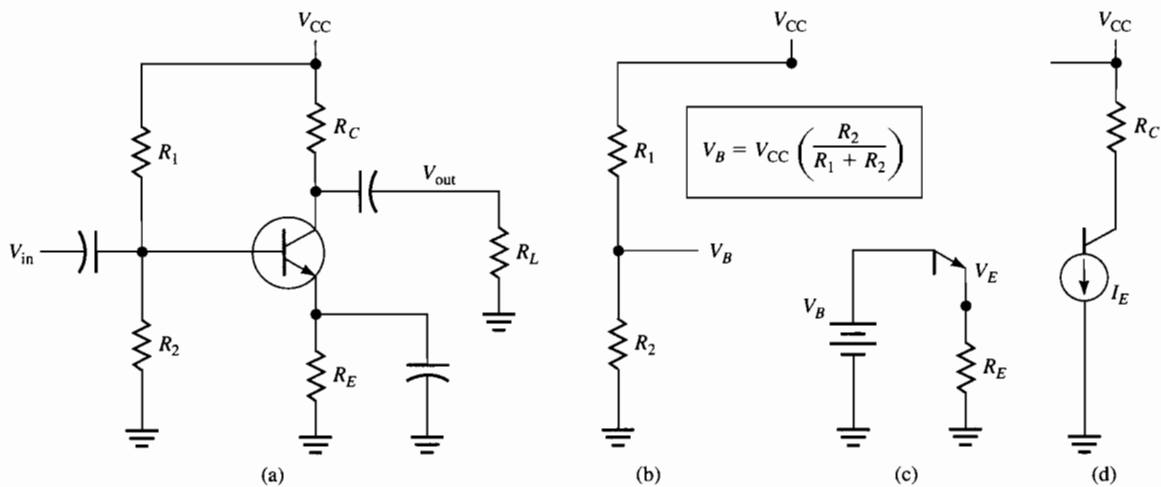


Figure 38–1 Steps in solving the dc parameters in CE amplifier with voltage divider bias. Note that the equation given in (b) assumes a “stiff” divider—that is, it ignores the small loading effect of the base current on the divider. As long as the base current is small compared to the divider current, this is satisfactory; otherwise use equation 18–7 in the text.

To analyze any amplifier, start with the dc parameters. The steps to solve for the dc parameters for the CE amplifier with voltage divider bias illustrated in Figure 38–1(a) are:

1. Mentally remove capacitors from the circuit since they appear open to dc. This causes the load resistor, R_L , to be removed. Solve for the base voltage, V_B , by applying the voltage divider to rule R_1 and R_2 , as illustrated in Figure 38–1(b).
2. Subtract the 0.7 V forward-bias drop across the base-emitter diode from V_B to obtain the emitter voltage, V_E , as illustrated in Figure 38–1(c).
3. The dc current in the emitter circuit is found by applying Ohm’s law to R_E . The emitter current, I_E , is approximately equal to the collector current, I_C . The transistor appears to be a current source of approximately I_E into the collector circuit, as shown in Figure 38–1(d).

The ac parameters for the amplifier can now be analyzed. The circuit and the ac equivalent circuit are shown in Figure 38–2. The capacitors appear to be an ac short. For this reason, the ac equivalent circuit does not contain R_E . Using the superposition theorem, V_{CC} is replaced with a short, placing it at ac ground. The analysis steps are:

1. Replace all capacitors with a short and place V_{CC} at ac ground. Compute the ac resistance of the emitter, r_e , from the equation:

$$r_e = \frac{25 \text{ mV}}{I_E}$$

2. Compute the amplifier’s voltage gain. Voltage gain is the ratio of the output voltage divided by the input voltage. The input voltage is across the ac emitter resistance to ground which, in this case, is r_e . The output voltage is taken across the ac resistance from collector to ground. Looking from the transistor’s collector, R_L appears to be in parallel with R_C . For the circuit in Figure 38–2(b), the output voltage divided by the input voltage can be written:

$$A_v = \frac{V_{out}}{V_{in}} = \frac{I_c (R_C \parallel R_L)}{I_e r_e} \cong \frac{R_C \parallel R_L}{r_e}$$

3. Compute the total input resistance seen by the ac signal:

$$R_{in(T)} = R_1 \parallel R_2 \parallel \beta_{ac} r_e$$

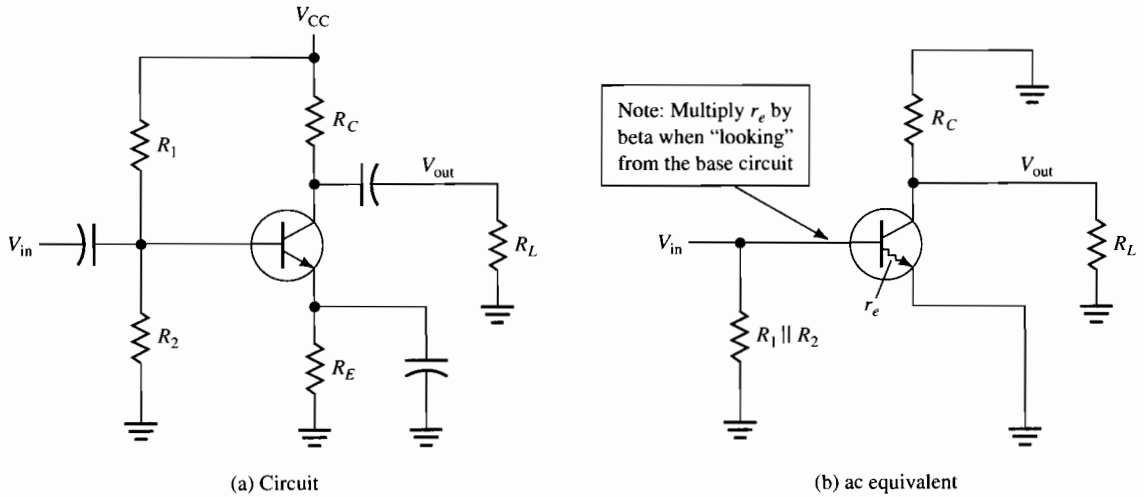


Figure 38-2

Materials Needed:

Resistors:

One 100 Ω, one 2.2 kΩ, one 6.8 kΩ, three 10 kΩ, one 47 kΩ

Capacitors:

Two 1 μF, one 100 μF

One 10 kΩ potentiometer

One 2N3904 NPN transistor (or equivalent)

Procedure:

1. Measure and record the resistance of the resistors listed in Table 38-1.

Table 38-1

Resistor	Listed Value	Measured Value
R_1	47 kΩ	
R_2	10 kΩ	
R_3	10 kΩ	
R_4	100 Ω	
R_E	2.2 kΩ	
R_C	6.8 kΩ	
R_L	10 kΩ	

Table 38-2

DC Parameter	Computed Value	Measured Value
V_B		
V_E		
I_E		
V_C		
V_{CE}		

2. Using measured resistances, compute the dc parameters listed in Table 38–2 for the CE amplifier shown in Figure 38–3. This circuit, like most voltage divider bias circuits, uses a “stiff” divider; therefore, the equation shown in the box in Figure 38–1 is satisfactory for finding the base voltage. Compute the base voltage, V_B , emitter voltage, V_E , and emitter current, I_E , as described in the Summary of Theory. The emitter current is assumed to be the same as the collector current. Use this idea and Ohm’s law to find the voltage drop across the collector resistor. V_C can then be found by subtracting this voltage drop from V_{CC} . V_{CE} is the difference between V_C and V_E .

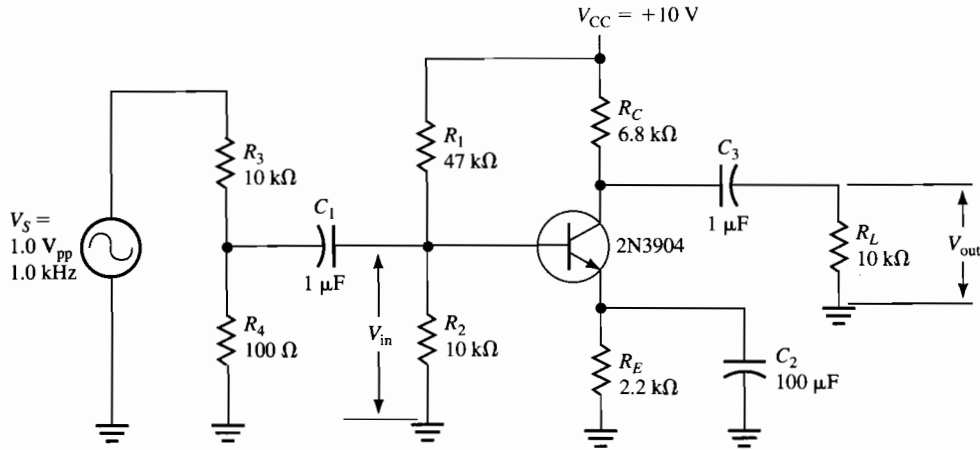


Figure 38–3

3. Construct the amplifier shown in Figure 38–3. The signal generator should be turned off. Measure and record the dc voltages listed in Table 38–2. Your measured and computed values should agree within 10%.
4. Compute the ac parameters listed in Table 38–3 using the method given in the Summary of Theory. The ac base voltage, V_b , represents the signal input to the amplifier, V_{in} . It is listed as 10 mV_{pp} based on the input voltage divider consisting of R_3 and R_4 . Multiply the input signal by the computed voltage gain to obtain the output signal. The ac collector voltage, V_c , represents the output signal, V_{out} . If you do not know β_{ac} for the input resistance calculation, assume a value of 100.
5. Turn on the signal generator and adjust V_S for a 1.0 V_{pp} signal at 1.0 kHz. The ac input at the base, V_b , is already listed in Table 38–3 as 10 mV_{pp} . Measure the ac collector signal, V_c , and record it in Table 38–3. Use the ac base voltage and measured collector voltage to obtain the measured voltage gain. Record the measured voltage gain in Table 38–3.

Table 38–3

AC Parameter	Computed Value	Measured Value
$V_b = V_{in}$	10 mV _{pp}	10 mV* _{pp}
r_e		
A_v		
$V_c = V_{out}$		
$R_{in(T)}$		

*Based on setting V_S to 1.0 V_{pp}

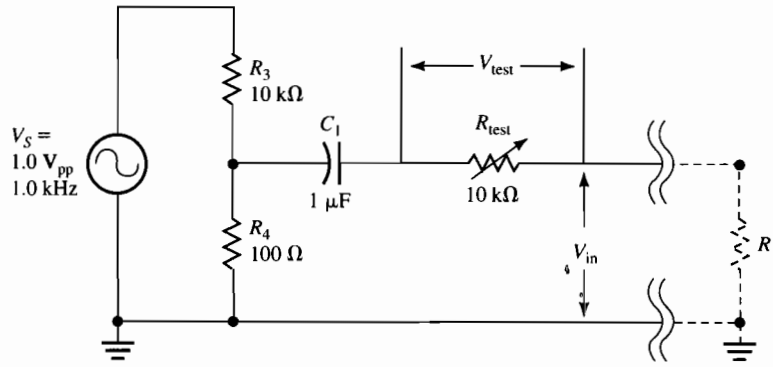


Figure 38–4 Measurement of $R_{in(T)}$

- The measurement of $R_{in(T)}$ must be done indirectly since it represents an ac resistance. The output signal (V_{out}) is monitored and noted. A variable test resistor (R_{test}) is then inserted in series with the source, as shown in Figure 38–4. The resistance of R_{test} is increased until V_{out} drops to one-half the value noted prior to inserting R_{test} . This means the voltage drop across R_{test} is equal to the voltage drop across $R_{in(T)}$; hence, the resistances are equal. R_{test} can then be removed and measured with an ohmmeter. Using this method, measure $R_{in(T)}$ and record the result in Table 38–3.
- Restore the circuit to that of Figure 38–3. With a two-channel oscilloscope, compare the input and output waveforms. What is the phase relationship between V_{in} and V_{out} ?
- Remove C_2 from the circuit. Measure the ac signal voltage at the transistor's base, emitter, and collector. Measure the voltage gain of the amplifier. What conclusion can you make about the amplifier's performance with C_2 open?
- Replace C_2 and remove R_L . Again measure the ac signal voltage at the transistor's base, emitter, and collector. Measure the voltage gain of the amplifier. What conclusion can you make about the amplifier's performance with R_L open?

10. Replace R_L and open R_E . Measure the dc voltages at the base, emitter, and collector. Is the transistor cut off or saturated? (Saturation is *maximum* current flow in the transistor; cutoff is *no* current flow in the transistor.) Explain your answer.

11. Replace R_E and open R_2 . Measure the dc voltages at the base, emitter, and collector. Is the transistor cut off or saturated? Explain your answer.

Conclusion:

Evaluation and Review Questions:

1. When C_2 is open, you found that the gain is affected. Explain.

2. In step 6, you were instructed to measure the input resistance while monitoring the output voltage. Why is the procedure better than monitoring the base voltage?

3. Assume the amplifier shown in Figure 38–3 has +1.8 V dc measured on the base, 1.1 V dc measured on the emitter, and +1.1 V dc measured on the collector.
 - (a) Is this normal?

 - (b) If not, what is the most likely cause of the problem?



39 The Common-Collector Amplifier

Name _____
Date _____
Class _____

Reading:

Floyd, Section 19-2

Objectives:

After performing this experiment, you will be able to:

1. Compute the dc and ac parameters for a common-collector amplifier with voltage divider bias.
2. Build a common-collector amplifier and measure the dc and ac parameters.
3. Predict the effect of faults in a common-collector amplifier.

Summary of Theory:

The common-collector (CC) amplifier (also called the *emitter-follower*) has the input signal applied to the base and the output signal is taken from the emitter as shown in Figure 39-1(a). The ac output voltage almost perfectly duplicates the input voltage waveform. Although this means the voltage gain is approximately 1, the current gain is not; hence, the emitter-follower can deliver increased signal power to a load. The CC amplifier is characterized by a high input impedance and a low output impedance. This is the most important characteristic of the emitter-follower.

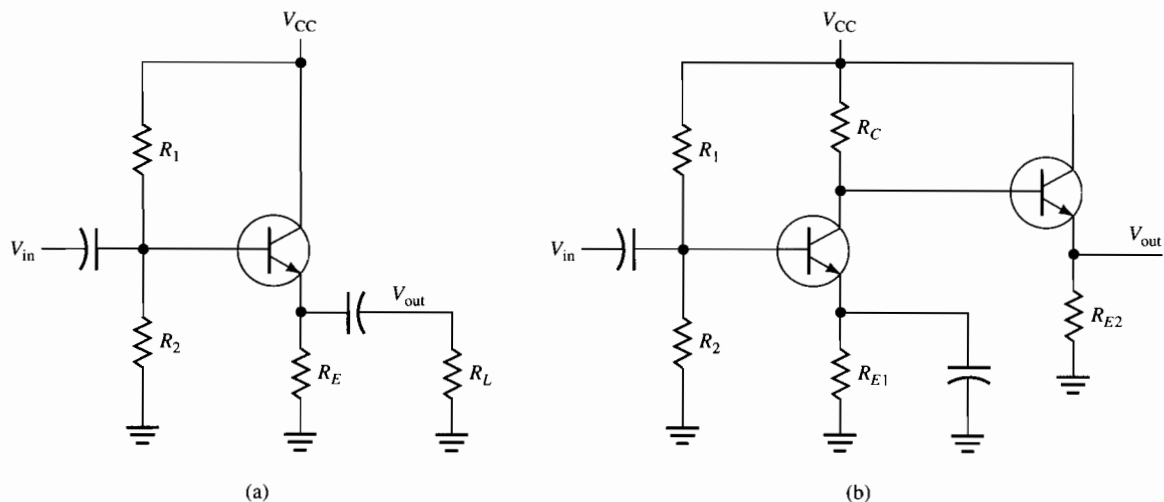


Figure 39-1

Voltage divider bias can be used as illustrated in Figure 39-1(a). Frequently, however, a CC amplifier is used immediately following a voltage amplifier, and bias may be obtained through a dc path connected to the previous stage, as illustrated in Figure 39-1(b). This technique is common in power amplifiers with push-pull output stages (Experiment 41) but cannot be used if the emitter-follower is capacitively coupled.

The procedure for finding the dc parameters with voltage divider bias is similar to the procedure described in Experiment 38 for the common-emitter amplifier. The steps for the circuit illustrated in Figure 39–1(a) are:

1. Mentally remove capacitors from the circuit since they appear open to dc. This causes the load resistor, R_L , to be removed. Solve for the base voltage, V_B , by applying the voltage divider rule to R_1 and R_2 .¹
2. Subtract the 0.7 V forward-bias drop across the base-emitter diode from V_B to obtain the emitter voltage, V_E .
3. The dc current in the emitter circuit is found by applying Ohm's law to R_E . The collector current is nearly equal to the emitter current, and the collector voltage is equal to V_{CC} .

The ac parameters for the amplifier can now be analyzed. The equivalent ac circuit is illustrated in Figure 39–2. The analysis steps are:

1. Mentally replace all capacitors with a short. Compute the ac resistance of the emitter, r_e , from the equation:

$$r_e = \frac{25 \text{ mV}}{I_E}$$

2. Compute the amplifier's voltage gain. Voltage gain is the ratio of the output voltage divided by the input voltage. The input voltage is applied across r_e and the ac emitter resistance, whereas the output voltage is taken only across the ac emitter resistance. Thus, the voltage gain is based on the voltage divider equation:

$$A_v = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{I_e R_E \parallel R_L}{I_e (r_e + R_E \parallel R_L)} = \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L}$$

3. Compute the total input resistance seen by the ac signal:

$$R_{\text{in}(T)} = R_1 \parallel R_2 \parallel \{\beta_{ac}(r_e + R_E \parallel R_L)\}$$

4. Compute the amplifier's power gain. In this case, we are interested only in the power delivered to the load resistor. The output power is V_{out}^2/R_L . The input power is $V_{\text{in}}^2/R_{\text{in}(T)}$. Since the voltage gain is approximately 1, the power gain can be expressed as a ratio of $R_{\text{in}(T)}$ to R_L :

¹This procedure is satisfactory for "stiff" dividers such as the one in this experiment. (See discussion with Figure 38–1.)

$$A_p = \frac{\left(\frac{V_{out}^2}{R_L}\right)}{\left(\frac{V_{in}^2}{R_{in(T)}}\right)} = A_v^2 \left(\frac{R_{in(T)}}{R_L}\right) = \frac{R_{in(T)}}{R_L}$$

It is emphasized that the previous equations were developed for a particular configuration of the emitter-follower circuit; that is, one with “stiff” voltage divider bias and a separate load resistor. The formulas are valid only for the circuits for which they were derived. You should *not* assume that these equations are valid for other configurations.

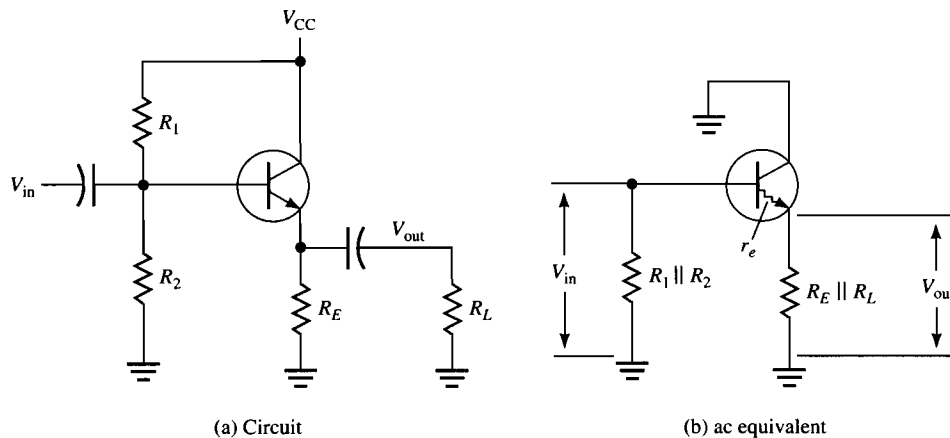


Figure 39-2

Materials Needed:

Resistors:

Two 1.0 kΩ, one 10 kΩ, one 33 kΩ

Capacitors:

One 1.0 μF, one 10 μF

One 10 kΩ variable resistor

One 2N3904 NPN transistor (or equivalent)

For Further Investigation:

Materials from Experiment 38

Procedure:

1. Measure and record the resistance of the resistors listed in Table 39-1.

Table 39-1

Resistor	Listed Value	Measured Value
R_1	10 k Ω	
R_2	33 k Ω	
R_E	1.0 k Ω	
R_L	1.0 k Ω	

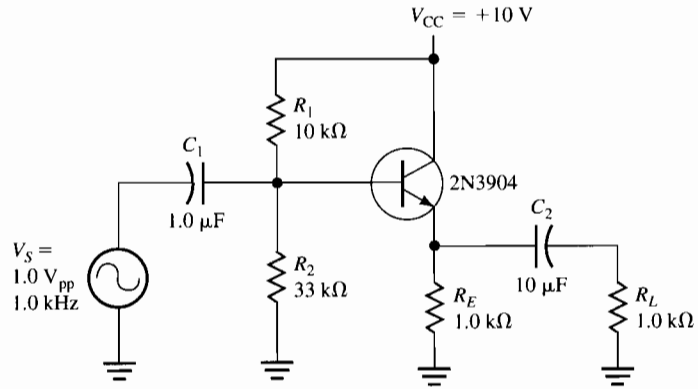


Figure 39-3

2. Compute the dc parameters listed in Table 39-2 for the emitter-follower amplifier shown in Figure 39-3. Compute V_{CE} by subtracting V_E from V_{CC} . Enter your computed values in Table 39-2.

Table 39-2

DC Parameter	Computed Value	Measured Value
V_B		
V_E		
I_E		
V_{CE}		

Table 39-3

AC Parameter	Computed Value	Measured Value
V_b	1.0 V _{pp}	
V_e		
r_e		
A_v		
$R_{in(T)}$		
A_p		

3. Construct the amplifier shown in Figure 39-3. The signal generator should be turned off. Measure and record the dc voltages listed in Table 39-2. Your measured and computed values should agree within 10%.
4. Compute the ac parameters listed in Table 39-3. Assume V_b is the same as the source voltage, V_S . Use the procedure outlined in the Summary of Theory to compute the remaining values.
5. Turn on the signal generator and set V_S for 1.0 V_{pp} at 1.0 kHz. Use the oscilloscope to set the proper voltage and check the frequency. Measure the ac signal voltage at the transistor's emitter, V_{out} , and determine the voltage gain, A_v . Measure $R_{in(T)}$ using the method employed for the CE amplifier. (See Experiment 38, step 6.) Use the measured $R_{in(T)}$ and R_L to determine the measured power gain as described in the Summary of Theory.

6. Use a two-channel oscilloscope, compare the input and output waveforms. What is the phase relationship between V_{in} and V_{out} ?
7. Table 39–4 lists some possible troubles with the CC amplifier. For each trouble listed, predict the effect on the dc voltages. Then insert the trouble into the circuit and test your prediction. Insert the open collector and open emitter troubles by removing the transistor lead and measuring the voltages at the circuit. For each fault, describe the effect on the ac output waveform (clipped, no output, etc.).

Table 39–4

Trouble	DC Predictions			DC Measurements			Effect of Trouble on V_{out}
	V_B	V_E	V_{CE}	V_B	V_E	V_{CE}	
R_1 open							
R_2 open							
R_1 shorted							
R_E open							
Open collector							
Open emitter							

8. Replace R_L with a 10 k Ω variable resistor set to 1.0 k Ω . Connect an oscilloscope probe to the emitter. Raise the signal amplitude until you just begin to observe clipping. If the negative peaks are clipped, this is called *cutoff* clipping because the transistor is turned off. If the positive peaks are clipped, this is called *saturation* clipping because the transistor is fully conducting. What types of clipping is first observed?
9. Vary R_L while observing the output waveform. Describe your observations.

10. Test the effect of V_{CC} on the clipping level by varying the power supply voltage. Describe your observations.

Conclusion:

Evaluation and Review Questions:

1. Compare the input resistance of the common-collector amplifier in this experiment with the common-emitter amplifier in Experiment 38. What is the major factor contributing to their differences?
2. Compare the phase you observed between the input and output voltage for the common-collector and common-emitter configurations.
3. In step 9, you observed the effect of clipping as R_L was varied. What type of clipping occurs when R_L is made very small?
4. What effect does an increase in V_{CC} have on:
 - (a) saturation clipping

(b) cutoff clipping

5. The emitter-follower can be used to drive a low-impedance load such as a loudspeaker. What characteristic of the emitter-follower makes this effective?

6. Assume that the circuit in Figure 39–3 had a shorted capacitor, C_2 . What effect would this have on the dc emitter voltage, V_E ?

For Further Investigation:

The common-collector circuit can be biased from the collector of a common-emitter circuit as illustrated in Figure 39–1(b). Construct the circuit shown using the common-emitter amplifier from Experiment 38 by removing the load resistor and the coupling capacitor. Compute and measure the dc and ac parameters for the circuit. How does the addition of the common-collector amplifier affect the overall gain? Summarize your results in a laboratory report.

40 FET Amplifiers

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 19–4 and 19–5

Objectives:

After performing this experiment, you will be able to:

1. Construct a two-stage bifet amplifier consisting of a JFET and a bipolar amplifier.
2. Predict and measure performance characteristics of the amplifier constructed in objective 1.

Summary of Theory:

Field-effect transistors are used in common-source, common-gate, and common-drain (source-follower) configurations similar to bipolar common-emitter, common-base, and emitter-follower amplifiers. The major advantage of FETs over bipolar transistors is their extremely high input impedance.

FETs are available as either JFETs or MOSFETs (see discussion in Experiment 35). Bias circuits depend on the type of FET and the application. One common bias circuit that is tested in this experiment is *self-bias*. Self-bias is used for JFET and DE MOSFETs but is sensitive to parameter changes between FETs, a common manufacturing problem. Figure 40–1(a) illustrates a self-biased N-channel JFET. The extremely high input resistance of the JFET causes virtually no current to be drawn by the gate circuit. This allows a very high gate resistor to be used and still maintains V_G near ground. The required negative bias is developed across the source resistor, R_S .

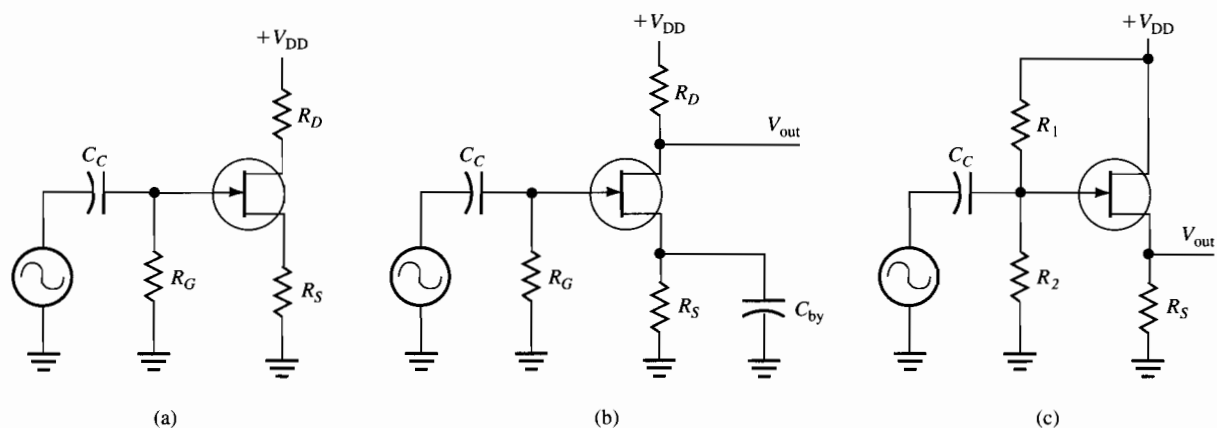


Figure 40–1

The most common circuit configurations, which take advantage of the FETs extremely high input impedance, are shown in Figure 40–1(b) and (c). The circuit in Figure 40–1(b) is a common-source with self-bias. The circuit in Figure 40–1(c) illustrates a common-drain configuration using a combination of self-bias and voltage divider bias, resulting in very stable bias.

JFETs have a nonlinear transfer characteristic, as you found in Experiment 35. A change in gate voltage does not produce a linear change in drain current unless the change is small. The analysis of a JFET amplifier is further complicated by parameter variations between transistors as well as temperature sensitivity. The accurate computation of gain, for example, is dependent on knowing the transconductance, g_m , of the transistor. This value can have a spread of a factor of 5 between transistors of the same type. Bipolar transistors, which are more predictable and have higher gain, are often used in combination with FETs. The result, called a *bifet* amplifier, contains the most desirable characteristics of each type of transistor.

Materials Needed:

Resistors:

One of each: 220 Ω , 1.0 k Ω , 2.7 k Ω , 4.7 k Ω , 10 k Ω , 22 k Ω , 100 k Ω , 1.0 M Ω

Capacitors:

One of each: 0.1 μF , 10 μF , 100 μF

Transistors:

One 2N5458 N-channel JFET, one 2N3906 PNP (or equivalent)

For Further Investigation:

One 2N3904 NPN transistor (or equivalent)

Procedure:

1. Measure and record the resistance of the resistors listed in Table 40–1.
2. Construct the common-source amplifier shown in Figure 40–2. Set the signal generator for a 300 mV_{pp} sine wave at 1.0 kHz. Measure the amplitude and frequency with your oscilloscope.

Table 40–1

Resistor	Listed Value	Measured Value
R_S	2.7 k Ω	
R_D	4.7 k Ω	
R_G	1 M Ω	
R_{L1}	10 k Ω	
R_1	22 k Ω	
R_2	100 k Ω	
R_{E1}	1.0 k Ω	
R_{E2}	220 Ω	

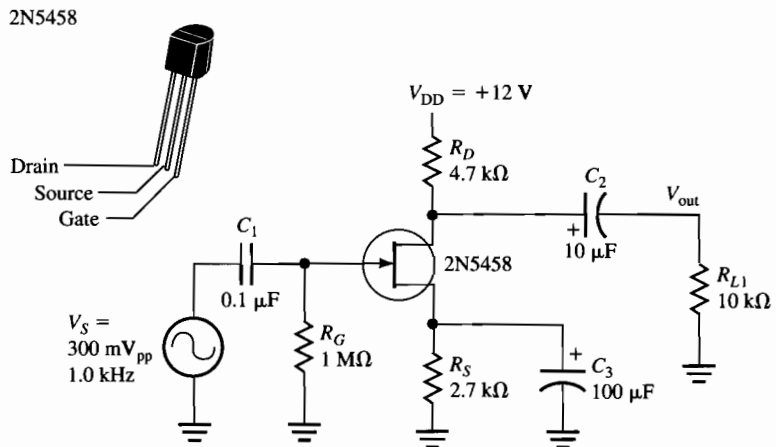


Figure 40–2

3. Measure the dc voltage at the drain, source, and gate. Use the source voltage and source resistance to compute I_D . Enter the data in Table 40–2 in the row labeled Common-Source Amplifier. Compare the input and output ac voltage by viewing V_S

and V_{out} simultaneously on a two-channel oscilloscope. Measure the voltage gain and compare the phase of the input and output signal.

Table 40–2

	DC Parameters				AC Parameters	
	V_G	V_S	V_D	I_D	A_v	Phase Reversal?
Common-Source Amplifier						
Common-Drain Amplifier						

4. Remove C_3 and R_D from the circuit and move C_2 and R_{L1} from the drain to the source, as shown in Figure 40–3. Connect the drain directly to +12 V. Measure the dc voltage at the drain, source, and gate and compute I_D . Observe the output voltage from the source with the oscilloscope. Measure the voltage gain and note the phase. Enter the data in Table 40–2 in the row labeled Common-Drain Amplifier.

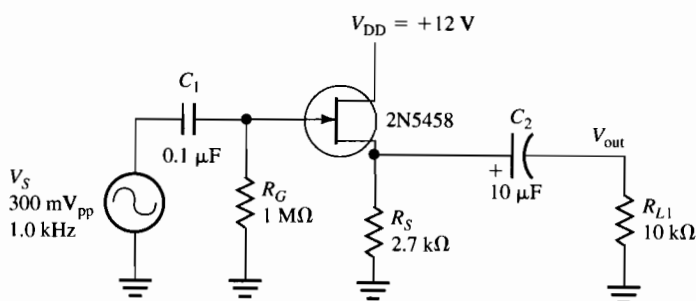


Figure 40–3

5. Remove R_{L1} from the CD circuit and add a bipolar CE amplifier, as shown in Figure 40–4. Use the 4.7 kΩ drain resistor for R_L . *Note the polarity of C_2 and C_3 .* Before connecting power, compute the dc parameters listed in Table 40–3 for the bipolar stage. The steps are as follows:
- Solve for the base voltage, V_B , by applying the voltage divider rule to R_1 and R_2 .
 - Add the 0.7 V forward-bias drop across the base-emitter diode to V_B to obtain the emitter voltage, V_E . (The 0.7 is *added* because the transistor is a PNP type.)
 - The dc current in the emitter circuit is found by applying Ohm's law to R_{E1} and R_{E2} . The voltage drop across the emitter resistors is $V_{CC} - V_E$. The emitter current, I_E , is approximately equal to the collector current, I_C .
 - Find the dc collector voltage by applying Ohm's law to the load resistor, R_{L2} .

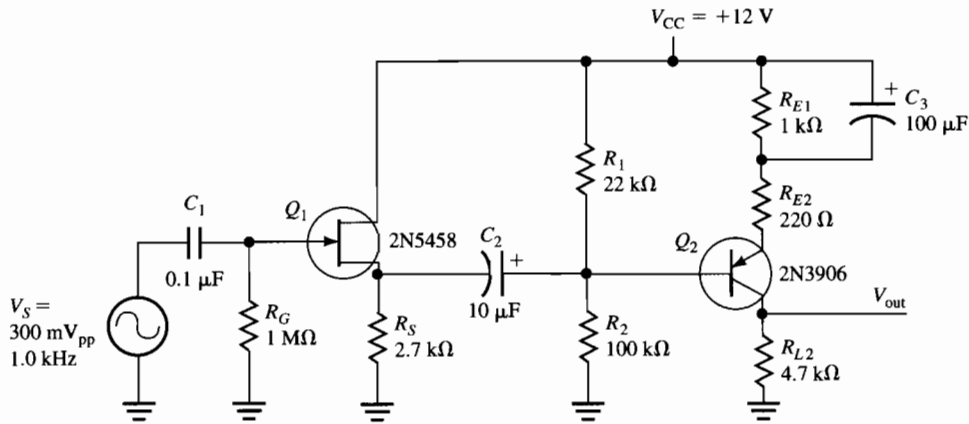


Figure 40-4

6. Compute the ac parameters listed in Table 40-4. The steps are as follows:
- Compute the ac base voltage, V_b , into the CE amplifier by multiplying A_v for the CD stage (Table 40-2) by the input voltage (300 mV).
 - Compute the ac resistance of the emitter, r_e , from the equation

$$r_e = \frac{25 \text{ mV}}{I_E}$$

- Compute the voltage gain of Q_2 . The input voltage is across the ac emitter resistance to ground which, in this case, is $r_e + R_{E2}$. The output voltage is taken across the ac resistance from collector to ground, which is just R_{L2} . The voltage gain is therefore written:

$$A_{v(Q2)} = \frac{I_e R_{L2}}{I_e (r_e + R_{E2})} = \frac{R_{L2}}{(r_e + R_{E2})}$$

- Compute the overall gain of both stages. For $A_{v(Q1)}$, use the measured value found in step 4 (common-drain). The input impedance of the bipolar transistor has only a small loading effect on the JFET and can be ignored. The overall gain of the bifet amplifier is then:

$$A_{v(\text{TOTAL})} = A_{v(Q1)} A_{v(Q2)}$$

Table 40-3

DC Parameter	Computed Value	Measured Value
V_B		
V_E		
I_E		
V_{CE}		

Table 40-4

AC Parameter	Computed Value	Measured Value
V_b		
r_e		
$A_{v(Q2)}$		
$A_{v(TOTAL)}$		

7. Connect power to the bifet amplifier and measure the dc and ac parameters listed in Tables 40-3 and 40-4. Record your data in the tables. To measure $A_{v(Q2)}$, divide V_{out} by V_b . The overall gain can be found by dividing V_{out} by the voltage from the signal generator, V_S .

Conclusion:

Evaluation and Review Questions:

1. How did the gain of the common-source amplifier (Figure 40-2) compare with the similar common-emitter amplifier tested in Experiment 38?
2. For the common-source amplifier (Figure 40-2), what would you expect to happen to the dc and ac parameters if C_3 were open?
3. Compare a common-collector amplifier with a common-drain amplifier. Which can have the higher input impedance? How do the voltage gains compare?

4. Assume the bifet amplifier in Figure 40–4 has no output signal. In testing the dc conditions, you find that the emitter of Q_2 is at +12 V. What could account for this?

5. What are the advantages of the bifet amplifier tested in this experiment?

For Further Investigation:

The bifet amplifier in this experiment was connected in *cascade*, which means that stages were connected in series. An interesting variation of the bifet amplifier is to connect it in *cascode*. In this configuration, the drain of the FET supplies ac signal current to the emitter of the next stage. The second stage is a common-base amplifier. While the overall gain is not high, the advantage of the cascode connection is that it has a higher frequency response than the cascade connection. Construct the cascode amplifier shown in Figure 40–5. Set the signal generator for a 1.0 V_{pp} input signal. Test the dc and ac parameters and submit a laboratory report describing your findings.

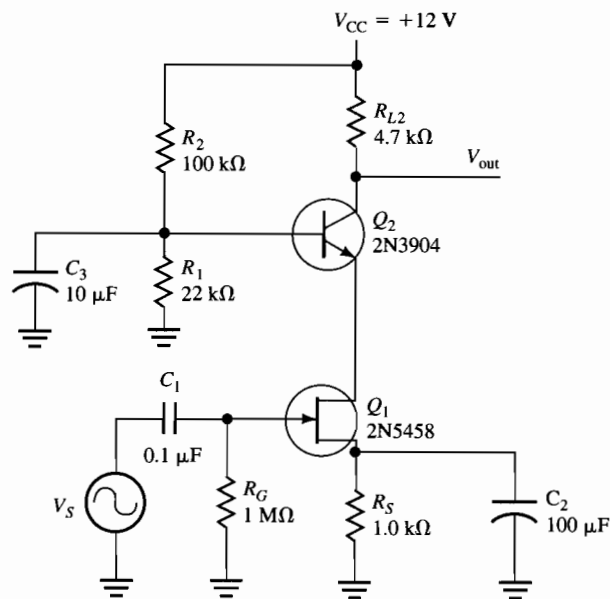


Figure 40–5

41 The Push-Pull Amplifier

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 19–6 and 19–7

Objectives:

After performing this experiment, you will be able to:

1. Construct a push-pull amplifier driven by a common-emitter voltage amplifier.
2. Predict and measure performance characteristics of the circuit constructed in objective 1.

Summary of Theory:

The amplifiers studied so far have all been small-signal amplifiers that are biased on continuously. This operation is called *class A* operation and is not particularly efficient. For small signals, this doesn't matter, but when a significant amount of power must be delivered, *class B* operation offers major advantages. In class B operation, there are two transistors, which alternately conduct on positive and negative half-cycles of the input waveform. This type of amplifier is given the picturesque name of *push-pull* to describe its operation. Figure 41–1(a) illustrates a basic push-pull amplifier.

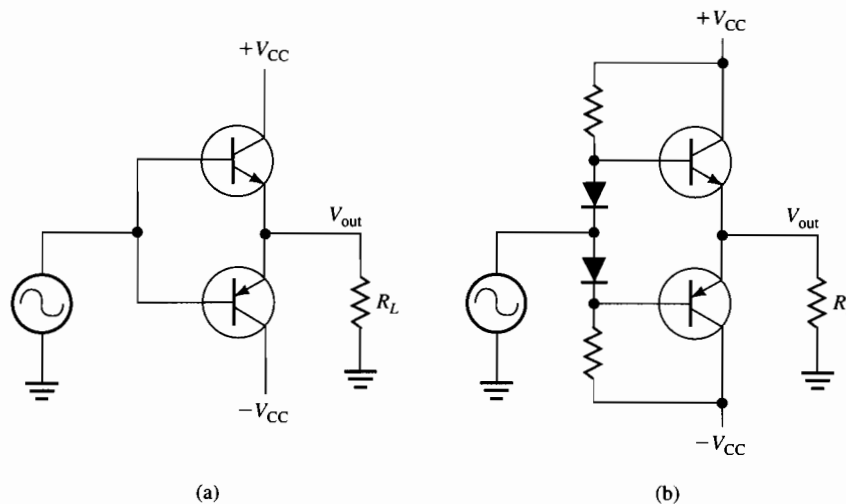


Figure 41–1

The circuit illustrated in Figure 41–1(a) has a problem. The base-emitter diode for each transistor requires approximately 0.7 V before it will conduct. The output signal follows the input except for the 0.7 V diode drop on both the positive and negative excursion. This causes distortion on the output called *crossover* distortion. Crossover distortion can be eliminated by using diodes to bias the transistors into slight conduction as illustrated in Figure 41–1(b). This type of bias is called *diode mirror bias* because if the diode is matched to the transistor's base-emitter diode, the current in the collector circuit is equal to the current in the diode.

The current mirror offers another advantage. If the temperature increases, the output current will tend to increase. If the diodes are identical to the base-emitter junction, any thermal change will tend to be compensated by the diodes, thus maintaining stable bias.

Materials Needed:

Resistors:

One 330 Ω, one 2.7 kΩ, two 10 kΩ, one 68 kΩ

Capacitors:

One 1.0 μF

Transistors:

One 2N3906 PNP, two 2N3904 NPN (or equivalent)

Two 1N914 diodes (or equivalent)

One 5 kΩ potentiometer

For Further Investigation: (Note: Further Investigation can be done as analysis only.)

Resistors:

Two 10 Ω, one 100 Ω, one 200 Ω, one 2.7 kΩ

Transistors:

Two PNP 2N3906 (or equivalent)

Transformers:

Input: Kelvin 155-08 (or equivalent)

Output: Kelvin type 175-45 (or equivalent)

Procedure:

1. Measure and record the resistance of the resistors listed in Table 41–1.
2. Construct the push-pull amplifier shown in Figure 41–2. The amplifier uses the input signal from the generator to bias the transistors on. Set the generator for a 10 V_{pp} sine wave at 1.0 kHz. Be sure there is *no* dc offset from the generator. The dual positive and negative power supplies offer the advantage of not requiring large coupling capacitors.

Table 41–1

Resistor	Listed Value	Measured Value
R_L	330 Ω	
R_1	10 kΩ	
R_2	10 kΩ	
R_3	68 kΩ	
R_4	2.7 kΩ	


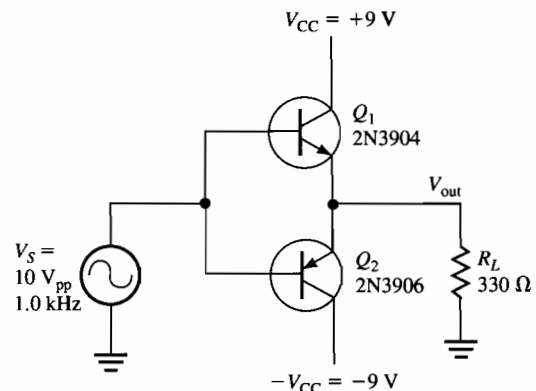


Figure 41–2

3. Sketch the input and output waveforms you observe on Plot 41–1. Show the amplitude difference between the peak input waveform and the output waveform and note the crossover distortion on your plot.

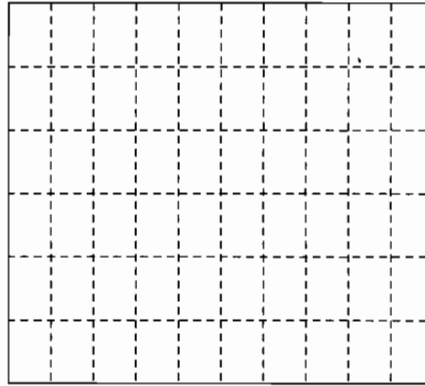

Plot 41–1

4. Remove power from the circuit and add the diode mirror bias shown in Figure 41–3. Compute the dc parameters listed in Table 41–2 for the circuit. The dc emitter voltage will be zero volts as shown, if each half of the circuit is identical. Assume that the 0.7 V base-emitter drop is the same as each diode. The current in R_1 can be found by applying Ohm's law. This current is identical to I_{CQ} because of current mirror action if the diodes match the base-emitter characteristic of the transistors.

Table 41–2

DC Parameter	Computed Value	Measured Value
V_E	0 V	
V_{B1}		
V_{B2}		
$I_1 = I_{CQ}$		

Table 41–3

AC Parameter	Computed Value	Measured Value
$V_{p(out)}$		
$I_{p(out)}$		
$P_{(out)}$		

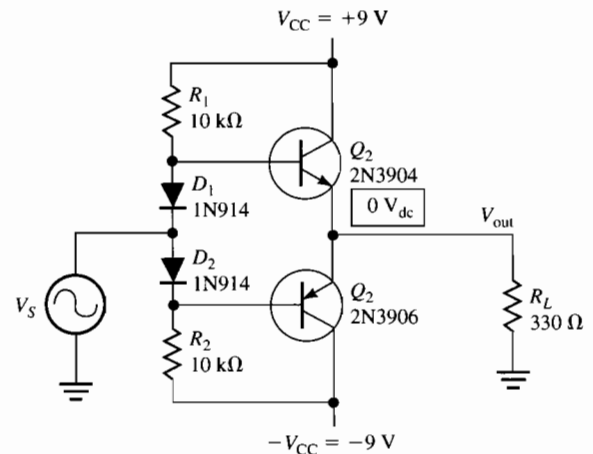


Figure 41–3

5. Compute the ac parameters listed in Table 41–3. Assume V_S is set for maximum undistorted output voltage. Compute the maximum output voltage and current. Unlike

the single power supply case, the output can swing nearly to positive and negative V_{CC} . Then compute the peak output current based on the load resistance. The ac power is found by $P_{out} = 0.5 I_{p(out)} V_{p(out)}$. By substituting for I_p , the ac power out can also be expressed as

$$P_{out} = \frac{V_{p(out)}^2}{2R_L}$$

6. With the signal generator off, apply power and measure to dc parameters listed in Table 41–2.
7. Turn on the signal generator and ensure there is no dc offset. While viewing V_{out} , adjust the generator for the maximum unclipped output. Enter $V_{p(out)}$ in Table 41–3.
8. One common method for applying a signal to a push-pull amplifier is shown in Figure 41–4. The signal is amplified by Q_3 , a common-emitter amplifier. The quiescent current in the collector circuit is designed to produce the same dc conditions as in the circuit of Figure 41–3. The bias adjust allows the dc output voltage to be set to zero to compensate for tolerance variations in the components. Compute the dc parameters listed in Table 41–4. Assume the bias potentiometer is set to 3 k Ω and apply the voltage divider rule to find V_{B3} . Note that the voltage across the divider string is the difference between $+V_{CC}$ and $-V_{CC}$.

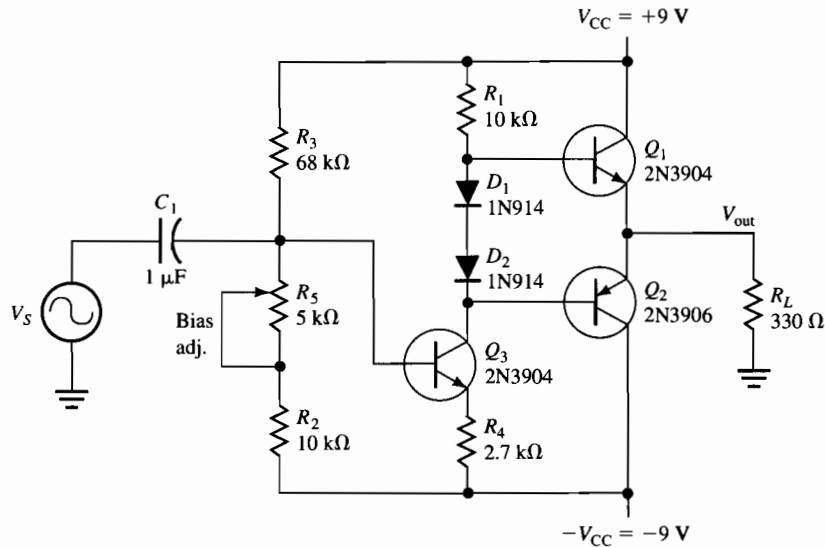


Figure 41–4

Table 41–4

DC Parameter	Computed Value	Measured Value
V_{B3}		
V_{E3}		
I_{CQ3}		

Table 41–5

AC Parameter	Computed Value	Measured Value
$A_{v(TOT)}$		

9. Compute the voltage gain of Q_3 by taking into account the load presented to the collector circuit by Q_3 by the push-pull amplifier and by dividing by the resistance of the Q_3 emitter circuit. The voltage gain of the push-pull amplifier is nearly 1.0, so the total voltage gain of the amplifier is approximately equal to the gain of Q_3 . That is,

$$A_{v(TOT)} \cong A_{v(Q3)} \cong \frac{R_1 \parallel \{\beta_{Q1}(R_L + r_{eQ1})\}}{(r_{eQ3} + R_4)}$$

10. Connect the circuit shown in Figure 41–4. Measure the dc voltage across the load resistor and vary the bias adjust potentiometer for 0 V. Measure the parameters listed in Table 41–4. Set the signal generator for a voltage that produces the maximum unclipped output voltage across the load resistor. Then measure the total voltage gain of the circuit. Enter the computed and measured gains in Table 41–5.

Conclusion:

Evaluation and Review Questions:

1. With no signal applied, what power is provided by the power supplies in Figure 41–3? (Remember the current in the diodes is equal to the current in the transistors.)
2. Assume the circuit in Figure 41–3 has a positive half-wave rectified output. What failure(s) could account for this?
3. If one of the diodes in Figure 41–3 shorts, what symptoms will it produce?

4. In step 10, you found that the total voltage gain was fairly low for the circuit of Figure 41–4. What change to the circuit would you suggest to increase the voltage gain?
5. The bias-adjust resistor in Figure 41–4 was chosen to allow a range of bias voltage to Q_3 in order to compensate for variations in components. Compute the minimum and maximum bias voltage based on setting R_5 to its smallest and largest values.

$$V_{(\text{bias})\text{min}} = \underline{\hspace{2cm}} \qquad V_{(\text{bias})\text{max}} = \underline{\hspace{2cm}}$$

For Further Investigation:

The circuits in this experiment used complementary symmetry, useful when NPN and PNP devices with similar characteristics are available. An older, but still widely used, technique uses the same type of transistor for each half of the push-pull amplifier. The signal is connected to an input transformer that splits it into two phases. Each half is amplified by one of the push-pull amplifiers and recombined in the output transformer. Collector voltage is applied through the center-tap of the transformer. The dc bias voltage for the transistors appears at point A and is just a voltage divider formed by R_1 and R_2 . The circuit is generally used as a power amplifier but is shown in Figure 41–5 using small-signal transistors. Analyze the circuit and submit a laboratory report describing your analysis. You should include the predicted dc conditions throughout the circuit. Predict the ac waveforms at each point in the circuit. If directed by your instructor, build the circuit and test your predictions.

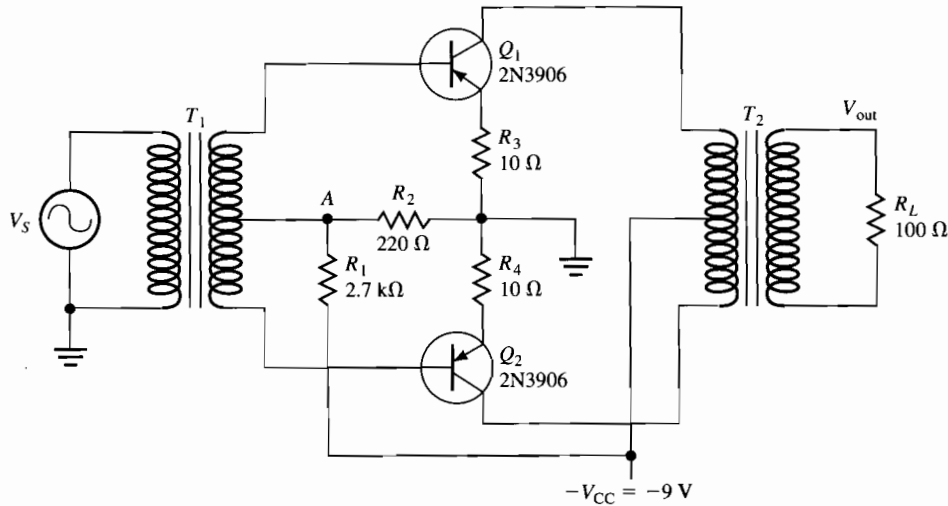


Figure 41–5

42 Oscillators

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 19–8 and 19–9

Objectives:

After performing this experiment, you will be able to:

1. Connect a class A amplifier; calculate and measure the dc and ac parameters.
2. Modify the amplifier with a feedback circuit that forms two versions of *LC* oscillators—the Colpitts and the Hartley.
3. Compare the computed and measured performance of the oscillators.

Summary of Theory:

In electronic systems, there is almost always a requirement for one or more circuits that generate a continuous waveform. The output voltage can be a square wave, sine wave, sawtooth, or other periodic waveform. A free-running oscillator is basically an amplifier that generates a continuous alternating voltage by feeding a portion of the output signal back to the input. You have already constructed and tested a relaxation oscillator in Experiment 37, a circuit that operated on the principle of charging and discharging a capacitor. Relaxation oscillators are useful for generating sawtooth, triangle, and square waves.

Sine wave oscillators are classified by the networks used to provide feedback. To sustain oscillations, the amplifier must have sufficient gain to overcome the losses in the feedback network. In addition, the feedback must be of the proper phase to ensure that the signal is reinforced at the output—in other words, there must be *positive* feedback. Feedback networks can be classified as *LC*, *RC*, or by a *crystal*, a special piezoelectric resonant network.

LC circuits have a parallel resonant circuit, commonly referred to as the *tank* circuit, that determines the frequency of oscillation. A portion of the output is returned to the input causing the amplifier to conduct only during a very small part of the total period. This means that the amplifier is actually run in class C mode. *LC* circuits are generally preferred for frequencies above 1 MHz, whereas *RC* oscillators are usually limited to frequencies below 10 MHz, where stability is not as critical. In applications where frequency stability is important, crystal oscillators have the advantage. In this experiment, you will test two *LC* oscillators, and in the For Further Investigation section, you will test a crystal oscillator. Later, in Experiment 47, you will test a low-frequency *RC* oscillator, the Wien bridge oscillator.

Materials Needed:

2N3904 NPN transistor (or equivalent)

One 100 Ω potentiometer

Resistors:

One 1.0 k Ω , one 2.7 k Ω , 3.3 k Ω , one 10 k Ω

Capacitors:

Two 1000 pF, one 0.01 μ F, three 0.1 μ F

Inductors:

One 2 μH (can be wound quickly from #22 wire), one 25 μH

For Further Investigation:

One 1 MHz crystal, one 2N5458 N-channel JFET, one 10 M Ω resistor

Procedure:

1. Measure and record the value of the resistors listed in Table 42–1.
2. Observe the class A amplifier shown in Figure 42–1. Using your measured resistor values, compute the dc parameters for the amplifier listed in Table 42–2. R_{E1} is a 100 Ω potentiometer that you should set to 50 Ω . Then construct the circuit and verify that your computed dc parameters are as expected.

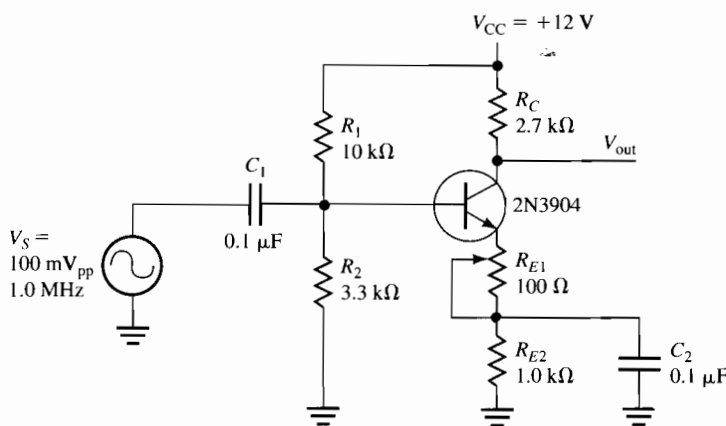


Figure 42–1

Table 42–1

Resistor	Listed Value	Measured Value
R_1	10 k Ω	
R_2	3.3 k Ω	
R_{E1}	50 Ω *	
R_{E2}	1.0 k Ω	
R_C	2.7 k Ω	

*Set potentiometer for 50 Ω

3. Compute the ac parameters listed in Table 42–3. After you find r_e , find the gain by dividing the collector resistance by the sum of the unbypassed emitter resistance and r_e . (Assume that the potentiometer remains set to 50 Ω .) Find the ac voltage at the collector by multiplying the gain by the ac base voltage. Set the generator for a 100 mV_{pp} sine wave at 1.0 MHz and measure the peak-to-peak collector voltage. Your computed quantities should agree with the measured values within experimental uncertainty. Record the measured ac parameters in Table 42–3.

Table 42–2

DC Parameter	Computed Value	Measured Value
V_B		
V_E		
I_E		
V_C		

Table 42–3

AC Parameter	Computed Value	Measured Value
V_b	100 mV _{pp}	
r_e		
A_v		
V_c		

4. Remove the generator and add the feedback network for a Colpitts oscillator, as shown in Figure 42–2. Adjust R_{E1} for the best output sine wave. Compute the frequency of the Colpitts oscillator and record the computed frequency in Table 42–4. Then, measure the frequency and the peak-to-peak voltage at the output and record them in Table 42–4.

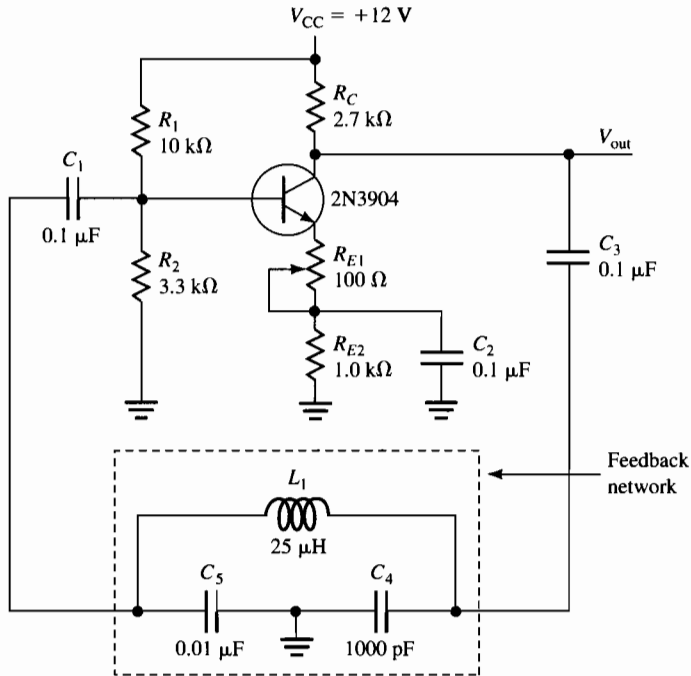


Figure 42–2

Table 42–4

Colpitts Oscillator	Computed Value	Measured Value
Frequency		
Amplitude		

5. Observe what happens to the frequency and amplitude of the output signal when another 1000 pF capacitor is placed in parallel with C_4 .
6. Observe the effect of freeze spray on the stability of the oscillator.
7. Replace the feedback network with the one shown in Figure 42–3. (L_2 can be wound by wrapping about 40 turns of #22 wire on a pencil.) Adjust R_{E1} for a good sine wave output. This configuration is that of a Hartley oscillator. Compute the frequency of the Hartley oscillator, and record the computed frequency in Table 42–2. Then, measure the frequency and the peak-to-peak voltage at the output and record them in Table 42–5.

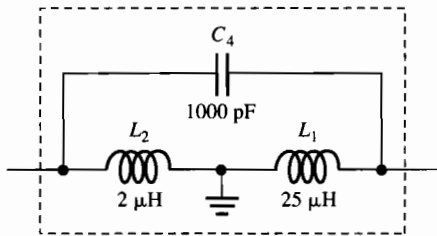


Figure 42-3

Table 42-5

Hartley Oscillator	Computed Value	Measured Value
Frequency		
Amplitude		

Conclusion:

Evaluation and Review Questions:

1. In step 5, you observed a change in the amplitude of the output signal when a capacitor was placed in parallel with C_4 . Since the gain of the class A amplifier remained the same, what conclusion can you draw about the effect of the change on the amount of feedback?
2. What are the two conditions required for oscillation to occur in an *LC* oscillator?
3. Give a reason that an oscillator might drift from its normal frequency.
4. Summarize the difference between a Colpitts and a Hartley oscillator.

5. For the circuit in Figure 42–2, predict the outcome in each case.
- R_{E1} is shorted.
 - C_4 and C_5 are reversed.
 - C_2 is open.
 - The power supply voltage is 6 V.

For Further Investigation:

When it is necessary to have high stability in an oscillator, the crystal oscillator is superior. For high-frequency crystal oscillators, FETs have advantages over bipolar transistors because of their high input impedance. This allows the tank circuit to be unloaded, resulting in a high Q . The circuit shown in Figure 42–4 has the advantage of being simple, yet very stable. Construct the circuit and observe the waveform at the drain. Compare the frequency with that stamped on the crystal case (to do this requires a frequency counter). Test the effect of freeze spray on the frequency and amplitude. Summarize your results.

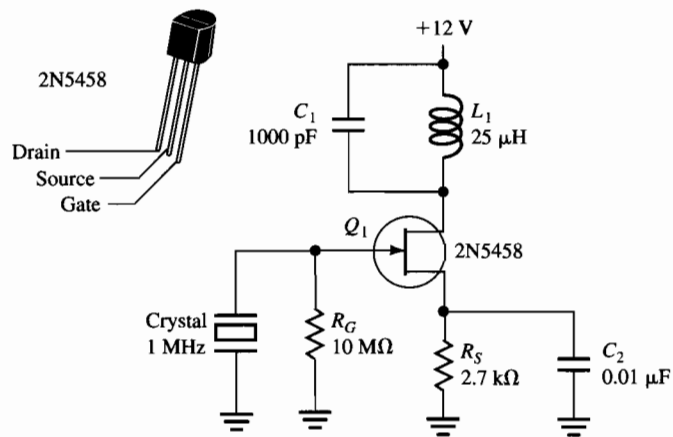


Figure 42–4

Application Assignment 19

Name _____
 Date _____
 Class _____

Reference:

Floyd, Chapter 19, Section 19-11: Application Assignment

Step 1

Relate the PC board to the schematic. The PC board and the schematic are shown in Figure AA-19-1. Label the components in the spaces provided.

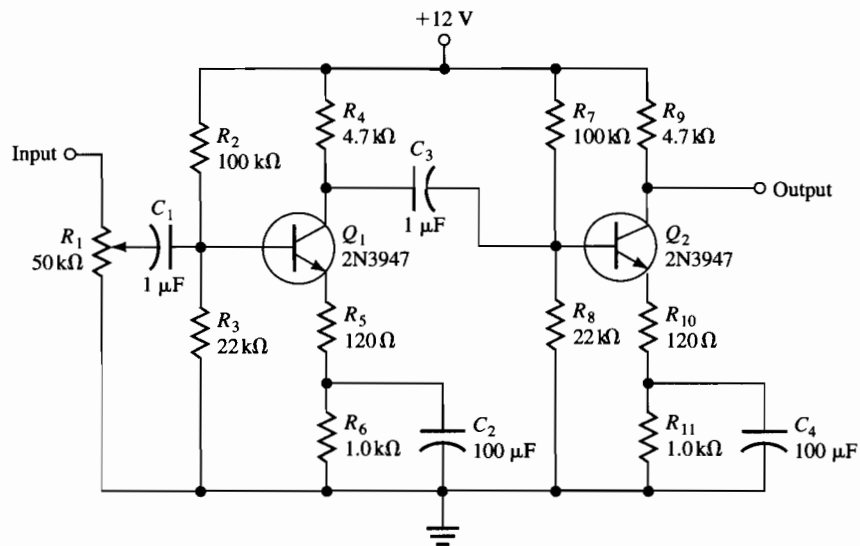
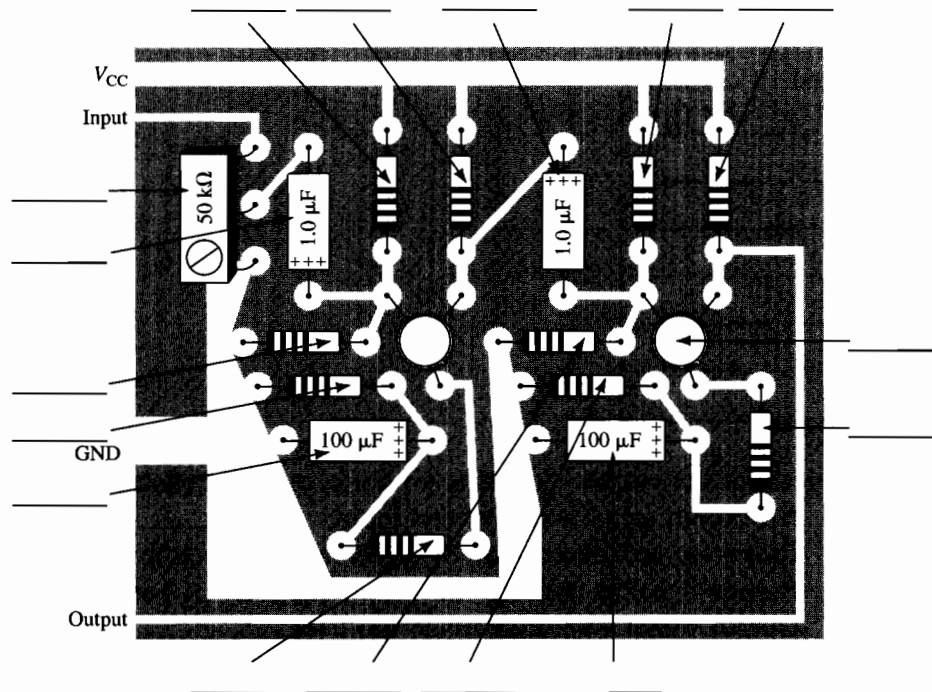


Figure AA-19-1

Step 2

Analyze the amplifier.

1. Compute the dc voltages and the input resistance as shown in the first four lines of Table AA-19-1. (Note: The voltage divider in this case is not stiff. Use equation 18-7 to compute V_B for each transistor.)
2. Compute the voltage gain of each stage and the overall voltage gain. You need to take into account loading effects for the overall gain. Record your computed values in Table AA-19-1.
3. Explain what happens if the input frequency is reduced to a very low value: _____
4. Compute the voltage gain for the case of a 15 k Ω load resistor: $A_v = \underline{\hspace{2cm}}$

Table AA-19-1

Parameter	Computed for Q_1	Computed for Q_2
V_B		
V_E		
V_C		
$R_{in(T)}$		
A_v		
$A_{v(overall)} =$		

Step 3

Troubleshoot the circuit. State the probable cause of each problem listed.

1. No output signal with verified input: _____
2. Proper ac and dc on base of Q_2 ; collector signal low: _____
3. Proper signal at collector of Q_1 ; no signal at Q_2 base: _____
4. Output signal amplitude much too low: _____
5. Q_2 collector at +12 V, no output signal with verified input: _____

Related Experiment:

Materials Needed:

Two small-signal NPN transistors (2N3947, 2N3904, or equivalent)

Resistors:

Two of each: 120 Ω , 1.0 k Ω , 4.7 k Ω , 22 k Ω , 100 k Ω

Capacitors:

Two of each: 1.0 μ F, 100 μ F

One 50 k Ω potentiometer

Discussion:

Construct the two-stage amplifier shown in Figure AA-19-1 and measure the parameters you computed in Table AA-19-1. Extend the table to indicate the measured data. Summarize your results in a written conclusion.

Checkup 19

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 19, and Buchla, Experiments 38 through 42

1. An effective way to increase the gain in a common-emitter amplifier is:
(a) bypass the emitter resistor with a capacitor
(b) increase the bias resistors
(c) bypass the collector resistor with a capacitor
(d) increase V_{CC}
2. An amplifier that inverts the phase between the input and output is a:
(a) common base
(b) common emitter
(c) common gate
(d) common collector
3. An amplifier that has approximately the same current gain and power gain is:
(a) common base
(b) common emitter
(c) common gate
(d) common collector
4. A common-collector amplifier supplies:
(a) only voltage gain
(b) only current gain
(c) both voltage and current gain
(d) neither voltage gain nor current gain
5. Assume an emitter bypass capacitor is open in a common-emitter amplifier. This would cause:
(a) a change in the gain
(b) a change in r_e
(c) decrease in the input impedance
(d) all of these
6. Compared to a common-emitter amplifier, an advantage of a common-source FET amplifier is greater:
(a) voltage gain
(b) current gain
(c) linearity
(d) input impedance
7. Compared to a class A amplifier, an advantage of a class B push-pull amplifier is greater:
(a) efficiency
(b) voltage gain
(c) linearity
(d) input impedance
8. An *LC* oscillator circuit must have:
(a) a crystal
(b) current gain
(c) a bipolar transistor
(d) positive feedback

9. The frequency of an LC oscillator can be changed by varying:
- (a) the bias
 - (b) the emitter bypass capacitor
 - (c) components in the feedback path
 - (d) the emitter resistance
10. Another name for a parallel LC circuit used in an oscillator is a:
- (a) feedback loop
 - (b) tank circuit
 - (c) bridge circuit
 - (d) phase-shift network
11. Explain how to *measure* the input resistance of a CE amplifier.
12. For the circuit in Figure C-19-1, assume the emitter and collector currents are the same. Compute the following dc parameters:
- (a) emitter current
 - (b) V_{CE}
13. For the circuit in Figure C-19-1(a), compute the following ac parameters:
- (a) r_e
 - (b) A_v (loaded)
14. For the circuits shown in Figure C-19-1, compare the input resistance of the bipolar transistor amplifier with the JFET amplifier.
15. For the JFET amplifier in Figure C-19-1(b), assume that g_m is $4000 \mu\text{S}$. Compute the gain.

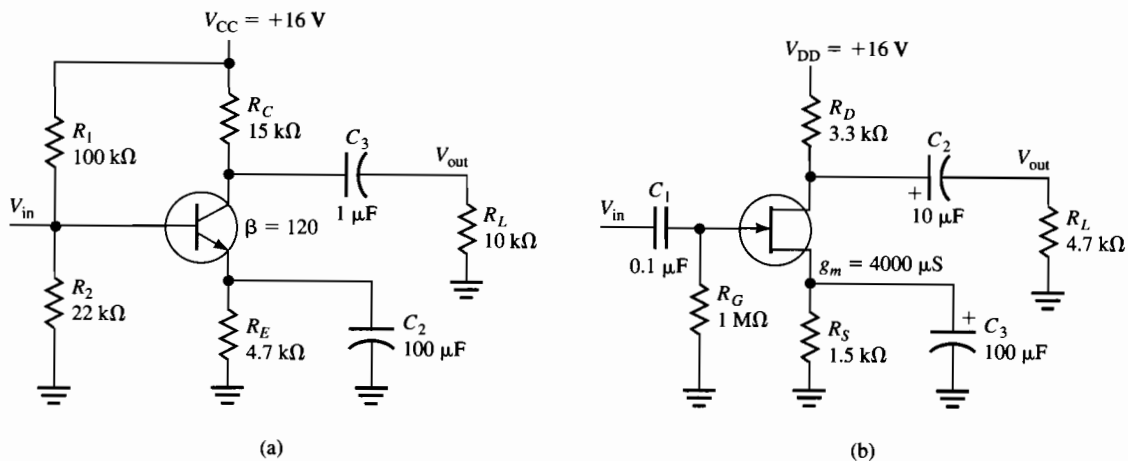


Figure C-19-1

43 The Differential Amplifier

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 20–1 and 20–2

Objectives:

After performing this experiment, you will be able to:

1. Compute dc and ac parameters of a differential amplifier with emitter bias.
2. Build a differential amplifier circuit, test it, and measure differential and common-mode gain.

Summary of Theory:

The differential amplifier (*diff amp*) is used to amplify the *difference* in two signals. The output is related only to the difference between the two inputs. If the input signals are identical, the operation is said to be *common-mode*. The output of the ideal difference amplifier will be zero for common-mode signals. When the inputs are different, the operation is said to be *normal-mode*. The normal-mode signal is amplified by the differential amplifier. The difference amplifier is important in applications in which a weak signal is in the presence of unwanted noise as illustrated in Figure 43–1. The desired transducer signal drives the diff amp in normal mode. The noise source will tend to induce equal voltages into the twisted pair wires, driving the diff amp in common-mode. The signal at the output will represent the original transducer signal without the induced noise voltage.

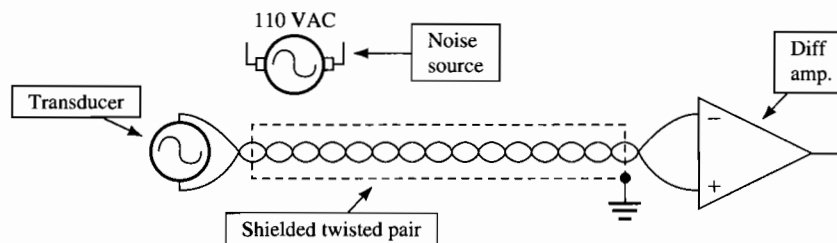


Figure 43–1

The diff amp's ability to reject unwanted common-mode signals while favoring the desired normal mode signals is called the amplifier's *common-mode rejection ratio* (CMRR). CMRR is often expressed in decibels (dB) and can be defined as:

$$\text{CMRR} = 20 \log \frac{A_{v(d)}}{A_{cm}}$$

In this equation, $A_{v(d)}$ represents the differential voltage gain and A_{cm} represents the common-mode voltage gain. The CMRR is a dimensionless number.

Materials Needed:

Resistors:

Two 47 Ω, two 10 kΩ, two 47 kΩ

Two 1 μF capacitors

Two 2N3904 NPN transistors (or equivalent)

For Further Investigation:

Two 10 kΩ resistors, one 4.7 kΩ resistor, one 2N3904 transistor

Procedure:

1. Measure and record the resistance of the resistors listed in Table 43–1.

Table 43–1

Resistor	Listed Value	Measured Value
R_{B1}	47 kΩ	
R_{B2}	47 kΩ	
R_{E1}	47 Ω	
R_{E2}	47 Ω	
R_T	10 kΩ	
R_C	10 kΩ	

Table 43–2

DC Parameter	Computed Value	Measured Values	
		Q_1	Q_2
I_E			
I_B			
V_B			
V_E			
V_A			
$V_{C(Q2)}$			

2. The circuit shown in Figure 43–2 is a differential amplifier with single-ended output and emitter bias. Except for V_C , the dc parameters should be identical for Q_1 and Q_2 . The transistors are forward biased by the negative supply connected to the common *tail* resistor, R_T . Notice that R_T has *two* emitter currents in it, one from each transistor. To solve for the dc parameters in the circuit, the first step is to write Kirchhoff’s voltage equation for the closed path indicated by the dotted line on Figure 43–2. The first sign of each voltage drop is used in writing the equation. (Note that Kirchhoff’s voltage law can be written in either direction and obtain the same result.)

$$+V_{EE} - 2I_E R_T - I_E R_{E1} - 0.7 \text{ V} - I_B R_{B1} = 0$$

The base current can be expressed in terms of the emitter current by using the approximation:

$$I_B \cong \frac{I_E}{\beta_{dc}}$$

By substitution, and solving for I_E :

$$I_E = \frac{V_{EE} - 0.7 \text{ V}}{\frac{R_{B1}}{\beta_{dc}} + R_{E1} + 2R_T}$$

Compute I_E for the circuit shown in Figure 43–2. If you do not know the β_{dc} for your transistor, assume a value of 100. Enter your computed I_E in Table 43–2.

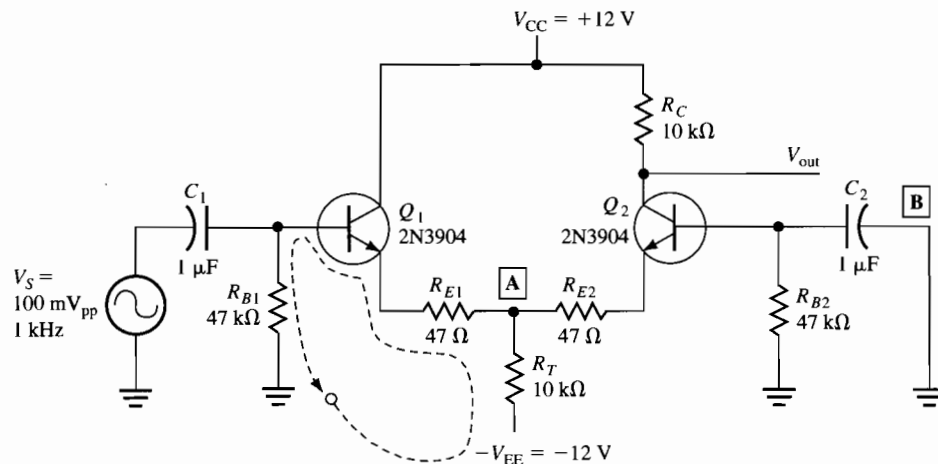


Figure 43–2

3. Compute the remaining dc parameters listed in Table 43–2. The base voltage for either transistor, V_B , can be found by subtracting $I_E R_{B1}$ from zero (ground). The emitter voltage for either transistor is 0.7 V less than V_B . The voltage at point A can be computed by subtracting $I_E R_{E1}$ from V_E . $V_{C(Q2)}$ is found by subtracting $I_E R_C$ from V_{CC} .
4. Construct the diff amp shown in Figure 43–2. The signal generator should be turned off. Measure and record the dc voltages listed in Table 43–2. Your measured and computed values should agree within 10%.
5. Using the computed I_E , calculate r_e for the transistors. Enter the computed r_e in Table 43–3.
6. Compute the differential gain, $A_{v(d)}$, for the circuit. The diff amp can be thought of as a common-collector amplifier (Q_1) driving a common base amplifier (Q_2). Point A represents the output of the CC amplifier and the input of the CB amplifier. The Q_1 base voltage, $V_{b(Q1)}$, is shown as equal to V_S . The gain to point A is approximately $\frac{1}{2}$, so $V_{A(ac)}$ is shown as a computed 50 mV_{pp}. The differential gain is the product of the gain of the CC amplifier and the CB amplifier.

$$A_{v(d)} = A_{CC} A_{CB} = \left(\frac{1}{2}\right) \left(\frac{R_C}{R_{E2} + r_{e(Q2)}}\right) = \frac{R_C}{2(R_{E2} + r_{e(Q2)})}$$

Table 43–3

AC Parameter	Computed Value	Measured Value
r_e		
$V_{b(Q1)}$	100 mV _{pp}	
$V_{A(ac)}$	50 mV _{pp}	
$V_{v(d)}$		
$V_{c(Q2)}$		
A_{cm}		

7. Compute the common-mode gain from the formula

$$A_{cm} \cong \frac{R_C}{2R_T}$$

Enter the computed A_{cm} in Table 43–3.

8. Turn on the signal generator and set V_S for 100 mV_{pp} at 1.0 kHz. Use the oscilloscope to set the proper voltage and check the frequency. (It may be necessary to attenuate the generator input to obtain a 100 mV signal.) Measure the ac signal voltage at Q_1 's base ($V_{b(Q1)}$), point A, and at Q_2 's collector ($V_{c(Q2)}$). Determine the differential gain, $A_{v(d)}$. (The overall voltage gain is the ratio of the output to the input voltage.) Using two channels, observe the phase relationship between these waveforms. Enter your measured results in Table 43–3.
9. To measure the common-mode gain, it is necessary to put an identical signal into both Q_1 and Q_2 . Do this by removing point B from ground and connecting point B to the signal generator. Increase V_S to 1.0 V_{pp} and measure V_{out} . Enter the measured A_{cm} in Table 43–3.

Conclusion:

Evaluation and Review Questions:

1. Using the measured differential gain and the measured common-mode gain, compute the CMRR for the differential amplifier. Express your answer in decibels.

2. In step 2, Kirchhoff's law was used to develop the equation for the emitter current. The second term of the equation contains $2I_E$ in it. Explain.

3. In step 6, it is stated that the voltage gain to point A is approximately one-half. Explain.

4. Predict the dc voltage at point A if the base of Q_2 is open.

5. Name at least three malfunctions that could account for a dc voltage of +12 V on Q_2 's collector.

For Further Investigation:

Because current sources have a high internal resistance, the CMRR can be improved by substituting the current source shown in Figure 43–3 for R_T . Measure the differential and common-mode gains and compute the CMRR for the diff amp tested in this experiment. Summarize your measurements including the differential- and common-mode gains.

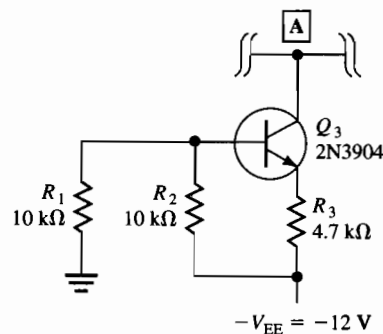


Figure 43–3

44 Op-Amp Characteristics

Name _____
Date _____
Class _____

Reading:

Floyd, Section 20–3

Objectives:

After performing this experiment, you will be able to:

1. Explain the meaning of common op-amp specifications.
2. Use IC op-amp specification sheets to determine op-amp characteristics.
3. Measure the input offset voltage, bias current, input offset current, and CMRR for a 741C op-amp.

Summary of Theory:

An operational amplifier (*op-amp*) is a linear integrated circuit that incorporates a dc-coupled, high-gain differential amplifier and other circuitry that give it specific characteristics. The ideal op-amp has certain unattainable specifications, but hundreds of types of operational amplifiers are available, which vary in specific ways from the ideal op-amp. Important specifications include open-loop gain, input impedance, output impedance, input offset voltage and current, bias current, and slew rate. Other characteristics that are important in certain applications include CMRR, current and voltage noise level, maximum output current, rolloff characteristics, and voltage and power requirements. The data sheet for a specific op-amp contains these specifications, a description of the op-amp, the device pin-out, internal schematic, maximum ratings, suggested applications, and performance curves.

Because the input stage of all op-amps is a differential amplifier, there are two inputs marked with the symbols (+) and (–). These symbols refer to the phase of the output signal compared to the input signal and should be read as noninverting (+) and inverting (–) rather than “plus” or “minus.” If the noninverting input is more positive than the inverting input, the output will be positive. If the inverting input is more positive, then the output will be negative. Two commonly used symbols for op-amps are shown in Figure 44–1. The power supplies are frequently not shown.

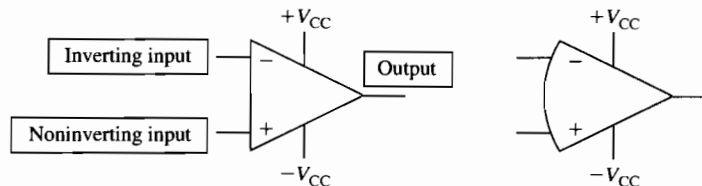


Figure 44–1

Materials Needed:

Resistors:

Two 100 Ω , two 10 k Ω , two 100 k Ω , one 1.0 M Ω

Two 1.0 μ F capacitors

One 741C op-amp

Procedure:

- Examine the specification sheet for the 741C op-amp (Appendix B). From the specification sheet, determine the typical and maximum values for each quantity listed in Table 44–1. Record the specified values for $T_A = 25^\circ\text{C}$. Note the measurement units listed on the right side of the specification sheet.

Table 44–1

Step	Parameter	Specified Value			Measured Value
		Minimum	Typical	Maximum	
2d	Input offset voltage, V_{IO}				
3d	Input bias current, I_{BIAS}				
3e	Input offset current, I_{OS}				
4b	Differential gain, $A_{v(d)}$				
4c	Common-mode gain, A_{cm}				
4d	CMRR				

- In this step, you will measure the input offset voltage, V_{IO} , of a 741C op-amp. The input offset voltage is the amount of voltage that must be applied between the *input* terminals of an op-amp to give zero *output* voltage.
 - Measure and record the resistors listed in Table 44–2.
 - Connect the circuit shown in Figure 44–2. Install $1\ \mu\text{F}$ bypass capacitors on the power supply leads as shown. Note the polarities of the capacitors.
 - Measure the output voltage, V_{OS} . The input offset voltage is found by dividing the output voltage by the closed-loop gain. The circuit will be considered as a noninverting amplifier for the purpose of the offset calculation.
 - Record the measured input offset voltage in Table 44–1.

Table 44–2

Resistor	Listed Value	Measured Value
R_f	$1.0\ \text{M}\Omega$	
R_i	$10\ \text{k}\Omega$	
R_c	$10\ \text{k}\Omega$	

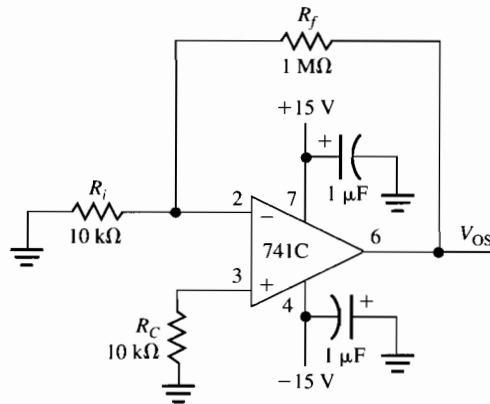


Figure 44–2

- In this step, you will measure the bias current, I_{BIAS} , and the input offset current, I_{OS} , of a 741C op-amp. The input bias current is the average of the input currents required at each input terminal of the op-amp. The input offset current is a measure of

how well these two currents match. The input offset current is the difference in the two bias currents when the output voltage is 0 V.

- Measure and record the resistors listed in Table 44–3.
- Connect the circuit shown in Figure 44–3.
- Measure the voltage across R_1 and R_2 of Figure 44–3. Use Ohm's law to calculate the current in each resistor.
- Record the *average* of these two currents in Table 44–1 as in the input bias current, I_{BIAS} .
- Record the *difference* in these two currents in Table 44–1 as in the input offset current, I_{OS} .

Table 44–3

Resistor	Listed Value	Measured Value
R_1	100 k Ω	
R_2	100 k Ω	

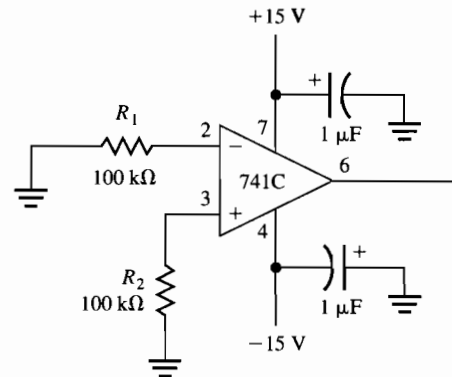


Figure 44–3

- In this step, you will measure the common-mode rejection ratio, CMRR, of a 741C op-amp. The CMRR is the ratio of the op-amp's differential gain divided by the common-mode gain. It is frequently expressed in decibels according to the definition

$$\text{CMRR} = 20 \log \frac{A_{v(d)}}{A_{cm}}$$

- Measure and record the resistors listed in Table 44–4. For an accurate measurement, resistors R_A and R_B should be closely matched as should R_C and R_D .
- It is more accurate to compute the differential gain, $A_{v(d)}$, based on the resistance ratio than to measure it directly. Determine the differential gain by dividing the measured value of R_C by R_A . Enter the differential gain, $A_{v(d)}$, in Table 44–1.
- Connect the circuit shown in Figure 44–4. Set the signal generator for 1.0 V_{pp} at 1 kHz. Measure the output voltage, $V_{out(cm)}$. Determine the common-mode gain, A_{cm} , by dividing $V_{out(cm)}$ by $V_{in(cm)}$.
- Determine the CMRR, in decibels, for your 741C op-amp. Record the result in Table 44–1.

Table 44-4

Resistor	Listed Value	Measured Value
R_A	100 Ω	
R_B	100 Ω	
R_C	100 k Ω	
R_D	100 k Ω	

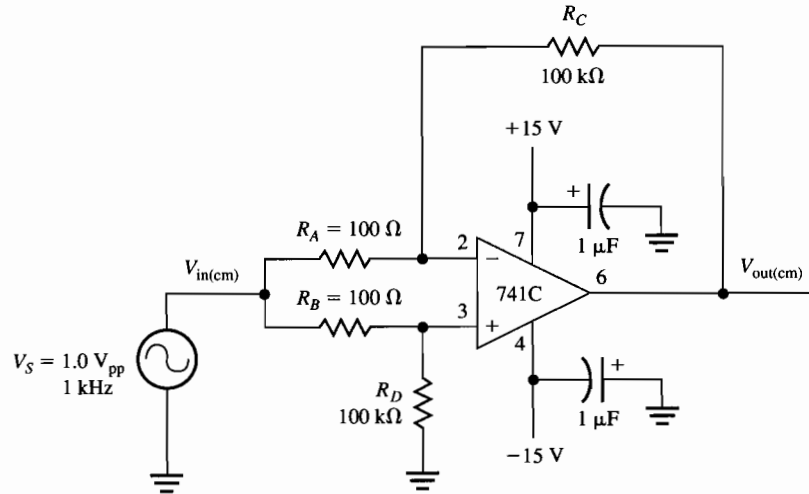


Figure 44-4

Conclusion:

Evaluation and Review Questions:

1. What is the meaning of the (+) and (-) terminal on the op-amp symbol?
2. Explain the meaning of input offset voltage.
3. What is the difference between the input bias current and the input offset current?
4. What is the difference between differential gain and common-mode gain?

5. (a) Explain how you measured the CMRR of the 741C.
- (b) What is the advantage of a high CMRR?

For Further Investigation:

Another important op-amp specification is the *slew rate*, which is defined as the maximum rate of change of the output voltage under large-signal conditions. Slew rate imposes a limit on how fast the output can change and affects the frequency response of the op-amp. It is measured in units of volts/microsecond. It is usually measured using a unity gain amplifier (voltage follower) with a fast-rising pulse.

Connect the unity gain circuit shown in Figure 44–5. Set the signal generator for a 10 V_{pp} square wave at 10 kHz. The output voltage will be slew-rate limited. It does not respond instantaneously to the change in the input voltage. Measure the rate of rise (slope) of the output waveform, as shown in Figure 44–6. Compare your measured slew rate with the typical value for a unity-gain 741C op-amp of 0.5 V/ μ s.

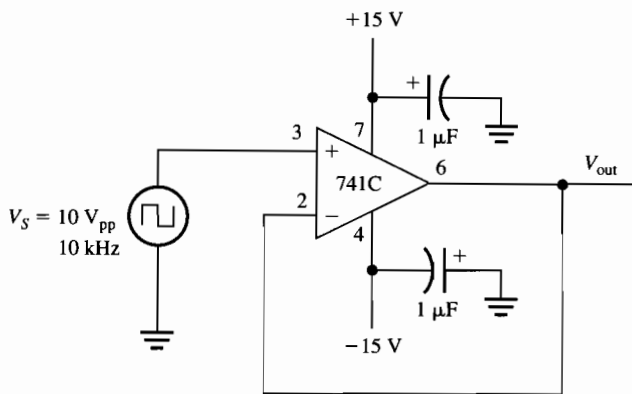


Figure 44–5

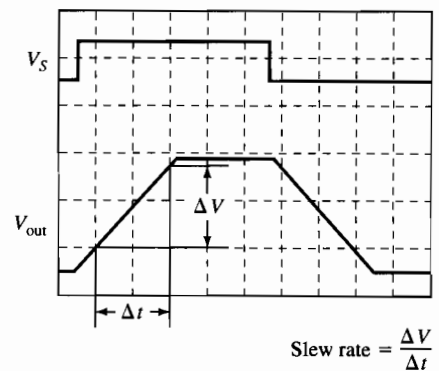


Figure 44–6

45 Linear Op-Amp Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 20–4 and 20–5

Objectives:


After performing this experiment, you will be able to:

1. Construct and test inverting and noninverting amplifiers using op-amps.
2. Specify components for inverting and noninverting amplifiers using op-amps.

Summary of Theory:

One of the most important ideas in electronics incorporates the idea of *feedback*, where a portion of the output is returned to the input. If the return signal tends to decrease the input amplitude, it is called *negative feedback*. Negative feedback produces a number of desirable qualities in an amplifier, increasing its stability and frequency response. It also allows the gain to be controlled independently of the device parameters or changes in temperature and other variables.

Operational amplifiers are almost always used with external feedback. The external feedback network determines the specific characteristics of the amplifier. By itself, an op-amp has an extremely high gain called the *open-loop* gain. When negative feedback is added, the overall gain of the amplifier decreases to an amount determined by the feedback. The overall gain of the amplifier, including the feedback network, is called the *closed-loop* gain, A_{cl} . The closed-loop gain is nearly equal to the reciprocal of the feedback fraction. Figure 45–1 illustrates a noninverting amplifier with negative feedback. The voltage divider samples a fraction of the output voltage and returns it to the inverting input. The closed-loop gain of this noninverting amplifier is given as $A_{cl(NI)}$. It is found by taking the reciprocal of the feedback fraction.

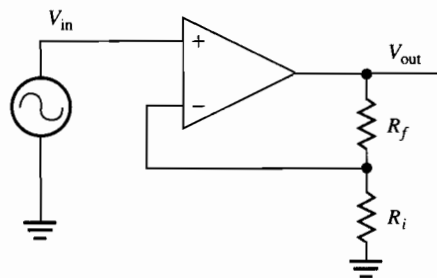

$$\text{Feedback fraction} = B = \frac{R_i}{R_i + R_f}$$

$$A_{cl(NI)} = \frac{1}{B} = \frac{R_i + R_f}{R_i} = 1 + \frac{R_f}{R_i}$$

Figure 45–1

Materials Needed:

Resistors:

Two 1.0 k Ω , one 10 k Ω , one 470 k Ω , one 1.0 M Ω

Two 1.0 μ F capacitors

One 741C op-amp

For Further Investigation:

One 1.0 kΩ potentiometer, one 100 kΩ resistor, assorted resistors to test

Procedure:

1. The circuit to be tested in this step is the noninverting amplifier illustrated in Figure 45-2. The closed-loop gain equation is given in Figure 45-1.
 - (a) Measure a 10 kΩ resistor for R_f and a 1.0 kΩ resistor for R_i . Record the measured value of resistance in Table 45-1.
 - (b) Using the measured resistance, compute the closed-loop gain of the noninverting amplifier.
 - (c) Calculate V_{out} by multiplying the closed-loop gain by V_{in} .
 - (d) Connect the circuit shown in Figure 45-2. Set the signal generator for a 500 mV_{pp} sine wave at 1 kHz. The generator should have no dc offset.
 - (e) Measure the output voltage, V_{out} . Record the measured value.
 - (f) Measure the feedback voltage at pin 2. Record the measured value.
 - (g) Place a 1.0 MΩ resistor in series with the generator. Compute the input impedance of the op-amp based on the voltage drop across the resistor.

Table 45-1

R_f	R_i	V_{in}	$A_{cl(I)}$	V_{out}	$V_{(-)}$	R_{in}
Measure Value	Measured Value	Measured	Computed	Computed	Measured (pin 6)	Measured
		500 mV _{pp}				

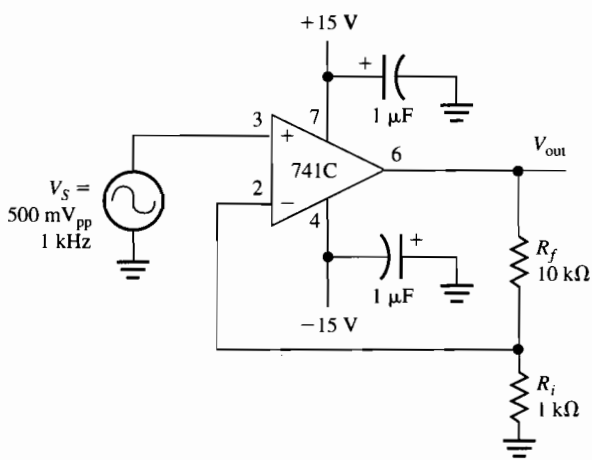


Figure 45-2

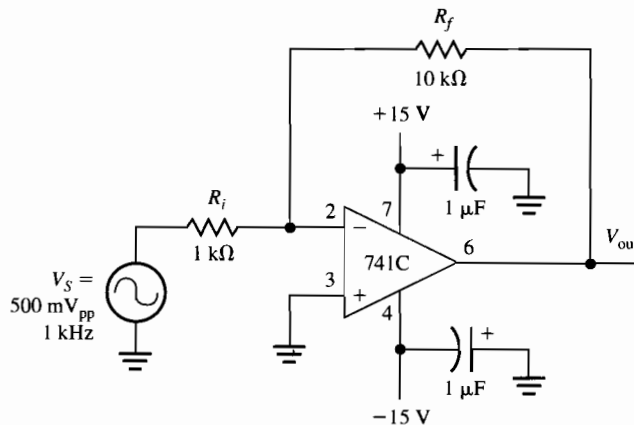


Figure 45-3

2. In this step you will test an inverting amplifier. Record all data in Table 45-2. The circuit is illustrated in Figure 45-3. The closed-loop gain is

$$A_{cl(I)} = -\frac{R_f}{R_i}$$

- (a) Use the same resistors for R_f and R_i as in step 1. Record the measured value of resistance in Table 45–2.
- (b) Using the measured resistance, compute and record the closed-loop gain of the inverting amplifier.
- (c) Calculate V_{out} by multiplying the closed-loop gain by V_{in} .
- (d) Connect the circuit shown in Figure 45–3. Set the signal generator for a 500 mV_{pp} sine wave at 1 kHz. The generator should have no dc offset.
- (e) Measure and record the output voltage, V_{out} .
- (f) Measure and record the voltage at pin 2. This point is called a *virtual ground* because of the feedback.
- (g) Place a 1.0 k Ω resistor in series with the generator and R_i . Compute the input impedance of the op-amp based on the voltage drop across the resistor.

Table 45–2

R_f	R_i	V_{in}	$A_{cl(l)}$	V_{out}		$V_{(-)}$	R_{in}
Measure Value	Measured Value	Measured	Computed	Computed	Measured (pin 6)	Measured (pin 2)	Measured
		500 mV _{pp}					

3. In this step you will specify the components for an inverting amplifier using a 741C op-amp. The amplifier is required to have an input impedance of 10 k Ω and a closed-loop gain of -47 . The input test signal is a 1 kHz, 100 mV_{pp} sine wave. (You may need to attenuate your signal generator to obtain this input.) Draw the amplifier. Then build and test your circuit. Find the maximum voltage the input signal can have before clipping occurs. Try increasing the frequency and note the frequency at which the output is distorted. Does the upper frequency response depend on the amplitude of the waveform? Summarize your results in the space provided.

Conclusion:

For Further Investigation:

An interesting application of an inverting amplifier is to use it as the basis of an ohmmeter for high-value resistors. The circuit is shown in Figure 45-4. The unknown resistor, labeled R_x , is placed between the terminals. The output voltage is proportional to the unknown resistance. Calibrate the meter by placing a known $10\text{ k}\Omega$ resistor in place of R_x and adjusting the potentiometer for exactly 100 mV output. The output then represents $10\text{ mV}/1000\ \Omega$. By reading the output voltage and moving the decimal point, you can directly read resistors from several thousand ohms to over $1\text{ M}\Omega$.

Construct the circuit and test it using different resistors. Calibrate output voltage against resistance and compare with theory. Find the percent error for a $1\text{ M}\Omega$ resistor using a lab meter as a standard. Summarize your results in a short report.

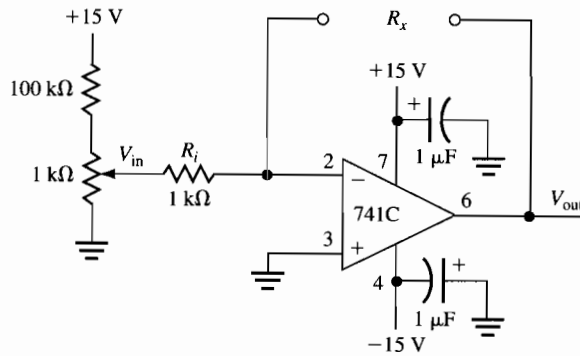


Figure 45-4

Application Assignment 20

Name _____
Date _____
Class _____

Reference:

Floyd, Chapter 20, Section 20-7: Application Assignment


Step 1 Relate the PC board to a schematic. Draw the schematic in the space provided below:

Step 2 Analyze the circuit.

1. Determine the resistance value to which the feedback rheostat must be adjusted for a voltage gain of 10. Rheostat setting = _____
2. Determine the voltage gain required and the setting of the feedback rheostat for maximum linear output for the specifications given in the text.

$A_v =$ _____ Rheostat setting = _____

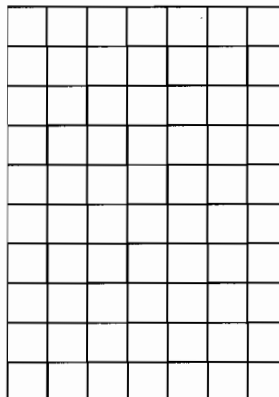3. With the gain set as determined in the previous step, on Plot AA-20-1 show the response characteristic of the circuit indicating the output voltage as a function of wavelength between 400 and 700 nm.



Plot AA-20-1

Step 3

Troubleshoot the circuit. State the probable cause of each of the following problems:

1. No voltage at the output of the op-amp (list three possible causes).

2. Output of op-amp stays at approximately -8 V .

3. A small voltage appears on the output with no light conditions.

Related Experiment:

Materials Needed:

Two $10\text{ k}\Omega$ resistors

Two $1\ \mu\text{F}$ capacitors

One $10\text{ k}\Omega$ potentiometer

One 741C op-amp

Discussion:

As you have seen, the gain of an op-amp can be easily adjusted over a wide range, depending on the requirements. The circuit shown in Figure AA-20-1 is another example of the versatility of op-amps. Can you figure out what the range of gain is? Construct the circuit and test the gain as you vary the potentiometer. Can you classify the amplifier as an inverting type or a noninverting type?

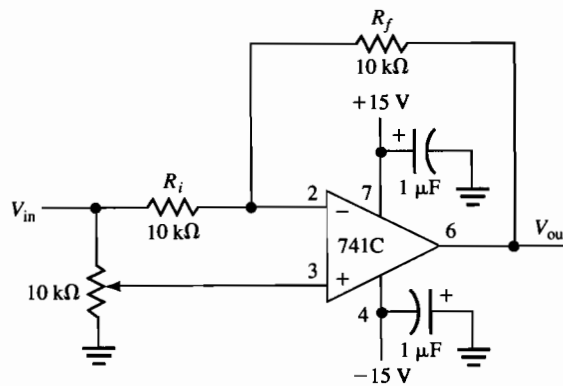


Figure AA-20-1

Checkup 20

Name _____

Date _____

Class _____

Reference:

Floyd, Chap. 20, and Buchla, Experiments 43 through 45

1. A differential amplifier is important in instrumentation systems because it preferentially amplifies:
(a) both normal- and common-mode signals (b) normal-mode signals only
(c) common-mode signals only (d) neither
2. Input offset voltage is the voltage applied to the input of an op-amp that will:
(a) cause the dc output voltage to be zero (b) cause the input current to be zero
(c) increase the CMRR (d) reduce noise in the output
3. A high CMRR is an advantage for applications requiring:
(a) high frequency response (b) high gain
(c) noise rejection (d) input protection
4. The input bias current of an op-amp is:
(a) the difference in two input currents (b) the average of two input currents
(c) the current required to produce no output (d) dependent on the gain of the circuit
5. When a portion of output is returned out of phase to the input, it is called:
(a) regenerative feedback (b) negative feedback
(c) common-mode feedback (d) closed-loop feedback
6. An ideal op-amp has an open-loop gain of:
(a) zero (b) 1 (c) 100,000 (d) infinity
7. An ideal op-amp has an input impedance of:
(a) zero (b) $1\ \Omega$ (c) $100,000\ \Omega$ (d) infinity
8. An op-amp connected as an inverting amplifier has a $4.7\ \text{k}\Omega$ input resistor and a $100\ \text{k}\Omega$ feedback resistor. The input impedance of the amplifier is closest to:
(a) $4.7\ \text{k}\Omega$ (b) $22\ \text{k}\Omega$ (c) $100\ \text{k}\Omega$ (d) $10\ \text{M}\Omega$
9. The amplifier in Question 8 has a voltage gain of approximately:
(a) 5 (b) 10 (c) 21 (d) 100
10. To measure the input offset current of an op-amp, you could:
(a) compare the output and input currents in an inverting amplifier
(b) compare the output and input currents in a noninverting amplifier
(c) determine the input current both with and without a signal on a diff amp
(d) use Ohm's law to determine the current in each of two large input resistors

11. Explain what is meant by a *virtual ground*.
12. Compare the difference between *open-loop* and *closed-loop* gain.
13. Assume you need a noninverting amplifier with a gain of 14.
 - (a) What ratio is required between the feedback resistor and the input resistor?
 - (b) Choose two standard-value resistors that will give the feedback fraction you determined in (a). Draw the circuit and label the resistors.
14. An op-amp can be operated from a single positive power supply, as shown in Figure C-20-1. (The noninverting input has a dc level applied to it to change the reference.) Assume V_{ref} is set for a +6.0 V level. Use the superposition theorem and the ideal op-amp model to answer the following questions.
 - (a) What is the dc level at the inverting input? _____
 - (b) What is the dc voltage across R_i ? _____
 - (c) What is the input current? _____
 - (d) What is the current in R_f ? _____
 - (e) What is V_{out} ? _____

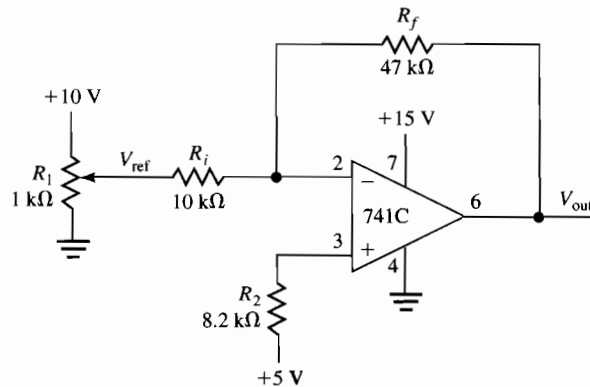


Figure C-20-1

46 Nonlinear Op-Amp Circuits

Name _____
Date _____
Class _____

Reading:

Floyd, Sections 21-1 through 21-3

Objectives:

After performing this experiment, you will be able to:

1. Construct and test an op-amp comparator, an integrator, and a differentiator circuit.
2. Determine the response of the circuits listed in objective 1 to various waveforms.
3. Troubleshoot faults in op-amp circuits.

Summary of Theory:

The basic op-amp is a linear device; however, many applications exist in which the op-amp is used in a nonlinear circuit. One of the most common nonlinear applications is the comparator. A comparator is used to detect which of two voltages is larger and drive the output into either positive or negative saturation. Comparators can be made from ordinary op-amps (and frequently are), but there are special ICs designed as comparators. They are designed with very high slew rates and frequently have open-collector outputs to allow interfacing to logic or bus systems.

Other uses of op-amps include a variety of signal processing applications. Op-amps are ideally suited to make precise integrators. Integration is the process of finding the area under a curve, as shown in the Summary of Theory for Experiment 30. An integrator produces an output voltage that is proportional to the *integral* of the input voltage waveform. The opposite of integration is differentiation. Differentiation circuits produce an output that is proportional to the *derivative* of the input voltage waveform. The basic op-amp comparator, integrator, and differentiator circuits with representative waveforms are illustrated in Figure 46-1.

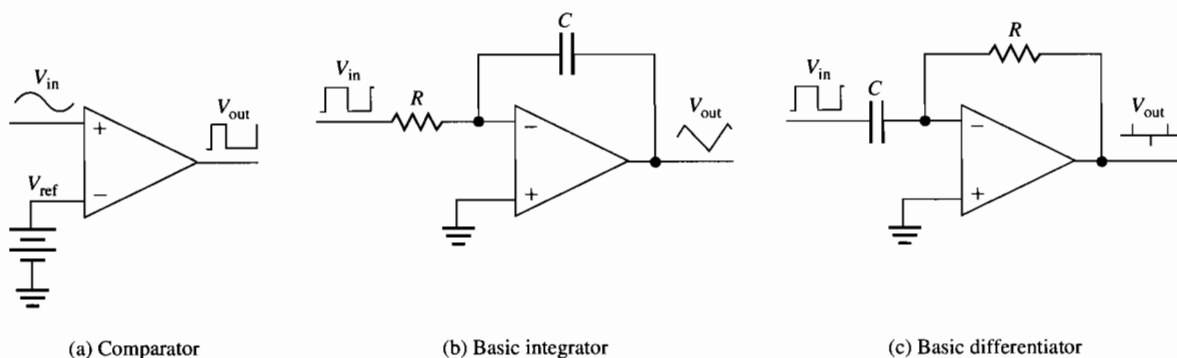


Figure 46-1

Materials Needed:

Resistors:

One 1.0 k Ω , four 10 k Ω , three 22 k Ω , one 330 Ω , one 330 k Ω

Capacitors:

One 2200 pF, one 0.01 μ F, two 1.0 μ F

Three 741C op-amps
 One 1 kΩ potentiometer
 Two LEDs (one red, one green)

Procedure:

- In this step you will construct and test an op-amp circuit connected as a comparator. Construct the circuit shown in Figure 46–2. Vary the potentiometer. Measure the output voltage when the red LED is on and then when the green LED is on. The 741C has current-limiting circuitry that prevents excessive current from destroying the LEDs. Record the output voltages, V_{OUT} , in Table 46–1. Notice that the LEDs prevent the output from going into positive and negative saturation. Then set the potentiometer to the threshold point. Measure and record V_{ref} at the threshold.

Table 46–1

V_{OUT}		V_{ref} Threshold
Red On	Green On	

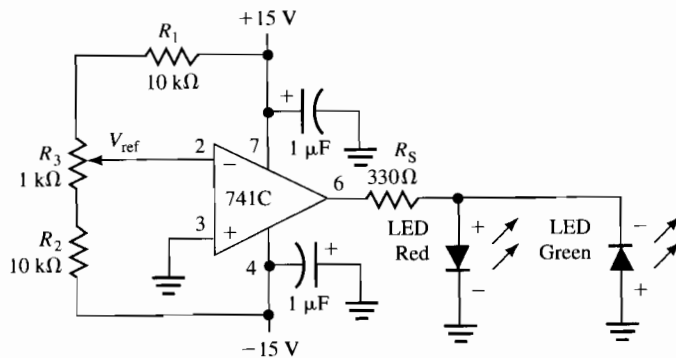


Figure 46–2

- In this step, you will test the effects of the comparator on a sine wave input and add an integrating circuit to the output of the comparator. Connect the circuit shown in Figure 46–3 and add a sine wave generator to the comparator as illustrated. Set the output for a 1.0 V_{pp} at 1 kHz with no dc offset. Observe the waveforms from the comparator (point A) and from the integrator (point B). Adjust R_3 so that the waveform at B is centered about zero volts. Sketch the observed waveforms in the correct time relationship on Plot 46–1. Show the voltages and time on your plot.


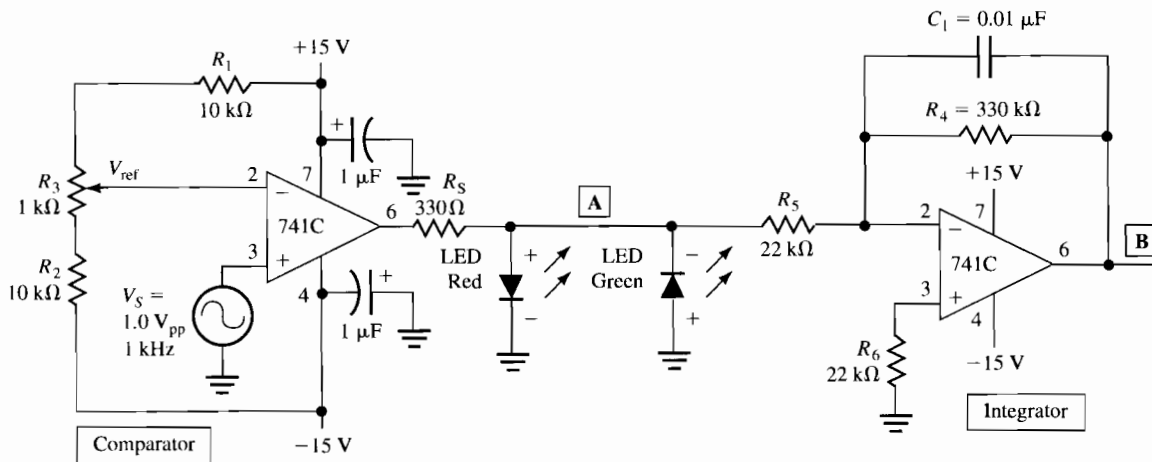


Figure 46–3

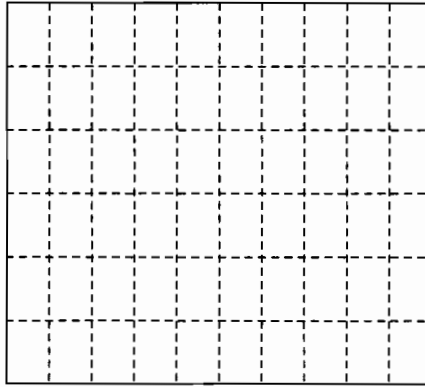

Plot 46-1

Vary R_3 while observing the output of the comparator and the integrator.
 Observations:

4. For each of the troubles listed in Table 46-2, see if you can predict the effect on the circuit. Then insert the trouble and check your prediction. At the end of this step, restore the circuit to normal operation.

Table 46-2

Trouble	Symptoms
No negative power supply	
Red LED open	
C_1 open	
R_4 open	

5. In this step, you will add a differentiating circuit to the previous circuit. The differentiator circuit is shown in Figure 46-4. Connect the input of the differentiator to the output of the integrator (point B). Observe the input and output waveforms of the differentiator. Sketch the observed waveforms on Plot 46-2. Label your plot and show voltage and time.



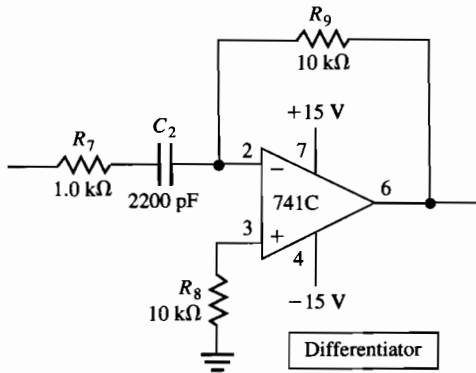


Figure 46-4

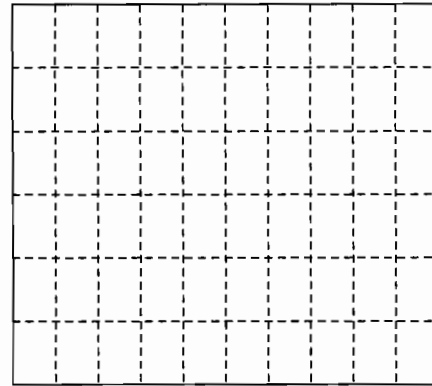

Plot 46-2

6. Remove the input from the differentiator and connect it to the output from the comparator (point A). Observe the new input and output waveforms of the differentiator. Sketch the observed waveforms on Plot 46-3. Label your plot.

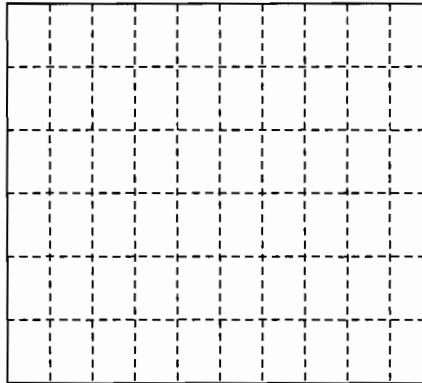

Plot 46-3

Conclusion:

For Further Investigation:

A useful variation of the comparator is the Schmitt trigger circuit shown in Figure 46–5. This circuit is basically a comparator that uses *positive* feedback to change the threshold voltage when the output switches. The trip point is dependent on whether the output is already saturated high or low. This effect is called *hysteresis*. Construct the circuit, test its operation, and summarize your findings in a short report.

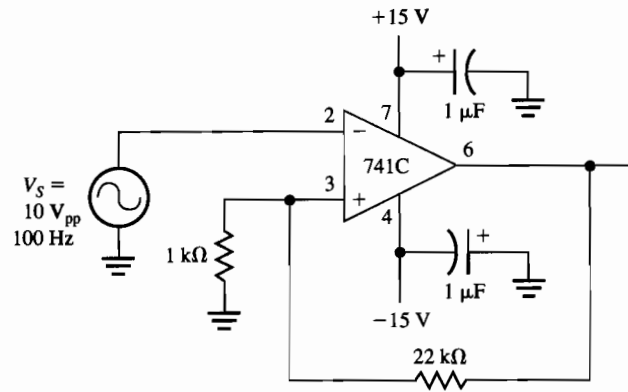


Figure 46–5

47 The Wien Bridge Oscillator

Name _____
Date _____
Class _____

Reading:
Floyd, Section 21–4

Objectives:

After performing this experiment, you will be able to:

1. Explain the requirements for a Wien bridge to oscillate, predict the feedback voltages and phases, and compute the frequency of oscillation.
2. Construct and test a Wien bridge oscillator with automatic gain control.

Summary of Theory:

The Wien bridge is a bridge-type circuit that is widely used as a sine wave oscillator for frequencies below about 1 MHz. Oscillation occurs when a portion of the output is returned to the input in the proper amplitude and phase to reinforce the input signal. This type of feedback is called *regenerative* or *positive* feedback. Regenerative oscillators require amplification to overcome the loss in the feedback network. For the Wien bridge, the signal returned to the noninverting input is one-third of the output signal. For this reason, the amplifier must provide a minimum gain of 3 to prevent oscillations from dying out.

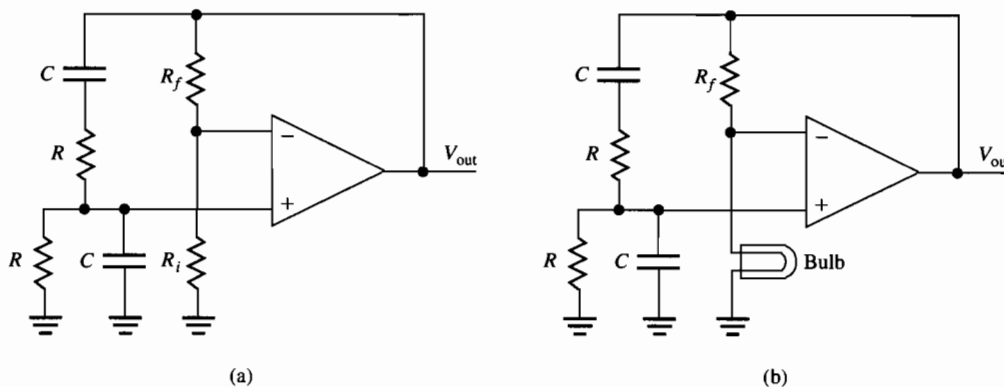


Figure 47–1

The basic Wien bridge circuit, is shown in Figure 47–1(a). The frequency of oscillation is determined by the lead-lag network connected to the noninverting input of the op-amp. The gain is controlled by R_f and R_i . The frequency of oscillation is found from the equation

$$f_r = \frac{1}{2\pi RC}$$

The gain must be at least 3 to maintain oscillations, but too much gain causes the output to saturate. Too little gain causes oscillations to cease. Various circuits have been

designed to stabilize loop gain at exactly 3. The basic requirement is to provide *automatic gain control*, or AGC for short. One common technique is to use a light bulb for AGC as illustrated in Figure 47–1(b). As the bulb’s filament warms, the resistance increases and reduces the gain. Other more sophisticated techniques use the variable resistance region of an FET to control gain. An FET automatic gain control circuit will be investigated in this experiment.

Materials Needed:

Resistors:

One 1.0 kΩ, three 10 kΩ

Capacitors:

Two 0.01 μF, three 1 μF

Two 1N914 signal diodes (or equivalent)

One 741C op-amp

One 2N5458 N-channel JFET transistor (or equivalent)

One 10 kΩ potentiometer

For Further Investigation:

Type 1869 or type 327 bulb

Procedure:

1. Measure R_1 , R_2 , C_1 , and C_2 . These components determine the frequency of the Wien bridge. Record the measured values in Table 47–1. If you cannot measure the capacitors, record the listed value.
2. Construct the basic Wien bridge illustrated in Figure 47–2. Adjust R_f so that the circuit just oscillates. You will see that it is nearly impossible to obtain a clean sine wave, as the control is too sensitive. With the bridge oscillating, try spraying some freeze spray on the components and observe the result. Observations:

Table 47–1

Component	Listed Value	Measured Value
R_1	10 kΩ	
R_2	10 kΩ	
C_1	0.01 μF	
C_2	0.01 μF	

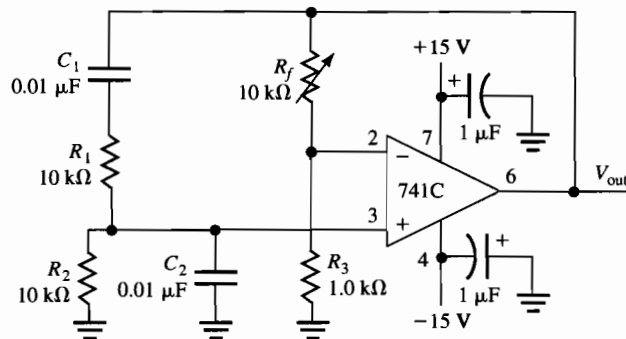


Figure 47–2

3. The basic Wien bridge in step 2 has unstable gain and requires some form of automatic gain control to work properly. Field-effect transistors are frequently used for AGC circuits because they can be used as voltage-controlled resistors for small applied voltages. The circuit illustrated in Figure 47-3 is an FET-stabilized Wien bridge. Compute the expected frequency of oscillation from the equation

$$f_r = \frac{1}{2\pi RC}$$

Use the *average* measured value of the resistance and capacitance listed in Table 47-1 to calculate f_r . Record the computed f_r in Table 47-2.

Table 47-2

f_r	
Computed	Measured (pin 6)

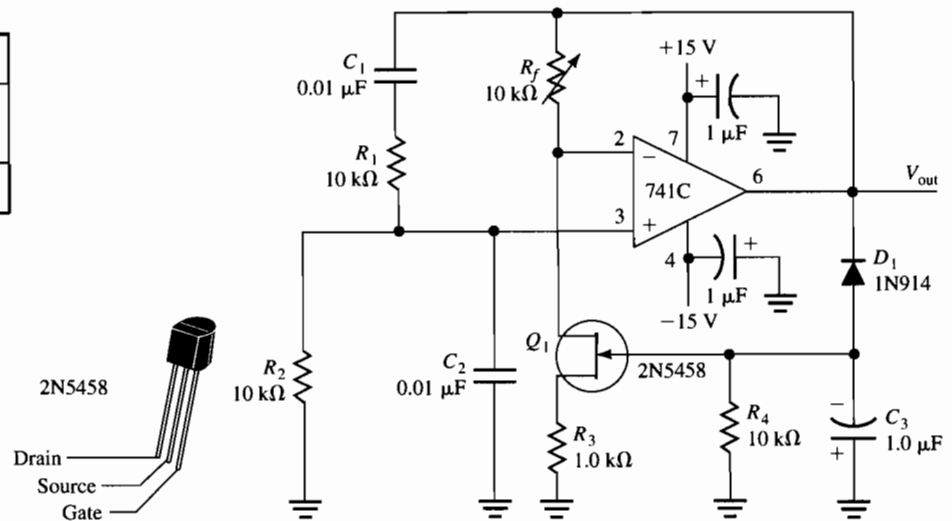


Figure 47-3

4. Construct the FET-stabilized Wien bridge shown in Figure 47-3. The diode causes negative peaks to charge C_3 and bias the FET. C_3 has a long time-constant discharge path, so the bias does not change rapidly. Note the polarity of C_3 . Adjust R_f for a good sine wave output. Measure the frequency and record it in Table 47-2.
5. Measure the peak-to-peak output voltage, $V_{out(pp)}$. Then measure the peak-to-peak positive and negative feedback voltages, $V_{(+)(pp)}$ and $V_{(-)(pp)}$ and the dc voltage on the gate of the FET. Use two channels and observe the phase relationship of the waveforms. Record the voltages in Table 47-3.

Table 47-3

Measured Voltages			
$V_{out(pp)}$ (pin 6)	$V_{(+)(pp)}$ (pin 3)	$V_{(-)(pp)}$ (pin 2)	V_{GATE}

What is the phase shift from the output voltage to the positive feedback voltage?

6. Try freeze spray on the various components while observing the output. Observations: _____ the voltages as before and record in Table 47-4.

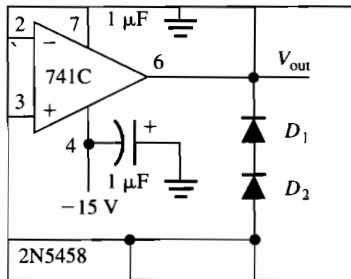


Figure 47-4

Table 47-4

Measured Voltages—Extra Diode			
$V_{out(pp)}$ (pin 6)	$V_{(+)(pp)}$ (pin 3)	$V_{(-)(pp)}$ (pin 2)	V_{GATE}

Conclusion:

Evaluation and Review Questions:

- In step 5, you measured the positive feedback voltage. What fraction of the output voltage did you find? Is this what you expected from theory?
- Explain why adding a second diode in series with the first caused the output voltage to increase.

3. For the circuit in Figure 47–3, what is the positive side of C_3 shown at ground?

4. At what frequency would the Wien bridge of Figure 47–3 oscillate if R_1 and R_2 were doubled?

5. How could you make a Wien bridge tune to different frequencies?

For Further Investigation:

Investigate the light-bulb-stabilized Wien bridge shown in Figure 47–1(b). A good bulb to try is a type 1869 or type 327. Other bulbs will work, but low-resistance filaments are not good. You can use the same components as in Figure 47–2 except replace R_3 with the bulb. Summarize your results in a short lab report.

48 Active Filters

Name _____
Date _____
Class _____

Reading:

Floyd, Section 21–5

Objectives:

After performing this experiment, you will be able to:

1. Specify the components required for a Butterworth low- or high-pass filter.
2. Build and test a Butterworth low- or high-pass active filter for a specific frequency.

Summary of Theory:

A filter is a circuit that produces a prescribed frequency response as described in Experiment 29. Passive filters are combination circuits containing only resistors, inductors, and capacitors (*RLC*). Active filters contain resistance and capacitance plus circuit elements that provide gain, such as transistors or operational amplifiers. The major advantage of active filters is that they can achieve frequency response characteristics that are nearly ideal and for reasonable cost for frequencies up to about 100 kHz. Above this, active filters are limited by bandwidth.

Active filters can be designed to optimize any of several characteristics. These include flatness of the response in the passband, steepness of the transition region, or minimum phase shift. The Butterworth form of filter has the flattest passband characteristic, but is not as steep as other filters and has poor phase characteristics. Since a flat passband is generally the most important characteristic, it will be used in this experiment.

The *order* of a filter, also called the number of *poles*, governs the steepness of the transition outside the frequencies of interest. In general, the higher the order, the steeper the response. The roll-off rate for active filters depends on the type of filter but is approximately –20 dB/decade for each pole. (A *decade* is a factor of 10 in frequency.) A four-pole filter, for example, has a roll-off of approximately –80 dB/decade. A quick way to determine the number of poles is to count the number of capacitors that are used in the frequency-determining part of the filter.

Figure 48–1 illustrates a two-pole active low-pass and a two-pole active high-pass filter. Each of these circuits is a *section*. To make a filter with more poles, simply cascade these sections, but change the gains of each section according to the values listed in Table 48–1. The cutoff frequency will be given by the equation

$$f = \frac{1}{2\pi RC}$$

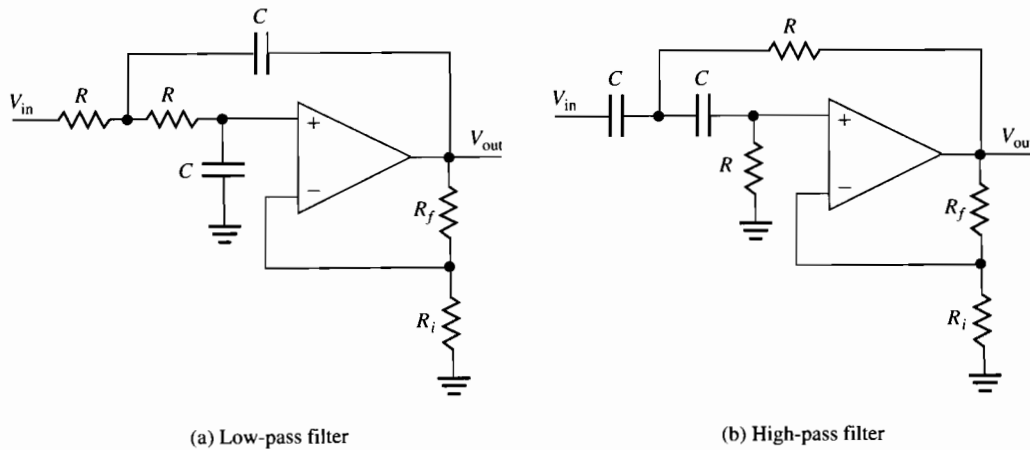


Figure 48-1

You can design your own Butterworth low-pass or high-pass active filter by using the following guidelines:

- (a) Determine the number of poles necessary based on the required roll-off rate. For example, if the required roll-off is -40 dB/decade, specify a two-pole filter.
- (b) Choose R and C values for the desired cutoff frequency. These components are labeled R and C on Figure 48-1. The resistors should be between 1 k Ω and 100 k Ω . The values chosen should satisfy the cutoff frequency as given by the equation

$$f = \frac{1}{2\pi RC}$$

- (c) Choose resistors R_f and R_i that give the gains for each section according to the values listed in Table 48-1. The gain is controlled only by R_f and R_i . Solving the closed-loop gain of a noninverting amplifier gives the equation for R_f in terms of R_i :

$$R_f = (A_v - 1)R_i$$

Table 48-1

Poles	Gain Required		
	Section 1	Section 2	Section 3
2	1.586		
4	1.152	2.235	
6	1.068	1.586	2.483

Example:

A low-pass Butterworth filter with a roll-off of approximately -80 dB/decade and a cutoff frequency of 2.0 kHz is required. Specify the components.

- Step 1** Determine the number of poles required. Since the design requirement is for approximately -80 dB/decade, a four-pole (two-section) filter is required.
- Step 2** Choose R and C . Try C as $0.01 \mu\text{F}$ and compute R . Computed $R = 7.96 \text{ k}\Omega$. Since the nearest standard value is $8.2 \text{ k}\Omega$, choose $C = 0.01 \mu\text{F}$ and $R = 8.2 \text{ k}\Omega$.
- Step 3** Determine the gain required for each section and specify R_f and R_i . From Table 48–1, the gain of section 1 is required to be 1.152, and the gain of section 2 is required to be 2.235. Choose resistors that will give these gains for a noninverting amplifier. The choices are determined by considering standard values and are shown on the completed schematic, Figure 48–2.

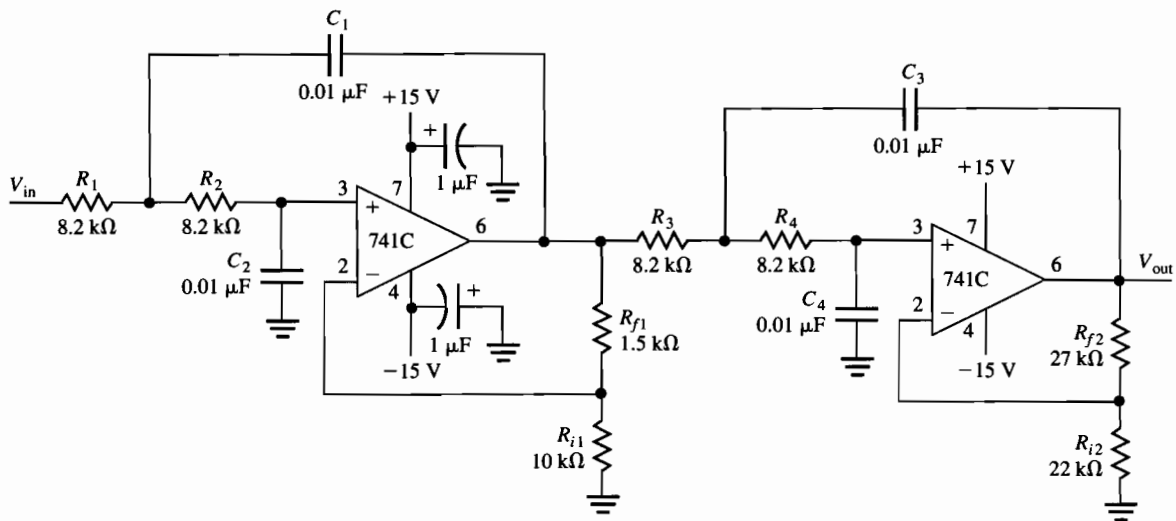


Figure 48–2

Materials Needed:

Resistors:

One $1.5 \text{ k}\Omega$, four $8.2 \text{ k}\Omega$, one $10 \text{ k}\Omega$, one $22 \text{ k}\Omega$, one $27 \text{ k}\Omega$

Capacitors:

Four $0.01 \mu\text{F}$, two $1 \mu\text{F}$

Two 741C op-amps

For Further Investigation:

One additional 741C op-amp and components to be specified by student

Procedure:

1. Measure and record the components listed in Table 48–2. If you cannot measure the capacitors, use the listed value.


Table 48-2

Component	Listed Values	Measured Values			
		1	2	3	4
R_1 to R_4	8.2 k Ω				
C_1 to C_4	0.01 μ F				
R_{i1}	10 k Ω				
R_{f1}	1.5 k Ω				
R_{i2}	22 k Ω				
R_{f2}	27 k Ω				

- Construct the four-pole low-pass active filter shown in Figure 48-2. Install a 10 k Ω load resistor. Connect a generator to the input and set it for a 500 Hz sine wave at 1.0 V_{rms} . The voltage should be measured at the generator with the circuit connected. Set the voltage with a voltmeter and check both voltage and frequency with the oscilloscope. Measure V_{RL} at a frequency of 500 Hz, and record it in Table 48-3.
- Change the frequency of the generator to 1000 Hz. Readjust the generator's amplitude to 1.0 V_{rms} . Measure V_{RL} , entering the data in Table 48-3. Continue in this manner for each frequency listed in Table 48-3.
- Graph the voltage across the load resistor (V_{RL}) as a function of frequency on Plot 48-1.

Table 48-3


Frequency	V_{RL}
500 Hz	
1000 Hz	
1500 Hz	
2000 Hz	
3000 Hz	
4000 Hz	
8000 Hz	

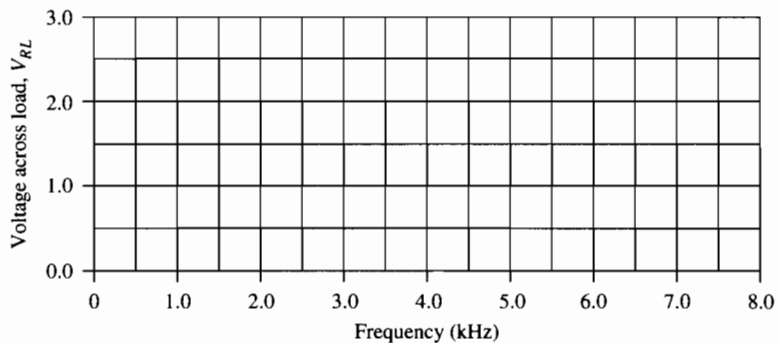

Plot 48-1

- A Bode plot is a log-log plot of voltage versus frequency. You can examine the data over a larger range than with linear plots. Plot the data from the filter onto the log-log Plot 48-2. The theoretical roll-off of -80 dB/decade is plotted for reference.

Conclusion:

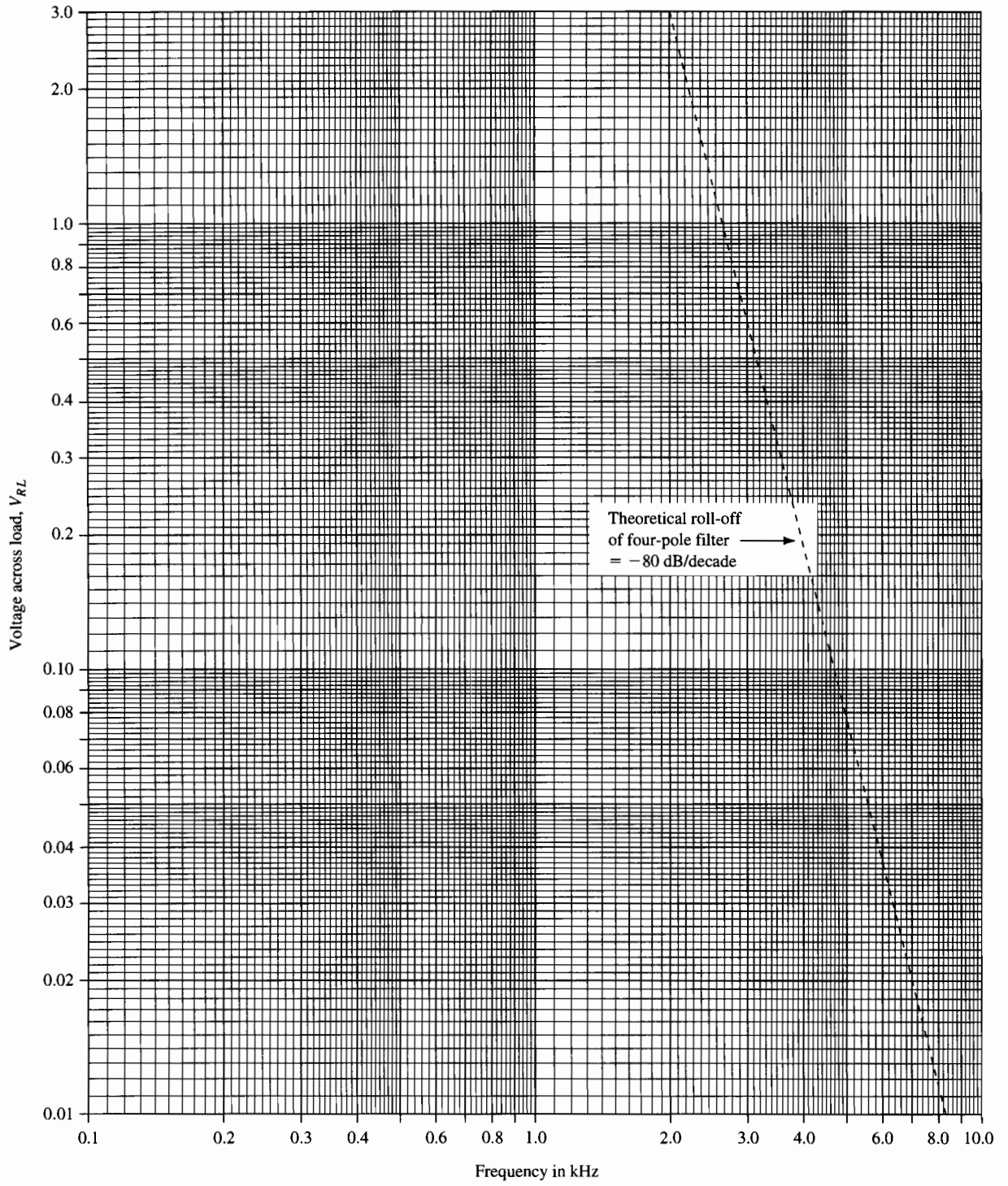

Plot 48-2

Evaluation and Review Questions:

1. (a) From the frequency response curves, determine the cutoff frequency for the filter in this experiment.

(b) Compute the average R and C for your active filter (Table 48–1). Use the average values of each to compute the cutoff frequency.
2. The cutoff frequency of the active filter in this experiment is about the same as that of Experiments 23 and 29. Compare the frequency response curves you obtained in those experiments with the response of the active filter.
3. Using the Bode plot, predict V_{out} at a frequency of 10 kHz.
4. The reference line on the Bode plot represents the theoretical roll-off rate of -80 dB/decade. How does your actual filter compare to this theoretical roll-off rate?
5. (a) Using the measured values of R_{i1} and R_{f1} , compute the actual gain of the first section. Compare this with the required gain in Table 48–1.

(b) Repeat for the second section using R_{i2} and R_{f2} .

For Further Investigation:

Design a six-pole high-pass Butterworth active filter with a cutoff frequency of 400 Hz. The procedures are outlined in the Summary of Theory. Construct the filter, measure its response, and submit a laboratory report. Show the response in your report.

Application Assignment 21

Name _____
 Date _____
 Class _____

Reference:

Floyd, Chapter 21, Section 21-7: Application Assignment

Step 1 Relate the PC board to a schematic. Draw the schematic in the space provided below:


Step 2 Analyze the power supply circuit.

- Determine the voltage with respect to ground at each of the four "corners" of the bridge. State if the voltage is ac or dc. Complete Table AA-21-1.

Table AA-21-1

Corner:	Voltage and Description
D_1-D_3	
D_2-D_3	
D_1-D_4	
D_2-D_4	

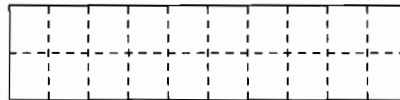- Compute the PIV for the diodes. PIV = _____
- Show the waveform across D_1 for a full cycle of the ac input.



Plot AA-21-1

Step 3

Troubleshoot the power supply for the following problems. State the probable cause.

1. Both positive and negative outputs are zero: _____
2. Positive output is zero; negative output is -12 V _____
3. Negative output is zero; positive output is $+12\text{ V}$ _____
4. Radical fluctuations on output of positive regulator: _____

Indicate the voltage you would measure for each of the following faults:

5. Diode D_1 open _____
6. Capacitor C_2 open _____

Related Experiment:

Materials Needed:

One 741C op-amp

Four $1.0\text{ k}\Omega$ resistors; additional resistors as determined by student

Discussion:

A scaling adder can be used to convert a binary number into an analog voltage level. Binary numbers employ only the digits 0 and 1 (called bits) to form numbers. Each bit can be represented as either a closed or open switch (0 or 1), as illustrated in Figure AA-21-1. As in any weighted counting system, the digits to the left take on higher “weights” based on their position—in the binary system, the weight of each column is a factor of two larger than the column on the immediate right.

For this related experiment, devise a scaling adder circuit that will convert a 4-bit binary number into analog voltage that is proportional to the input binary number. You may choose any gain you like, but the gain should not be so high as to drive the op-amp into saturation for the largest binary number (1111). The least significant bit will have a weight of 1 and the most significant bit will have a weight of 8. Draw your circuit and include measured values for the sixteen combinations of inputs.

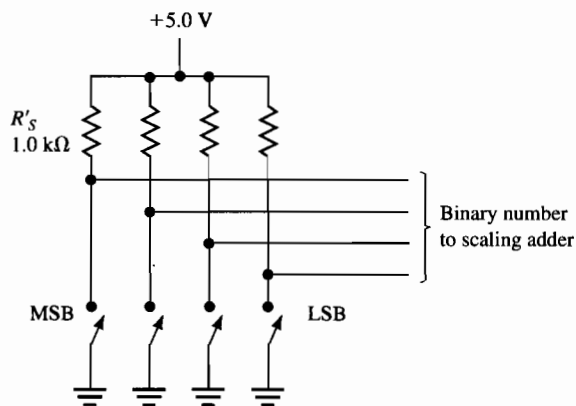


Figure AA-21-1

Checkup 21

Name _____
Date _____
Class _____

Reference:

Floyd, Chap. 21, and Buchla, Experiments 46, 47, and 48

- To connect an op-amp as a comparator, it is *not* necessary to have:
(a) power supplies (b) a reference
(c) feedback resistors (d) an input voltage
- When the input voltage crosses the reference voltage of a comparator, the output:
(a) changes state (b) becomes zero (c) oscillates (d) goes to +5.0 V
- When a square wave is the input signal of an integrating circuit, the output is a:
(a) triangle waveform (b) sinusoidal waveform
(c) step waveform (d) series of positive and negative pulses
- When a square wave is the input signal of differentiating circuit, the output is a:
(a) triangle waveform (b) sinusoidal waveform
(c) step waveform (d) series of positive and negative pulses
- A circuit that can be used to generate a sinusoidal waveform is:
(a) an integrator (b) a differentiator
(c) a Wien bridge (d) a comparator
- The gain for a Wien bridge oscillator must be at least:
(a) 3 (b) 15 (c) 29 (d) depends on the op-amp used
- The critical frequency of a low-pass filter is the frequency at which the output signal, when compared to the midband level, is attenuated by:
(a) 0 dB (b) -3 dB (c) -6 dB (d) depends on the number of poles
- A four-pole Butterworth filter has a roll-off rate of approximately:
(a) -20 dB per decade (b) -40 dB per decade
(c) -60 dB per decade (d) -80 dB per decade
- If the resistors and capacitors are interchanged on a low-pass filter, the result is:
(a) another low-pass filter (b) a high-pass filter
(c) a bandpass filter (d) a notch filter
- In a series regulator, if the output voltage decreases because the input voltage drops, the voltage on the base of the pass transistor
(a) increases (b) decreases (c) remains the same

11. Assume that a zero-crossing detector has a 10 V_{pp} sine wave on the inverting terminal and ground on the noninverting terminal, as shown in Figure C-21-1. Sketch the input and output waveforms.

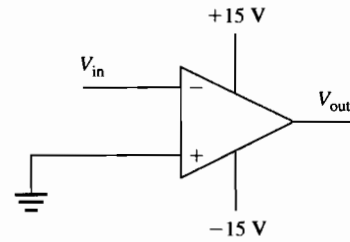


Figure C-21-1

12. Determine the reference voltage for the comparator shown in Figure C-21-2.
13. Assume two input signals from different microphones are connected to the summing network shown in Figure C-21-3.
- (a) What is the gain of the summing amplifier to each input?

- (b) Write an expression for the output signal in terms of the two inputs.

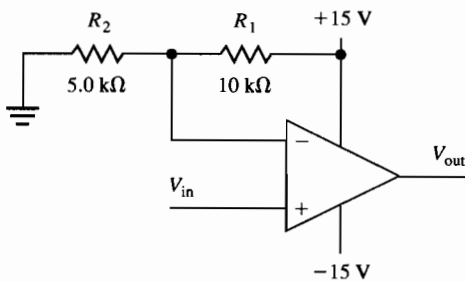


Figure C-21-2

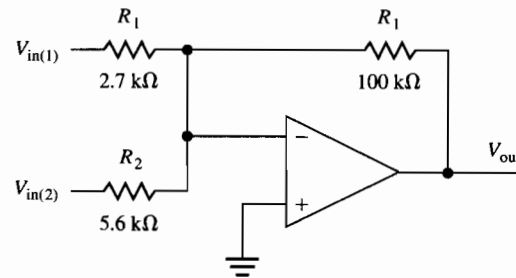


Figure C-21-3

14. (a) Compare the basic operation of an integrating circuit with a differentiating circuit.
- (b) Could an integrating or differentiating circuit be constructed using a resistor and inductor? Why do you think that inductors are not used?

Appendix A:

List of Materials for the Experiments

Note: Equivalent components may be substituted for diodes, transistors, etc.

Resistors:

Most resistors are preferred values for 10% tolerance and can be 1/4 W. Sizes (not quantities) are listed:

47 Ω	2.7 k Ω
68 Ω	3.3 k Ω
100 Ω	4.7 k Ω
120 Ω	5.1 k Ω
150 Ω	5.6 k Ω
160 Ω	6.8 k Ω
220 Ω	8.2 k Ω
270 Ω	10 k Ω
330 Ω	15 k Ω
470 Ω	22 k Ω
560 Ω	27 k Ω
680 Ω	33 k Ω
820 Ω	47 k Ω
1.0 k Ω	68 k Ω
1.5 k Ω	100 k Ω
1.6 k Ω	470 k Ω
1.8 k Ω	1.0 M Ω
2.0 k Ω	10.0 M Ω
2.2 k Ω	

Variable resistors:

1.0 k Ω , 5.0 k Ω , 10 k Ω , 50 k Ω , and 100 k Ω
20 Ω (optional)

Capacitors:

All capacitors are preferred values for 20% tolerance, 35 WV. Sizes (not quantities) are listed:

1000 pF
2200 pF
0.01 μ F
0.033 μ F
0.047 μ F
0.1 μ F
1.0 μ F
10 μ F
47 μ F
100 μ F
1000 μ F

Diodes:

Two 1N914 signal diodes
Four 1N4001 rectifier diodes
Six small light-emitting diodes (LEDs)

Inductors:

One 2 μ H (can be “homemade”)

One 25 μ H
Two 100 mH
One 7 H (second inductor optional)

Miscellaneous:

Crystal, 1.0 MHz
LEDs (one red, one green)
Meter: dc ammeter 0–10 mA
Metric ruler
Neon bulb (NE-2 or equivalent)
Relay: DPDT, 6 V dc or 12 V dc
Small speaker (4 or 8 Ω)
Switch: SPST
2N2646 UJT
Opto-coupler (4N35 or equivalent)

Operational amplifiers:

Three 741C op-amps

Materials for Further Investigations: (one of each)

Analog ohmmeter
Bulb: type 1869 or 327, one #44
CdS photocell:
 Radio Shack 276-116
Decade Resistance Boxes (two)
Inductor, 100 μ H
Meter calibrator
Regulators: 7812 or 78L12, 7809 or 78L09
Transformers:
 Input: Kelvin 155-08 (or equivalent)
 Output: Kelvin 175-45 (or equivalent)
Transistor curve tracer
Variable capacitor 12–100 pF (Mouser ME242-3610-100)
Wheatstone bridge
Zener diode: 5 V (1N4733 or equivalent)
7414 Schmitt trigger hex inverter

Thyristors:

One SK3950 SCR

Transformers: (one of each)

12.6 V_{rms} center-tapped
Small impedance matching:
(approximately 600 Ω or 800 Ω)

Transistors:

Three 2N3904 2N3947 NPN small-signal (or equivalent)
Two 2N3906 PNP small-signal
One 2N5458 JFET small-signal

Appendix B: Manufacturers' Data Sheets



Operational Amplifiers/Buffers

LM741/LM741A/LM741C/LM741E Operational Amplifier

General Description


The LM741 series are general purpose operational amplifiers which feature improved performance over industry standards like the LM709. They are direct, plug-in replacements for the 709C, LM201, MC1439 and 748 in most applications.

tion on the input and output, no latch-up when the common mode range is exceeded, as well as freedom from oscillations.


The LM741C/LM741E are identical to the LM741/LM741A except that the LM741C/LM741E have their performance guaranteed over a 0°C to +70°C temperature range, instead of -55°C to +125°C.

The amplifiers offer many features which make their application nearly foolproof: overload pro-

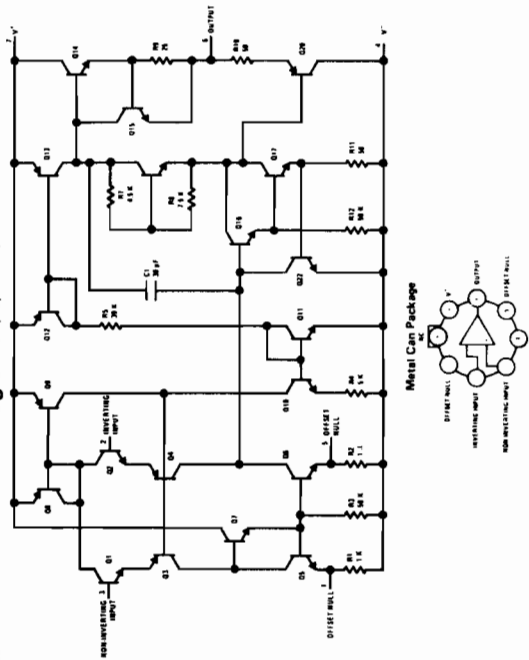
Schematic and Connection Diagrams (Top Views)



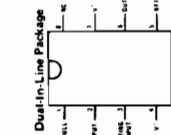Order Number LM741AH, LM741AH,
LM741CH or LM741EH
See NS Package N08C.



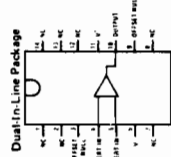Order Number LM741CN or LM741EN
See NS Package N08B
Order Number LM741CJ
See NS Package J08A



Order Number LM741CN-14
See NS Package N14A
Order Number LM741J-14, LM741AJ-14
or LM741CJ-14
See NS Package J14A

Absolute Maximum Ratings

	LM741A	LM741E	LM741	LM741C
Supply Voltage	±22V	±22V	±22V	±18V
Power Dissipation (Note 1)	500 mW	500 mW	500 mW	500 mW
Differential Input Voltage	±30V	±30V	±30V	±30V
Input Voltage (Note 2)	±15V	±15V	±15V	±15V
Output Short Circuit Duration	Indefinite	Indefinite	Indefinite	Indefinite
Operating Temperature Range	-55°C to +125°C	0°C to +70°C	-55°C to +125°C	0°C to +70°C
Storage Temperature Range	-65°C to +150°C	-65°C to +150°C	-65°C to +150°C	-65°C to +150°C
Lead Temperature (Soldering, 10 seconds)	300°C	300°C	300°C	300°C

Electrical Characteristics (Note 3)

PARAMETER	CONDITIONS		LM741A/LM741E		LM741		LM741C		UNITS
	MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	
Input Offset Voltage	TA = 25°C								
	RS < 10 kΩ	0.8	3.0	1.0	5.0	2.0	6.0	mV	
	TAMIN ≤ TA ≤ TAMAX	4.0		6.0		7.5		mV	
	RS ≤ 50 Ω	15						mV	
Average Input Offset Voltage Drift	TA = 25°C, VS = ±20V								
	TA = 25°C	-10	3.0	3.0	30	20	200	μA	
	TAMIN ≤ TA ≤ TAMAX	0.5		85	500	300		μA	
	VS = ±20V	1.0	6.0	0.3	2.0	0.3	2.0	μA	
Input Bias Current	TA = 25°C								
	TAMIN ≤ TA ≤ TAMAX	30	80	80	500	80	500	nA	
	TA = 25°C, VS = ±20V	0.210		15		0.8		nA	
	TAMIN ≤ TA ≤ TAMAX	0.5						nA	
Input Resistance	TA = 25°C								
	TAMIN ≤ TA ≤ TAMAX	50		50		200		MΩ	
	TA = 25°C, VS = ±20V	32		25		15		MΩ	
	VS = ±15V, VO = -10V	10						MΩ	
Input Voltage Range	TA = 25°C								
	TAMIN ≤ TA ≤ TAMAX	-12	-13	-12	-13	-12	-13	V	
	TA = 25°C, RL ≥ 2 kΩ							V	
	VS = ±20V, VO = -15V							V	
Large Signal Voltage Gain	TA = 25°C, RL ≥ 2 kΩ								
	VS = ±20V, VO = -15V	50		50		200		V/mV	
	TAMIN ≤ TA ≤ TAMAX	32		25		15		V/mV	
	VS = ±15V, VO = -10V	10						V/mV	
Output Voltage Swing	VS = ±20V								
	RL ≥ 10 kΩ	-16		-16		-16		V	
	RL ≥ 2 kΩ	-15		-15		-15		V	
	VS = ±15V							V	
Output Short Circuit Current	RL ≥ 10 kΩ								
	TA = 25°C	10	25	35	40	10	25	25	mA
	TAMIN ≤ TA ≤ TAMAX	10				70	90	90	mA
	TAMIN ≤ TA ≤ TAMAX, RS ≤ 10 kΩ, VCM = -12V, RS ≤ 50 kΩ, VCM = -12V	80	95						dB



MOTOROLA

SEMICONDUCTORS

P.O. BOX 20912 • PHOENIX, ARIZONA 85036

NPN SILICON ANNULAR TRANSISTORS

... designed for general purpose switching and amplifier applications and for complementary circuitry with types 2N3905 and 2N3906.

- High Voltage Ratings — $V_{(BR)CEO} = 40$ Volts (Min)
- Current Gain Specified from 100 μ A to 100 mA
- Complete Switching and Amplifier Specifications
- Low Capacitance — $C_{ob} = 4.0$ pF (Max)

MAXIMUM RATINGS

Rating	Symbol	Value	Unit
*Collector-Emitter Voltage	V_{CEO}	40	Vdc
*Collector-Base Voltage	V_{CBO}	60	Vdc
*Emitter-Base Voltage	V_{EBO}	6.0	Vdc
*Collector Current — Continuous	I_C	200	mAdc
**Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/ $^\circ\text{C}$
Total Power Dissipation @ $T_A = 60^\circ\text{C}$	P_D	450	mW
**Total Device Dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	1.5 12	Watts mW/ $^\circ\text{C}$
**Operating and Storage Junction Temperature Range	T_J, T_{stg}	-55 to 150	$^\circ\text{C}$

THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	$^\circ\text{C}/\text{W}$
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	$^\circ\text{C}/\text{W}$

*Indicates JEDEC Registered Data.

**Motorola guarantees this data in addition to the JEDEC Registered Data.

EQUIVALENT SWITCHING TIME TEST CIRCUITS

FIGURE 1 — TURN-ON TIME


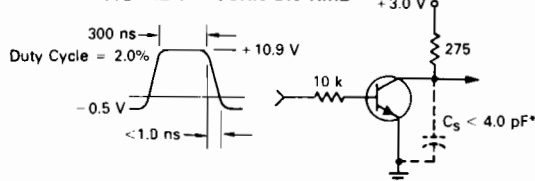




FIGURE 2 — TURN-OFF TIME

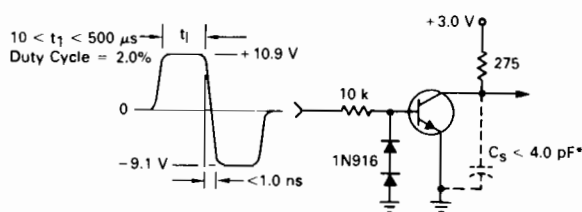

*Total shunt capacitance of test jig and connectors

2N3903 2N3904

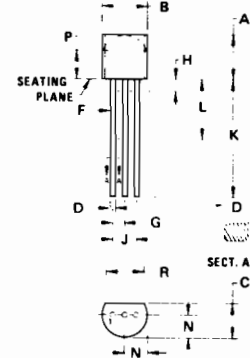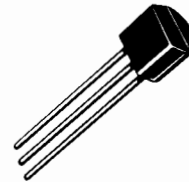NPN SILICON SWITCHING & AMPLIFIER TRANSISTORS



NOTES

- 1 CONTOUR OF PACKAGE BEYOND ZONE "P" IS UNCONTROLLED.
- 2 DIM "F" APPLIES BETWEEN "H" AND "L". DIM "O" & "S" APPLIES BETWEEN "L" & 12.70 mm (0.5") FROM SEATING PLANE. LEAD DIM IS UNCONTROLLED IN "H" & BEYOND 12.70 mm (0.5") FROM SEATING PLANE.

DIM	MILLIMETERS		INCHES	
	MIN	MAX	MIN	MAX
A	4.32	5.33	0.170	0.210
B	4.44	5.21	0.175	0.205
C	3.18	4.19	0.125	0.165
D	0.41	0.56	0.016	0.022
F	0.41	0.48	0.016	0.019
G	1.14	1.40	0.045	0.055
H	—	2.54	—	0.100
J	2.41	2.67	0.095	0.105
K	12.70	—	0.500	—
L	6.35	—	0.250	—
N	2.03	2.67	0.080	0.105
P	2.92	—	0.115	—
R	3.43	—	0.135	—
S	0.36	0.41	0.014	0.016

All JEDEC dimensions and notes apply

CASE 29-02
(TO-226AA)


(Courtesy of Motorola Inc.)

MOTOROLA INC. 1985

DS5127 R2

**2N5457
2N5458
2N5459**

**CASE 29-04, STYLE 5
TO-92 (TO-226AA)**

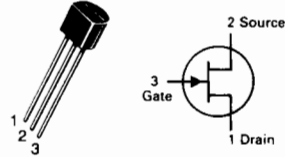

**JFET
GENERAL PURPOSE
N-CHANNEL — DEPLETION**

Refer to 2N4220 for graphs.

MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Drain-Source Voltage	V_{DS}	25	Vdc
Drain-Gate Voltage	V_{DG}	25	Vdc
Reverse Gate-Source Voltage	V_{GSR}	-25	Vdc
Gate Current	I_G	10	mAdc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	310 2.82	mW mW/°C
Junction Temperature Range	T_J	125	°C
Storage Channel Temperature Range	T_{stg}	-65 to +150	°C

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted.)

Characteristic	Symbol	Min	Typ	Max	Unit
OFF CHARACTERISTICS					
Gate-Source Breakdown Voltage ($I_G = -10 \mu\text{Adc}$, $V_{DS} = 0$)	$V_{(BR)GSS}$	-25	—	—	Vdc
Gate Reverse Current ($V_{GS} = -15 \text{Vdc}$, $V_{DS} = 0$) ($V_{GS} = -15 \text{Vdc}$, $V_{DS} = 0$, $T_A = 100^\circ\text{C}$)	I_{GSS}	—	—	-1.0 -200	nAdc
Gate Source Cutoff Voltage ($V_{DS} = 15 \text{Vdc}$, $I_D = 10 \text{nAdc}$)	$V_{GS(off)}$	-0.5 -1.0 -2.0	—	-6.0 -7.0 -8.0	Vdc
Gate Source Voltage ($V_{DS} = 15 \text{Vdc}$, $I_D = 100 \mu\text{Adc}$) ($V_{DS} = 15 \text{Vdc}$, $I_D = 200 \mu\text{Adc}$) ($V_{DS} = 15 \text{Vdc}$, $I_D = 400 \mu\text{Adc}$)	V_{GS}	—	-2.5 -3.5 -4.5	—	Vdc
ON CHARACTERISTICS					
Zero-Gate-Voltage Drain Current* ($V_{DS} = 15 \text{Vdc}$, $V_{GS} = 0$)	I_{DSS}	1.0 2.0 4.0	3.0 6.0 9.0	5.0 9.0 16	mAdc
SMALL-SIGNAL CHARACTERISTICS					
Forward Transfer Admittance Common Source* ($V_{DS} = 15 \text{Vdc}$, $V_{GS} = 0$, $f = 1.0 \text{kHz}$)	$ y_{fs} $	1000 1500 2000	—	5000 5500 6000	μmhos
Output Admittance Common Source* ($V_{DS} = 15 \text{Vdc}$, $V_{GS} = 0$, $f = 1.0 \text{kHz}$)	$ y_{os} $	—	10	50	μmhos
Input Capacitance ($V_{DS} = 15 \text{Vdc}$, $V_{GS} = 0$, $f = 1.0 \text{MHz}$)	C_{iss}	—	4.5	7.0	pF
Reverse Transfer Capacitance ($V_{DS} = 15 \text{Vdc}$, $V_{GS} = 0$, $f = 1.0 \text{MHz}$)	C_{rss}	—	1.5	3.0	pF

*Pulse Test: Pulse Width $\leq 630 \text{ms}$; Duty Cycle $\leq 10\%$.

6

